

Chapter: **AFX_Abstract_**

“Abstract” for the “AFX” project :

**Title: “Analog Phase-Filtering
in OpAmp Active-Band-Pass Circuits”**

**This project presents an experimental study
of original Analog Phase-Filters and Parallel-Channel-Filters
which provide near DSP narrow filtering characteristics,
with-out computer processing.**

This project circuit utilizes

- (a) Pre-Amp**
- (b) Triad-Roofing-Differential Filters, BW = 350 Hz, f(700).**
- (c) Active Log-Limiter**
- (d) Main Filter of Quad Multiple-FeedBack band-pass stages
which are adjustable 600 - 700 - 800 Hz by user.**
- (e) Phase-Filtered Non-Resonant Dual-Notch stage
producing notches at 560 Hz and 860 Hz,
very Deep (aprox. -80 dB)
Octave Stop-Band very low (aprox. -110 dB).
These Notches are Not Quadrature in concept.**
- (f) Variable Narrow Q=20 final band-pass filter, user variable.**
- (g) Audio Amp.**

**This project has applications that include
in-lab analog instrument filters
(proto-boarded and no PC computer required)**



Chapter: **AFX_Introduction_**

Title: “Analog Phase-Filtering in OpAmp Active-Band-Pass Circuits”

PreRequisite for Reading this Paper:

This is not an academic Algebra / Calculus based tutorial.

This is not a tutorial in Linear I.C. Design Applications.

It is expected that the reader will have

...(1) a good understanding of Linear I.C. Design Applications.

(2) a good understanding of Active BandPass Filter Concepts

(3) an open mind to new ideas.

[The Multi-Feed-Back Band-Pass Filter is the basic filter used

[because it is very versatile, tunable, and stable.

[This website & project does not contain an in-depth presentation

[of this basic Delyanis-Friend Multi-Feed-Back Filter (MFB) .

[The primary I.C. is the LM-324 as it is 10x viable for audio.

MFB schematic and equations:

R(2) is the Resonant Loading resistor
used for minor tuning of f(0) .

Fundamental Transfer Function

$$\frac{v_o}{v_i} = \frac{-\frac{1}{R_1 C_1} s}{s^2 + s \left(\frac{1}{R_3 C_2} + \frac{1}{R_3 C_1} \right) + \frac{1}{R_3 C_1 C_2} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)}$$

All concepts presented herein are common to Active BandPass Filters as presented in tutorials and academic course-work presented for Electronic Engineering Technology students. Concepts presented here are ONLY the SYNTHESIS of common ideas into radically new approaches.

Your Imagination is more important than prior academic learning.

Design choices:

*** Simple repetitive application of Modified *Delyannis-Friend-Multiple-FeedBack* design.

*** MFB topology was chosen because :

*** (1) input vs output impedances match well, loading is naturally controlled, stage to stage.

*** (2) one single resistor frequency control each stage.

*** (3) frequency adjustments alters gain by only the square-root of the f(change) .

*** (4) the Roof-Triad-Differential design provides superior side-band suppression. and is wide enough to be very tolerant of component variations for central channel f(0) signal.

MULTIPLE FEEDBACK BAND-PASS DESIGN EQUATIONS

$$\frac{-H \omega_0 s}{s^2 + \alpha \omega_0 s + \omega_0^2}$$

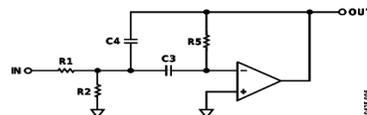


Figure 6.

$$\frac{V_O}{V_{IN}} = \frac{-s \frac{1}{R1 C4}}{s^2 + s \frac{C3 + C4}{C3 C4 R5} + \frac{1}{R5 C3 C4} \left(\frac{1}{R1} + \frac{1}{R2} \right)}$$

To design the filter, choose C3.

Then

$$k = 2 \pi F_0 C3$$

$$C4 = C3$$

$$R1 = \frac{1}{H k}$$

$$R2 = \frac{1}{(2Q - H) k}$$

$$R5 = \frac{2Q}{k}$$

Just for reference:

Delyannis-Friend Multiple-Feed-Back design

Your Imagination is more important than prior academic learning.

- >> **First, please read through the “Intro” chapter !**
- >> **Second,**
read the sub-chapters for greater basic details
about each of the modules comprising the AFX project.
- >>> **several additional chapters have been added**
which expand greatly on the applications of “AFX”

The extra chapters are about

Phase-Filter Non-Resonant Filter Applications:

- (1) **AF’V’ variable AFX version with Dual-Notches.**
- (2) **AF’T’ Simple No-Notch circuit.**
- (3) **AP’C’ All-Pass Band-Pass with Dual-Notches.**


The AFX designs include these features :

- *** BandPass 90Hz @ -3dB and 340Hz @ -60dB,
- *** SideBand Spread = 5Hz per dB attenuation ("variance").
- *** Dual-Notch BandPass = -90 dB @ 350Hz bandpass
- *** Variable-Frequency PassBand ability ($f(0) = 600-700-800$)

Note:

AFX Dual Notch PassBands are not Gaussian shaped. and are not I/Q Quadrature generated.

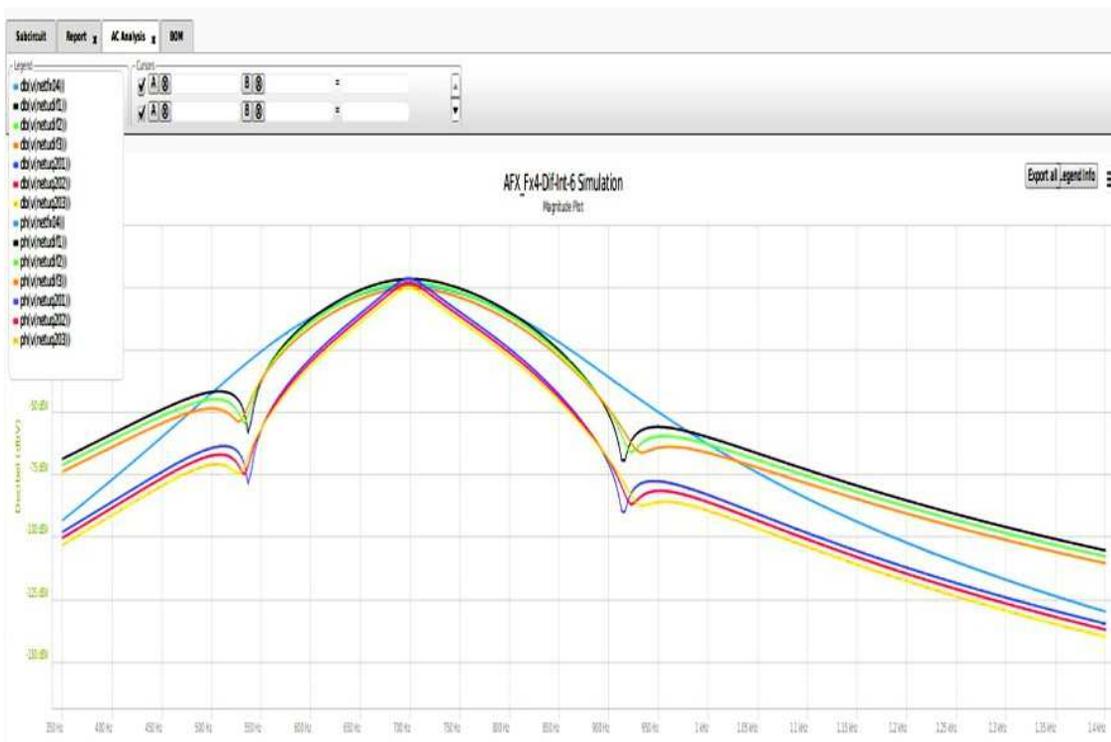Magnitude Plot: Phase-Filter Dual-Notch Band-Pass



Above:

the 1... blue trace is the Quad-Filter BandPass
the 2,3,4 three traces are Notched BandPass.
the 5,6,7 three traces are High 'Q' BandPass.

About this project :

This project was begun before 2014 in my personal lab, using radio equipment at my Amateur Radio Station "K4KKQ" and was presented to the ResearchGate.Net forum thereafter, where it received critical review.

This project is our Current research in Analog I.C. Applications, as applied to CW (morse code) Radio Operations
... posted at www.GeoCities.WS/glene77is
... posted at www.ResearchGate.net
... posted at Yahoo HW8 Group (in years past)

Our Analog Project shows the evolution of filter design from common Resonant Active BandPass circuits into Active Phased-Filtered Non-Resonant circuits. Presented in circuits "AFX'V'", "AFX'T'", "AFX'C'".

About The "AFX" project :

- (1) "AFX" is about Analog Electronic Technology applied to Amateur Radio CW operations.
- (2) "AFX" applies concepts to Narrow Band-Pass Morse Code CW operations.
- (3) "AFX" has produced a Series of Analog Filters approaching DSP quality in narrow band-pass CW operations.
- (4) "AFX" emphasizes Parallel-Channel-Filtering and Phase-Filtering to generate Narrow Band-Pass Dual-Notched effects.
- (5) "AFX" emphasizes a radical Phase-Filtered Non-Resonant design in the final stage.
- (6) "AFX" is not a digital project requiring a PC computer to function.

Applications include

in-lab analog instrument filters
where the circuit is proto-boarded as a stand-alone device.

Rationale for this project:

In Amateur Radio CW operations, we commonly tune for a 700 Hz audio signal, but other signals may also be present, interfering with the 700 Hz signal. These 'other' interfering signals are presented here as 600 Hz and 800 Hz.

Below:

Transient Plot shows Phase Delays and inter-actions based on triple-signals (600Hz , 700Hz , 800Hz) injected simultaneously. Triple-Signals are shown as they phase-shift across time.

Triple-Signals are similar to CW radio signals of differing frequencies as received for processing in the radio receiver and operator ears. The purpose of the Filter is to select the center signal, while attenuating the other two.


* (red-green-blue trace on top)

Shows Triple-Signals phase differences on input signal .

* (blue trace on bottom)

Filter forces phase shifting on input signal and produces a symmetrical output signal. Filter responds to the beat frequencies with peaks and nulls in its output.

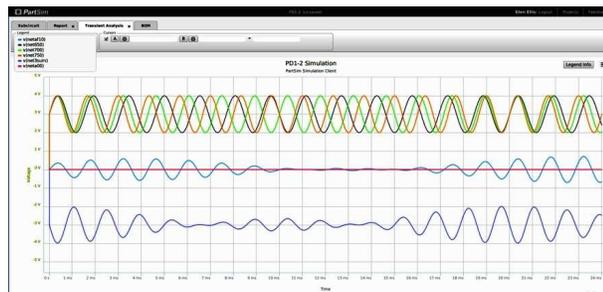* Without any Filtering, we are left with only the bottom Blue trace and information is lost .



Note about the Non-Gaussian Band-Pass shape :


“Variance” is used to describe the “BW” vs “Q” relation.

**"v" = slope of best fit for the non-Gaussian sideband shape]
[(BW@-12dB) - (BW@-3dB) / 9dB**

Therefore,


v=25 is very wide sidebands (similar to low “Q’)

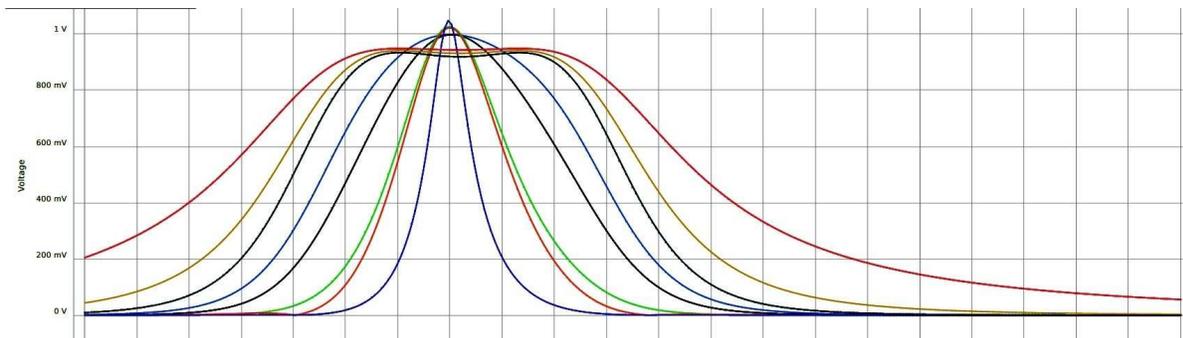v=5 is a very steep sideband (similar to high “Q”)



© 2005 Analog Devices, Inc. All rights reserved. AD-598

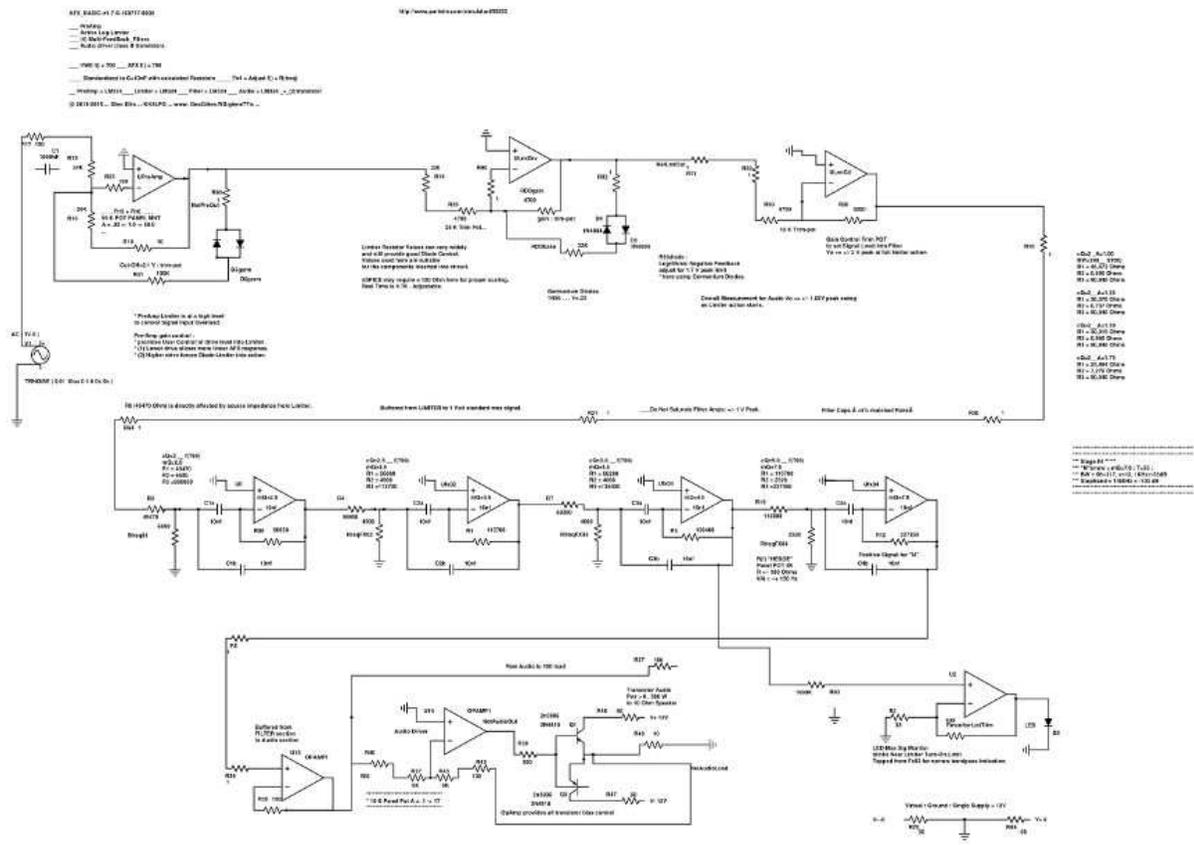 the "AFX" B.A.S.I.C. Simple Schematic
 where it all started simply.



- Examine the modular function blocks:
- (1) PreAmp
 - (2) Active Log-Limiter
 - (3) Quad MFB resonant Active Band-Pass Filters.
 - (4) Audio amp
 - (5) Level Indicator for signal in center of band-pass..

PAGE LEFT INTENTIONALLY LEFT BLANK FOR HARDCOPY VERSIONS OF THIS DOCUMENT



Chapter: **AFX_Main_0**



“Analog Active Band-Pass Phase Filtering”

The initial Problem for the “AFX” Research Project :

**This project is about designing
a very selective CW Audio Filter.**

**In C.W. (morse-code) radio operations
we may have three signals within a 300Hz audio passband.
Typical signals may be 650Hz, 700Hz , 750Hz.
Commonly we listen for a 700Hz target signal tone,
but we may also hear signals +/- 50 Hz, +/- 150 Hz, +/- 250 Hz,
which can make accurate copy of the target signal difficult.**

**Therefore we design Narrow CW Audio Band-Pass Filters,
to pass only the 700Hz target tone +/- 50 Hz (BW=100Hz).**

**Frequently, adjacent signals are 30 dB louder than the target signal
and these strong adjacent signals need to be attenuated
for clear hearing of the morse-code message signal.**

**Having several Morse Code signals at nearly the same audio pitch
is Very confusing to the ear/brain.**

**Our ear/brain system can only focus on one of them
thus, we need to filter for the 700Hz signal in the pass-band.**


**Our “AFX” analog passband filtering method
may be described as ‘phasing-out’ the odd signals
and ‘phasing-in’ the desired signals ;
ie, by controlling / comparing / differentiating the phases
of the many signals passing through the circuit.**



**Our “AFX” analog design is comprised of modular sub-sections
which could be utilized as stand-alone stages in other applications.**

Our “AFX” analog design functions with out computer processing.

Chapter: **AFX_Main_0**

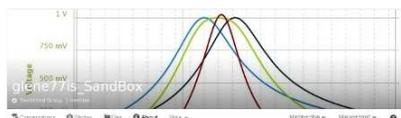Radical Analog Designs for 'CW' narrow filtering circuits



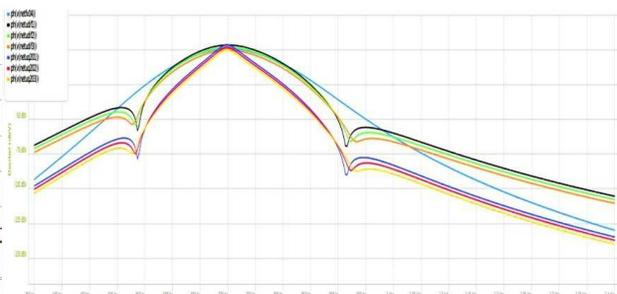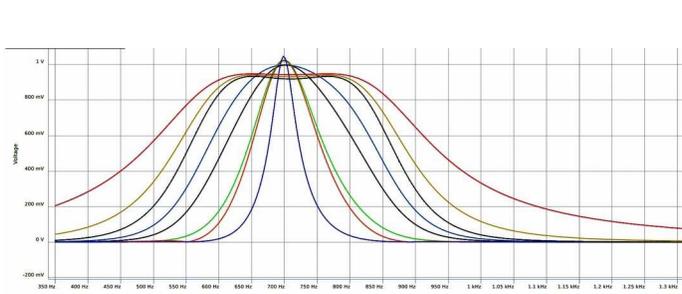


all about Analog Active Filters
and Electronic Technology and Ham Radio
circuits for Receiving CW Morse-Code

Modules in the "AFX" Analog Signal Processor

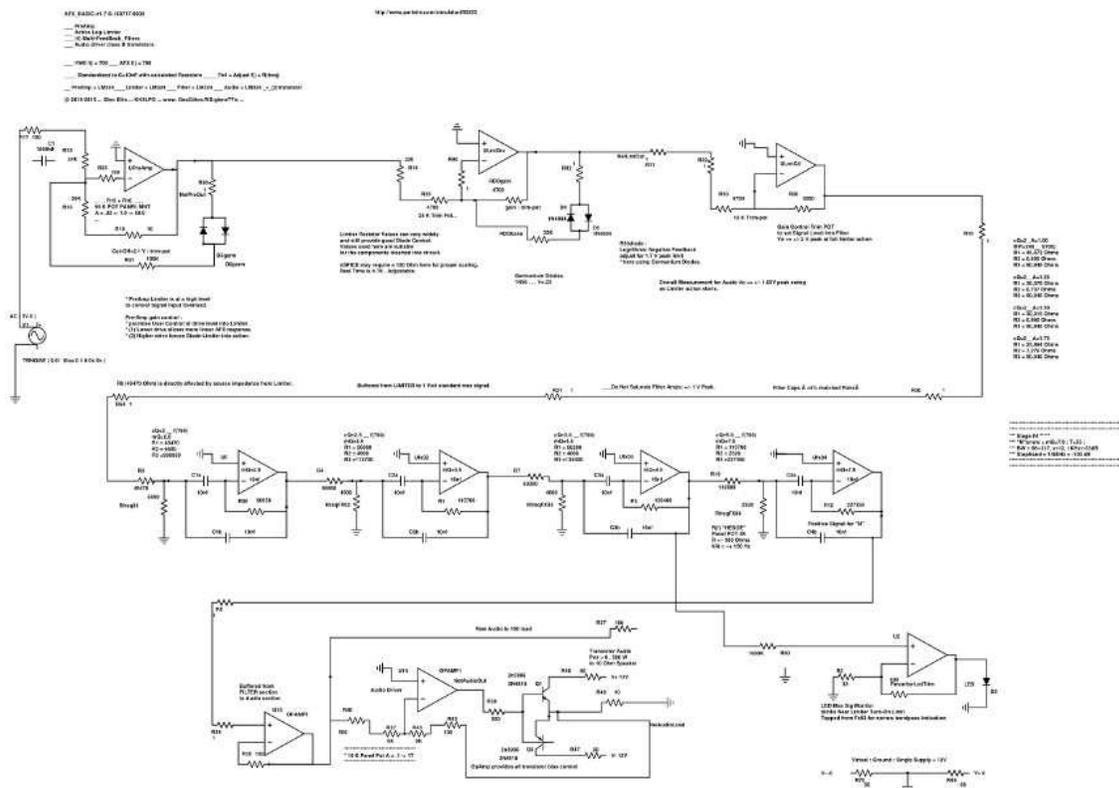1. Pre-Amp-driver with Over-Load-Limiter
Roofing Dual-Channel+Differential Filter
2. Active-Log_limiter
3. Quad-MFB Band Pass audio filter (Resonant)
Differential-Phase Filter (Double-Notch = Non-Resonant)
6. Audio out 0.5 W class-B

Circuit-1: the "AFX" B.A.S.I.C. Simple Schematic

where it all started simply
without Roof-Filters,
without Phase-Filtering.



Examine the modular function blocks:

- (1) PreAmp
- (2) Active Log-Limiter
- (3) Quad MFB resonant Active Band-Pass Filters.
- (4) Audio amp
- (5) Level Indicator .


Below are the **Functional Blocks** of the General AFX circuit development

*** The following pages are an Index into the **Modular Stages that Build the AFX**



the **Pre-Amp and AFX Roofing-Triad-Differential Filter**
(see page: AFX_Main_1_Roof_)

AFX_RLFADIQB-v10-pbare-S-7-160906-2110

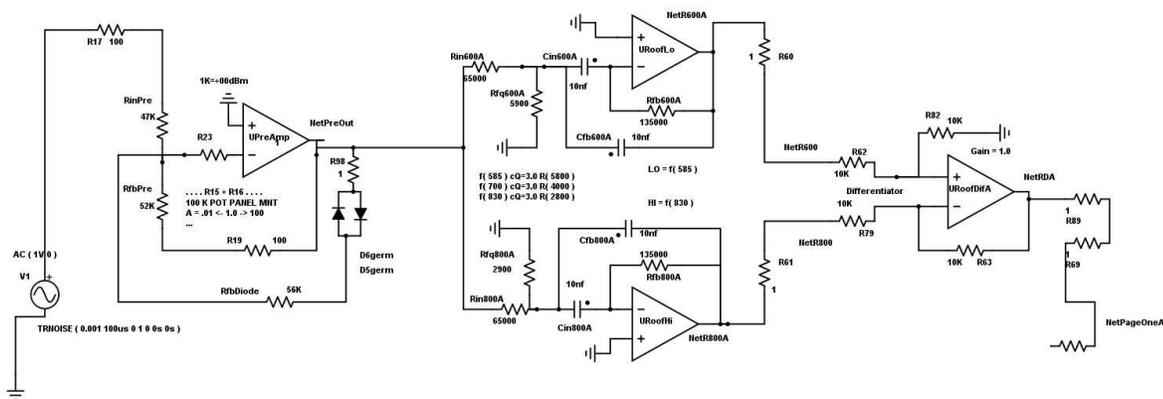


*** **Pre-Amp with Over-Load Limiter.**
*** **Dual Channels 600Hz and 800Hz driving the Differential Final stage to produce a 700Hz Roof Signal Output.**



the **AFX Active-Log-Limiter** :


(see page: AFX_Main_2_Limiter_)

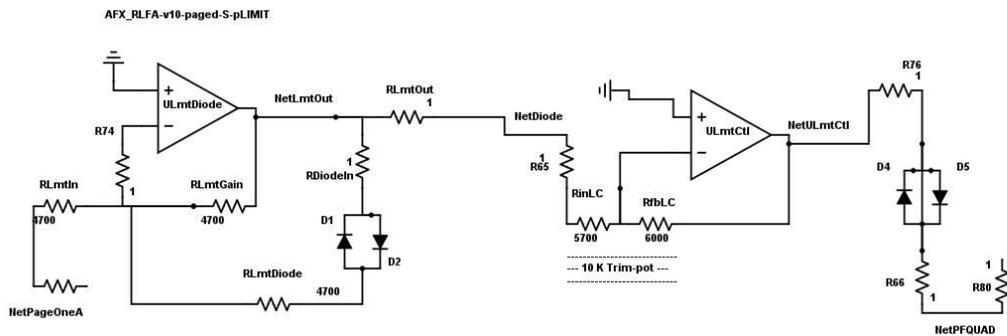

The Negative FeedBack has an additional R(series).
The R(series) adds to the combined “Diode-Internal-Resistance”
and “Diode-Dynamic-Impedance”.



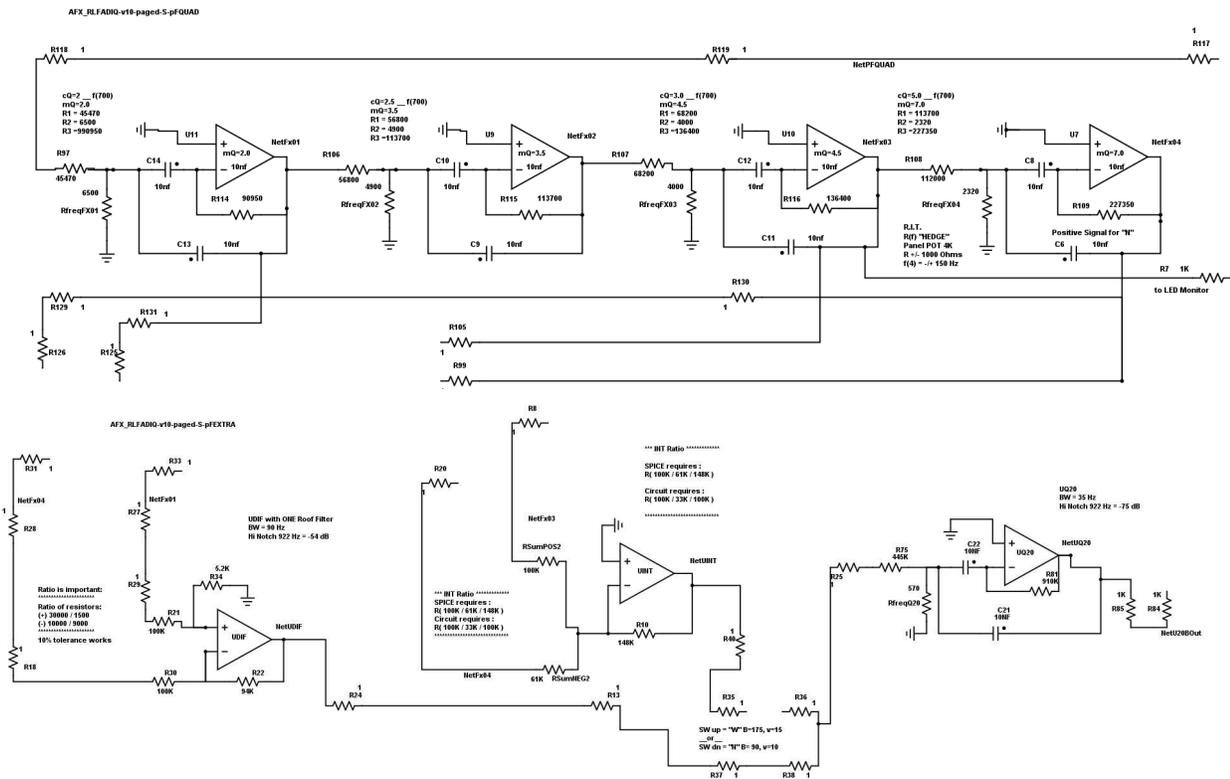the **AFX Quad-MFB Filter** with the **Non-Resonant Phase-Filter Dual-Notch module** (see chapter: AFX_Main_3_Filter_)




When the Roof-Triad-Differential-Filters, and the Quad-MFB-Band-Pass Filters, and a final High 'Q' filter are all combined, then this Differential-Phase-Filter can produce Dual-Notches at -98 dB Variance = 7 Hz sideband spread per dB attenuation .



AFX Audio Driver

(see page: AFX_Main_4_Audio_)

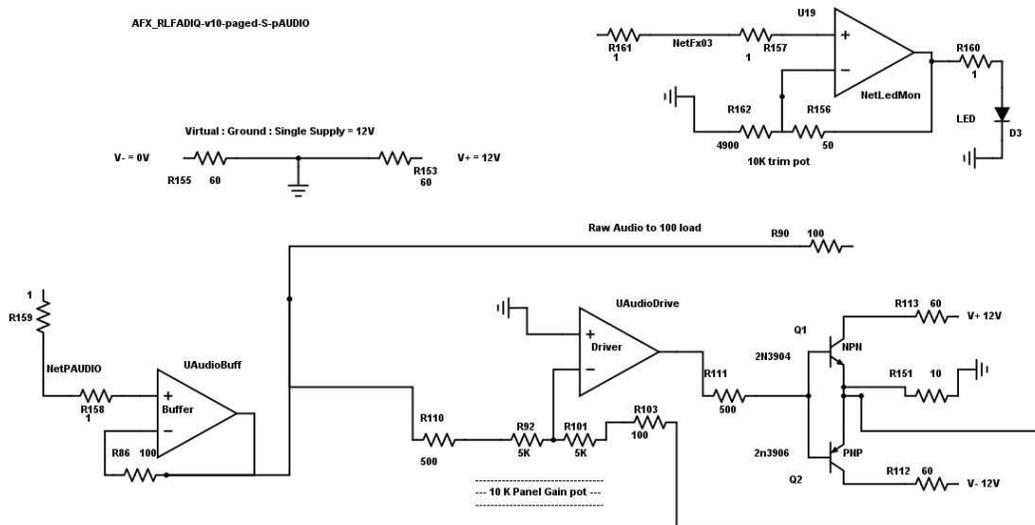

Simply a raw Cutcher Audio Amp (without the base-bias)

V(audio) output has increased third harmonics.

Above :
Functional Blocks of the General AFX circuit development



Chapter: PreAmp + Roof-Triad-Differential Filter



*** Triad of Dual Channels and Differential Final


- *** test signal is $V(\text{signal}) = TR(\text{noise})$ signal from ngSPICE
- *** Differentiated Signal Output is 330Hz wide at -3dB
- *** and $f(\text{center}) = 700\text{Hz}$
- *** SideBand Falloff is -27 dB per octave cumulative for each triplet-stage ; ie, 350 Hz = -27 dB; 700 Hz = 0 dB ; 1400 Hz = -27 dB for each triplet-stage.

The preliminary OPA stage is basically gain control with limiter. Low Impedance Out.

First Roof Stage: High Impedance Input Normal $V(\text{input})$ is from a Transceiver's audio output .

Since the signal is well above noise level at this point, we wanted to prevent pop-corn radio band noise from shocking the Roofing-Filter and Active-Limiter stage.

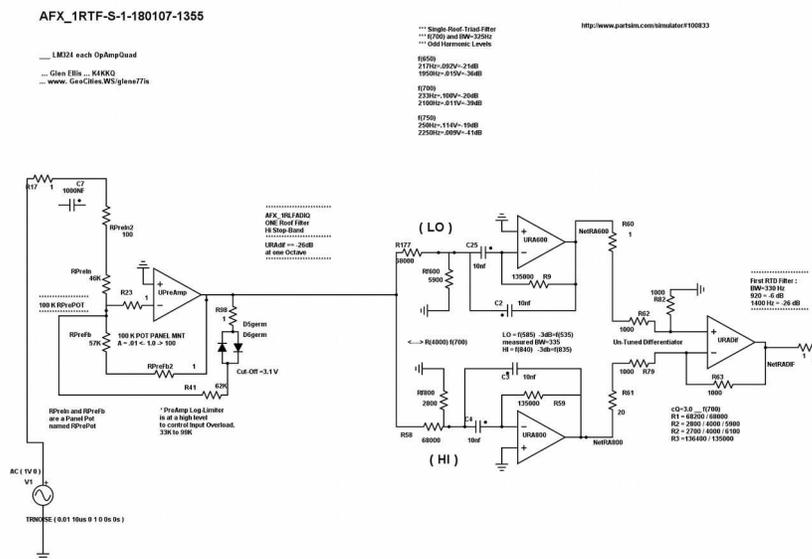We included a PreAmp with Log-Negative-FeedBack function, Purpose of Gain Control is to deliver enough $V(\text{out})$ through the Roof-Triad-Filter on into the Active-Limiter stage so that the Active-Limiter module can be forced into Limiting Level.





Functional Process of the “Roof-Triad-Filter”:

We split the V(input) into two paths:

- * The “High” Filter is tuned to 800 Hz approx. See schematic.
- * The “Low” Filter is tuned to 600 Hz approx. See schematic.
- * These two signals are Subtracted by the Differential Amp.

(1) This Single Roofing Triad-Filter circuit produces f(700) a flat-topped (BW = 330 Hz @ -3dB) signal with sideband attenuation of -27 dB per Octave .

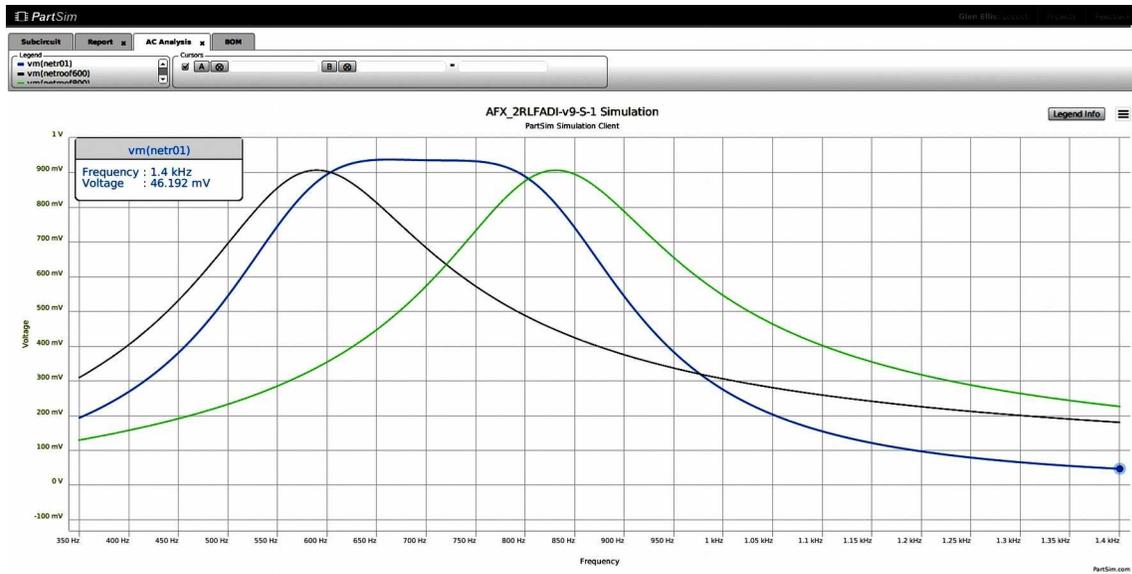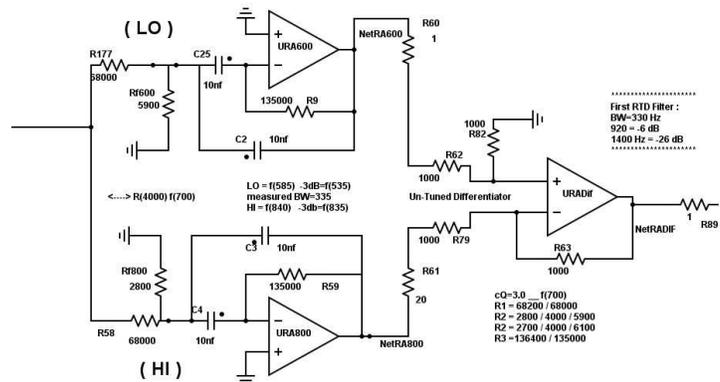(2) The Roofing Signal output has “symmetrical” waveform This reduces intermodulation distortion within the following “Active Limiter” module.



- *** Roofing Filter BW=300Hz, with Wide, Flat Top.
ie, 350 Hz = -27 dB; 700 Hz = 0 dB ; 1400 Hz = -27 dB
for each triplet-stage.
- *** Low Impedance Output.


Description : **Single Roofing-Triad Filter circuit :**

*** Roofing Filter BW=300Hz, with Wide, Flat Top.

*** Sideband FallOff is -27 dB per octave;

"v" = 32 Hz band-width expansion per dB attenuation.

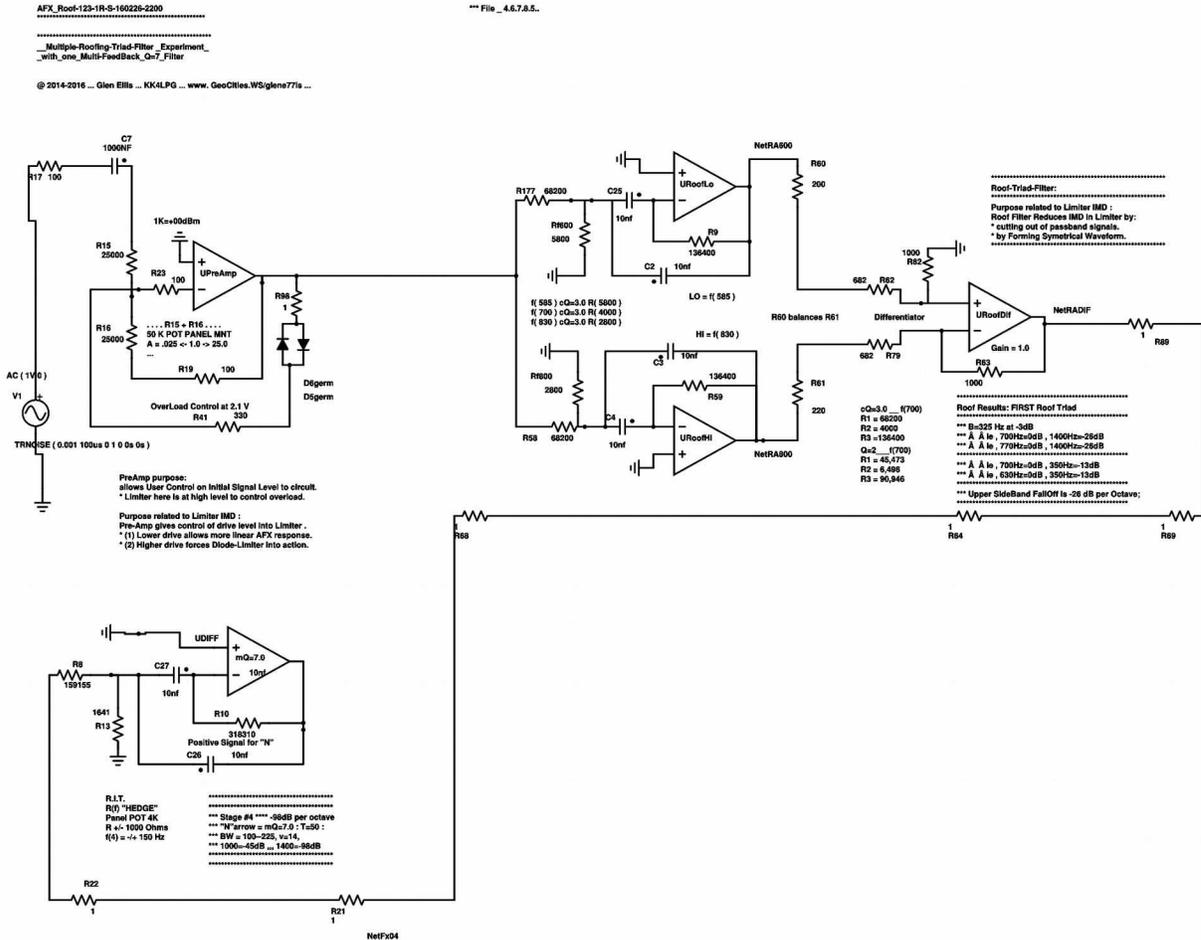"v"ariance = sideband slope of best fit is calculated by :
 ((BW@-12dB) - (BW@-3dB)) / (9dB)



Simply run this Single Roofing-Triad-Filter circuit before any standard CW audio filter circuitry. The Single Roofing-Triad filter can be sequenced (1, 2, 3 stages) for a summing effect.

Triple Roof-Triad Filter circuit :


*** $V(\text{signal}) = TR(\text{noise})$ from ngSPICE and $f(\text{center}) = 700\text{Hz}$

*** File_4.6.7.a.2.

AFT_Roof-123-3-6-160226-2200

 Multiple-Roofing-Triad-Filter_Expemint_
 With_one_Multi-Feedback_Co7_Filter

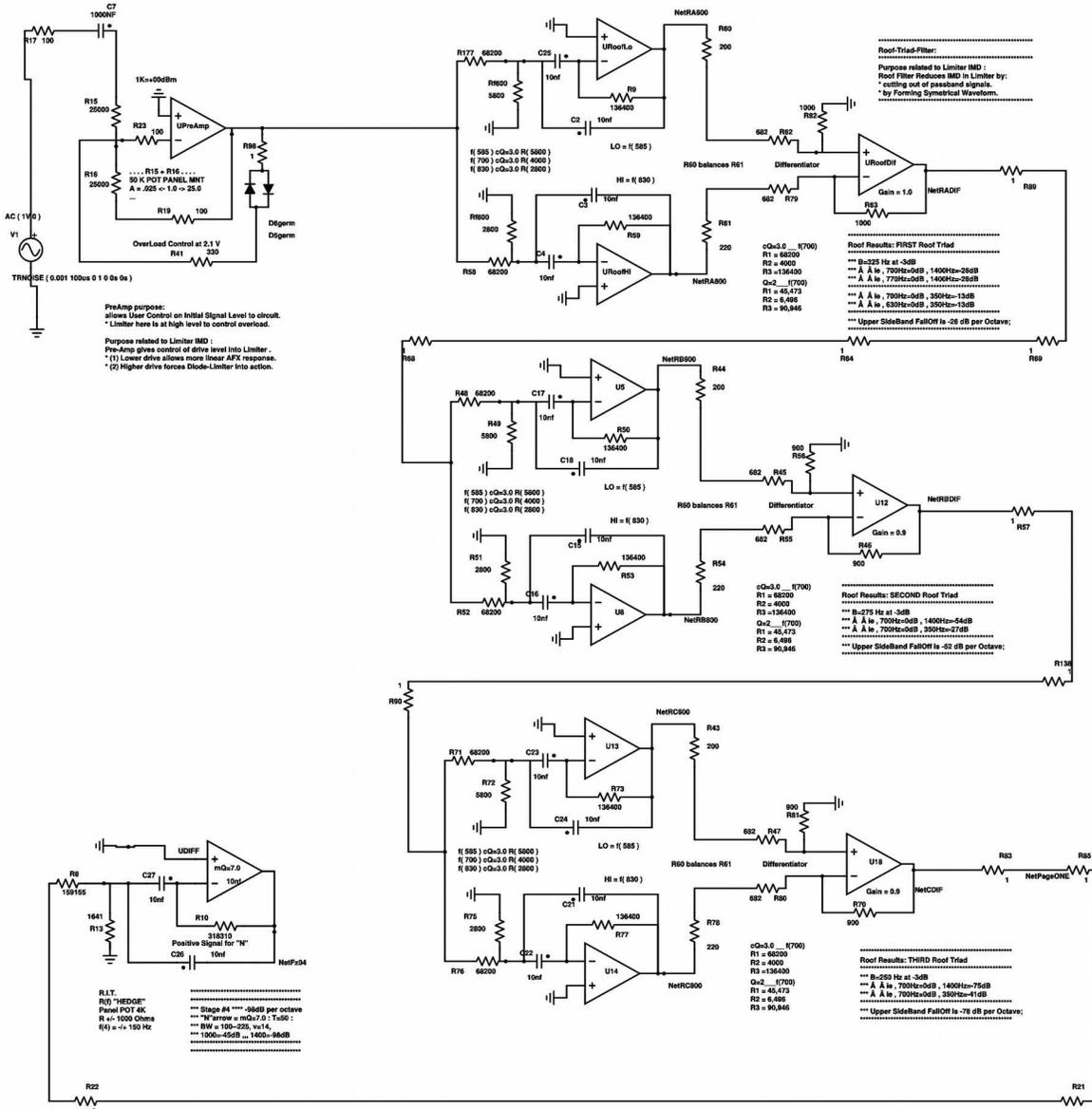 © 2014-2016 ... Glen Ellis ... KK4LPG ... www.GeoCities.WSsiglene77is ...




*** Stacked Triad-Roof-Filter

= Differentiated Signal is about 250Hz wide at -3dB

Triple Roof-Triad Filter bode plot :

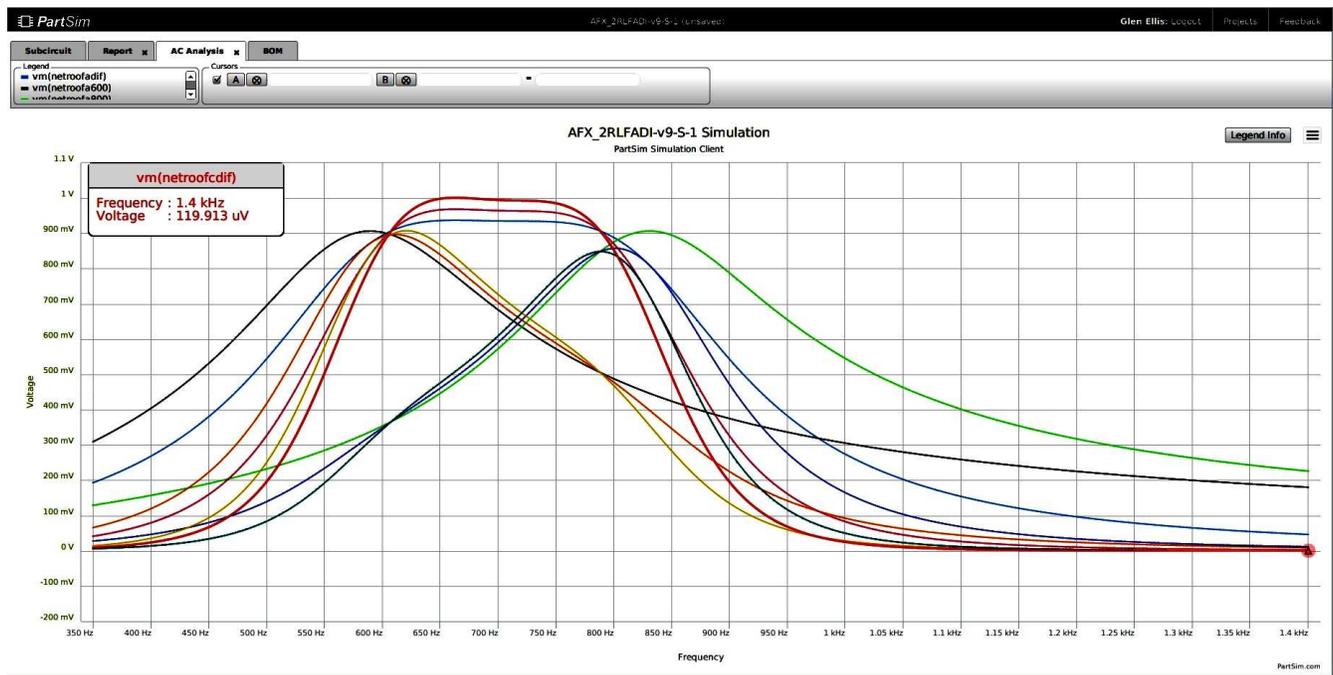- *** Sideband FallOff is -78 dB per octave
ie, 350 Hz = -78 dB and 1400 Hz = -78 dB (red trace)
- *** Stop-Band = -78 dB to the limits .



Results of Stacked Roof Triad Filters

Roof Results: FIRST Roof Triad

design BW=325 Hz at -3dB
*** ie , 700Hz=0dB , 1400Hz=-26dB
*** ie , 700Hz=0dB , 350Hz=-13dB
*** SideBand FallOff is -26 dB per Octave;

Roof Results: SECOND Roof Triad

design BW=325 Hz at -3dB
*** ie , 700Hz=0dB , 1400Hz=-54dB
*** ie , 700Hz=0dB , 350Hz=-15dB
*** SideBand FallOff is -54 dB per Octave;

Roof Results: THIRD Roof Triad

design BW=325 Hz at -3dB
*** ie , 700Hz=0dB , 1400Hz=-75dB
*** ie , 700Hz=0dB , 350Hz=-18dB
*** SideBand FallOff is -75 dB per Octave;

*** Cumulative Results after the Sharp Filter
*** cumulative measured results : Q=7
*** cumulative measured -98dB per octave
*** BW = 35 @ -3dB , range 35---126, v= 10,
*** 1000 Hz=-75dB ,,, 1400 Hz = -110 dB

Preliminary Info about 'WHY' to use a Roofing Filter :

- *** Transient Analysis showing Time Domain Phase data.***
- *** The 'black/blue' is the signal noise injected for testing.***
- *** The Noise signal has random frequencies,
very little 700 Hz C.W. signal.***
- *** The Roof filtering action is the 'green' smooth trace.***
- *** This is a most basic idea behind
a Roof-Triad Filter.***
- *** Roof-Triad Filter controls Common Mode noise from the radio band
and minimizes IMD in signal sent to the Active-Limiter stage
by producing a "Symetrical Waveform Signal".***

- *** Center band 300 Hz wide
is free from narrow-band phase-shift/phase-delay.***
- *** Only Sidebands outside of the 300 Hz center band are supressed
to minimize Limiter InterModulation-Distortion (IMD).***

*** a **First Reason for using a Roof Filter :**

*** The Vinput "aSymetrical" Noise signal
is converted into a Voutput "Symetrical Signal."

*** **Symetrical signals produce far less InterModulation Distortion
during Hard Limiter Action (in the Active Limiter stage).**

*** **The Noise Signal Common Mode energy
is canceled by the Differentiator.**


*** **See the full "AFX" circuit for the context of this Roofing Function.**

*** Black and Blue trace is Random noise signal injecting common-mode signals.

*** These have been filtered by the 600Hz and 800Hz filters.

*** The **Green** trace is the Differentiated C.W. signal Vout without any Common Mode Noise.

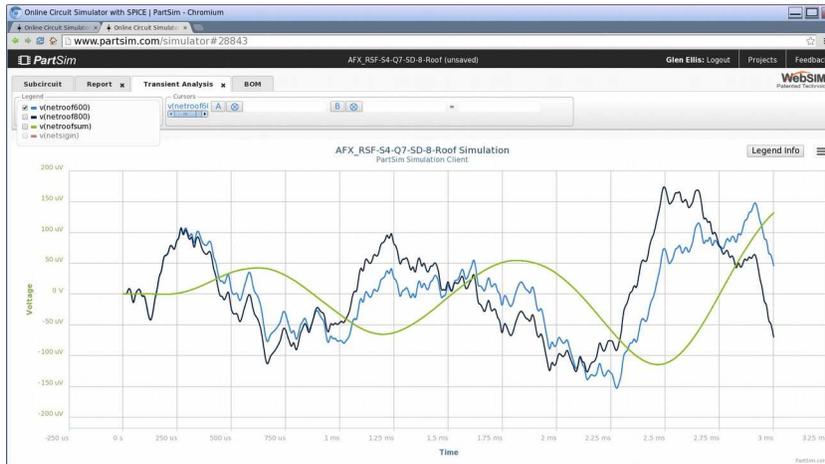*** The **Green** trace shows the combined 600Hz and 800Hz signals centering on 700Hz.



*** **Notice** that the Vinput "aSymetrical" Noise signal
is converted into the "Symetrical" Voutput Signal,
balanced on 0V line and phase-aligned.


*** This is the same action that occurs in an All-Pass Filter;

*** "Symetrical" signals produce far less InterModulation Distortion
during Hard Limiter Action in the "Active-Limiter" stage.



*** See the full "AFX" circuit for the context of
this Roofing Function and the Active-Limiter.

A Second Reason for using a Roof Filter :

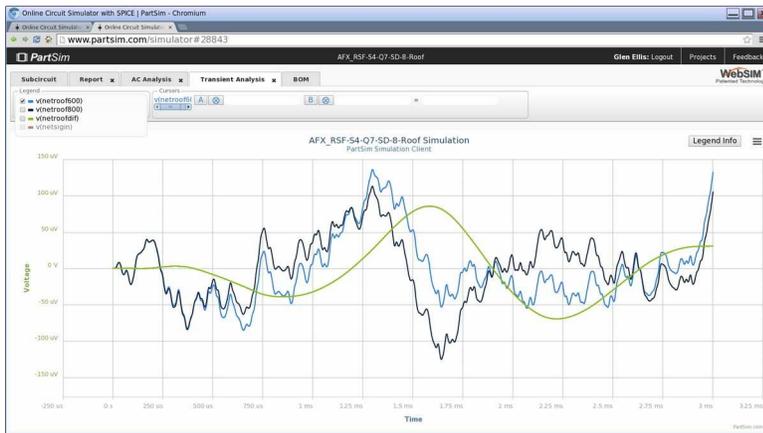- *** Differentiated Signal is about 300Hz wide at -3dB
- *** which attenuates much Out-Of-BandPass signal, and possible overload IMD in the Active-Limiter stage.
- *** The wide BandPass has little effect on the Phase Relations of the 'target' center-of-passband information signals.



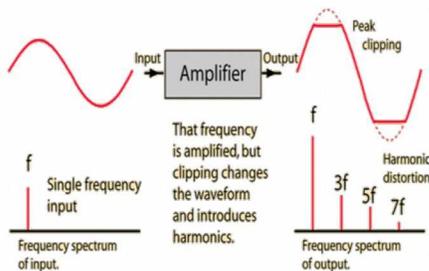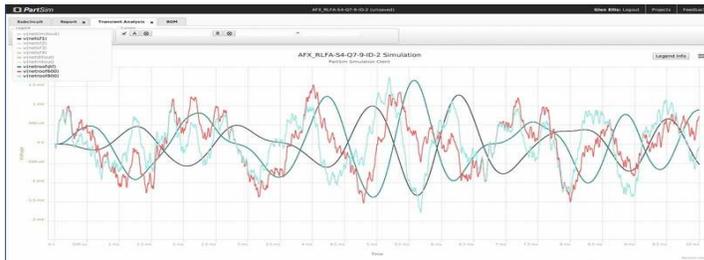Example of Noise Signals passing through stages of Roof-Triad-Filters.



(fig source unknown)
 Example of Inter-Modulation Distortion Effects at saturation in a Limiter circuit.

Do "Exotic" amplifiers even exist? - ResearchGate.

Available from:

https://www.researchgate.net/post/Do_Exotic_amplifiers_even_exist
[accessed Dec 17, 2015].

(Regarding a query about final purpose of the Roofing Triad Filter)

First off, the preliminary stage is only gain control.

The Higher Filter is tuned to 800 Hz. See schematic.

The Lower Filter is tuned to 600 Hz. See schematic.

These two different signals are Subtracted by the Differential Amp.

(1) This Roofing Filter circuit produces a flat-topped
(300 Hz @ -3dB) signal
with sideband attenuation of -27 dB per Octave.

(2) The Roofing Signal out has symmetrical waveform.
That is the most obvious function, for this one triad stage.

This Roofing and the total of the AFX project functions
within the context of Amateur Radio C.W. (morse-code) operations,
to produce narrow pass-band filtering, making use of analog phase-sensitive filters.

Looking at the whole AFX circuit,
I am working with phase relations amongst signals that are surrounding 700Hz,
feeding an Active Log-Limiter, and four MFB bandpass filters, and a final Differential untuned-filter.
The overall AFX circuit object is
to produce a Double-Notched Narrow-passband Audio Signal,
centered on 700Hz.

The Roofing Filter is for clarity in CW operations,
where in I need to reduce the wide sideband signals,
and form symmetrical waveforms for the Limiter.

The quad filter and Differential are used to produce a Narrow bandpass,
We need to subtract two particular phase related signals
to produce double -48dB notches at plus/minus 230 Hz
around 700 Hz.

The above numbers are aprox. to simplify the description.

I hope the two attached plots will assist directly.

I use the larger AFX circuit daily 'on the air',
and there is a simpler version we put on the market.
The whole project is at my website linked below.
We found this to be an interesting and effective analog project,
with clarifying suggestions by Dr. Barrie Gilbert, Analog Devices, Inc.
and much commentary by engineer/professors on ResearchGate.Net.

Glen Ellis

added: attached a schematic with more readable detail.

I should note that i did run a series of experiments
using analog sequential circuits
comprised basically of the same high and low filters,
and also using a simple Summing stage, and also a simple MFB $Q=2$ passband at
700Hz
... but found much better results using current parallel + differential 'triad' filter.
Much of this information is on my website.

The use of the differential stage and the phase-sensitive approach
has intrigued me and caused me to stop
and 'put on the robes of the electron' as Barrie describes the intuitive analysis.
The concepts involved were not immediately apparent to me,
and I had little descriptive math from my readings,
and no models to guide.

The project as part of a long term interest,
with many approaches designed, Spiced, and prototyped,
and tested with real-time C.W. on-the-air contacts
and analyzed via critical O'scope monitored listening.
Eventually, all designs were passed through ngSPICE
and re-developed to these published stages.

quote taken from :

Do "Exotic" amplifiers even exist? - ResearchGate.

Available from: https://www.researchgate.net/post/Do_Exotic_amplifiers_even_exist
[accessed Dec 17, 2015].




Chapter: **Active-Log-Limiter**

Intro:

AGC : uses feedback to ensure that the output signal always has a certain amplitude, whereas a

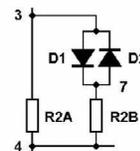LIMITER : merely ensures that the output doesn't exceed a certain amplitude.



Log-Limiter circuits based on personal designs from 1975, from consult with Dr. Joseph Laughter, Bio-Med-Instrumentation, University of TN, Medical Units, Memphis, TN.

Ref: http://en.wikipedia.org/wiki/Diode_modeling

Note: Basic Log Diode Limiter is a single stage , Negative-Feedback , Germanium Diode , nearly instant response design.

R(series with diodes) adjusts limiting level in combination with R(feedback gain).

Germanium Diodes are 'matched'.


***** (!) We apply this "Anti-Parallel Diode"**

in order to obtain a full-wave audio effect.

One Volt Input can be adjusted to One Volt Output at onset of Limiting, or as needed throughout the following circuitry.

Standard "normalized" Working Signal Voltage is 1 Volt, for 'testing' all stages of AFX circuit at one time.

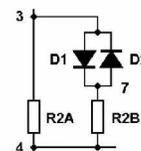The V(out) Limiter stages varies from 1.7V up to 2.24V.



Resistors in series will push the Diode Turn-On Curve up the scale, to the greater than 1V range, which is the author's choice for Standard Operating Voltage.

R(limitdiode) 777 Ohms can be varied up towards 3333 Ohms for higher turn-on curves within this circuit.


Logging Diodes are Germanium and measure 0.23 V , 'matched' by comparison , using the diode measuring circuit on the author's VOM (Amprobe AM-270).

Below:

Graph of the “Advantage of Germanium over Silicon” diodes.

***** Softer Knee produces much less InterModulation Distortion during Limiting Action.**

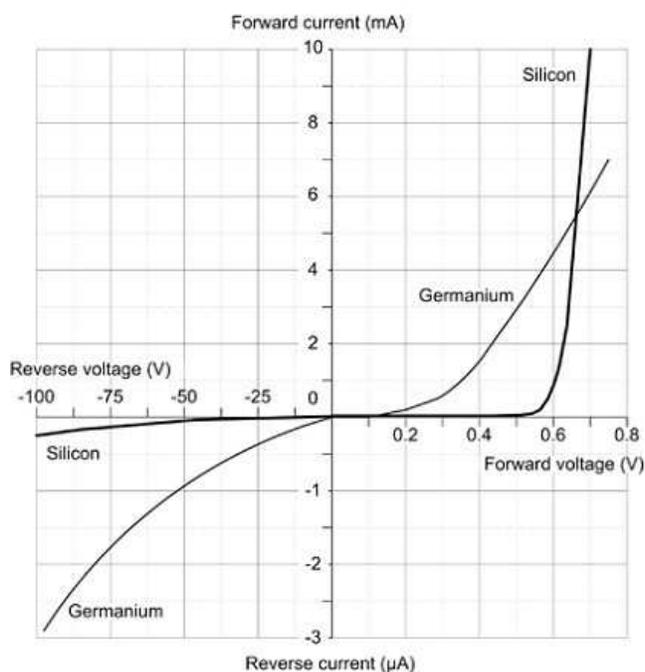***** This a dynamic affect is produced by diode forward current conduction, and varies widely with the particular diode internal impedance, and varies widely with the particular circuit impedance.**



(((Germanium provides Lower Slope on load curve than silicon)))

(((Germanium produces Less InterModulation-Distortion during limiter action.)))


(((Germanium diodes produces Less Odd-Harmonic Distortion during limiter action.)))

(source of fig unknown)

Below:

Note that Diode Conduction (limiting) occurs at all levels of current flow. The author has observed (measured) this from 1 micro-Volt upward to 3 V in test circuits. (below: author's Log-Amp circuits presented on chapter for " [Notes from University of Tennessee](#) .

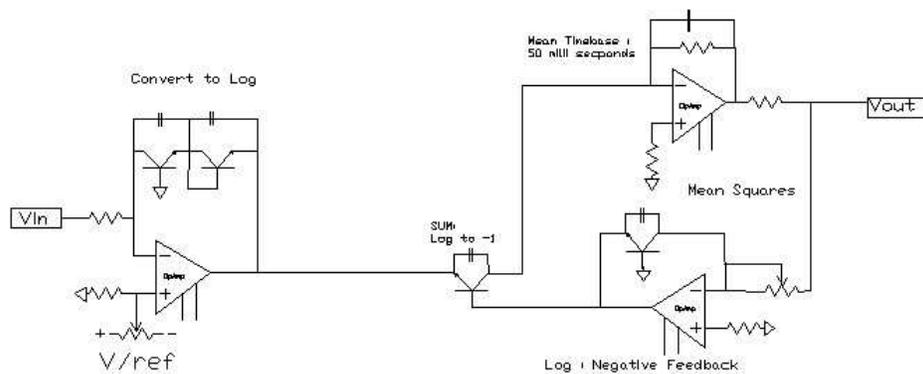True R.M.S. Calculating Amplifier, Glen Ellis, UT/STIM, June82.



ET_True_RMS_Calculating_Amp_Drawing2a.dwg

In common Limiter circuits, this effect is used from the 0.5V forward to 0.7V forward range for Silicon diodes, at aprox. 10 milli-Amp current.

In author's Active-Limiter circuits, this effect is used from the 10 micro-Amp to 10 milli-Amp for matched Germanium diodes.

This circuit was just one of six advanced circuits prototyped/tested/submitted/approved for graduation, 1982.

Background on the author's Active Limiter circuit :

There are two stages in the AFX version.

(1) The First stage is the actual “Limiter”.

In General, the Negative FeedBack has an additional R(series).
The R(series) adds to the Diode-Internal-Resistance
and Diode-Dynamic-Impedance,

...

Stated this way :

$$V_f = V_K \log (I_f/I_s(T))$$

where “ I_f ” is I(forward)

real world current "I"

always = $V / (R + \text{Dynamic-Impedance})$

and we are adding to the "R" .

(2) The Second stage is a simple Post-Amp

with a wide-range gain control,
which allows adjusting the “actively limited” signal
to a standard 1 Volt for the following circuitry.

In tests, the resulting combination works well , just as described :

(1) R(series) linear resistance.

(2) Diode-Internal-Resistance , dynamic and Logrithmic.

**(3) Diode-Dynamic-Impedance from the PN junction,
dynamic and Logrithmic.**

All function together to **lengthen the initial slope
(which ‘softens’ the limiters ‘attack’)**

**but will still produce abrupt “Roll-Over-the-Log”
at some upper level.**

**1 V signal works well into the Roof-Triad-Filter
and also matches the Roll-Over in the Limiter.**

**More than 1.7V pushes the Signal into the Limiter
enough to begin activating Limiter action.**

**1 V standard max signal makes run time measurements
much easier between stages/modules.**

O’scope Visual Comparision is much faster.

Same idea applies later in the dedicated Limiter Stage
with the log-Negative-Feed-Back diodes.

**Similar idea of using ~ 1 V standard max signal
applies in filter stages.**

We did Transient plots to compare various combinations, of diode bias and added-resistance, and did real circuit adjustments with O'scope to check.

For some people, it helps to verbalize this “Resistor-in-Series-with-Diodes FeedBack” as :

(1) normal Resistive Negative-FeedBack R(fb)

(2) with the Diodes limiting any signal going above the R(fb) gain setting.

**The ‘soft-limiter’ effect is desired :
(Germanium is ‘softer’ than Silicon)**

- 1) as it generates lower harmonic distortion.
- 2) as a human criteria for what the ear/brain system can hear/read more clearly.

The Roof-Triad-Filter produces a very “symetrical” signal output.

This reduces the Inter-Modulation-Distortion (IMD) created when the Limiter section is active doing 'hard' limiting ; ie, "Hard" limiting of an “Asymetrical” signal will produce more IMD and odd-harmonic distortion.

The stage for Monitoring the Limiter Action (LED (D3))

is not traced through SPICE since it does not transfer a signal. In practice, the LM324 has about 50 Ohms Z(out) and the voltage swing is limited to 4.5 V up or down by the chip itself (+/- 6 V supply) and is thusly ‘current-controlled’. . The monitoring LED runs OK as-is because the Front to Back Voltage ratings on the single LED are tolerant of this level of push/pull voltage.

These ideas were introduced to peer discussion in the below listed article.

What is the secret of diode clippers? Can we build these diode circuits in a logical manner rather than giving them as ready-made circuit solutions? - ResearchGate. Available from:


[https://www.researchgate.net/post/What is the secret of diode clippers Can we build these diode circuits in a logical manner rather than giving them as ready-made circuit solutions#view=56ff9c6693553b2e143e5750](https://www.researchgate.net/post/What_is_the_secret_of_diode_clippers_Can_we_build_these_diode_circuits_in_a_logical_manner_rather_than_giving_them_as_ready-made_circuit_solutions#view=56ff9c6693553b2e143e5750) [accessed Apr 2, 2016].

We did an earlier Limiter

which was Pre-Processed with All-Pass Phase-Rotating stages to shift Asymetrical signals to be Symetrical, at F(700) Hz, in order to reduce odd harmonic distortion as created by the instant acting diode limiters.

We observed that

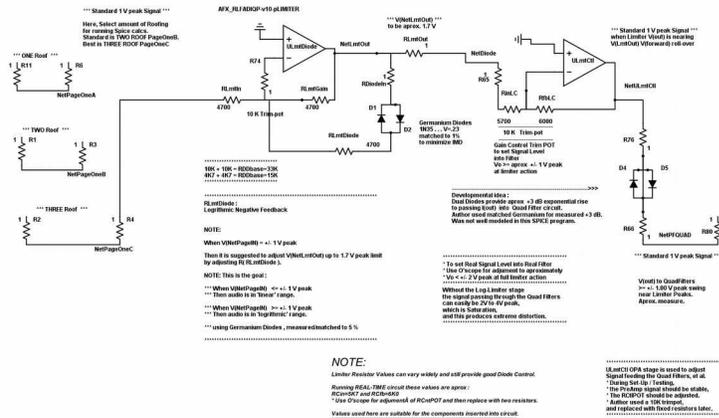Inter-Modulation-Distortion can occur during heavy limiting action, when signals are close together in frequency and/or "Asymetrical". Through experiment, it was observed that multiple All-Pass stages were not equal to the Roofing-Triad-Filter.




The All-Pass Filters method was discarded because the Roofing-Filter had measurably better results

in aligning the phases and producing Symetrical waveforms .

R(Limiter Diode) = 4700 Ohms can be varied up towards 33000 Ohms for longer linear shaped attack curves, with good diode curve at very top. Diode current flow is from aprox. 10 microAmps to 10 milliAmps.

Below:


***** Negative-FeedBack Diode-Base-Biasing applied at the grounding of the Shunt Diodes :**
This experiment produced dual levels of Diode Conduction (turn-on) at V(out).
This shows the Negative Feedback signal being used to control the base-bias of the shunt-diode matrix.
There was a difference to this more complex design, as it has two distinct turn-on curves.
Higher level pulse noise would receive tighter (quicker) diode limiting.

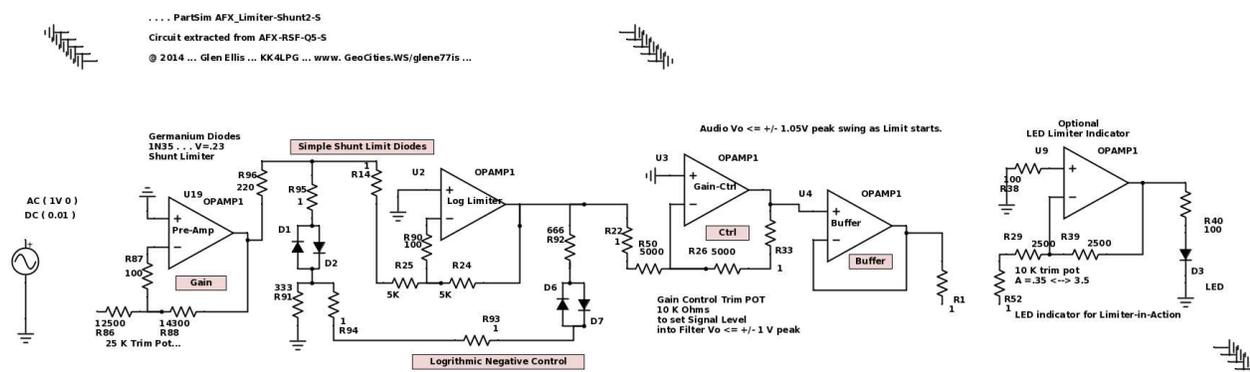


**It was discarded in favor of a simpler circuit:
 the simple Resistor+Diode Negative-FeedBack method.**

***** Transient analysis
for various combinations of Shut vs Negative-FeedBack methods.
*** These Transient plots are from above Test Circuit with
(1) Shunt-Limiting
(2) combined with Negative-FeedBack Diode Base Bias.**

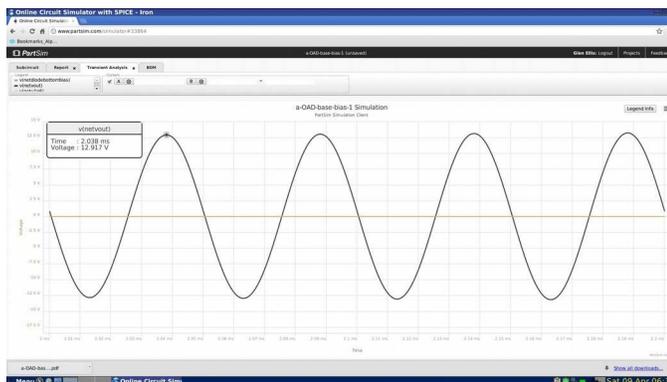***** First No Shunt Limit and No Negative-FeedBack
*** Vout max = 12.9V**



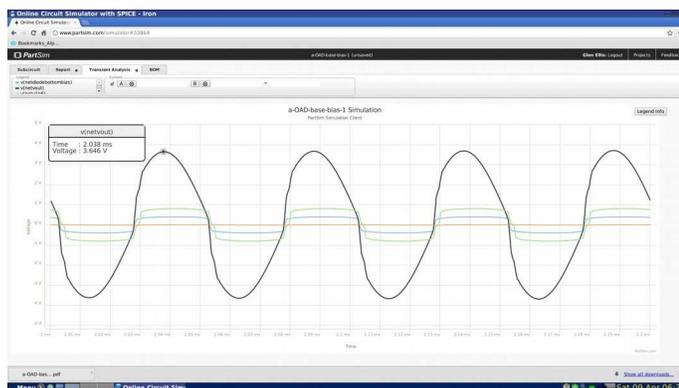***** Second, Transient for Shut Limit combined
*** with Negative-FeedBack base-biasing the Shunt Diodes.
*** Vout max = 3.6V**



***** Below**

**The Author's Pre-Amp includes an Active Log-Limiter,
whose Limit Level is based on the Gain of the OPA stage.
Gain is calculated by $R(\text{in}) / R(\text{feedback})$.**

**As the stage gain is adjusted, in normal usage,
the V(Limit-out) also changes.**

The Non-Linear Limiter is altered by a Linear relation with Gain.


**As Gain is increased, so the V(limit-log-out) also increases,
providing more head room for the possibly larger V(out) signal.
(Any pro/con to this method is up for discussion.)**

**The attached Bode demonstrates
the results of a full swing of gain from minimum to maximum.
Blue signal is V(in), and rainbow signals
are various logs of the V(in) signal.**

**We Published this in the thread "*What is the secret of diode clippers?*" -
ResearchGate.**

Available from: <https://www.researchgate.net>

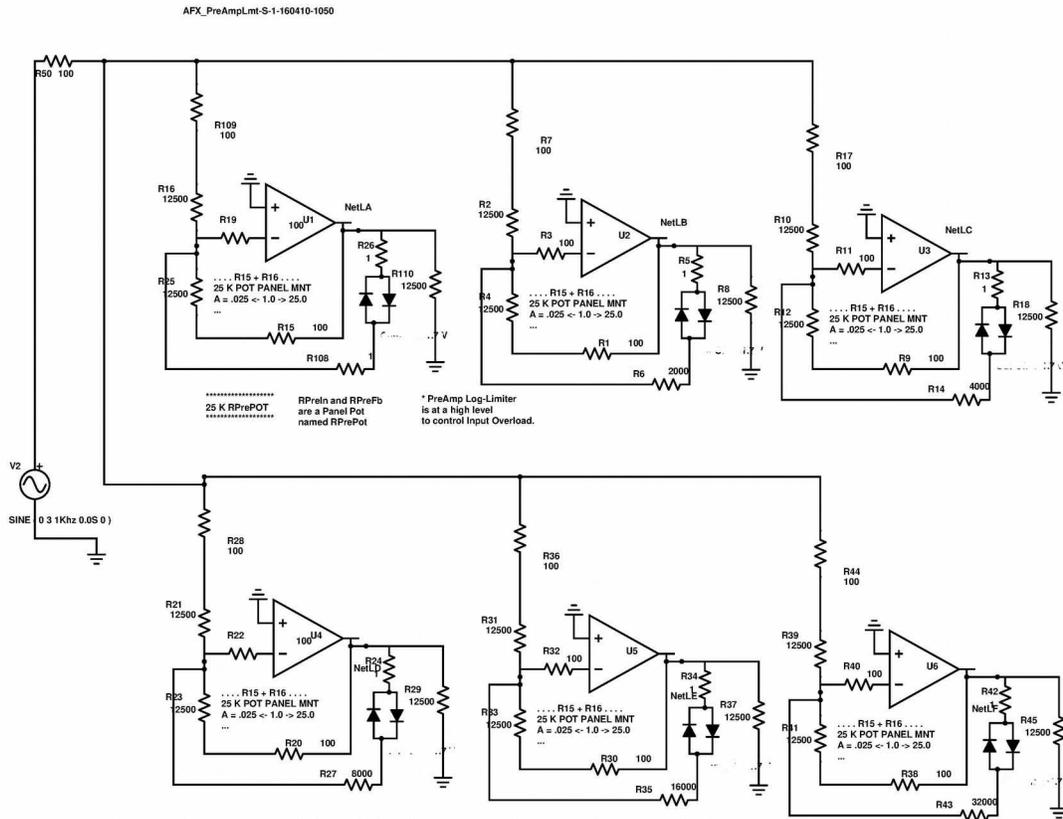Another test schematic to demonstrate variations of the Linearized-Log Negative-FeedBack method.



Below:
***** Given V(in) = 3V (blue sine trace),**
the V(out)Limiter varies from 1.7V up to 2.124V. (rainbow traces)



Below:

These Bodes show the various types of diode limiting signals and their natural shape.

Normalized to about 1V for display, as in actual use, which also aids in visualizing their effects.

Vsignal is the dark-red trace at 3V,


Vdiodes are rainbow traces taken at V(out) and are in the 1V range.

Vdiodes are actually in the .23V to .60V range

(Schottky , Germanium , Silicon)

and the circuit is adjusted to a standard 1V V(out)

in the selected circuit as prototyped.

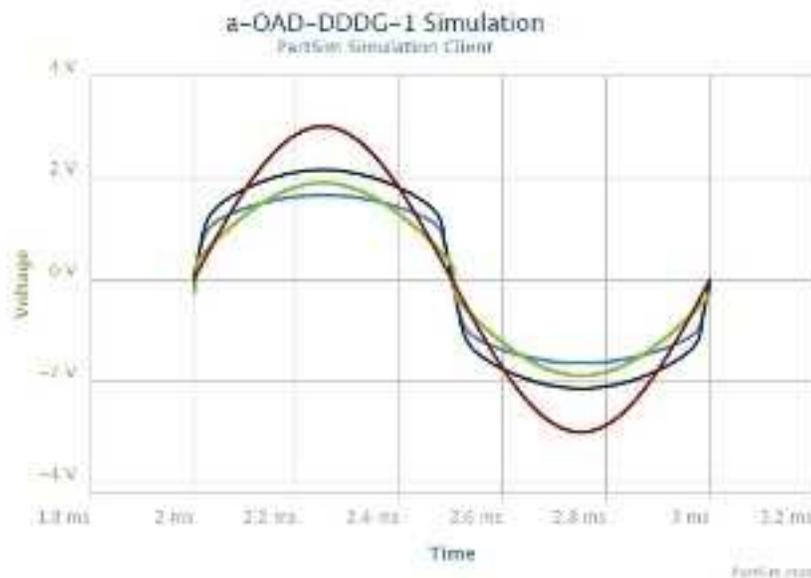

Author's Spice traces :

optimized/normalized to normal 1V standard so that the curve shape can be visually compared.

Silicon has as a sharper cut-off and Schottky has a more sloping cut-off.

The author selected the Germanium soft curve

for use in AFX Limiter stage

because the characteristic curve could be measured


and thus 'matched' diodes were selected in pairs.

Another research associate selected silicon (KC90N)

for our commercial production model.

The dark-red sine wave is the applied test signal.

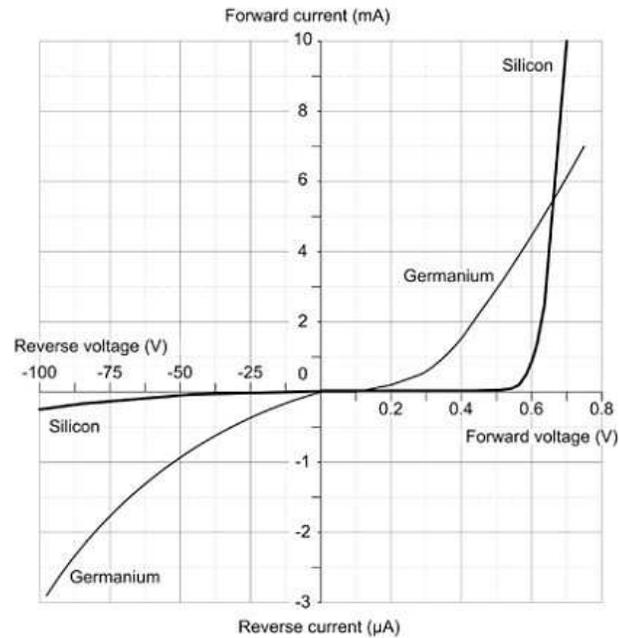Comparison of Germanium vs Silicon diodes from Data Sheets.



(graphicsource unknown)

*** Summary


Sharper Knee produces more InterModulation Distortion during Limiting Action.
More IMD means more odd Harmonic Distortion.
More Harmonic Distortion means more distorted message signal, ie, loss of information.

Author's set-up for Studying and Comparing

(1) the Simple-Shunt

vs.

(2) the Negative-FeedBack Limiters


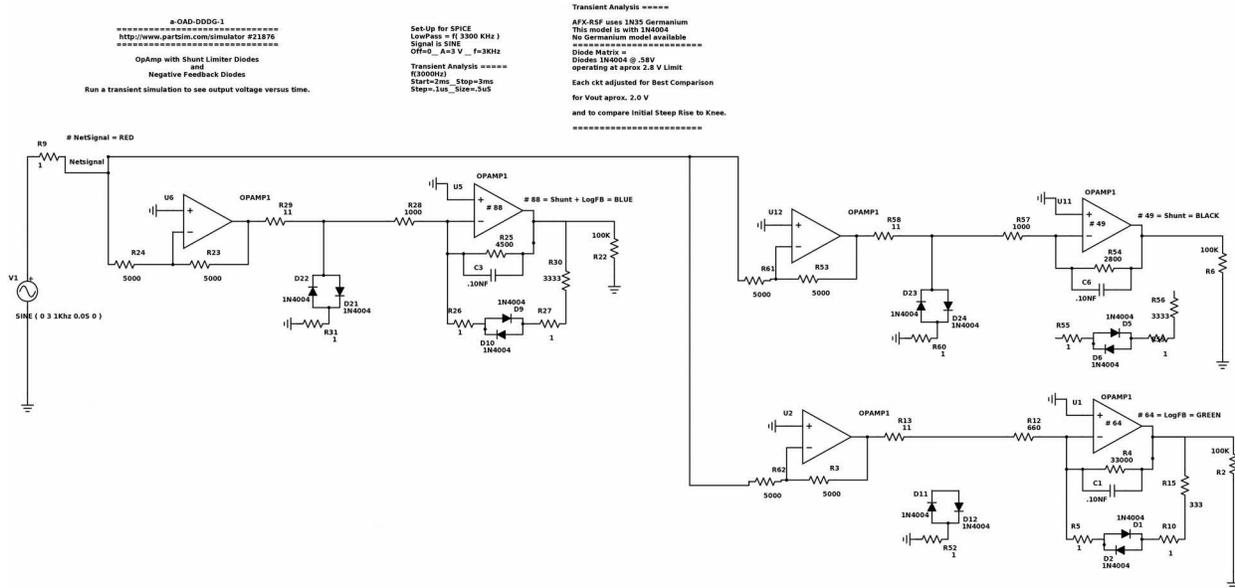


***** Below : Normalized to the standard 1 V.**

Vsignal is 3V, and Vdiodes is actually in the .23 to .60 range.

***** In a real circuit the Vout is always normalized to some standard, such as 1V out Peak, by the user.**

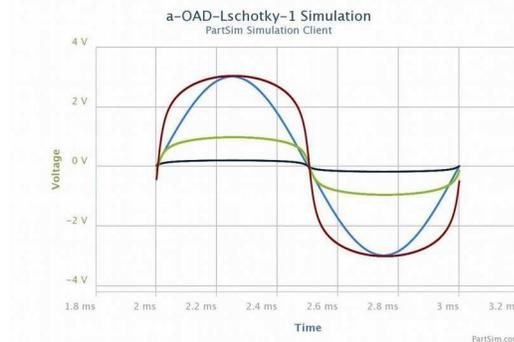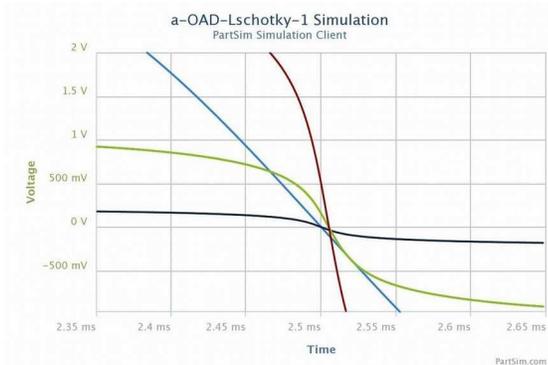***** Each type of Diode has a different Vout curve, and here they are Normalized for easier visual comparison.**



Left plot shows the 'corner curve'.

Right plot shows over-all curve. .

Blue is Sine Sig at 3 V input, for reference.

Red is Germanium Diode gain controlled to compare with the Sine Sig.

Green is Germanium Diode at the standard 1 V .

Black is Germanium Diode at real turn-on level.of 0.189 V in this circuit.

Real world Turn-On curves are relative to the actual current flowing through the 'circuit' and through 'diode'.

Thus, a diode's impedance is dynamic.

(The authors have designed working circuits,

using negative-feedback,

which work in the 10 microA through 6 milliA range,

using Germanium diodes in circuits including extra "R" .)

Note: The Author did a study of Simple-Shunt Limiting using Schotty Diode array, for "softer" log curves.




Various modules were inserted / disconnected.

Schotty show a very soft curve but were difficult to match

which is important in using "Anti-Parallel Diode" configuration.



Chapter: **Main-Filter**

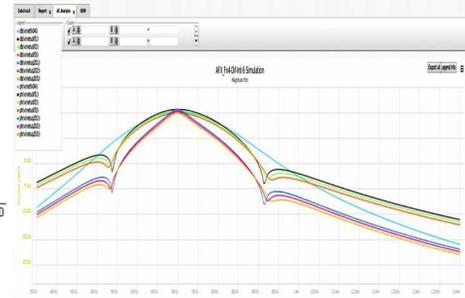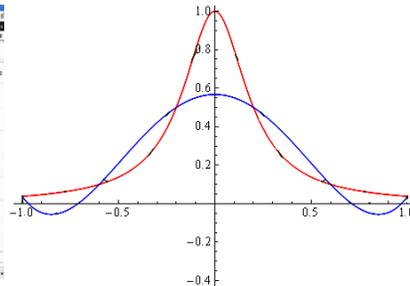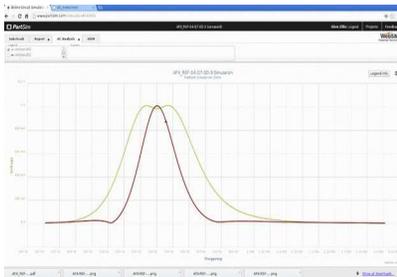

"AFX" filter circuit

This Page is about the author's AFX core filter circuit with Non-Resonant Double-Notch Phase-Filter module

Design choices in concept :

***** Simple repetitive application of Modified *Deliyannis-Friend-Multi-FeedBack* topology.**

***** Multi-FeedBack design was chosen because :**

- (1) input vs output stage impedances match well,**
- (2) single resistor frequency control each stage.**
- (3) frequency adjustments alters gain by only the square-root of the $f(\text{change})$.**

***** Phase-Filter stage for generating a Dual-Notch Band-Pass.**

Circuit : **AFX 'V'** which has the Double-Notch Phase-Filter module

AFX-3RL-V4F-D-VQ-Man-S-313-180116-0741

Specs :
f(500) Notches = 460 Hz and 810 Hz
f(700) Notches = 550 Hz and 890 Hz
f(700) Notch BW = 350 Hz @ -60dB
f(800) Notches = 650 Hz and 1000 Hz

http://www.parcimon.com/arcimon/07001

Results:


800 Hz @ 3 dB
800 Hz @ 60 dB
150 Hz @ 100 dB
150 Hz @ 120 dB
150 Hz @ 140 dB
150 Hz @ 160 dB
150 Hz @ 180 dB
150 Hz @ 200 dB
150 Hz @ 220 dB
150 Hz @ 240 dB
150 Hz @ 260 dB
150 Hz @ 280 dB
150 Hz @ 300 dB

Substrate:

Developmental Plans:
1) Add a 2nd stage of filtering
2) Add a 3rd stage of filtering
3) Add a 4th stage of filtering
4) Add a 5th stage of filtering
5) Add a 6th stage of filtering
6) Add a 7th stage of filtering
7) Add a 8th stage of filtering
8) Add a 9th stage of filtering
9) Add a 10th stage of filtering

Developmental Plans :

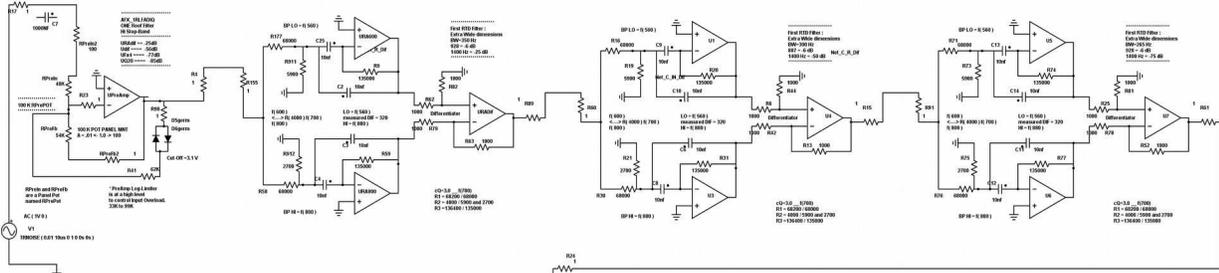1) Add a 2nd stage of filtering
2) Add a 3rd stage of filtering
3) Add a 4th stage of filtering
4) Add a 5th stage of filtering
5) Add a 6th stage of filtering
6) Add a 7th stage of filtering
7) Add a 8th stage of filtering
8) Add a 9th stage of filtering
9) Add a 10th stage of filtering



BASIC-700 Hz

Variable Cutoff Filter
Manual Control by User

Adjustable R(freq)
100 Hz = 100000
200 Hz = 200000
300 Hz = 300000
400 Hz = 400000
500 Hz = 500000
600 Hz = 600000
700 Hz = 700000
800 Hz = 800000
900 Hz = 900000
1000 Hz = 1000000

Notch Results :

@ -60 dB
Lo Notch = 550 Hz
Hi Notch = 890 KHz
BW Notch ~ 340 Hz
+/- = 170 Hz

Notch Results :

@ -60 dB
Lo Notch = 550 Hz
Hi Notch = 890 KHz
BW Notch ~ 340 Hz
+/- = 170 Hz

Notch Results :

@ -60 dB
Lo Notch = 550 Hz
Hi Notch = 890 KHz
BW Notch ~ 340 Hz
+/- = 170 Hz

Notch Results :

@ -60 dB
Lo Notch = 550 Hz
Hi Notch = 890 KHz
BW Notch ~ 340 Hz
+/- = 170 Hz

Note: circuit dox.
in the following diagrams for the Operational Amplifiers,
Filter resistor R2 is the R(freq) for adjusting f(center) .
R2 adjusts the primary current source into the tuned circuit.

Note:
The -1dB level is equivalent to 900 mV level .

Note:
The -3dB level is equivalent to 700 mV level
which is the usual BandWidth point.

Note: about the Non-Gaussian Band-Pass shape :
"Variance" is used to describe the "BW" vs "Q" relation.
"v" = slope of best fit for the non-Gaussian sideband shape]
[(BW@-12dB) - (BW@-3dB) / 9dB
Therefore,
v=25 is very wide sidebands (similar to low "Q")
v=5 is a very steep sideband (similar to high "Q")

Note:
All Filter stages are set to run at aprox standard 1V peak
for easy O'scope tracing.

Note:
Power Supply ByPass caps are not shown.
OpAmp Null trim pots were not necessary
in this development
with LM-324 quad OpAmp chips.

Note: Non-Resonant modules

- (1) “u-Differential” stage is the **Phase-Filter** stage which produces "N"arrow Double-Notch passband. Stage “u-DIF” will **DIFFerentiate** Fx01 with Fx04 to produce a "N"arrow Double-Notched **Phase-Filtered** signal.
- (2) “u-Integration” produces "W"ide Flat-Topped Steep Skirt passband. Stage “u-INT” will **INTEgrate** #3 negative and #4 positive signals.

Note:

These plots and specs are from PartSIM.com , ngSPICE.

Note:

Author did the build-up on ProtoBoards.
Author used this AFX daily in the radio operations, several years.
Active in-use measurements with o’scope
compare favorably with ngSPICE plots.

Schematic specs show both

- (1) the "**cQ**" calculated "Q" , specific to each stage,
- (2) the "**mQ**" measured "Q", accumulated progressively.

Below is the section about the Quad Filter

the reader should note these filter characteristics :

(1) the Quad Filters have **Gaussian Curves, normal to band-pass filter.**

(2) The u-DIFFerential and u-INTEgration Filter Stages have passband curves that **ARE NOT GAUSSIAN CURVES.**

The DIFF stage is used to create the Dual-Notch effects, et al .

The "Q" of the passband, based on BandWidth at -3dB down to -12dB does **not** compare with regular band-pass circuits.

A modified **slope-of-best-fit** is used to better describe these curves.

This is the 'variance' calculation :

$$'v' = [(BW@-12dB) - (BW@-3dB)] / 9dB = v$$

where 'variance' is a special **slope-of-best-fit** .

(3) The **Non-Resonant DIFFerential Phase-Filter stage**

produces a "N"arrow signal,

via a Subtraction Operation,

which is useful for singling out one precise signal in a group.

This module (alone) produces two -48dB notches with BW=100 Hz at aprox. 150 Hz from f(700).

This is further narrowed by the Final High 'Q' Resonant filters.

(4) The **Non-Resonant INTEgration stage**

produces a "W"ide top-band signal,

via a simple Summing Operation,

producing a flat top, and steep side-bands

which is useful for tuning/searching in a radio band.


Note :

Non-Resonant Differentiated Phase-Filtered Narrow Output

*** Dual Notch= 535 Hz & 920 Hz ,
which is loosely aprox. +/- 90 degrees from f(700) by design.

*** Dual Notch concept IS NOT the same as "I/Q" Quadrature.

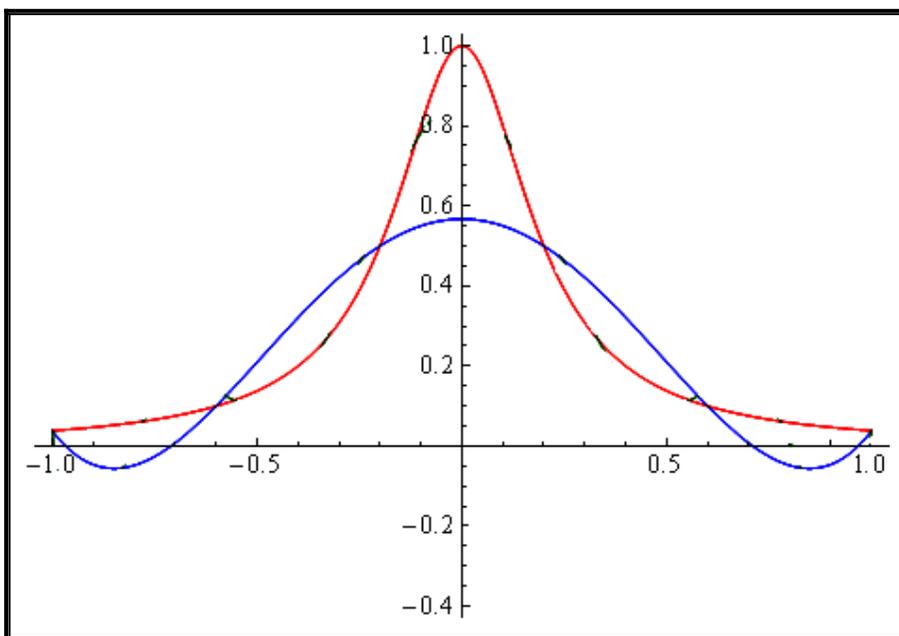*** **Below: Graphical Concept for the Dual-Notches**



Dual Notch is **developed** via
a Phase-Differentiation at the **Cross-Over Points**.
which, in this example, are approximately
where Y=+0.5
where X=-0.2 and X=+0.2 .
Other cross-over points are buried near ground level.

circuit detail:

Phase-Filter Differential Notch-Generator


Notch Results :

@ -60 dB
 Lo Notch = 550 Hz
 Hi Notch = 890 KHz
 BW Notch ~ 340 Hz
 +/- = 170 Hz

.....
 * Resistor RATIO
 (*) is 300 / 16.5
 (:) is 10 / 9

 Measured Single Roof
 BW= 530, 930
 R.Lo-Q, Notch, Hump
 R=21K, .45, .35
 R=18K, .61, .38
 R=17K, .65, .38
 R=16.5K, .61, .39 ***
 R=16K, .56, .40
 R=15K, .53, .41
 R=14K, .50, .41
 R=12K, .48, .44
 R=10K, .48, .47
 BW= 530, 930

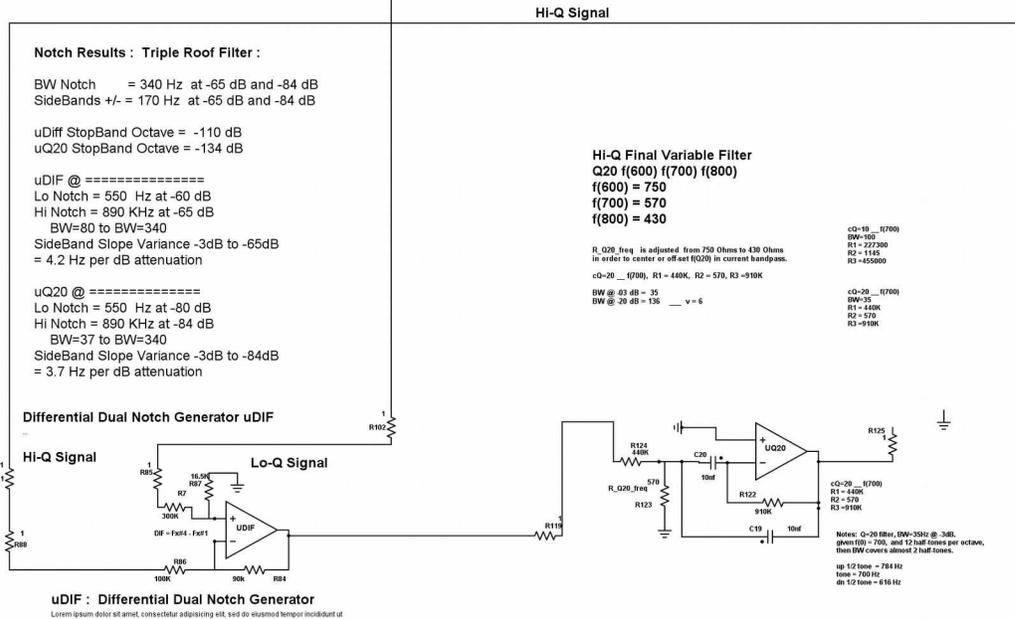 *** Diff Dual Notch ***
 * AFV has this
 * basic Resistor RATIO
 (*) is 300 / 16.5
 (:) is 10 / 9



- (1) BandPass shape is NOT gaussian.
- (2) Sideband falloff is -48 dB per octave .
- (3) BW @ -3dB = 90Hz
- (4) BW @ -12dB = 185Hz
- (5) BW @ -48dB (Notch-to-Notch) =385Hz
- (6) Notches at : 535Hz = Low Notch and 920Hz = High Notch.
- (7) NOT a Quadrature Filter by design
and NOT Conceptually related to a "I/Q" Quadrature Filter.
- (8) 920Hz is 27 dB under Fx04 band-pass curve.
920Hz is 48 dB down from 1V standard "0 dB" signal.
- (9) Variance=12 Hz via BW measured from 89Hz to 196Hz
(V = Hz passband spread per dB attenuation)
- (10) When Differential output is followed by a Q=20 filter
then then Narrow results are much enhanced.

Only the single u-Differential stage has critical components.


Band-Width Notch-Depth Measurements vary according to the number of Roof-Filters used in the actual circuit.-

Bode Plot : **Basic Wave-forms**

Single-Roof (black)

Quad-Filter sharp band-pass (blue)


Differential-Dual-Notch Generator (red).

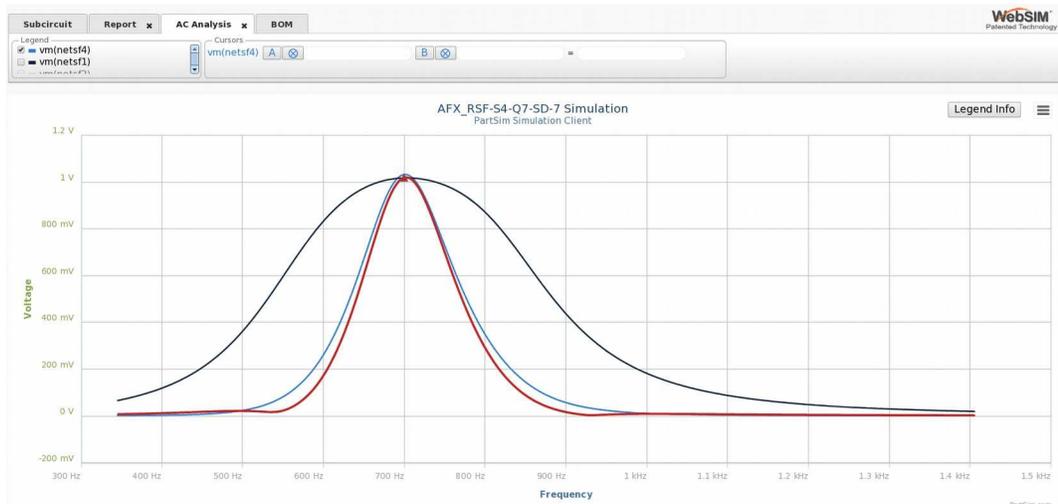

Magnitude Plot : **Basic Wave-forms**

from a Single-Roof **plus Differential-Dual-Notch Generator.**

AFX_3RLFADI-v9-S-9 Simulation

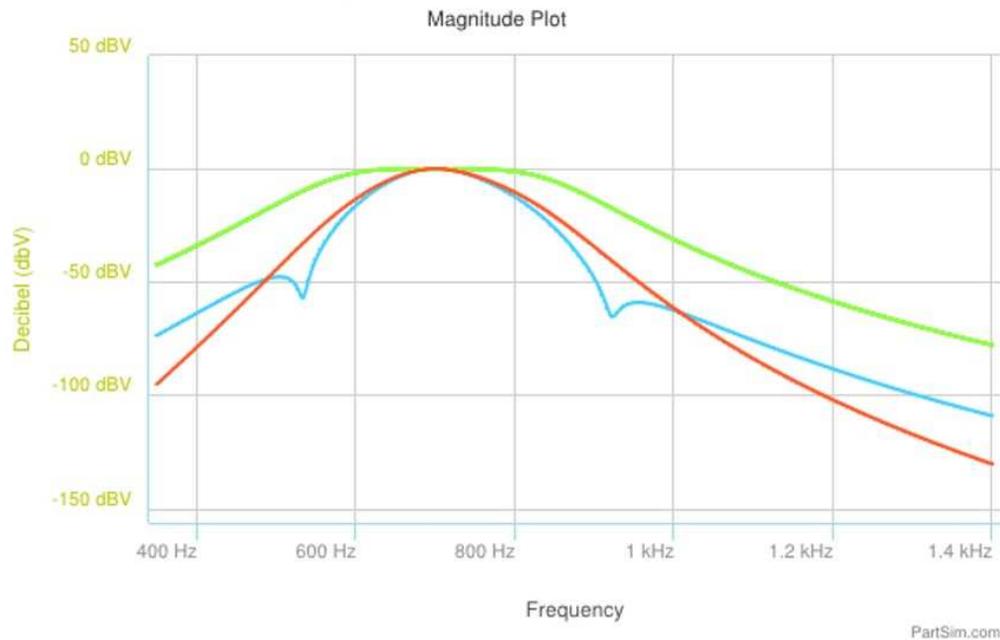


Basic Roof-Filter (green)

QuadFilters (red)

—Basic Dual-Notches dip at 48 dB. (blue)

—=== as much as -96dB Notches.

Magnitude Plot: Main Waveforms

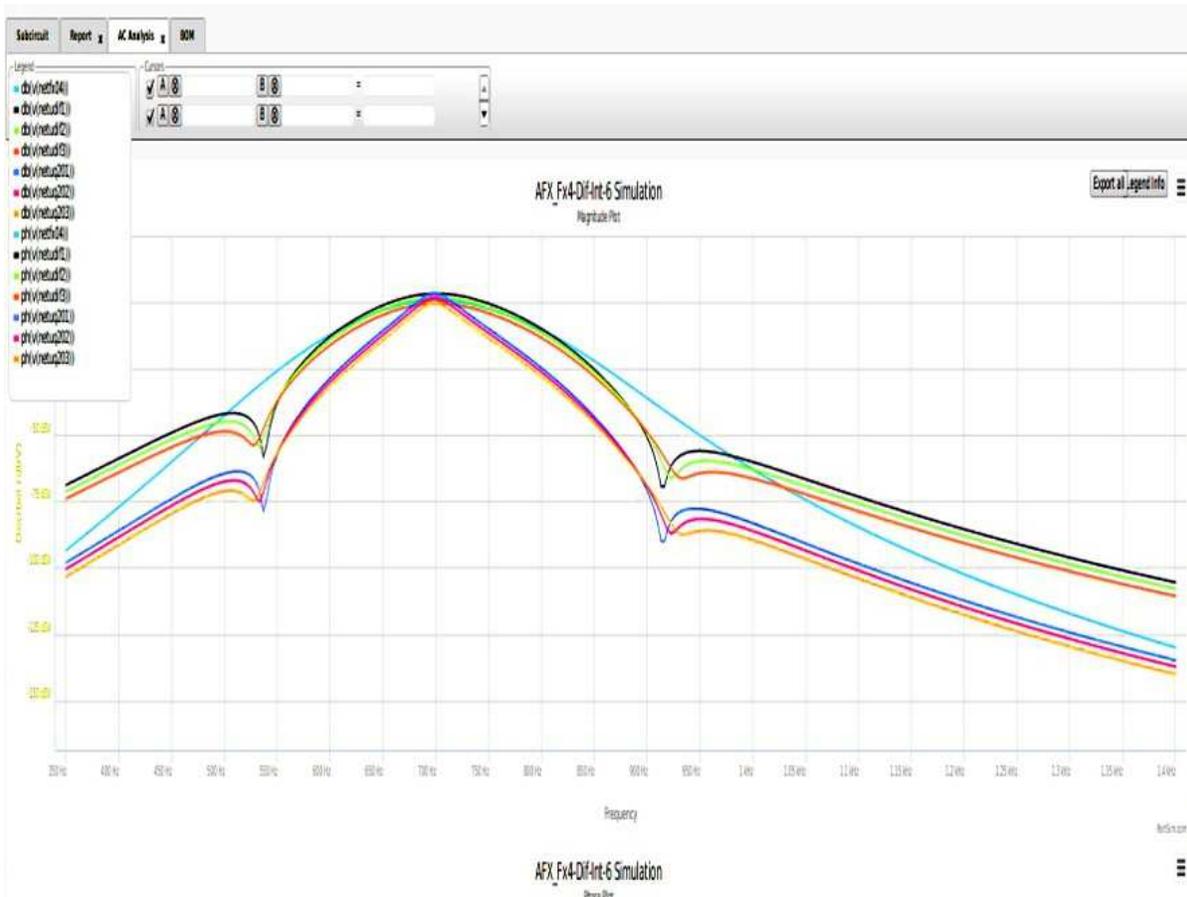

**Here: Initial Signal (blue) and three adjusted Notch settings.
Top (1) : blue trace is V(output) from Filter #4.
Upper (2) : Basic Dual-Notch, -58dB notch depth.
Lower (3) : signal has been passed through a Q=20 Filter
at -78dB notch depth..**

**Plots are from PartSIM.com and ngSPICE .
O'scope observations follow this pattern.**

***** Special Note for Plots : *******

***** F1-F4+DIF = Notches are -25dB below Fx04**

***** DIF :**

***** BW=86--190__v=12**

***** Notch at 533 @ -50dB**

***** Notch at 920 @ -50dB**

***** StopBand= -48dB to limits**

***** F3+F4+INT**

***** BW taken from 176-and-369__v=-22**

***** StopBand = -19dB to -42dB**


Excellent **Digital Model** has been provided by professor Dobromir Dobrev ... Ph.D ... **Bulgarian Academy of Sciences**

This digital documentation was developed following discussion on ResearchGate.Net .

Developed using an entirely Digital Analysis of the AFX circuit concept.

It is remarkably close to the Analog Spice Results that the author obtained.

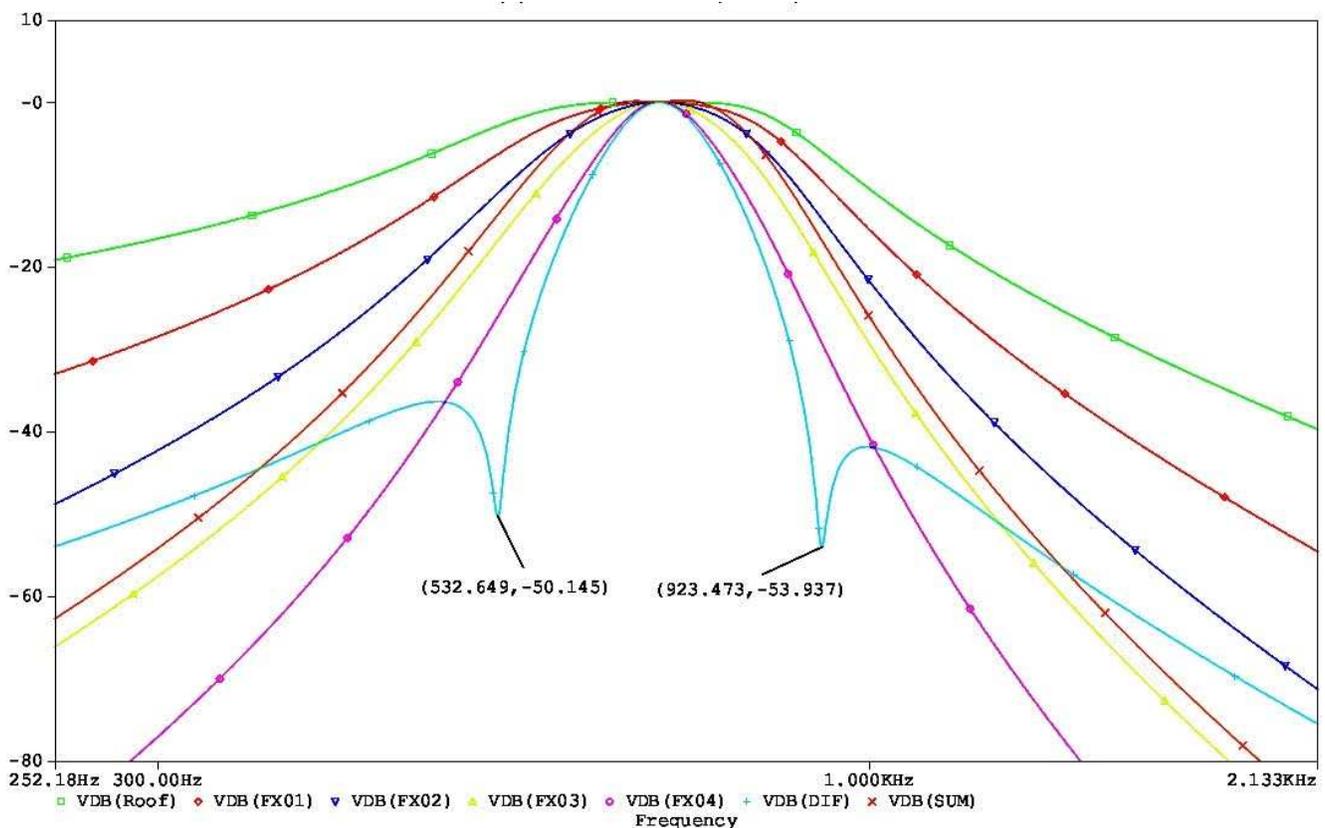At the -48dB level, the digital results are the same as the author's analog development.



More Discussion: about the Standard "AFX" Circuit

Summary:

- 1) Bullet-Proof Construction and Easy to tune just using a VOM and ordinary signal source off the (radio) air.**
- 2) Very steep side-band skirts .**
- 3) very low passband signal level at 1000 Hz.**

*** Initial PreAmp has wide gain in order to drive the Limiter into action.

*** Roofing Filter is very wide Band-Pass => 300 Hz t -3dB.

*** Log Diode Limiter is a single stage, instant response,
Actively Driven by user control in Initial Pre-Amp stage.

*** LED indicator shows "Diode-Limiter-in-Action"
(if tapped from Fx04, then indicates the Center-of-Passband).

*** Filtering stage BandWidth Ranges :

"W"ide calculated $Q=2.5$ $BW=250$, measured "Q" = 3.5

"N"arrow calculated $Q=5$ $BW=100$ measured "Q" = 6.5

*** Quad Filter has Variable $f(0)$ in Stage #4
which acts like an RIT tuner for +/- 100 Hz
within the overall band-pass..

*** Hedge $f(0)$ by shifting the Stage #4 $f(0)$ within the source passband,
to better capture a slightly QSY signal.

*** Standard Design options :

* a Stage **UDIF** (DIfferentiating Fx01 with Fx04)
to produce a "N"arrow Double-Notched signal.

*** Optional :


* a Stage **UINT** (INTegrating #3 negative and #4 positive signals)
to produce a "W"ide flat-top steep sided signal.

* Note: the Calculated "cQ" and Measured "mQ" are shown.

* Because circuit measurements show the cumulative effect of several stages.

* the Measured "mQ" is always much higher than the Calculated "cQ"
of the sequence of four filters. .

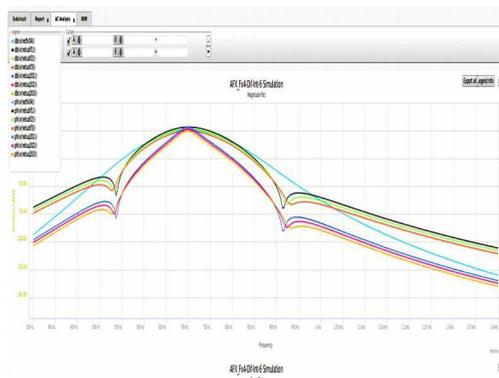* The **Cumulative Measured "mQ" is the Real-Time Signal out of this filter.**



::: Some Circuit specs:

::: 12V split supply. So, +/- 6V supply

::: LM741 & LM308 Vout max = +/- 4.2V. (only tested)

::: LM324 Vout max = +/- 5.2V (actually used in the AFX)

General Setup :

::: Set Diode Limiting at 1.25 V as aprox. Limit Function roll-over.

**::: Set Limiter V(out) = +/- 1.0V peak into audio filters ,
as approximate Standard 'max' Signal Level.**

**::: Filters run at +/- 1V peak aprox. at max. signal level.
analogous to the Log-Limiter Peak range.**

**::: Filter Stage #4,
calculated cQ=5, ,measured mQ=7 cumulative,
measured BW=100.**

This Chapter has been about the author's AFX core filter circuit

**The project is for use with Vintage and Analog QRP rigs,
such as the Heathkit HW-8**

It also provides excellent results attached to a Kenwood 830-S.



Chapter: **Audio Stage**



***** Cutcher style Audio Circuit & LED drivers**

At this point, the previous filter stages have produced a 'soft' sine-shaped CW audio pulse . All sub-harmonics and supra-harmonics have been filtered out, leaving principally a narrow filtered passband of 650 to 750 Hz.

What is needed is a "crisp" CW signal for better ear/brain function in reading the CW message. High fidelity music audio is NOT desired. "Crisp" CW pulse , extra treble, is required.

This stage is an OpAmp-Driven Two-Transistor Push-Pull Class "B". OpAmp directly drives all Transistor Biasing, which produces cross-over distortion.


Our Design introduces third-harmonic distortion , without saturating the amplifier, without compressing the signal amplitude, without losing amplitude variations between the possible multiple signals in the passband.

In radio operations with CW at $f(700)$ Hz , signals closer than 50Hz can occur and enter the passband to be discerned by the ear.

Our goal is to produce a "crisper" CW audio for better ear/brain copy.

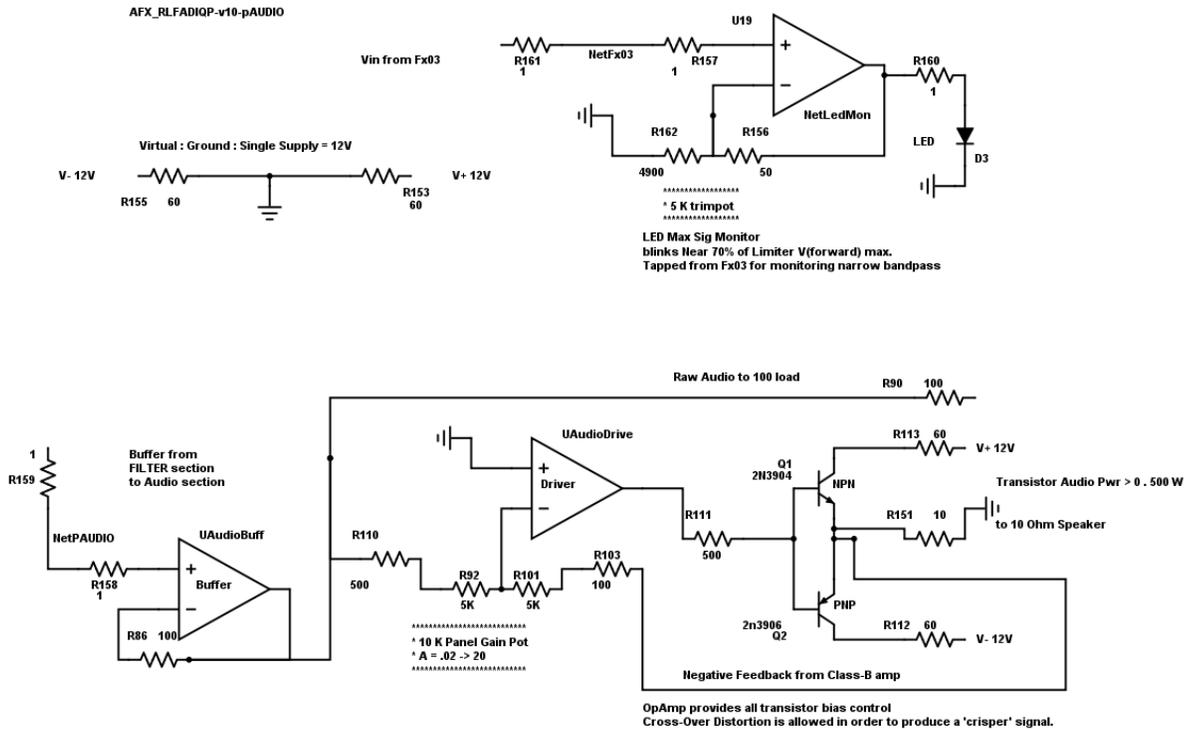***** Below: the Standard Audio Circuit schematic (with simple LED monitor on top right)**

OpAmp directly drives the Class-B audio stage, without diode-offset base-bias thus producing obvious cross-over distortion and thus producing a 'crisp' CW audio signal.




In this AFX circuit, the OpAmp Drives Two Transistor Push-Pull Class "B" produces a Saw-Tooth signal. This is a common Cutcher Amp, un-biased.

Received signal is a 'soft' sine-shaped CW audio pulse. This stage produces a distorted Audio to the loud-speaker which is a sawtooth.

Design Goal of this un-biased class-B amp is to introduce third-harmonic distortion to produce a "crisper" CW audio for better ear/brain copy.

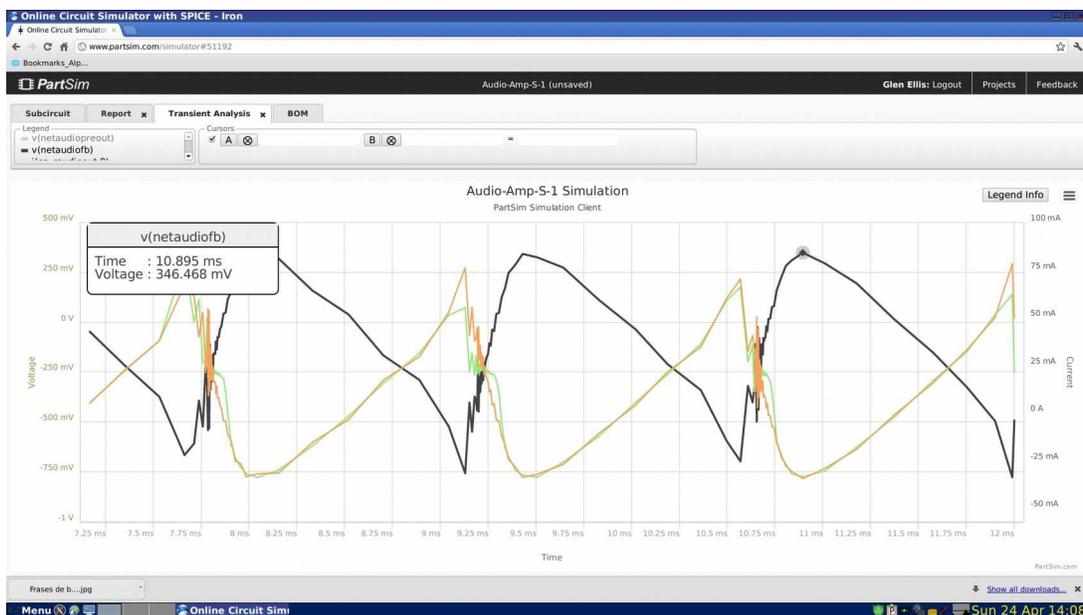The circuit produces an Audio V(out) shown in the below Transient Plot.



This Transient Plot shows the Distorted Audio Output which has more third harmonic which is a "crisper" signal to the ear.