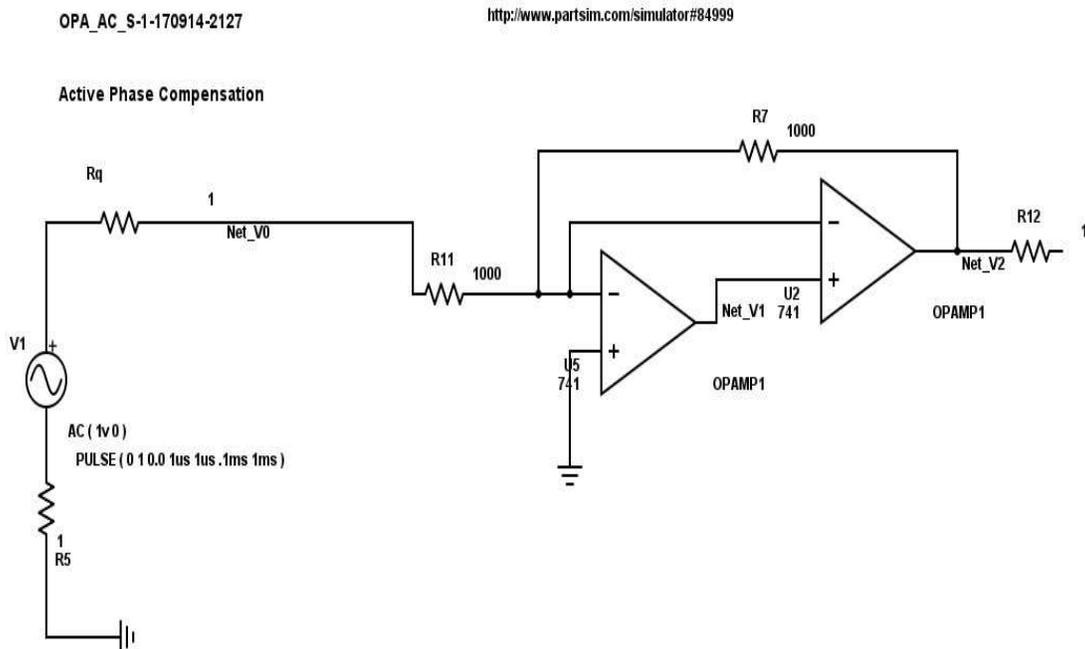


Chapter: GC_ET-OPA-AC

Circuit: Op Amp with **Active Compensation** for inherent **F3 phase shift**

Generously suggested by Dr. Barry Gilbert, Analog Devices, Inc.





Transient Plot:





Results:

Controlled F3 phase shift.

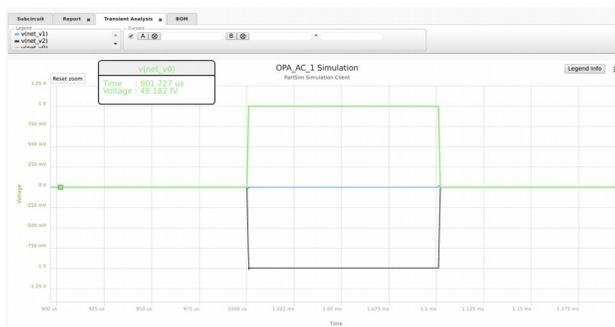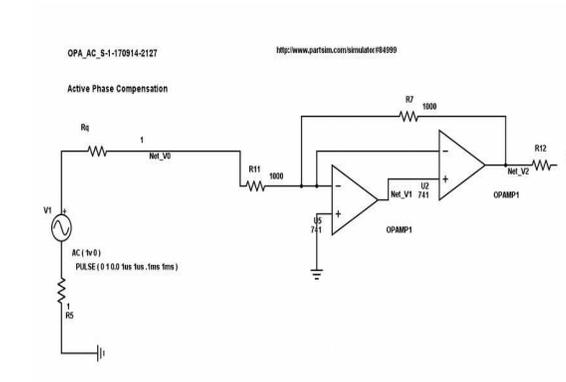Circuit: Op Amp with **Active Compensation** for **F3 phase shift** inherent to OPA



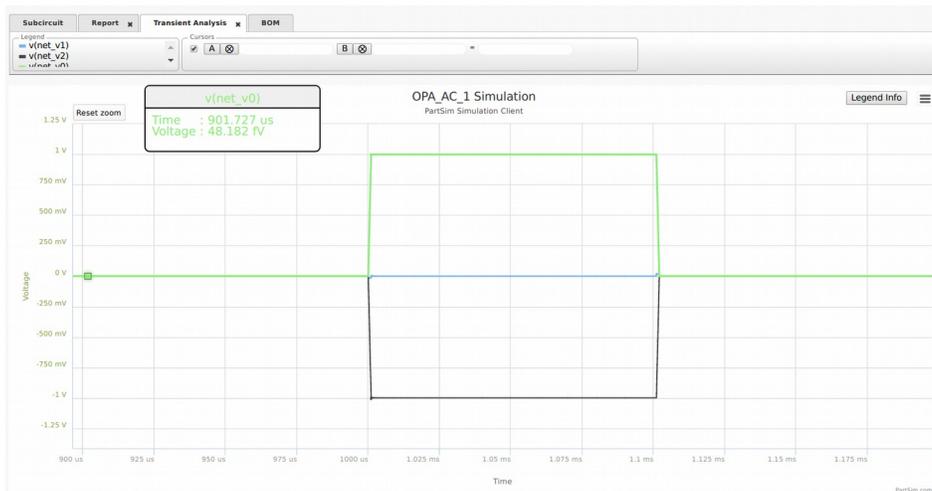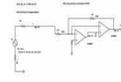

Chapter: AFX_mFilter_4_P2A



"P2" version A

Resonant Dual-Channel Audio Filters

Circuit : PC2D-CCD-100x-4P


*** The Final Narrow BandPass is BW=100 @ -3dB, and BW=150 @ -12dB.

*** 'v' = 5

*** Slope of bandpass is a variation of 5 Hz per dB of attenuation.

*** Several versions of this design have been tested, and results are similar.

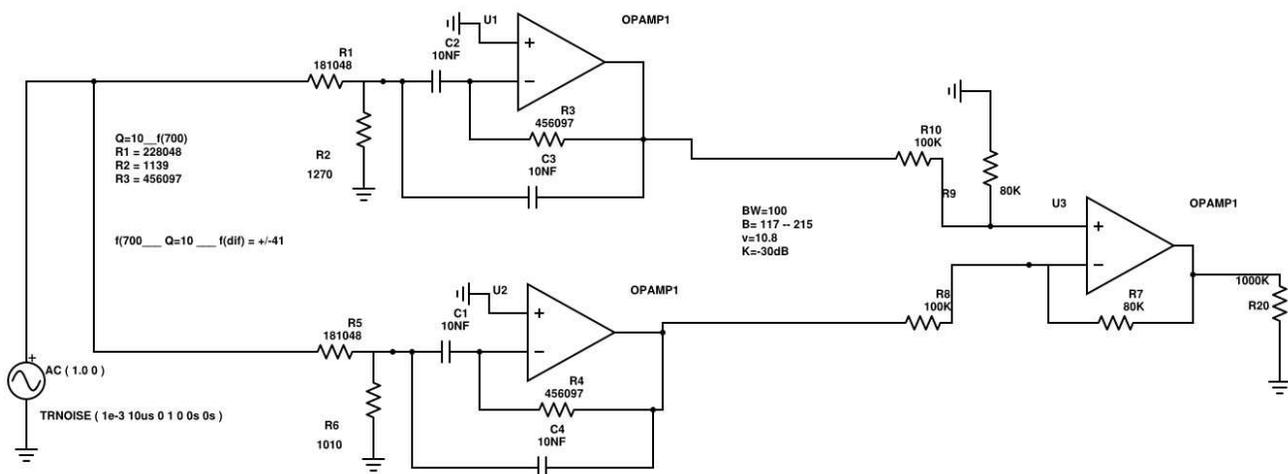
P2D-CCD-100x-4P-1-S-150623-1400
Parallel Cheby Four Pole 700 Hz
Differentiated to f(700)
Q=10 ___ f(diff) = +/- 42 Hz



Bode Plot : **PC2D-CCD-100x-4P**

***** Narrow BandWidth of 100 Hz, with 7 Hz spread per dB attenuation.**

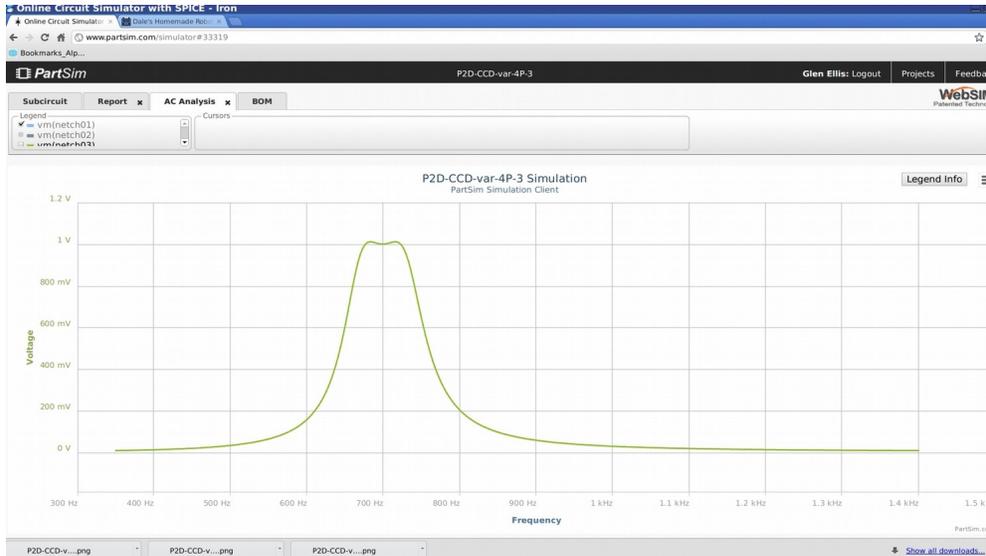***** Notice the Flat-Top PassBand of this Narrow filter.**




***** Dual Notches are used to attenuate the sidebands.**



Circuit: P2D-DIF-WN-1-S

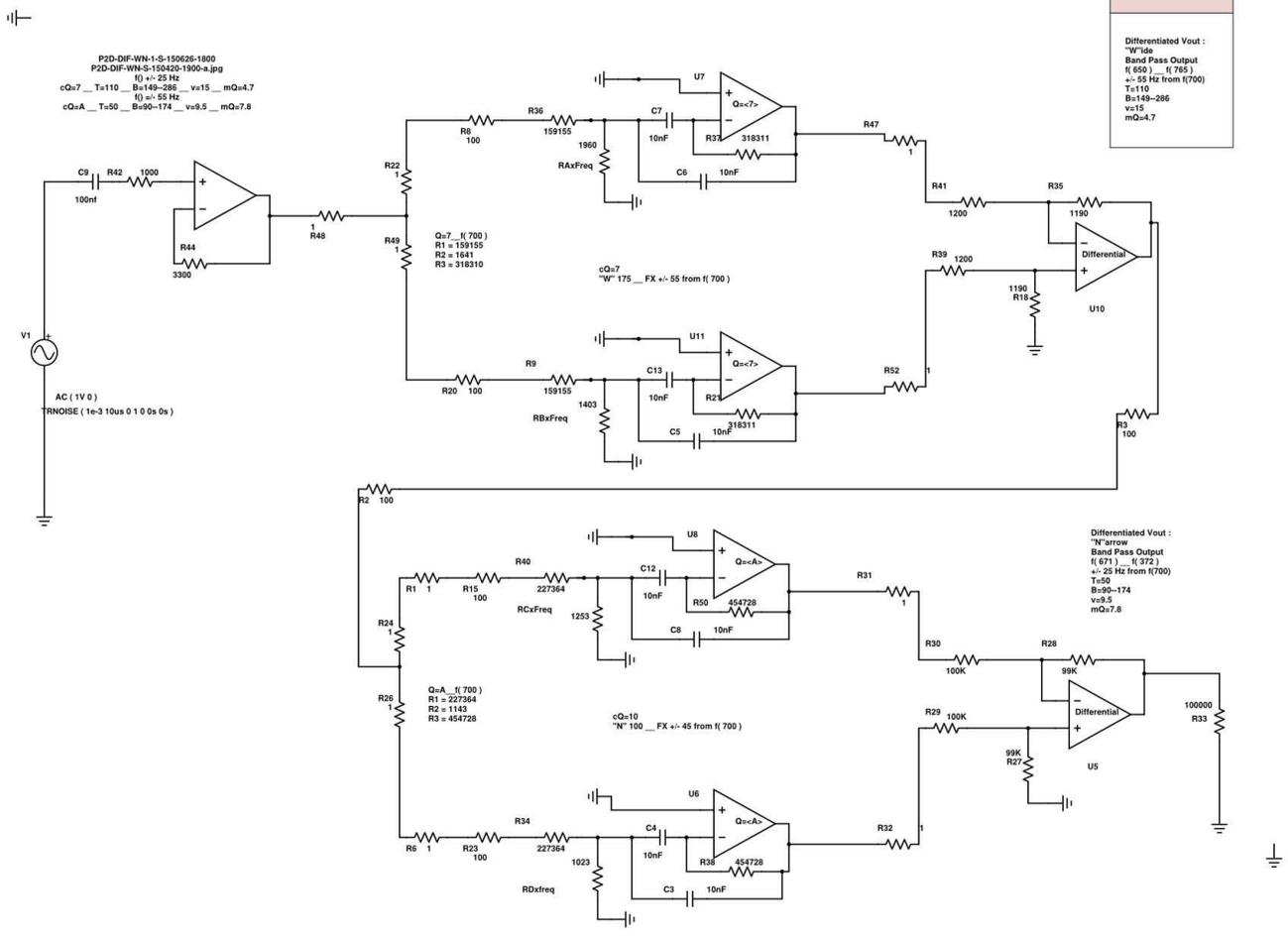***** Narrow BandWidth of 90 Hz, with 7 Hz spread per dB attenuation.**





Bode Plot : P2D-DIF-WN-1-S

*** Notice the Flat-Top PassBand of this Narrow filter.

*** Developed into a "W"ide and "N"arrow circuit :

BW=175Hz and BW=90Hz

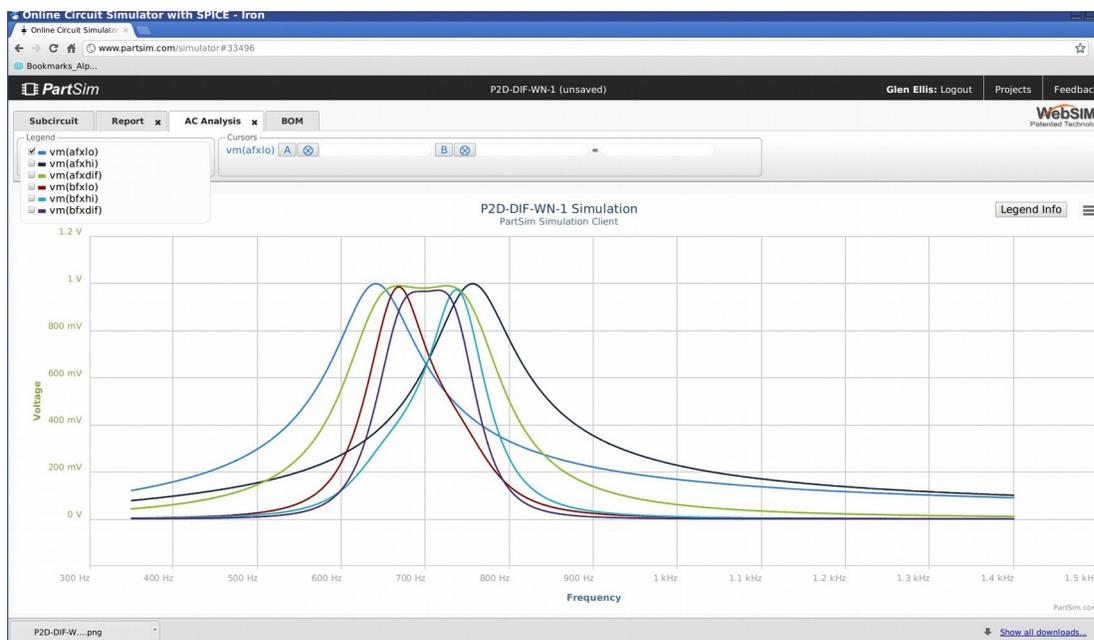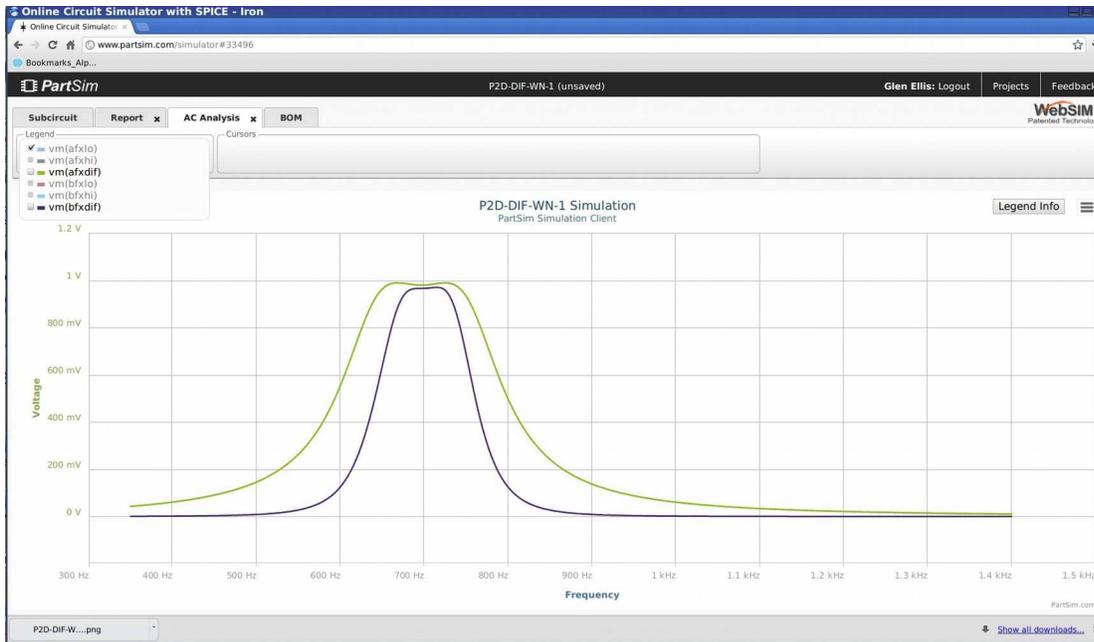** Showing the f(0) Pass-Band and four auxillary peaks.





Chapter : AFX_mFilter_5_P2B



"P2" version B



Resonant Dual-Channel Audio Filters

The designed advantages coming from the this approach are :

- 1) a flat-topped Passband, for easier capture of CW signals.
- 2) steeper sideband skirts,
(one circuit at 12 stages approaches Brick-Wall measurements).

The disadvantage is
greater complexity in tuning the many dual channel stages.


Bode Plot :

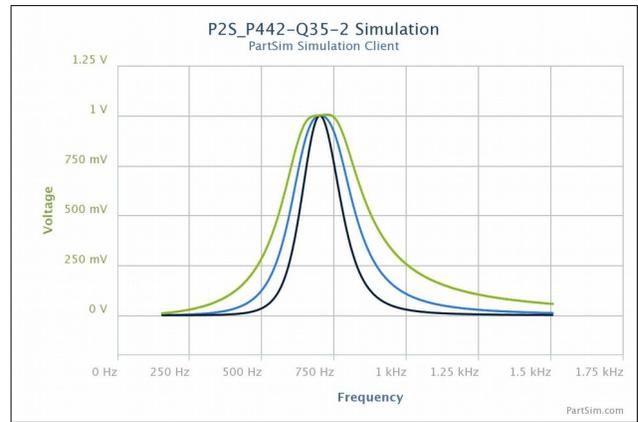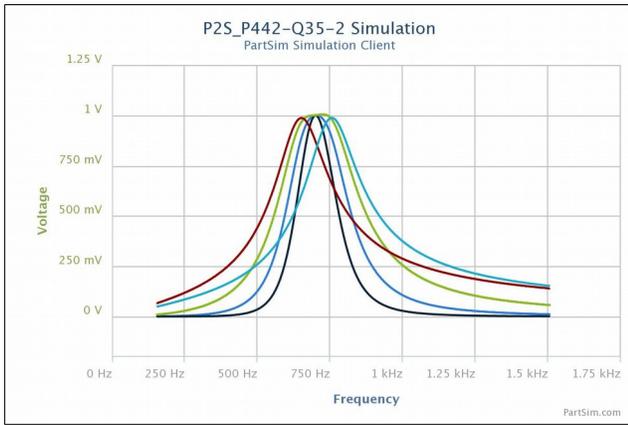

Top = 65Hz __ at -1dB and BW = 110 __ at -3dB
Variance = 14 Hz per dB attenuation __
Last Stage Filter: measured "Q" = 6.5 __ max

Circuit: P2S-P332-P445

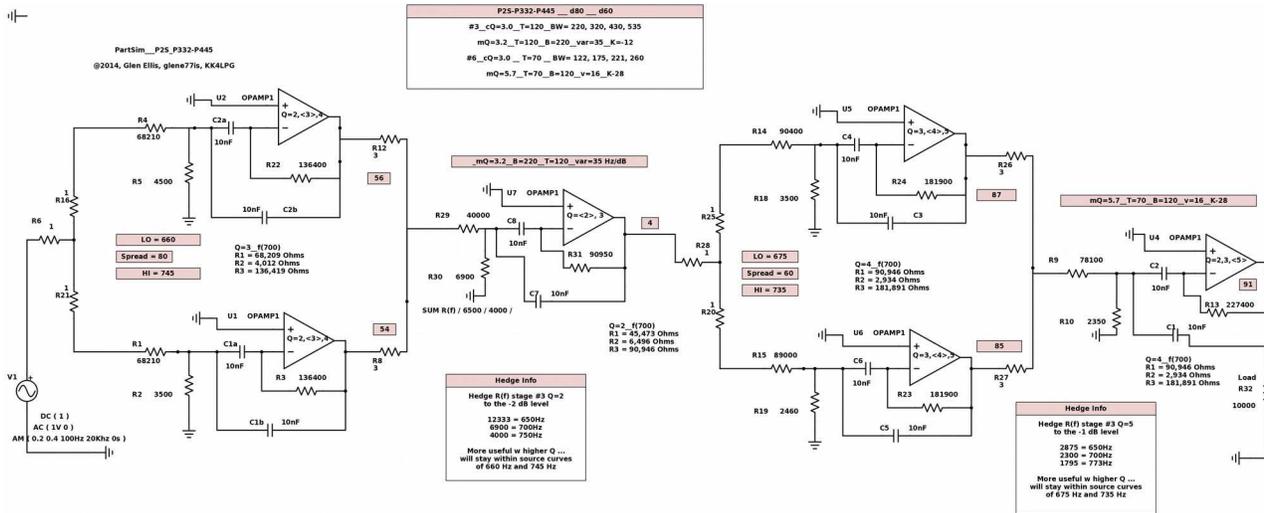
This circuit is developed as a Narrow CW Filter in six stages. Two sets of Dual-Channel filters.



Results depend on specific amount of Dual-Channel Spread and "Q".

Wide mQ=3.0_T=120_BW=220_var=35_K=-12
Narrow mQ=5.7_T=70_BW=120_var=16_K=-28

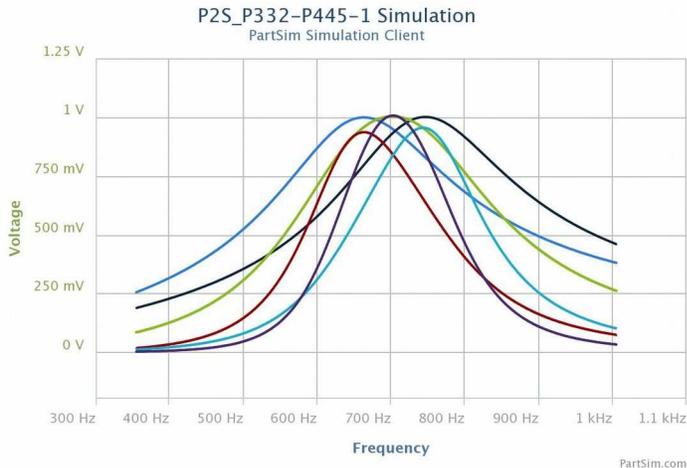measured "Q" = 5.7 __ Top = 70Hz __ BW = 120 __
Variance = 16 Hz per dB attenuation __
Kilo = -28dB at 1000 Hz




In each of the Triplet Groups, the OpAmp filters #1 and #2 are staggered (hi / lo of each other)

**and #3 is a Summing stage with a Low "Q".
Staggers here are +/- 45Hz for First Triplet, and then +/- 30Hz for Second Triplet.**

**The result is a Flat-Top Bode plot,
and steeper than normal SideBand Skirts.**

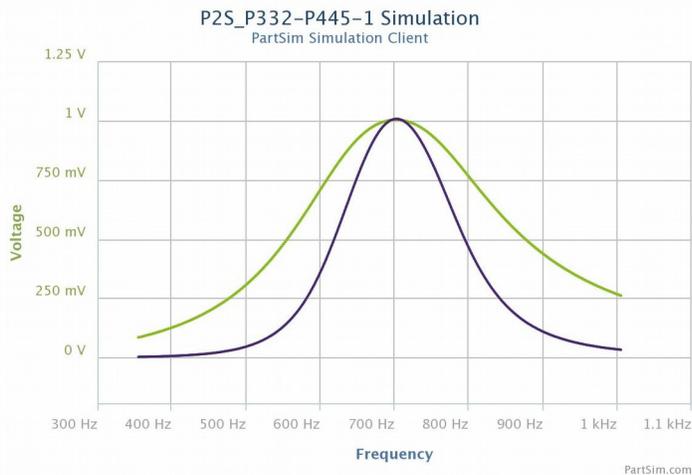**Resulting Final Top BW at -1 dB is 70 Hz (Flat).
Resulting Final BandWidths are 120, 195, 240, 285 at the -3dB, -6dB, -9dB, -12dB levels.
Resulting Final Variance of BandWidth is 16 Hz per dB attenuation (Extremely Steep).**



Resulting signal level of K = -28 dB at 1000 Hz. Results depend on amount of Dual-Channel Spread. No precision components required. Caps are +/- 5%, f() is corrected by the MFB circuit at R(freq) for each stage.

The P2SQ Triplet Filter #1 is caculated as Q=3,3,2, and measured as Q= 3.0, 3.0, 4.0 , due to the cumulative effect of sequential stages.


The P2SQ Triplet Filter #2 is caculated as Q=4,4,5, and measured as Q= 4.0, 4.0, 6.0 , due to the cumulative effect of sequential stages.

**Stage #1 & #2: R(freq) is R5 and R2 for the base parallel filters.
Stage #3: R(freq) is R30, for the Summing "W"ide filter.**

Circuit: **P2S-3-AA1A1AA1** special RTTY Filter*

This "P2" filter is applied as an Audio R.T.T.Y. Filter,
at 600 Hz & 800 Hz.

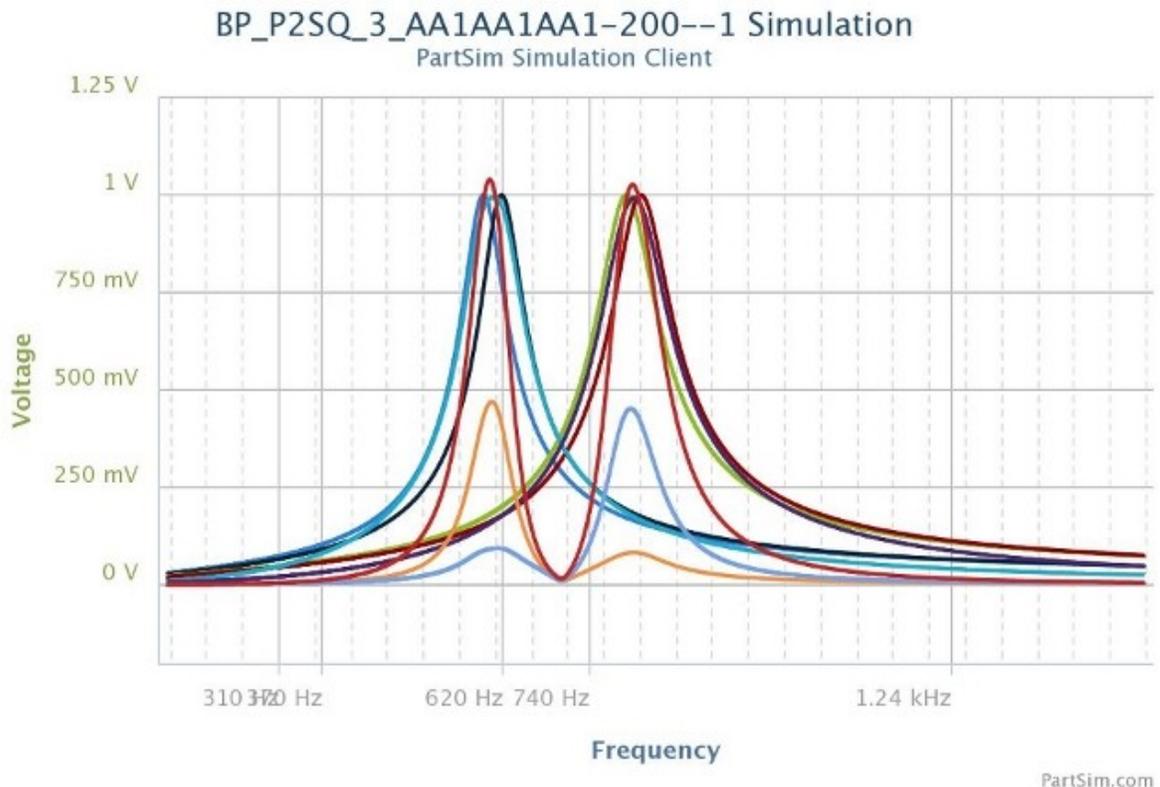
The RTTY Twin-Peak has been phase inverted
and acts as a Twin-Notch around the narrow C.W. filter. (see below)



Designed for WB8YY. *** Cumulative Filter Bode for RTTY Filter, all phases showing :


P2S-PAA1AA1AA1

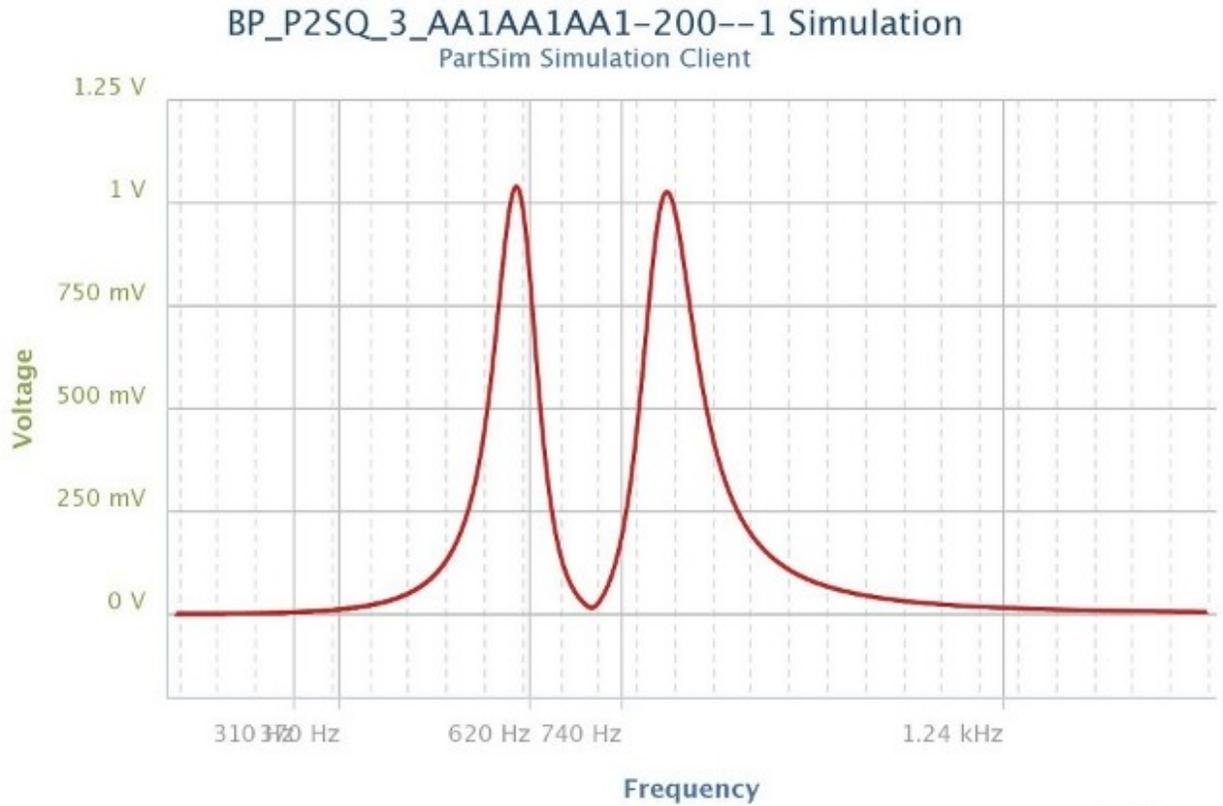*** RED trace shows -48 dB Notch between RTTY peaks :



Circuit: P2S-PAA1AA1AA1

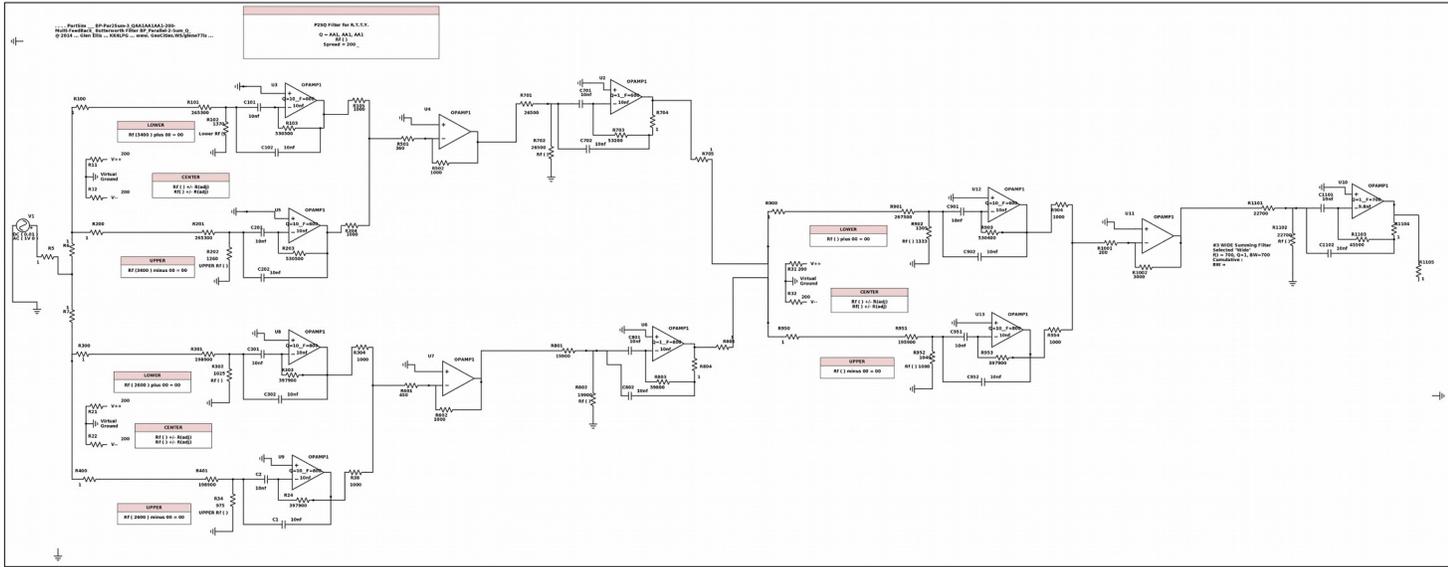***** Schematic of RTTY audio filter (12 filter stages). Designed for WB8YYY.**




Circuit: **P2S-PAA1-Q7**
an Audio C.W. Filter, Final Q=7, at 700 Hz,

Design goal was to broaden the Top of the BandPass at the -3dB level and Steepen the SideBand Skirts between -3dB and -30 dB.

Here, the Twin-Peak signal is phase inverted and acts as a Twin-Notch when summed around the narrow C.W. signal.

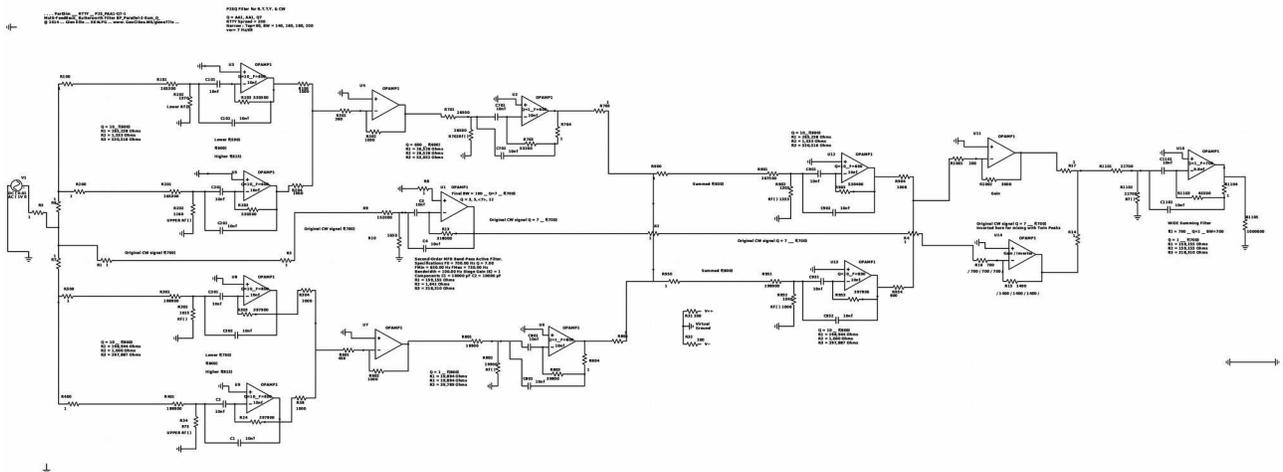This Q=7 BandPass is about 100 Hz wide at -3dB, Extremely steep skirts, spreading at 7 Hz per dB attenuation down to -30dB.




Circuit: P2S-PAA1-445-Q7

Schematic (18 stages)

Design goal was to broaden the Top of the BandPass,
and Steepen the SideBand Skirts.


Documentation embedded : P2S-PAA1-P445

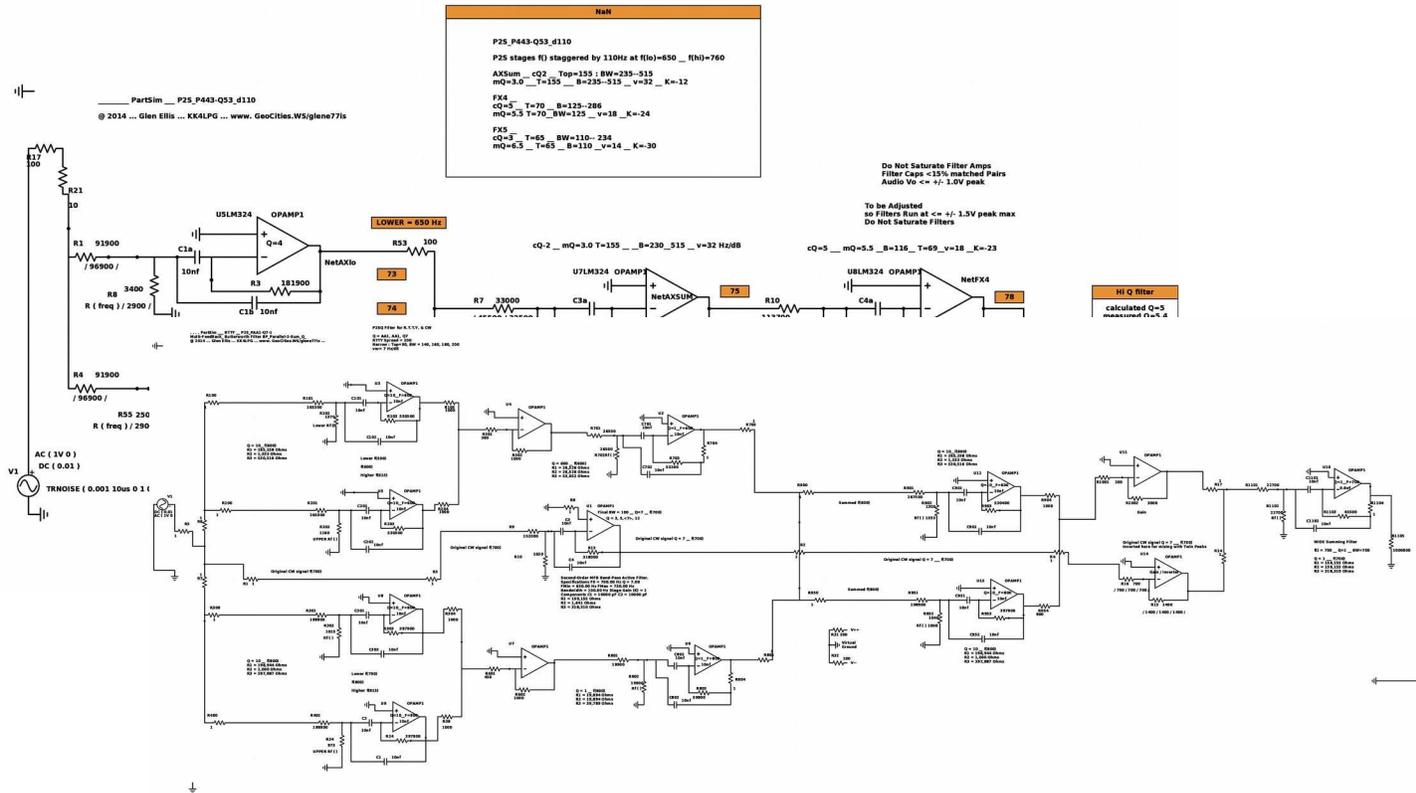This filter circuit has approx. BW=90 and Sidebands Extremely Steep,




Bode: P2S_PAA1-P445-3_

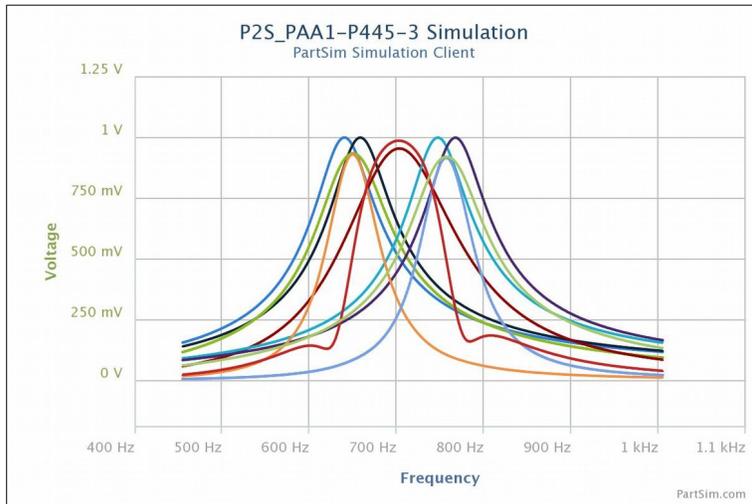Final Stage Measurements :
BW=100,120,130,145 @ -3dB,-6dB,-9dB,-12dB,
Variance=5 Hz per dB and K=-24 dB



P2SQ_6_AA1_Q7-2 : Magnitude plot.

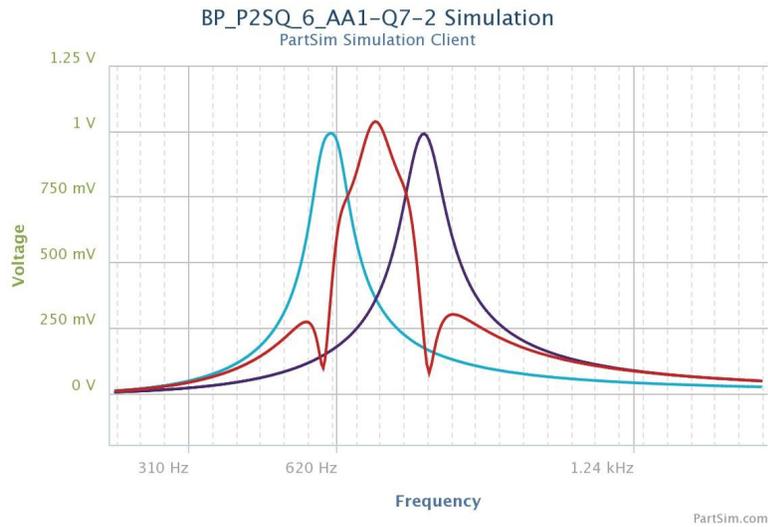
The sideband steepness has a rating a $v=5$ rating, $K=-27$ and will sound like a brick wall to signals outside of $BP=120\text{Hz}$.



P2S_PAA1-P445-3 : Final Stage Measurements : Bode plot

BW=100,120,130,145 @ -3dB,-6dB,-9dB,-12dB

Variance=5 Hz per dB and K=-24 dB

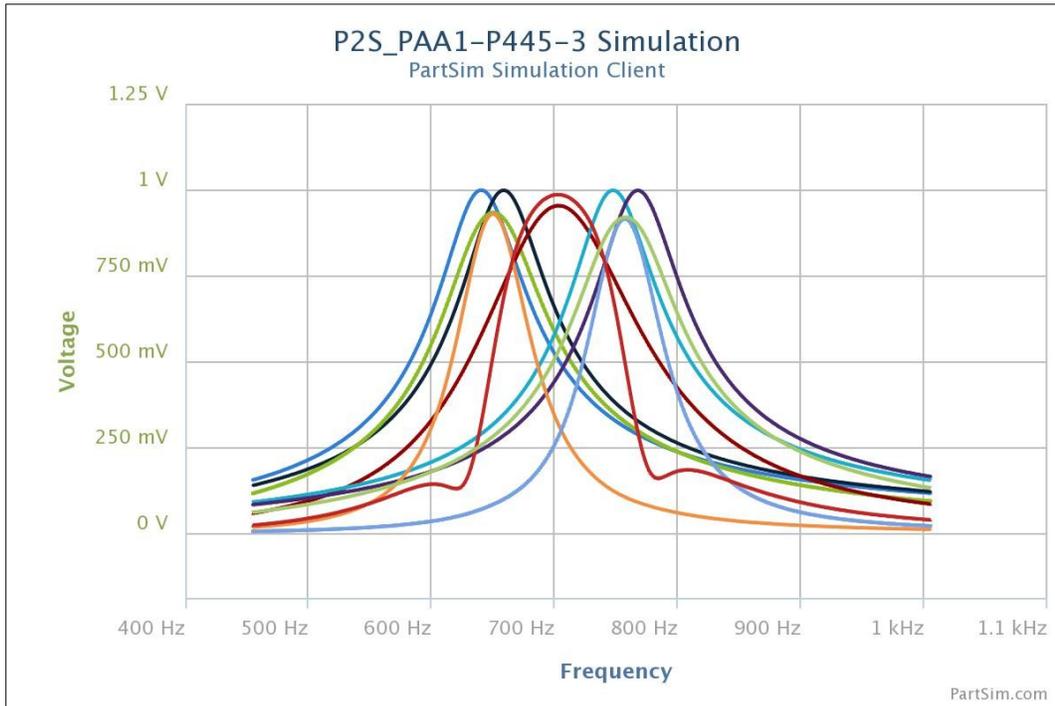


The Dark-Red trace is the broader original CW signal
The Light-Red trace is the narrow Double-Notched PassBand Signal.

Not a Club Kit Project !
Tuning is very critical.
Interaction between the the (inverted) Notch Peaks is always nearby.

P2SQ_6_AA1_Q7-2 : Magnitude plot.

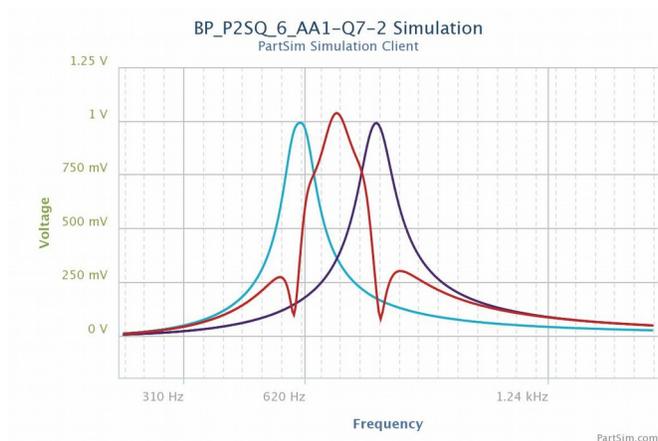The sideband steepness has a rating a v=5 rating, K=-27 and will sound like a brick wall to signals outside of BP=120Hz.





Chaper: AFX_mFilter_6_P2C



"P2" version C

Resonant Dual-Channel Audio Filters

The designed advantages coming from the this approach are :


- 1) a flat-topped "W"ide Passband, for easier capture of CW signals.
- 2) a "N"arrow Passband with extremely steep sideband skirts,
- 3) uses Parallel Filters followed by un-tuned Differential stages
- 4) if followed by a MFB $Q=7$ stage, then a single $R(\text{freq})$ can vary the $f()$ narrow passband frequency.

Note: In the following diagrams, $R2$ to Virtual Ground is the $R(\text{freq})$ for adjusting $f(\text{center})$


Note: the -3dB level is equivalent to the 700 mV level in these Bode Plots.

Circuit: P2D-P33D-P44D

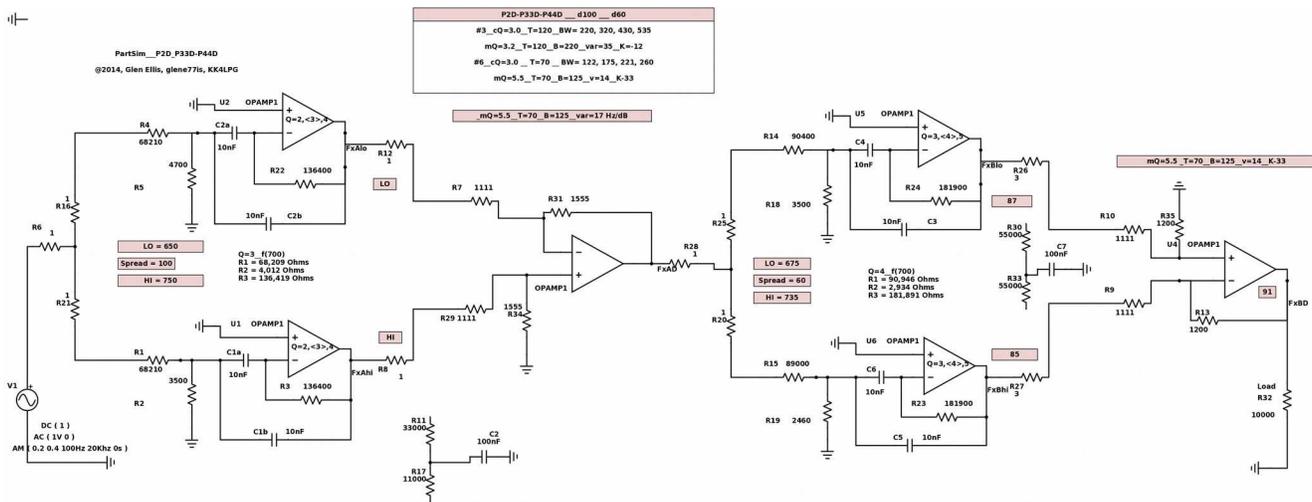Special Differentiated Stages to replace Filter stages.
Two Tuned Summing Stages replaced by Two Un-Tuned Differentiation Stages.
Same Results !!!



Bode Plot: P2D-P33D-P44D

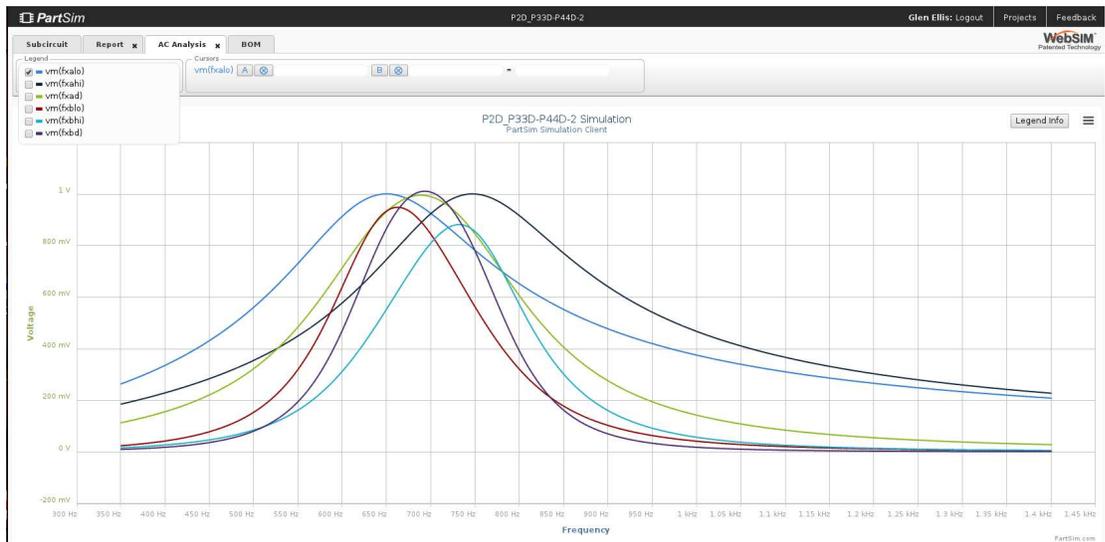

Transient Plot: P2D-P33D-P44D Analysis, Sine Input, showing Phase-Shifting to obtain the required Band-Pass.



Intro: P2D-DIF-WN

P2D-P77D-P55D


**This design is- for extremely steep "N" sidebands.
Special Differentiated Stages to replace Filter stages.
Two Tuned Summing Stages
replaced by Two Un-Tuned Differentiation Stages.
Same Results !!!**

**First Triad is $Q=7 \pm 50$ Hz , then Differentiated.
Second Triad is $Q=5 \pm 25$ Hz , then Differentiated.**

**First Triad is "W"ide $v=15$.
Pass-Band is extremely steep for a "W"ide Filter.**


**Second Triad is "N"arrow $v=9.5$!!!
Pass-Band sidebands are Close to DSP
and already analog for Audio Output.
At ± 90 degrees from $f(700)$ the signal is near -48dB down.**

Circuit: P2D-DIF-WN

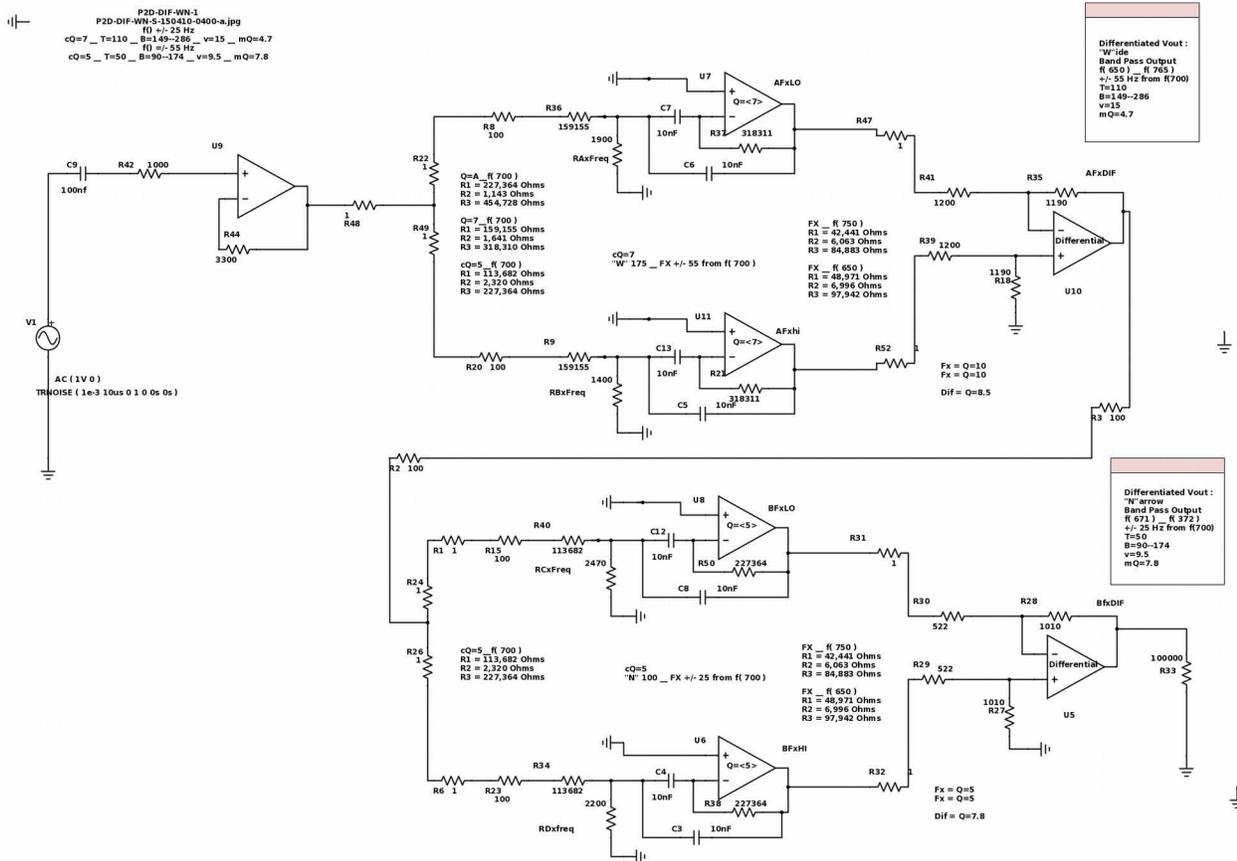

Bode Plot: P2D-DIF-WN

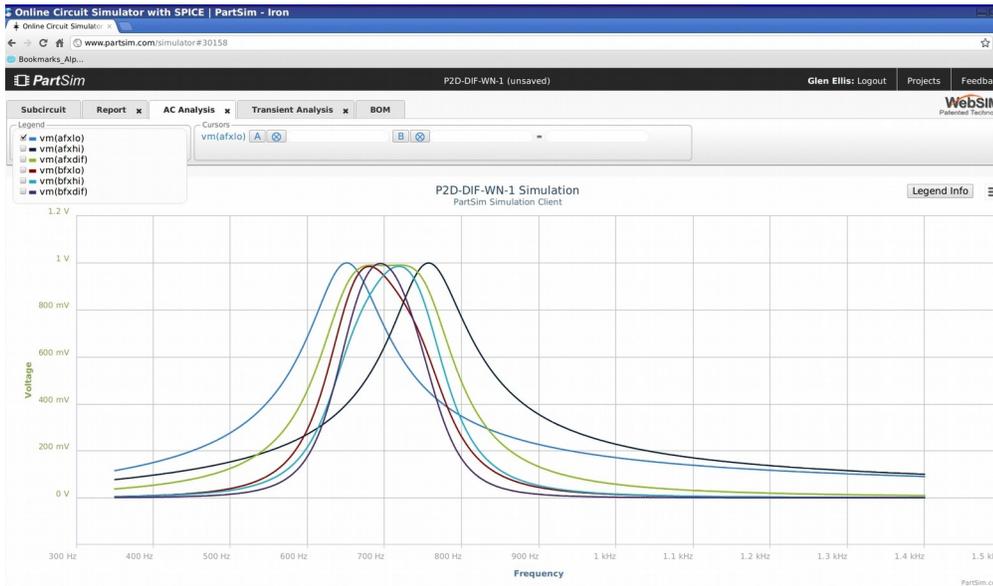Differential Traces are : "W"ide GREEN . "N"arrow Black .
There are two passbands for "W" and two passbands for "N",
each passband is followed by a Differential Stage.



Transient Plot: P2D-DIF-WN

Signal injected was "Noise".
Shown is the effectiveness of a Differentiator
in eliminating Common Mode noise signal.



Conclusions: about the **P2'C'** design approach :

The Parallel designs have been intriguing to develop.

These are really radical 'techy' circuits and good to brag about.

*** The 12 stage (P2S-QAA-P445) circuit produces a "N"arrow filter output that compares favorably with DSP (after run through a DAC for the earphone signal).**

but are **very ticky to construct and **very tricky** to tune.**

Compared to the P2'A' and P2'B' design approach :

*** The P2'C' designs are much simpler, and produce passbands similar to DSP, and are easy to tune,**

*** The P2'A' and P2'B' designs are much simpler, and produce passbands similar to DSP, but are **difficult** to tune.**

* The [AFX-RSE-S4-Q7](#) version #8 Filter circuit could be improved by using the P2D-DIF filter section.

AFX design , the thrust of this "AFX" project with

(1) Roofing stage based on P2D triad,

(2) driving the log-limiter,

(3) driving the Quad Filter Stage ,

(4) followed by the "W" Integrated and "N" Differentiated Stages

can produce excellent results,

and is a well-developed good-working project.

AFX "W"ide and "N"arrow stages produce similar results, and is much better for building and tuning.

▪

That is the author's General Conclusion on this series of **P2'C' filters.**

▪



Chapter: AFX_mFilter_5_PFB

Resonant Filter Positive-Feed-Back

GC_ET_PFB.html

2021-01-06 11:31:45



Associate Professor **Dr. Josef Punčochář**
VŠB-Technical University of Ostrava, · Department of Electrical Engineering

Original Design for Positive-FeedBack BandPass Filter.
(GC_ET_PFB-rg.html)

GC_ET_PFB-rg.html

2018-01-10

11:08:01

Based on circuit design by Dr. Josef Punchochar

Associate Professor

VŠB-Technical University of Ostrava, Ostrava · Department of Electrical Engineering

Copy from Josef Punchochar article :

This is a frequency dependent positive feedback - under-critical (a "bootstrap") if $k \cdot m = 1$ - only on the frequency ω_0 is on output FBP voltage U_1 - input divider therefore does not apply. The input divider is beginning "to work" for all other frequencies. **The circuit can operate with amplitudes of volts order - without degrading of performance.** Decisive is basically the size of the supply voltages, which defines the limitation of signal.

An example for $|k|=|m| = 1$ is in Fig.2. The R_b was realized by means of output resistance of the FBP in 1987.


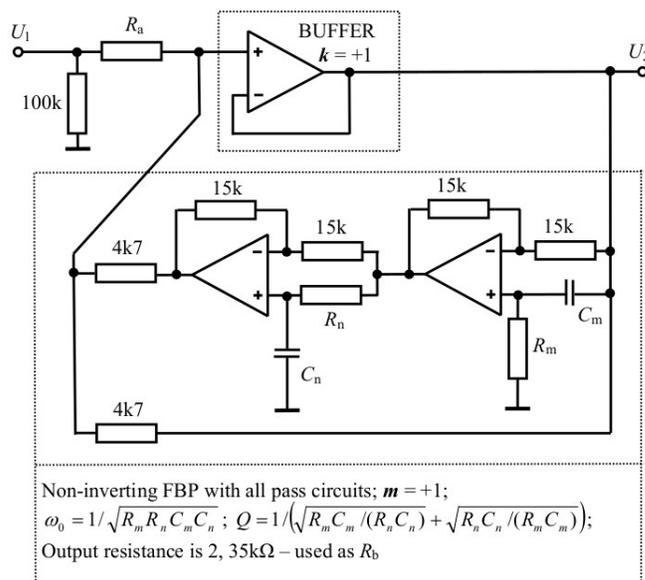


Fig.2. Realization by means of buffer and noninverting FBP; „3 x 741“; supply $U_{CC} = \pm 15$ V; $R_a = 122k$; $R_m = R_n = 1k3$; $C = 10$ nF; measured $f_0 = 11$ kHz; $Q_c = 27,5$; for U_1 less than 4 V (for larger amplitudes take effect slew rate)

Developed into this by Glen Ellis :

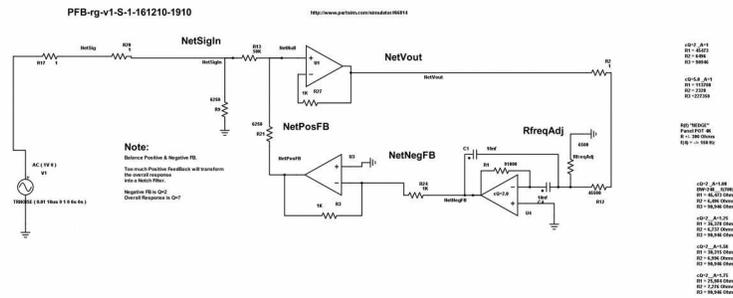Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.

Advantage is : Adjust $f(0)$ via a single resistor $R(\text{freqAdj}) \pm 300$ Hz.



SPICE circuit, 161210, Glen Ellis.

Based on circuit design by Josef Punchochar, Research Gate Net

Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.

Advantage : Adjust $f(0)$ via a single resistor $R(\text{freqAdj})$ +/- 300 Hz.

Balance between Positive & Negative FB

Too much FeedBack will transform circuit into a Notch Filter.

V(out) is NetVout

$f(0) = 700$ Hz

FeedBack $Q=2$


Effective $Q=7$

BW=100 Hz

Original NetSigIn (source signal) is flat (green).

FeedBack inverted (black) (generated at $Q=2$)

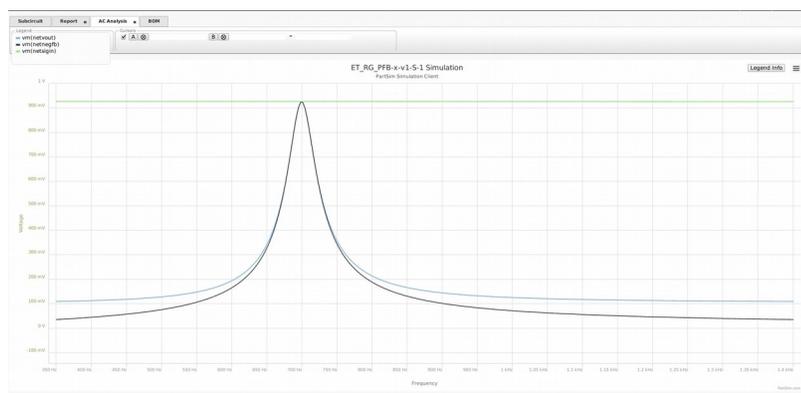Overall Response is $Q=7$ Positive BandPass (blue).



Transient Plot



Adjust $f(0)$ via a Single Resistor $R(\text{freqAdj}) \pm 300 \text{ Hz}$.

Change $f(0)$ via $R6$.

Initially $R(\text{freq})$ is 6500 Ohm. Adjust : Up = lower $f(0)$ and Down = higher $f(0)$.

In $f(0)$ change,


Gain will change as the minor ratio of $R(\text{in}) / R(\text{freq})$.

Q will change as squareroot of Δf change.


But BW will remain same.

(Author uses this method for adjusting $f(0)$ change of $\pm 300 \text{ Hz}$)

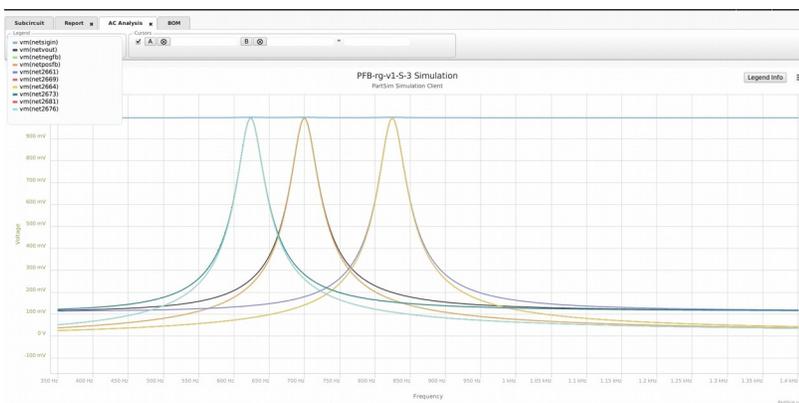***** Demonstrating shifting $f(0)$ via $R(\text{freqAdj})$**



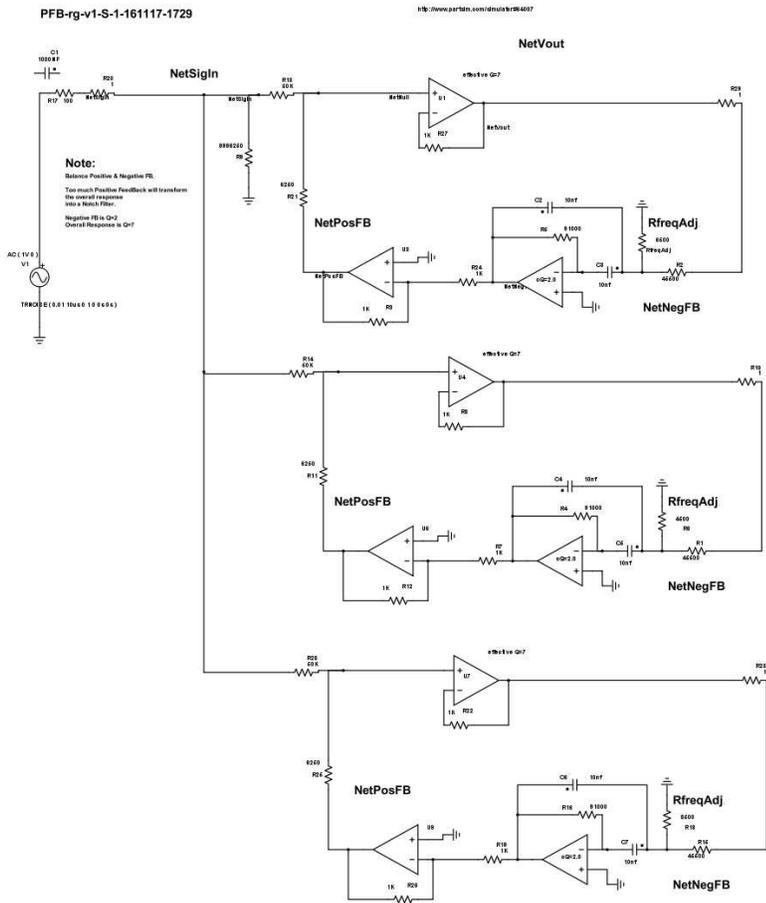***** Demonstrating circuit to generate bode of shifting $f(0)$ via $R(\text{freqAdj})$**



Further Reading on Positive Feed-Back developments :



[AAA GC_ET_PFB-bpf.html](#)

GC_ET_PFB-bpf.html

2018-01-10

11:05:01

***** Based on circuit design by Dr. Josef Punchochar , Research Gate Net**

***** the Positive-FeedBack Band-Pass Filter, with single resistor $f()$ control.
Negative FeedBack is Q2 and PFB BandPass $V(out)$ is Q7**

Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.

Advantage is : Adjust $f(0)$ via a single resistor $R(freqAdj)$ +/- 500 Hz.

***** SPICE circuit, Glen Ellis.**




***** Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.**

***** Advantage : Adjust $f(0)$ via a single resistor $R(freqAdj)$ +/- 300 Hz.**

***** Balance between Positive & Negative FB**

***** else will transform circuit into a Notch Filter or into an Oscillator.**

Chapter: AFX_rFilter_5_PFB 7 / 30

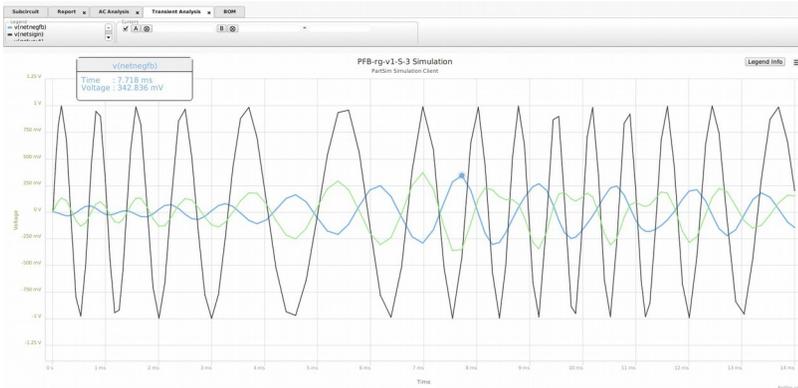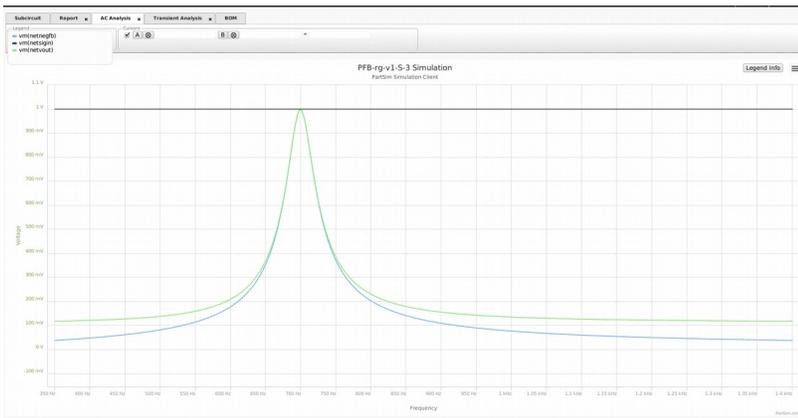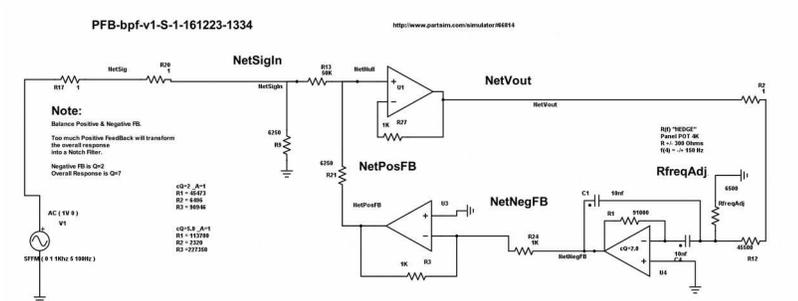

V(out) is NetVout

f(0) = 700 Hz

FeedBack Q=2


Effecive Q=7

BW=100 Hz

***** Original NetSigIn (source signal) is flat (green).**

***** FeedBack inverted (blue) (generated at Q=7)**

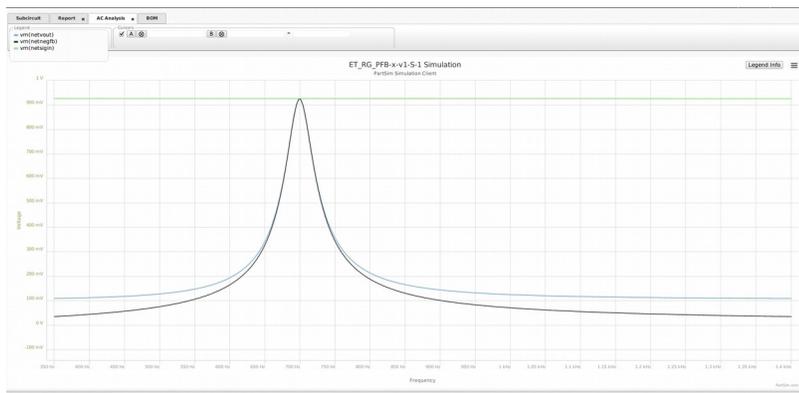***** Overall Response is Q=7 Positive BandPass (black).**



Transient Plot : Noise Input and Positive-FeedBack and f(700) filtered V(out) . Green Noise, Black Positive-FeedBack, Blue f(700) V(out) .



Adjust $f(0)$ via a Single Resistor $R(\text{freqAdj})$ +/- 300 Hz.

Change $f(0)$ via $R6$ [$R(\text{freq})$].

Initially $R(\text{freq})$ is 6500 Ohm. Adjust : Up = lower $f(0)$ and Down = higher $f(0)$.

In $f(0)$ change,


Gain will change as the minor ratio of $R(\text{in}) / R(\text{freq})$.

Q will change as squareroot of $\Delta(f)$ change.

But BW will remain same.

(Author uses this method for adjusting $f(0)$ change of +/- 300 Hz.)

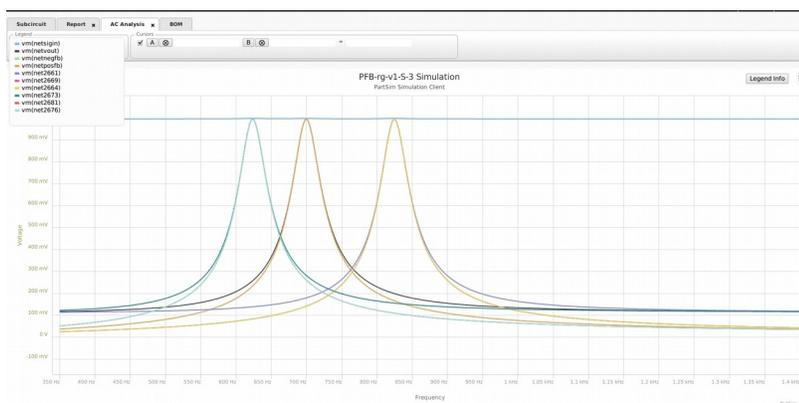*** Demonstrating shifting $f(0)$ via $R(\text{freqAdj})$



*** Demonstrating circuit to generate bode of shifting $f(0)$ via $R(\text{freqAdj})$



[BBB GC_ET_PFB-osc.html](#)

GC_ET_PFB-osc.html


2018-03-08

19:06:07

***** Our further development of the Positive Feed-Back Oscillator concept.


***** Positive Feed-Back with NO limiter control

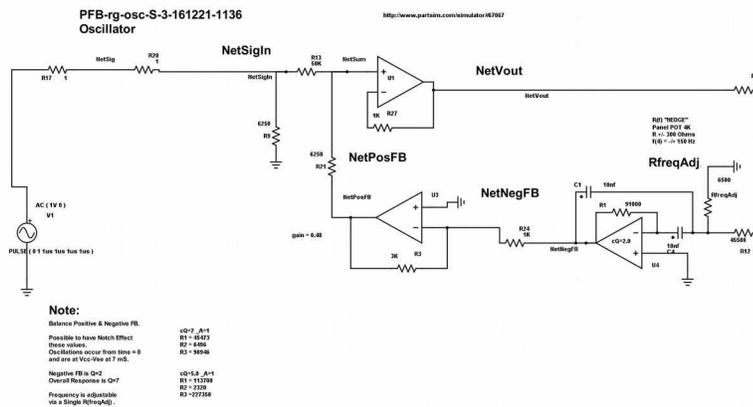***** produces a "SQUARE" V(out) , with single resistor f() control.



***** Positive Feed-Back with limiter control

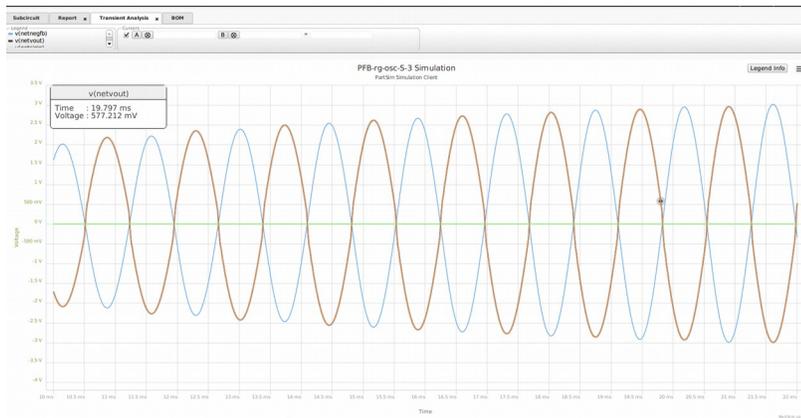***** produces a "SINE" V(out) , with single resistor f() control.



GC_ET_PFB.html

2021-01-06 11:31:45



Associate Professor **Dr. [Josef Punčochář](#)**
[VŠB-Technical University of Ostrava](#), · Department of Electrical Engineering

Original Design for Positive-Feedback BandPass Filter.
(GC_ET_PFB-rg.html)

GC_ET_PFB-rg.html

2018-01-10

11:08:01

Based on circuit design by Dr. Josef Punchochar

Associate Professor

VŠB-Technical University of Ostrava, Ostrava · Department of Electrical Engineering

Copy from Josef Punchochar article :

This is a frequency dependent positive feedback - under-critical (a "bootstrap") if $k \cdot m = 1$ - only on the frequency ω_0 is on output FBP voltage U_1 - input divider therefore does not apply. The input divider is beginning "to work" for all other frequencies. **The circuit can operate with amplitudes of volts order - without degrading of performance.** Decisive is basically the size of the supply voltages, which defines the limitation of signal.

An example for $|k| = |m| = 1$ is in Fig.2. The R_b was realized by means of output resistance of the FBP in 1987.


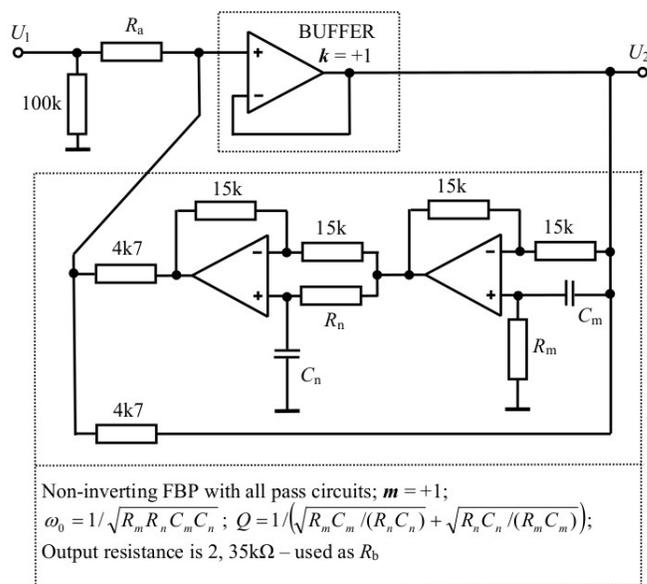


Fig.2. Realization by means of buffer and noninverting FBP; „3 x 741“; supply $U_{CC} = \pm 15$ V; $R_a = 122k$; $R_m = R_n = 1k3$; $C = 10$ nF; measured $f_0 = 11$ kHz; $Q_e = 27,5$; for U_1 less than 4 V (for larger amplitudes take effect slew rate)

Developed into this by Glen Ellis :

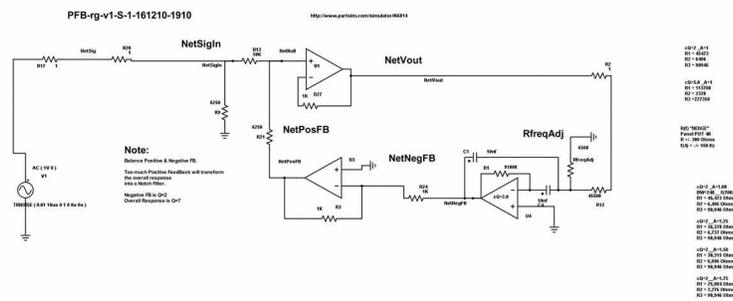Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.

Advantage is : Adjust $f(0)$ via a single resistor $R(\text{freqAdj})$ +/- 300 Hz.



SPICE circuit, 161210, Glen Ellis.

Based on circuit design by Josef Punchochar, Research Gate Net

Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.

Advantage : Adjust $f(0)$ via a single resistor $R(\text{freqAdj})$ +/- 300 Hz.

Balance between Positive & Negative FB

Too much FeedBack will transform circuit into a Notch Filter.

V(out) is NetVout

$f(0) = 700$ Hz

FeedBack $Q=2$


Effective $Q=7$

BW=100 Hz

Original NetSigIn (source signal) is flat (green).

FeedBack inverted (black) (generated at $Q=2$)

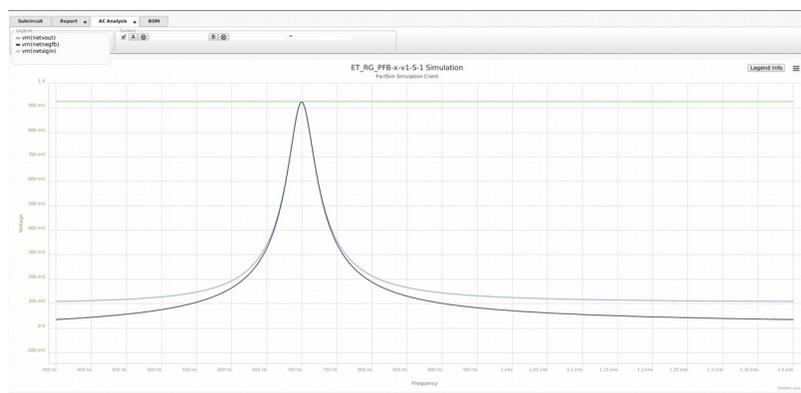Overall Response is $Q=7$ Positive BandPass (blue).



Transient Plot



Adjust $f(0)$ via a Single Resistor $R(\text{freqAdj}) \pm 300 \text{ Hz}$.

Change $f(0)$ via $R6$.

Initially $R(\text{freq})$ is 6500 Ohm. Adjust : Up = lower $f(0)$ and Down = higher $f(0)$.

In $f(0)$ change,


Gain will change as the minor ratio of $R(\text{in}) / R(\text{freq})$.

Q will change as squareroot of Δf change.


But BW will remain same.

(Author uses this method for adjusting $f(0)$ change of $\pm 300 \text{ Hz}$)

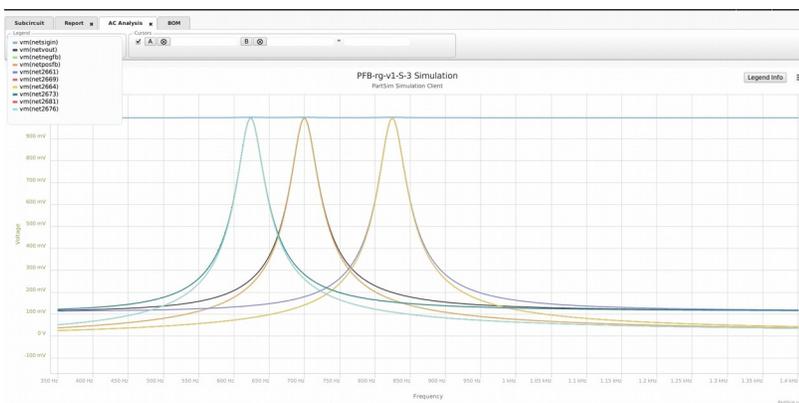***** Demonstrating shifting $f(0)$ via $R(\text{freqAdj})$**



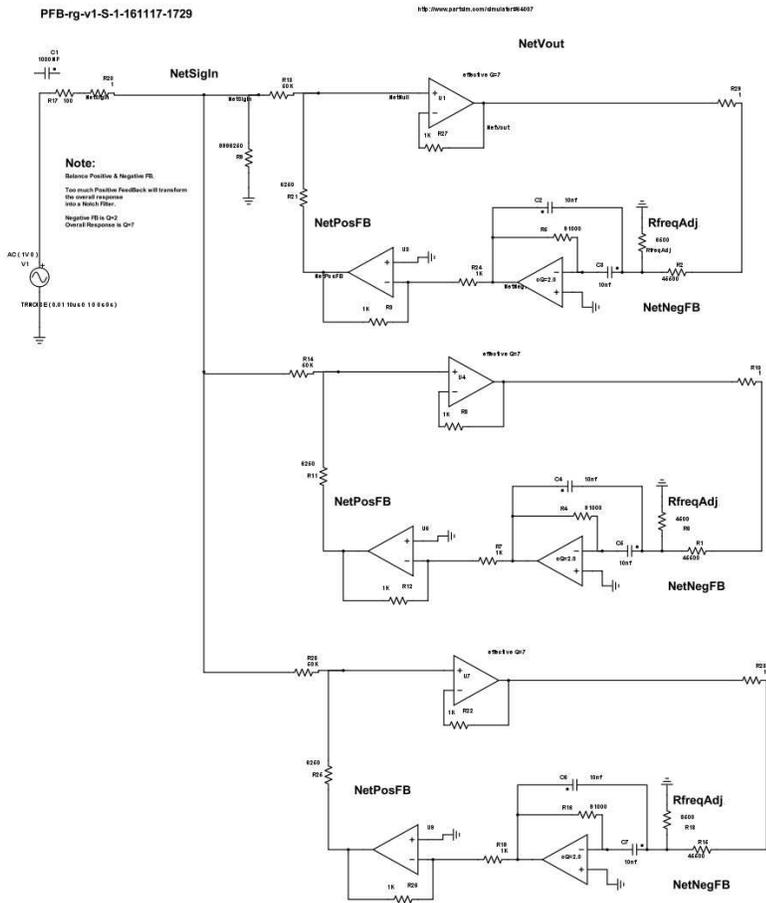***** Demonstrating circuit to generate bode of shifting $f(0)$ via $R(\text{freqAdj})$**



Circuit: Positive-Boot-Strapped Band-Pass



[AAA](#) GC_ET_PFB-bpf.html

GC_ET_PFB-bpf.html

2018-01-10

11:05:01

*** Based on circuit design by Dr. Josef Punchochar , Research Gate Net

Positive Boot-Strap Feedback

Circuit: Positive-FeedBack Filter – by Dr. Punchochar

***** the Positive-FeedBack Band-Pass Filter,
with single resistor f() control.**

Negative FeedBack is Q2 and PFB BandPass V(out) is Q7

This is a frequency dependent positive feedback - under-critical (a "bootstrap") if $k \cdot m = 1$ - only on the frequency ω_0 is on output FBP voltage U_1 - input divider therefore does not apply. The input divider is beginning "to work" for all other frequencies. **The circuit can operate with amplitudes of volts order - without degrading of performance.** Decisive is basically the size of the supply voltages, which defines the limitation of signal.

An example for $|k| = |m| = 1$ is in Fig.2. The R_b was realized by means of output resistance of the FBP in 1987.

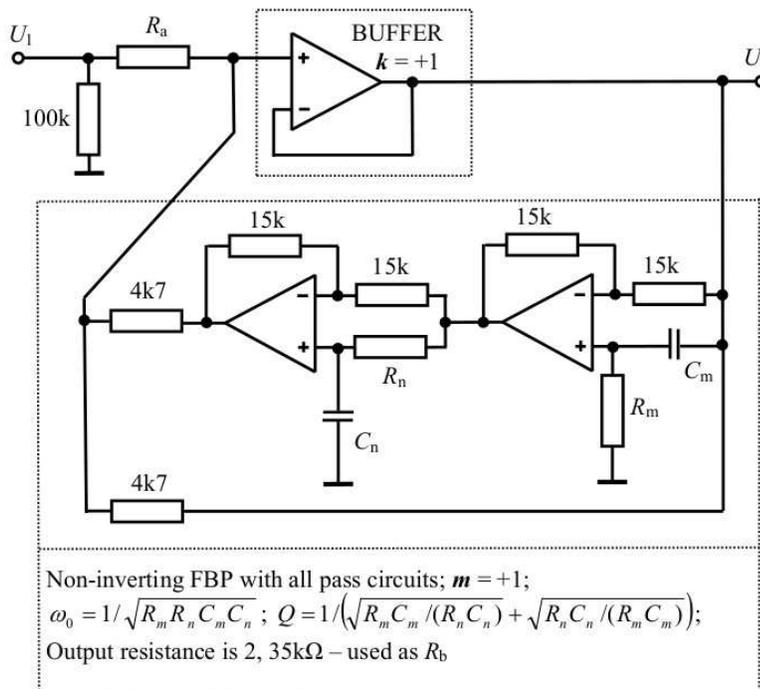


Fig.2. Realization by means of buffer and noninverting FBP; „3 x 741“; supply $U_{CC} = \pm 15$ V; $R_a = 122k$; $R_m = R_n = 1k3$; $C = 10$ nF; measured $f_0 = 11$ kHz; $Q_c = 27, 5$; for U_1 less than 4 V (for larger amplitudes take effect slew rate)

Circuit: **Positive-FeedBack-by Glen Ellis**

Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.

Advantage is : Adjust $f(0)$ via a single resistor $R(\text{freqAdj})$ +/- 500 Hz.

Circuit: Positive Feed-Back Filter


***** SPICE circuit, Glen Ellis.**

***** Example of circuit modification to handle Positive Boot-Strap Feedback via Multiple-Feedback Band Pass Filter.**


***** Advantage : Adjust $f(0)$ via a single resistor $R(\text{freqAdj})$ +/- 300 Hz.**

***** Balance between Positive & Negative FB**

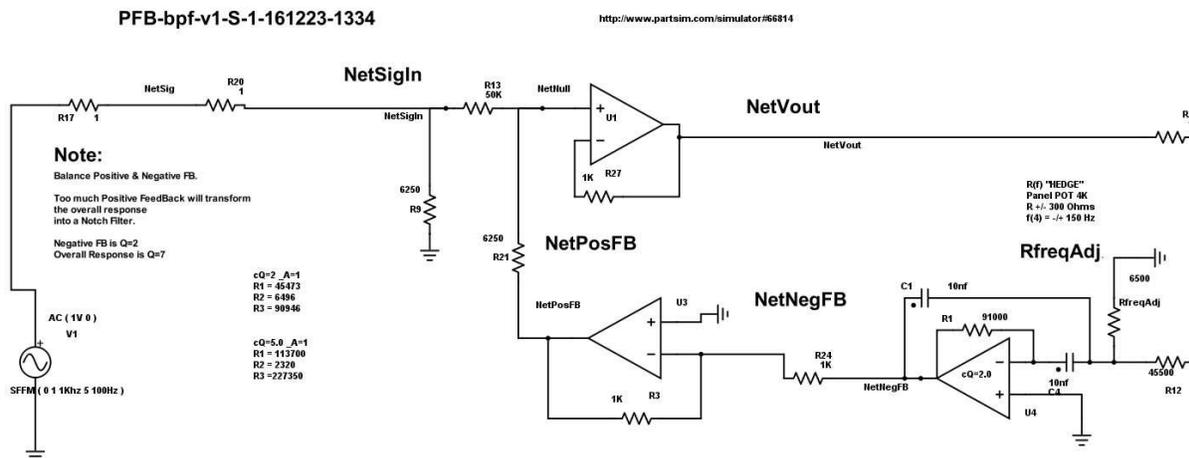
***** else will transform circuit into a Notch Filter or into an Oscillator.**



Bode Plot: **Positive Feed-Back Filter**

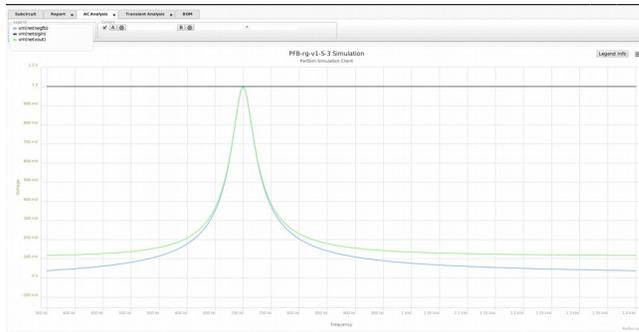

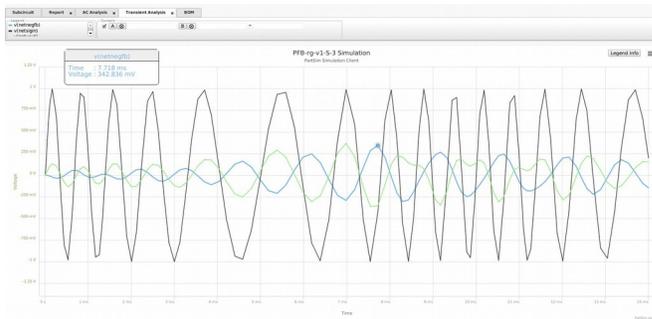Transient Plot: **Positive Feed-Back Filter**



Plots: **Positive Feed-Back Filter**

V(out) is NetVout

f(0) = 700 Hz

FeedBack Q=2


Effective Q=7

BW=100 Hz

***** Original NetSigIn (source signal) is flat (green).**

***** FeedBack inverted (blue) (generated at Q=7)**

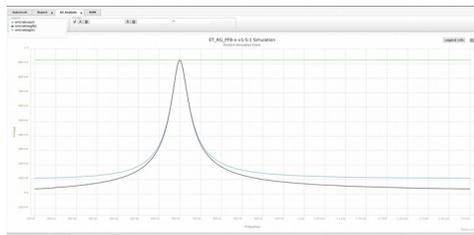***** Overall Response is Q=7 Positive BandPass (black).**



Transient Plot : Noise Input and Positive-FeedBack and f(700) filtered V(out) . Green Noise, Black Positive-FeedBack, Blue f(700) V(out) .



Adjust $f(0)$ via a Single Resistor $R(\text{freqAdj})$ +/- 300 Hz.

Change $f(0)$ via $R6$ [$R(\text{freq})$].

Initially $R(\text{freq})$ is 6500 Ohm. Adjust : Up = lower $f(0)$ and Down = higher $f(0)$.

In $f(0)$ change,


Gain will change as the minor ratio of $R(\text{in}) / R(\text{freq})$.

Q will change as squareroot of Δf change.


But BW will remain same.

(Author uses this method for adjusting $f(0)$ change of +/- 300 Hz.)

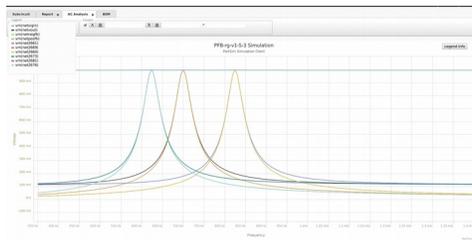*** Demonstrating shifting $f(0)$ via $R(\text{freqAdj})$



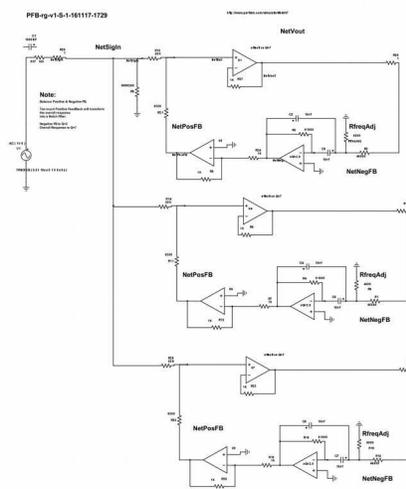*** Demonstrating circuit to generate bode of shifting $f(0)$ via $R(\text{freqAdj})$



[BBB](#) GC_ET_PFB-osc.html


GC_ET_PFB-osc.html




2018-03-08

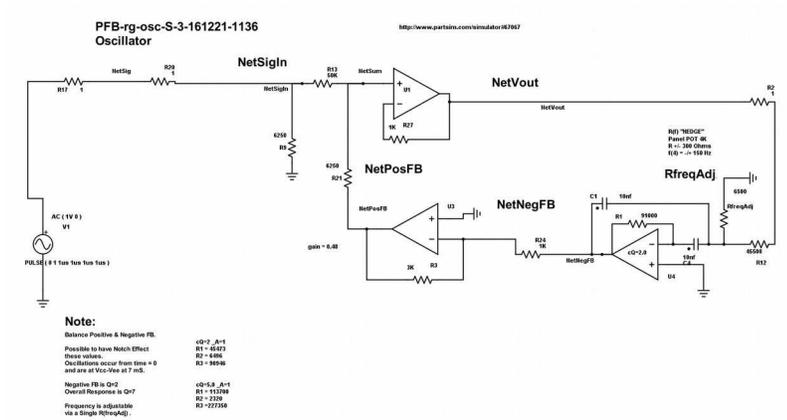19:06:07




- ***** Our further development of the Positive Feed-Back Oscillator concept.
- ***** Positive Feed-Back with NO limiter control
- ***** produces a "SQUARE" V(out) , with single resistor f() control.



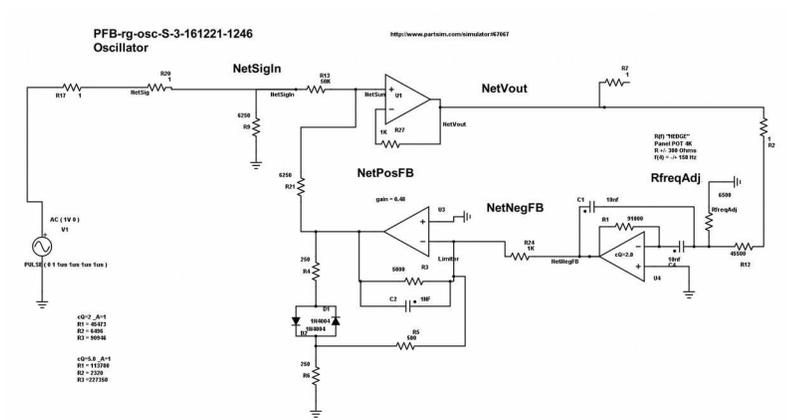- ***** Positive Feed-Back with limiter control
- ***** produces a "SINE" V(out) , with single resistor f() control.



Chapter: AFX_rFilter_5_PFB 29 / 30

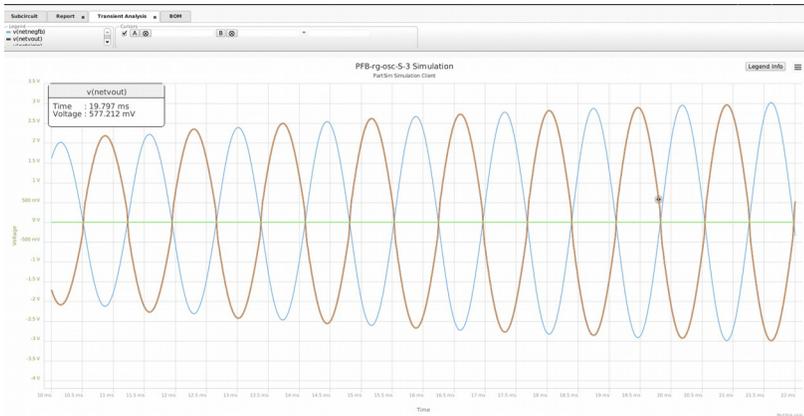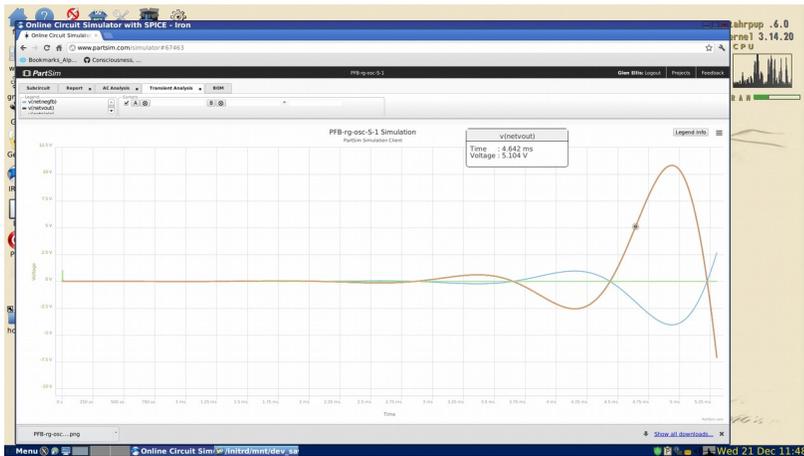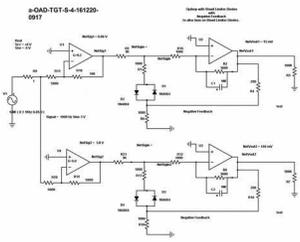

**

