

## Introduction To Amplifiers

ET 210 Discrete Semiconductors

---

---

---

---

---

---

---

### Introduction

- The amplifier is probably the most common circuit used in electronics
- Most systems have many amplifiers not just one and these circuits are implemented in many ways
- However all amplifiers share some common characteristics

---

---

---

---

---

---

---

### Amplifier Properties

- Amplifiers have three basic properties
  - gain
  - input impedance
  - output impedance

---

---

---

---

---

---

---

## Gain

- Gain is the multiplier between the amplifier input and output
- There are three types of gain
  - voltage gain ( $A_V$ )
  - current gain ( $A_I$ )
  - power gain ( $A_P$ )
- All amplifiers have all three types of gain - but usually only one is “of interest”

---

---

---

---

---

---

---

## Gain

- Gain is defined as the ratio of the output value in relation to the input value

$$A_V = \frac{V_{OUT}}{V_{IN}} \quad A_I = \frac{I_{OUT}}{I_{IN}} \quad A_P = \frac{P_{OUT}}{P_{IN}}$$

Voltage Gain    Current Gain    Power Gain

---

---

---

---


---

---

---

## Amplifier Gain

- An Example

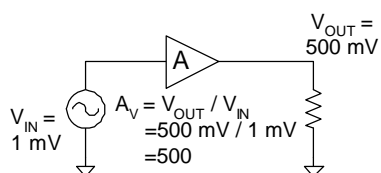


---

---

---

---

---

---

---

## Amplifier Gain

- The gain equation can be manipulated depending on what we need to solve for
  - Voltage gain is used but the same manipulations can be used for current and power

$$A_V = \frac{V_{OUT}}{V_{IN}}$$

$$\Rightarrow V_{OUT} = A_V V_{IN}$$

$$\Rightarrow V_{IN} = \frac{V_{OUT}}{A_V}$$

---

---

---

---


---

---

---

## The General Amplifier Model

- Schematic

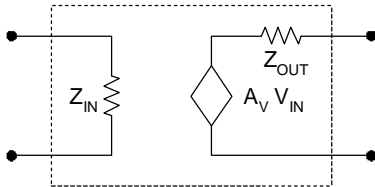


---

---

---

---


---

---

---

## The General Amplifier Model

- Input Voltage

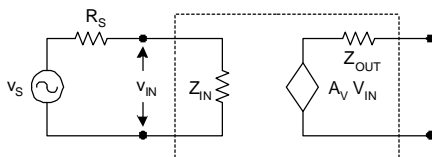

$$v_{IN} = \frac{Z_{IN}}{R_S + Z_{IN}} v_S$$

---

---

---

---

---

---

---

## The General Amplifier Model

- Input Voltage – An Example

$$A_v = 10, v_s = 100\text{mV}, R_s = 500\Omega, Z_{IN} = 1\text{k}\Omega$$

$$\text{ideally } v_{OUT} = A_v v_s = 10 \times 100\text{mV} = 1\text{V}$$

$$\text{but } v_{IN} = \frac{Z_{IN}}{R_s + Z_{IN}} v_s$$

$$v_{OUT} = A_v v_{IN} = A_v \left( \frac{Z_{IN}}{R_s + Z_{IN}} \right) v_s$$

$$= 10 \left( \frac{1\text{k}\Omega}{500\Omega + 1\text{k}\Omega} \right) 100\text{mV} = 667\text{mV}$$

---

---

---

---


---

---

---

## The General Amplifier Model

- Effect of Output Impedance

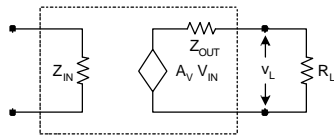

$$v_{OUT} = A_v v_{in}$$

$$v_L = \frac{R_L}{Z_{OUT} + R_L} v_{OUT}$$

---

---

---

---

---

---

---

## The General Amplifier Model

- The Effect of Output Impedance – An Example

$$v_{OUT} = 1\text{V}, Z_{OUT} = 100\Omega, R_L = 500\Omega$$

$$\text{ideally } v_L = v_{OUT} = 1\text{V}$$

$$\text{but } v_L = \frac{R_L}{Z_{OUT} + R_L} v_{OUT}$$

$$= \frac{500\Omega}{100\Omega + 500\Omega} 1\text{V} = 833\text{mV}$$

---

---

---

---

---

---

---

## The General Amplifier Model

- Effective Voltage Gain

- When we combine the effects of the source resistance, amplifier input and output impedance and load resistance the actual gain will be considerably less than the ideal gain ( $A_V$ )
- This reduced gain is called the *effective gain* ( $A_{V(\text{eff})}$ )

$$A_{V(\text{eff})} = \frac{v_L}{v_S}$$

---

---

---

---

---

---

---

---

## The General Amplifier Model


- Effective Gain – An Example

$$v_S = 10\text{mV}, R_S = 150\Omega.$$

$$A_V = 100, Z_{IN} = 1\text{k}\Omega, Z_{OUT} = 200\Omega$$

$$R_L = 1.5\text{k}\Omega$$
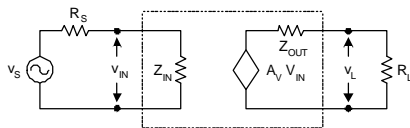
$$\text{quick and dirty - } v_L = A_V v_S = 100 \times 10\text{mV} = 1\text{V}$$




---

---

---

---

---

---

---

---

## The General Amplifier Model

- Effective Gain – An Example

$$v_S = 10\text{mV}, R_S = 150\Omega.$$

$$A_V = 100, Z_{IN} = 1\text{k}\Omega, Z_{OUT} = 200\Omega$$

$$R_L = 1.5\text{k}\Omega$$

$$v_{IN} = \frac{Z_{IN}}{R_S + Z_{IN}} v_S = \frac{1\text{k}\Omega}{150\Omega + 1\text{k}\Omega} 10\text{mV} = 8.70\text{mV}$$

$$v_{OUT} = A_V v_{IN} = 100 \times 8.70\text{mV} = 870\text{mV}$$

$$v_L = \frac{R_L}{Z_{OUT} + R_L} v_{OUT} = \frac{1.5\text{k}\Omega}{200\Omega + 1.5\text{k}\Omega} 870\text{mV} = 768\text{mV}$$

$$A_{V(\text{eff})} = \frac{v_L}{v_S} = \frac{768\text{mV}}{10\text{mV}} = 76.8$$

---

---

---

---

---

---

---

---

## The Ideal Voltage Amplifier

- Characteristics
  - The ideal voltage amplifier has the characteristics:
    - Infinite Gain
    - Infinite input impedance ( $v_{IN} = v_S$ )
    - Zero output impedance ( $v_L = v_{OUT}$ )
  - While no amplifier is truly ideal - we will find the op amp comes close enough to “effectively” have these characteristics

---

---

---

---

---

---

---

## BJT Amplifier Configurations

- Amplifier Properties

| Property  | Low   | Midrange | High   |
|-----------|-------|----------|--------|
| Gain      | < 100 | 100-1000 | > 1000 |
| Impedance | < 1k  | 1k – 10k | > 10k  |

---

---

---

---


---

---

---
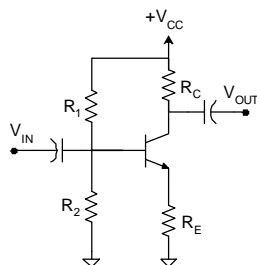
## The Common-Emitter (CE) Amplifier

- The most widely used of all BJT amplifiers
  - Midrange voltage and current gain
  - High power gain
  - Midrange input and output impedance




---

---

---

---


---

---

---
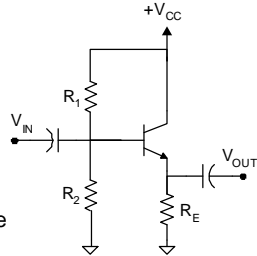
## The Common-Collector (CC) Amplifier

- Used for its current gain and impedance characteristics
  - Midrange current gain
  - Low voltage gain
  - High input impedance
  - Low output impedance




---

---

---

---

---


---

---

---
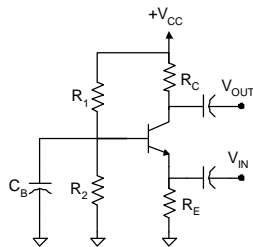
## The Common-Base (CB) Amplifier

- Rarely used except in high frequency circuits
  - Midrange voltage gain
  - Low current gain
  - Low input impedance
  - High output impedance




---

---

---

---

---

---

---

---

## Amplifier Characteristics

- Comparison of CE, CC & CB Characteristics

|    | $A_V$    | $A_I$    | $A_P$    | $Z_{IN}$ | $Z_{OUT}$ |
|----|----------|----------|----------|----------|-----------|
| CE | Midrange | Midrange | High     | Midrange | Midrange  |
| CC | <1       | Midrange | Midrange | High     | Low       |
| CB | Midrange | <1       | Midrange | Low      | High      |

---

---

---

---

---

---

---

---

## BJT Amplifiers

- Determining The Configuration
  - To determine what configuration amplifier one terminal of the transistor will not have in input or output - this is the “common” terminal
    - Common Emitter (CE)
    - Common Collector (CC)
    - Common Base (CB)

---

---

---

---

---

---

---

## Amplifier Classifications

- Class A amplifiers
  - a single transistor that conducts during the entire period of the input
- Class B amplifier
  - two transistors each of which conduct during one-half of the input period
- Class C amplifier
  - a single transistor that conducts for less than one-half the input period

---

---

---

---

---

---

---

## Amplifier Efficiency

- Transistor amplifiers increase the power of the ac input signal by drawing power from the dc supply
- An ideal amplifier would have an efficiency of 100%
  - real world amplifier efficiencies are always less than 100 %

---

---

---

---

---

---

---



### Amplifier Efficiency

- When calculating amplifier efficiency we usually disregard the input signal power
- Efficiency is represented by the Greek letter  $\eta$  ?

$$\eta = \frac{P_L}{P_{dc}} \times 100$$

---

---

---

---

---

---

---

### General Amplifier Characteristics

- Distortion
  - An ideal amplifier produces an exact replica of the input signal
  - Distortion is any deviation of the output signal from the exact wave shape of the input signal

---

---

---

---

---

---

---

### General Amplifier Characteristics

- **Class A amplifiers** have the following characteristics
  - an active device that conducts during the entire input period
  - an output that contains very little distortion
  - a maximum theoretical efficiency of 25%
- Generally used as “small signal” amplifiers

---

---

---

---


---

---

---

### General Amplifier Characteristics

- Class A Amplifier

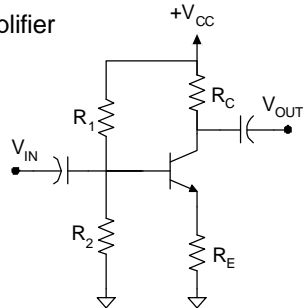

---

---

---

---

---

---

---

### General Amplifier Characteristics

- **Class B amplifiers** have the following characteristics
  - two transistors biased at cutoff - each conducts during one-half the input signal period
  - an output that contains little distortion
  - a maximum theoretical efficiency of 78.5%
- Primarily used as a power amplifier

---

---

---

---


---

---

---

### General Amplifier Characteristics

- Class B Amplifier

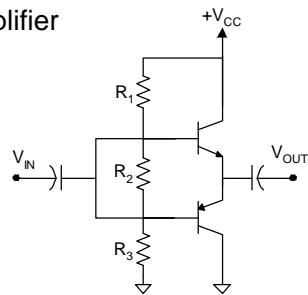

---

---

---

---

---

---

---

### General Amplifier Characteristics

- The **class AB amplifier** is a variation of the class B amplifier that uses diodes to bias the transistors so they conduct over slightly more than one-half the input period
- Class AB amplifiers are used to avoid *crossover distortion* which is often a problem in class B amplifiers

---

---

---

---


---

---

---

### General Amplifier Characteristics

- Class AB Amplifier

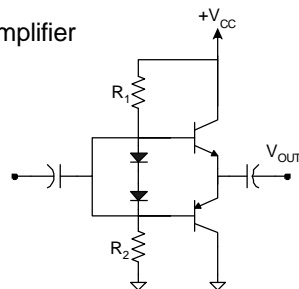

---

---

---

---

---

---

---

### General Amplifier Characteristics

- Class C amplifiers have the following characteristics
  - a single transistor that conducts for less than one-half the input period
  - an output that probably has some distortion
  - a maximum theoretical efficiency of 99%
- A *tuned amplifier* that finds limited use due to its distortion characteristics

---

---

---

---


---

---

---

## General Amplifier Characteristics

- Class C Amplifier

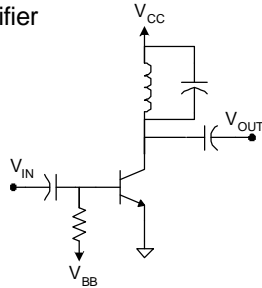

## Decibels

- Gains - power, voltage or current are often given in decibels (dB)
- The decibel is a power ratio measurement used to simplify the recording of very large (or very small) numbers

## Decibels

- Definition

– A decibel (dB) is 10 times the common logarithm of the ratio of output power divided by the input power or:

$$A_{P(dB)} = 10 \log A_P = 10 \log \frac{P_{OUT}}{P_{IN}}$$

## Decibels

- Definition

- To “reverse” the process or find the straight power gain from the power gain in dB we simply:

$$A_p = \log^{-1} \frac{A_{p(dB)}}{10} = 10^{\frac{A_{p(dB)}}{10}}$$

---

---

---

---

---

---

---

## Decibels

- An Example

$$A_p = 2500$$

$$A_{p(dB)} = 10 \log A_p = 10 \log(2500) = 34dB$$

convert back to straight power gain

$$A_p = \log^{-1} \left( \frac{A_{p(dB)}}{10} \right) = 10^{\left( \frac{A_{p(dB)}}{10} \right)} = 10^{\left( \frac{34}{10} \right)} = 2512$$

---

---

---

---

---

---

---

## Decibels

| Gain   | dB value | Gain     | dB value |
|--------|----------|----------|----------|
| 2      | 3        | ½        | -3       |
| 4      | 6        | ¼        | -6       |
| 16     | 12       | 1/16     | -12      |
| 100    | 20       | 1/100    | -20      |
| 1,000  | 30       | 1/1,000  | -30      |
| 10,000 | 40       | 1/10,000 | -40      |

---

---

---

---

---

---

---

## The dBm Reference

- Definition
  - Power values are sometimes expressed as a ratio to a power level – in this case 1 mW

$$P_{dBm} = 10 \log \frac{P}{1mW}$$

---

---

---

---

---

---

---

## The dBm Reference

- Definition
  - Of course we may need to transform a power in dBm back to watts

$$P = \log^{-1} \left( \frac{P_{dBm}}{10} \right) mW = 10^{\left( \frac{P_{dBm}}{10} \right)} mW$$

---

---

---

---

---

---

---

## dB Voltage Gain

- Definition
  - Often we are interested in voltage gain instead of power gain – but we must remember dB is a power ratio

$$A_{V(dB)} = 20 \log(A_v) = 20 \log \frac{V_{OUT}}{V_{IN}}$$

---

---

---

---

---

---

---

## dB Voltage Gain

- Definition
  - Of course there will be times we have the voltage gain in dB and want straight voltage gain

$$A_V = \log^{-1} \left( \frac{A_{V(dB)}}{20} \right)$$

---

---

---

---

---

---

---

## The dBV Reference

- Definition
  - You may also run into dBV or decibel referenced to one volt
  - This is calculated exactly the same as dBm except you must remember the extra factor of two required working with dB and volts

$$V_{dBV} = 20 \log \frac{V_V}{1V}$$
$$V_V = \log^{-1} \frac{V_{dBV}}{20}$$
$$= 10^{\frac{V_{dBV}}{20}}$$

---

---

---

---

---

---

---

## Working With dB

- Changes in dB Gain
  - If the voltage gain of an amplifier (or system) changes by X dB then the power gain has also changed by the same X dB  
this assumes the load the amplifier is driving doesn't change
  - note this does not mean the power gain will be the same value as the voltage gain - just that if they change they will change by the same amount

---

---

---

---

---

---

---

## Working With dB

- Review
  - dB are logarithmic forms of the power or voltage gain
  - Power gain in db is found by -  $10 \log A_p$
  - Voltage gain in db is found by -  $20 \log A_v$
  - Never multiply dB values - see 1st bullet
  - Do not mix values in dB and normal format - use only one or the other

---

---

---

---

---

---

---