

BOĞAZIÇI UNIVERSITY
ELECTRICAL&ELECTRONIC ENGINEERING DEPARTMENT

EE 327-ELECTRICAL NETWORK LAB. REPORT

Number of The Experiment : **3**.....
Name of The Experiment : **Transients in Linear Circuits**

Name of The Student: Çağdaş Kayra Akman
Name of The Partners: Onur Derin
Group No: Wednesday 1
Name of The Lab. Assistant:

Date of The Experiment:	23.10.2002
Dadline for The Submission of the Report	30.10.2002
Date of The Submission of the Report:	30.10.2002
Delay	

Do not fill in the grading table. It is for the instructor

Grading

General		/20
Data		/30
Discussion		/20
Answers		/30
Total		/100
Delay		
SCORE		/100

1. THE EQUIPMENT USED IN THE LAB

1. HAMEG HM-203-7 Dual Trace Oscilloscope with x10 probe
2. Escort EDM 168A Digital Multimeter
3. Black Star Jupiter 2000 Signal Generator
4. Resistors, capacitors and inductors of different values (see section 3 for these values)

2. THEORY AND METHOD

The objective of this experiment was to inspect the transient responses of different circuits, RC, RL and RLC circuits, with varying component values and at different pulse input frequencies.


The energy storage elements such as capacitors and inductors store energy by building an electric and a magnetic field, respectively. The building-up of these fields, or their weakening, occurs due to the accumulated charge and induced voltage in the capacitor and across the inductor, respectively. These don't occur immediately but according to general formulas:

$V = A * (1 - e^{-t/\tau})$ during the building up the fields, where V is the voltage across the capacitor in an RC circuit and across the resistor in an RL circuit, A is the amplitude of the input voltage, τ is the time constant ($\tau = R * C$ for RC circuit, $\tau = L/R$ for RL circuit), and


$V = A * e^{-t/\tau}$ during the weakening of the fields.

5τ is assumed to be the time period in which the exponential $e^{-t/\tau}$ reaches practically zero. f_{max} is calculated according to $f_{max} = 1/10\tau$ since the capacitor voltage, resistor voltage in the RL circuit, has to reach the input voltage (1V) and then 0V within a period, i.e. 5τ for charging up and 5τ for discharging has to pass.


Experimental Setup 1:

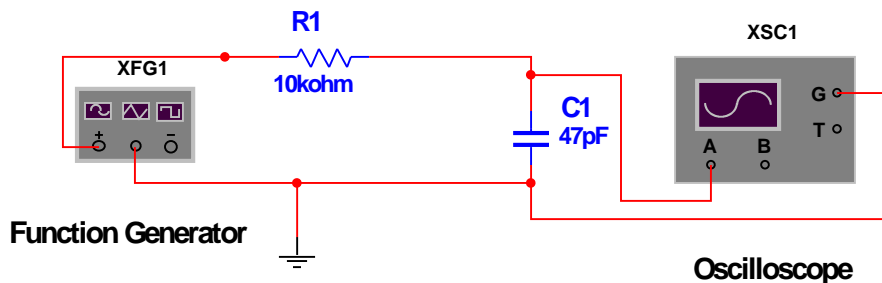

Experimental Setup 2:

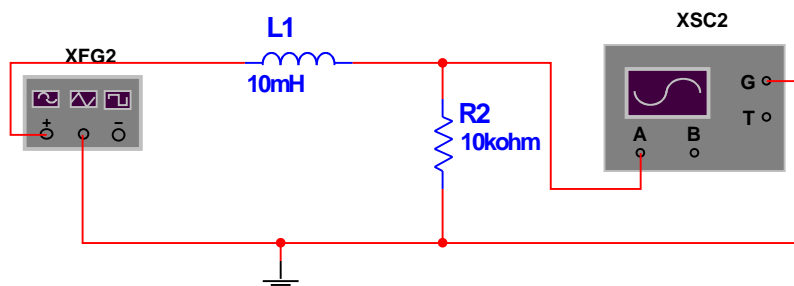

Experimental Setup 3:

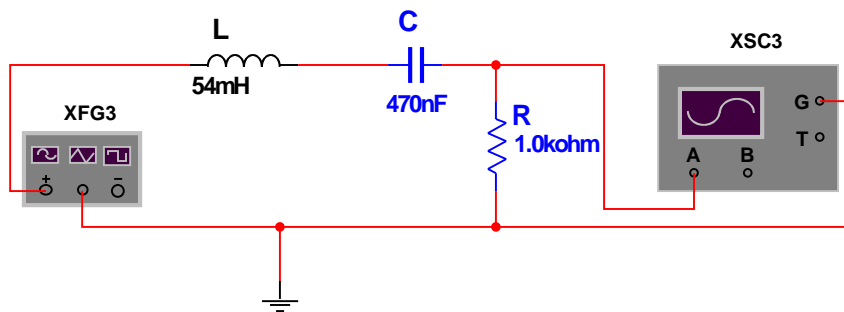

The first two circuits shown above are implemented with the component values tabulated below.

3. DATA

Table 1

	R (Ω)	C (F)	t (s)	$5t$ (s)	f_{max} (Hz)	f_{max} (Hz) (experimental)
1	1k	47p	47n	235n	2.13M	1.8M
2	1k	1n	1 μ	5 μ	100k	108k
3	1k	470n	470 μ	2.35m	213	200
4	10k	47p	470n	2.35 μ	213k	200k
5	10k	1n	10 μ	50 μ	10k	9.2k

t	<i>Charging Period</i>		<i>Discharging Period</i>	
	<i>Calculated</i>	<i>Measured</i>	<i>Calculated</i>	<i>Measured</i>
1	0.632	0.55	0.37	0.4
2	0.865	0.7	0.135	0.15
3	0.950	0.85	0.050	0.07
4	0.982	0.96	0.018	0.02
5	0.993	0.98	0.007	0.01

	R (Ω)	L (H)	t (s)	$5t$ (s)	f_{max} (Hz)	f_{max} (Hz) (experimental)
1	1k	10m	10 μ	50 μ	10k	10k
2	4k7	10m	2.13 μ	10.65 μ	47k	50k
3	10k	10m	1 μ	5 μ	100k	105k

<i>t</i>	<i>Charging Period</i>		<i>Discharging Period</i>	
	<i>Calculated</i>	<i>Measured</i>	<i>Calculated</i>	<i>Measured</i>
1	0.632	0.6	0.37	0.4
2	0.865	0.85	0.135	0.15
3	0.950	0.93	0.050	0.05
4	0.982	0.95	0.018	0.02
5	0.993	0.98	0.007	0.01


For all graphs, the amplitude of the input signal is 1V. The time axis is adjusted according to the frequency of the signal.

RC circuit:


$R=10\text{k}\Omega$, $C=47\text{pF}$

Voltages across the capacitor:


$f=1\text{kHz}$

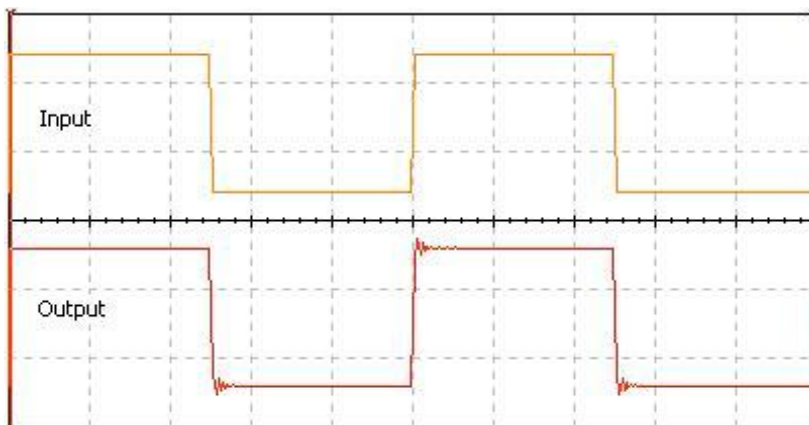


$f=f_{\text{max}}=200\text{kHz}$

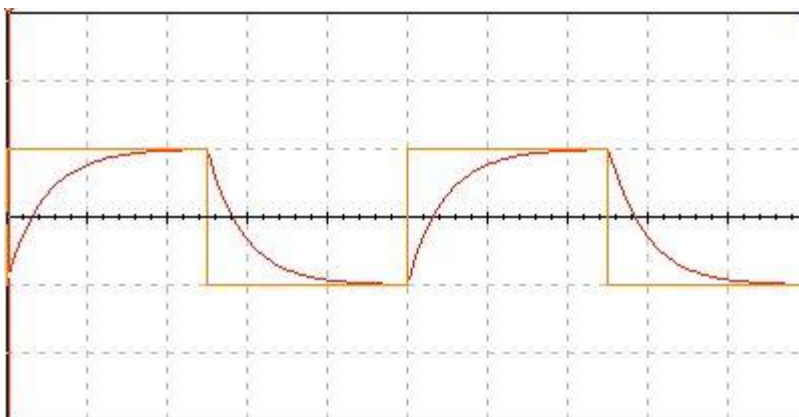

$f=1.06\text{MHz}=1/2\tau$

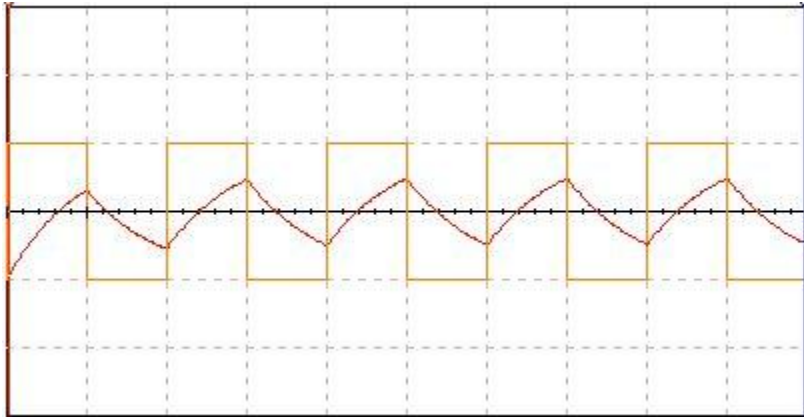

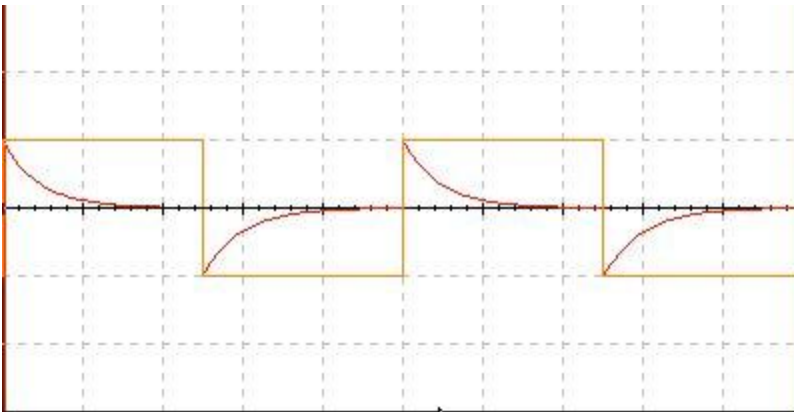
Voltage across the resistor:
 $f=200\text{kHz}$




For other R and C values, the graphs look like the first one, and at their f_{max} values for input frequencies, the graphs look like the second graph.

$R=10\text{k}\Omega$, $L=10\text{mH}$

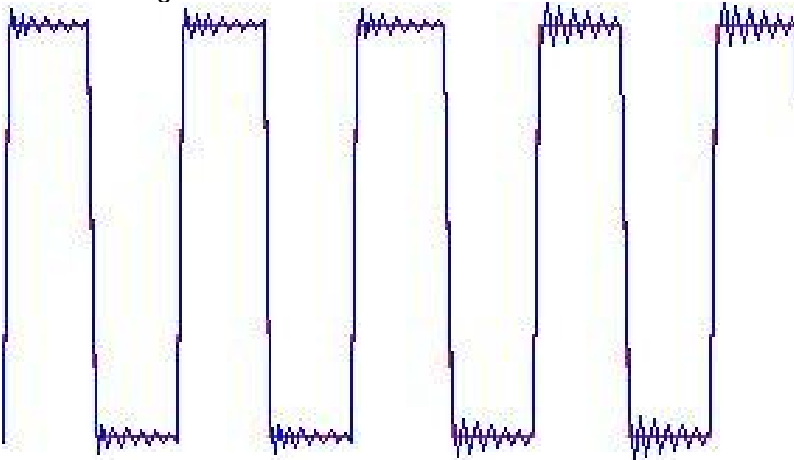Voltage across the resistor at $f=1\text{kHz}$




$f = f_{\max} = 105\text{kHz}$

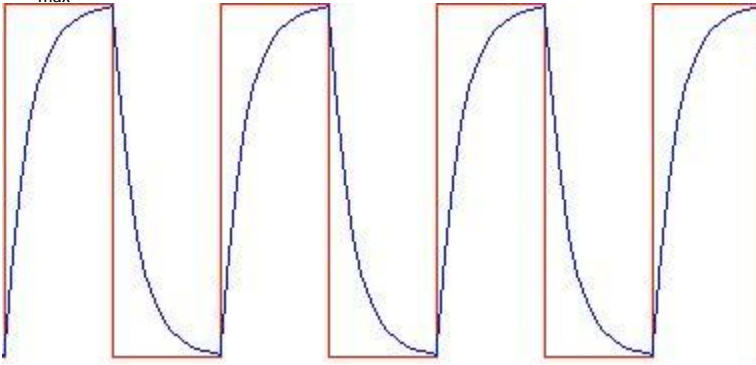

For other R and L values, similar graphs are obtained.

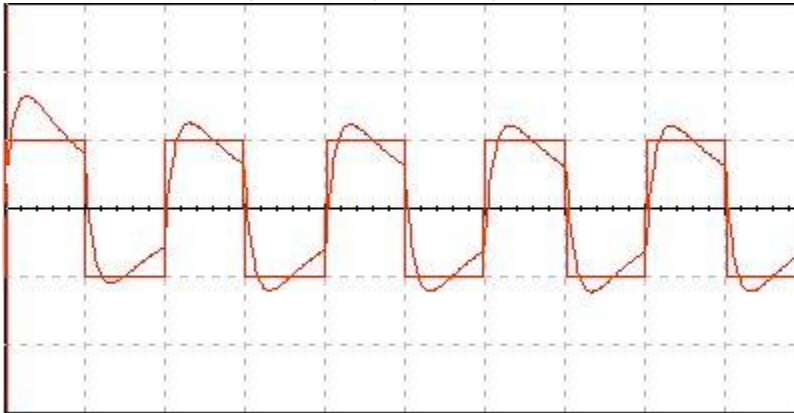RLC circuit: $R=1\text{k}\Omega$, $C=470\text{nF}$, $L=54\text{mH}$, $f=1\text{kHz}$:



For $\frac{R}{2L}C = 1$, R should be $230\text{ k}\Omega$, given that $C=470\text{nF}$ and $L=54\text{mH}$. However, due to absence of adequate resistors, the circuit was experimented only with a $1\text{k}\Omega$ resistor, ie. For $\frac{R}{2L}C < 1$.

4. ANALYSIS AND DISCUSSION

The theoretical experimental f_{\max} values conformed to the experimental values very well. The minor differences are due to reading errors on the oscilloscope screen. The imperfections of function generator affected the signal quality considerably, which in return affected the signal output observed with the oscilloscope. Especially at the edges of the square wave, unwanted glitches occurred.

The effect of 5τ was observed clearly. At the frequency $1/10\tau$, the capacitor voltage in the RC circuit, or the resistor voltage in the RL circuit reached the input voltage at $T/2$, the half period as shown in the graphs.

5. ANSWERS TO THE QUESTIONS

No questions were given.