

**Ley de tensiones de Kirchhoff en el dominio de la frecuencia**

$$v_1(t) + v_2(t) + \dots + v_n(t) = 0$$

$$V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \dots + V_{mn} \cos(\omega t + \theta_n) = 0$$

$$V_{m1} e^{j(\omega t + \theta_1)} + V_{m2} e^{j(\omega t + \theta_2)} + \dots + V_{mn} e^{j(\omega t + \theta_n)} = 0$$

$$\text{Re} \left[ V_{m1} e^{j(\omega t + \theta_1)} + V_{m2} e^{j(\omega t + \theta_2)} + \dots + V_{mn} e^{j(\omega t + \theta_n)} = 0 \right]$$

$$\text{Re} \left[ (V_1 + V_2 + \dots + V_n) e^{j\omega t} = 0 \right]$$

$$V_1 + V_2 + \dots + V_n = 0$$

1

**Ley de corrientes de Kirchhoff en el dominio de la frecuencia**

$$i_1(t) + i_2(t) + \dots + i_n(t) = 0$$

$$I_{m1} \cos(\omega t + \phi_1) + I_{m2} \cos(\omega t + \phi_2) + \dots + I_{mn} \cos(\omega t + \phi_n) = 0$$


$$I_{m1} e^{j(\omega t + \phi_1)} + I_{m2} e^{j(\omega t + \phi_2)} + \dots + I_{mn} e^{j(\omega t + \phi_n)} = 0$$

$$\text{Re} \left[ I_{m1} e^{j(\omega t + \phi_1)} + I_{m2} e^{j(\omega t + \phi_2)} + \dots + I_{mn} e^{j(\omega t + \phi_n)} = 0 \right]$$

$$\text{Re} \left[ (I_1 + I_2 + \dots + I_n) e^{j\omega t} = 0 \right]$$

$$I_1 + I_2 + \dots + I_n = 0$$

2

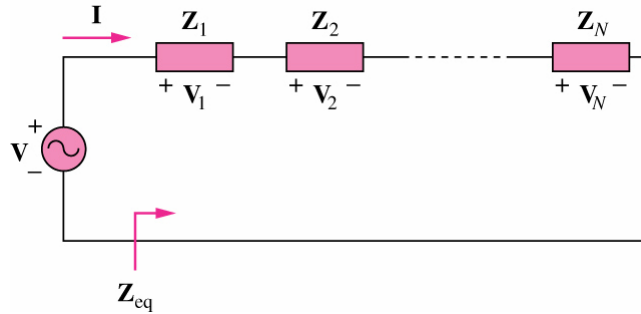
**Combinaciones de impedancias en serie**

$$V = V_1 + V_2 + \dots + V_n = I(Z_1 + Z_2 + \dots + Z_n)$$

$$Z = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_n$$

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$


3

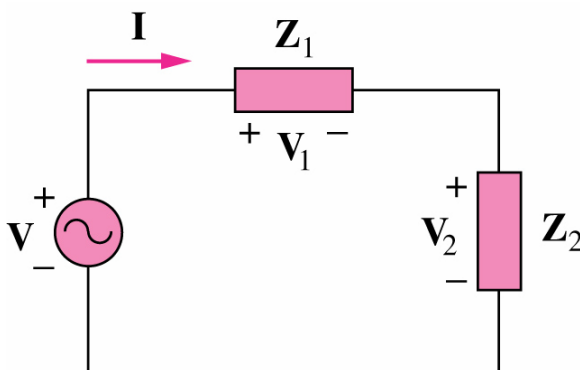**Divisor de tensión**

$$I = \frac{V}{Z_1 + Z_2}$$

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$


4

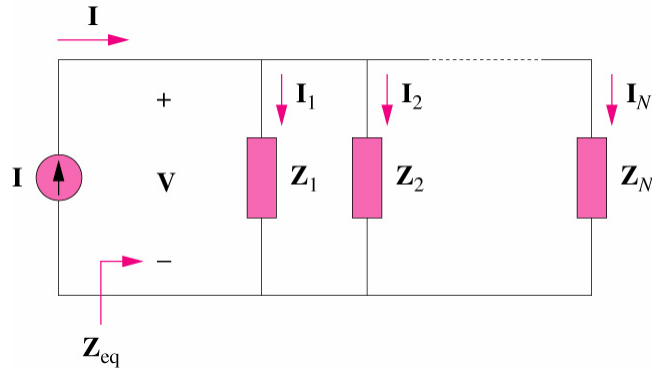**Combinaciones de impedancias en paralelo**

$$I = I_1 + I_2 + \dots + I_n = \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \right) V$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \quad Y_{eq} = Y_1 + Y_2 + \dots + Y_n$$


5

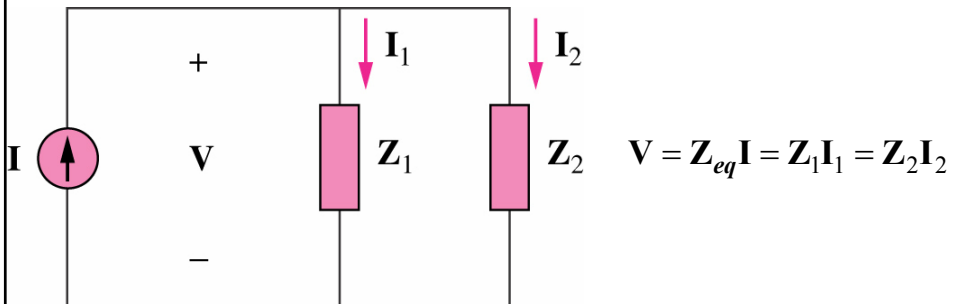**Divisor de corriente**

$$V = Z_{eq} I = Z_1 I_1 = Z_2 I_2$$

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

6

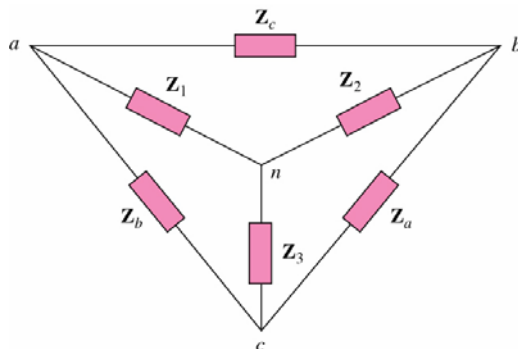
**Transformación estrella – delta (Y – Δ)**

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

7

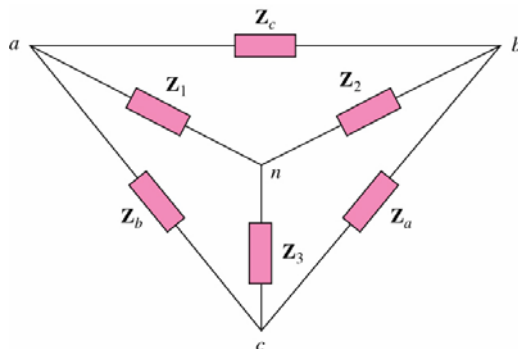**Transformación delta – estrella (Δ – Y)**

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$


$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

8

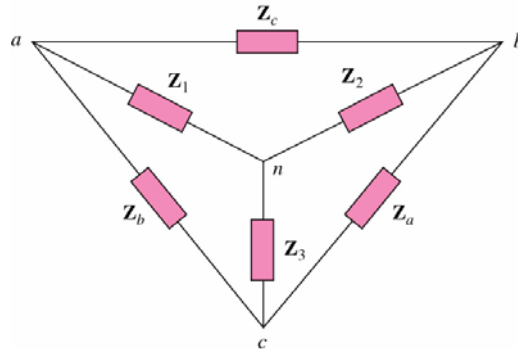**Transformaciones en circuitos equilibrados**

- Se dice que un circuito delta o estrella está equilibrado si las impedancias en las tres ramas son iguales entre sí



$$Z_{\Delta} = 3Z_Y \quad \text{o} \quad Z_Y = 3Z_{\Delta}$$

$$Z_Y = Z_1 = Z_2 = Z_3 \quad \text{y} \quad Z_{\Delta} = Z_a = Z_b = Z_c$$

9

**Ejemplo I**

$$Z_a = 10 \, \Omega$$


$$Z_b = 5 - j2 \, \Omega$$

$$Z_c = 8 + j5 \, \Omega$$

$$Z_1 = 2.19 + j0.11 \, \Omega$$

$$Z_2 = 3.70 - j1.69 \, \Omega$$

$$Z_3 = 2.03 - j1.33 \, \Omega$$

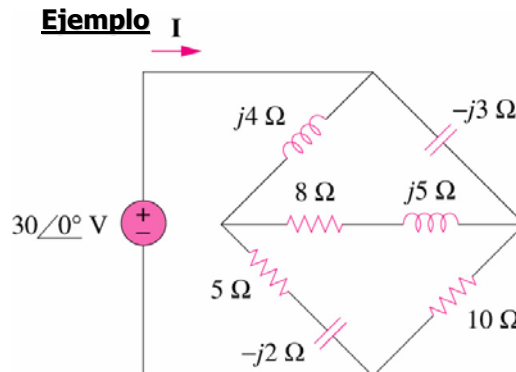

$$Z_{eq} = (Z_1 + j4 \, \Omega) \parallel (Z_2 - j3 \, \Omega) + Z_3$$

$$Z_{eq} = 4.70 - j0.31 \, \Omega = 4.71 \angle -3.80^\circ \, \Omega$$

$$I = 30 \angle 0^\circ \, V / 4.71 \angle -3.80^\circ \, \Omega = 6.36 \angle +3.80^\circ \, A$$

10