

EEE523 Home Work #1

Fuding Ge

1. **Question:** The transition (cutoff) frequency, f_T , is defined as follows:


$$f_T = \frac{g_m}{2\pi(C_{gd} + C_{gs})}$$

- (1) Suppose the gate resistance is significant (R_G) and the device is modeled as a distributed set of n transistors each with a gate resistance equal to R_G/n . Find f_T .
- (2) For a given bias current, the minimum allowable drain-source voltage for operation in saturation can be reduced by increasing the width and hence the capacitance of the transistor. Prove the following relationship

$$f_T = \frac{3}{2} \frac{\mu_n}{2\pi} \frac{V_{gs} - V_t}{L^2}$$

Answer:

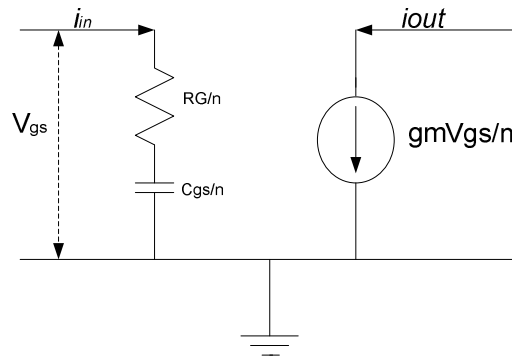(1) We built a simplified model as shown in the following figure:



$$V_{gs} = i_{in} \cdot \left(\frac{RG}{n} + \frac{1}{\omega C_{gs}/n} \right) = i_{in} \cdot \left(\frac{RG}{n} + \frac{n}{\omega C_{gs}} \right)$$

$$i_{out} = \frac{g_m}{n} \cdot i_{in} \cdot \left(\frac{RG}{n} + \frac{n}{\omega C_{gs}} \right)$$

Let

$$\frac{i_{out}}{i_{in}} = \frac{g_m}{n} \cdot \left(\frac{RG}{n} + \frac{n}{\omega C_{gs}} \right) = 1$$

We get

$$\omega_T = \frac{1}{C_{gs}} - RG$$

We can rewrite it as:

$$f_T = \frac{\frac{1}{RG} - RG}{2\pi C_{gs} g_m}$$

We can see that the transition frequency becomes smaller when we consider the gate resistance.

(2) When the transistor is in saturation region, C_{gd} is quite small and can be neglected. We also have:

$$C_{gs} = \frac{2}{3} WLCox$$


and

$$g_m = \mu_n Cox \frac{W}{L} (V_{gs} - V_t)$$

Then

$$f_T = \frac{3}{2} \frac{g_m}{2\pi WLCox} = \frac{3}{2} \frac{\mu_n Cox \frac{W}{L} (V_{gs} - V_t)}{2\pi WLCox} = \frac{3}{2} \frac{\mu_n (V_{gs} - V_t)}{2\pi L^2}$$

2

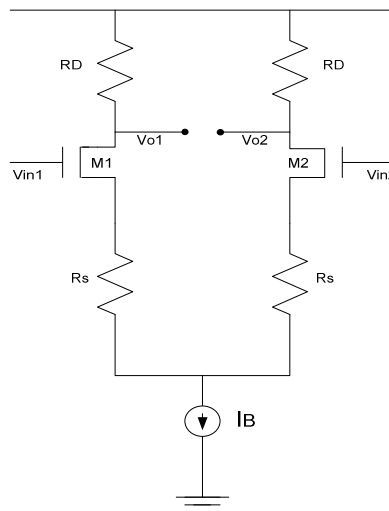

Calculate the small signal voltage gain:

$$A_v = \frac{V_{o2} - V_{o1}}{V_{in2} - V_{in1}}$$

Answer: This is a fully differential amplifier with source degeneration. We can use the “half-circuit” technique to calculate the gain.


We know that the equivalent transconductance of the circuit is:

$$G_m = \frac{\partial I_D}{\partial V_{in}} = \frac{g_m}{1 + g_m R_s}$$

Then

$$A_v = \frac{V_{o2} - V_{o1}}{V_{in2} - V_{in1}} = -G_m R_D = \frac{-g_m R_D}{1 + g_m R_s}$$

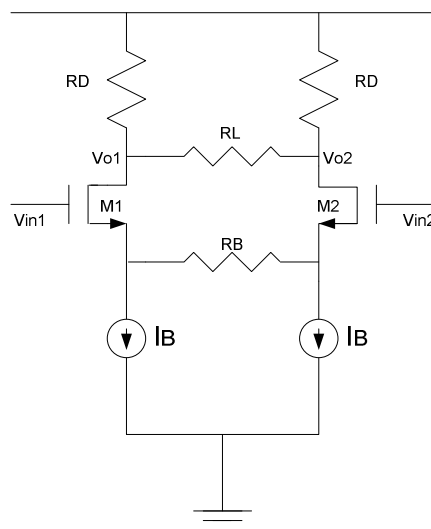3 Calculate the differential-mode and common-mode gain.



Answer:

Differential-mode gain:

The circuit can be treated as an amplifier with source degeneration with a resistor of $R_B/2$. The load will be $R_D // R_L/2$.

Then the differential mode gain is:

$$A_{vd} = \frac{V_{o2} - V_{o1}}{V_{in2} - V_{in1}} = \frac{-g_m R_D \parallel \frac{R_L}{2}}{1 + g_m \frac{R_B}{2}}$$


Common mode gain:

When the small signal input $v_{in}=0$, there is no current flow through R_B or R_L . If we assume the resistance of the current source I_B is R_{SS} , then the equivalent resistance of the 2 I_B is $R_{SS}/2$. Us the equation (4.28) in the textbook, we have:

$$A_{vc} = \frac{RD/2}{1/(2gm) + RSS/2} = \frac{RD}{1/gm + RSS}$$

4 Show the shielding effect of cascode current mirror circuit. Use the transistor parameter in the text book (Table 2.1). You can use any voltage, current, and transistor size -Simulation

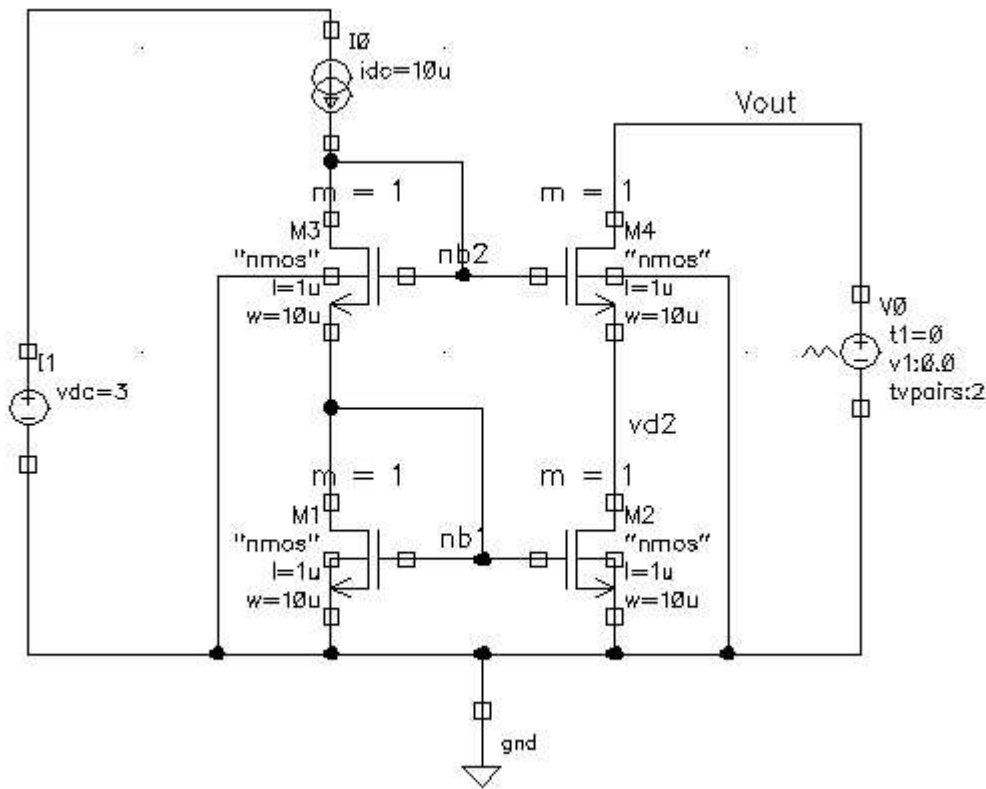The test circuit is shown in the following figure. The voltage V_{out} is swept from 0 V to 3 V in 100 ns. We checked the voltage V_{d2} .



Test circuit for shielding effects in cascode current mirror

The simulated result is shown in the following figure. It can be see that once the output voltage V_{out} in the range that M_2 and M_4 working in the saturation region, though V_{out} change a lot, V_{d2} almost keep the same value. This is the shielding effects of cascode current mirror.

(1) The output impedance is:

$$R_o = R(1 + A_L)$$

Where R is the output impedance without the feedback due to M1 and M3. Treated M2 as the source degeneration resistance of M4, we have:

$$R = 2r_{o4}$$

We also have:

$$A_L = \frac{gm1(r_{o1} \parallel r_{in})}{2}$$

Assume $r_{in} = r_{o1}$ we have:

$$R_o = 2r_{o4} \left(1 + \frac{gm1r_{o1}}{4}\right) = r_{o4} \frac{gm1r_{o1}}{2}$$

(2) Minimum output voltage $V_{o\min}$:

For the operation of M2 in saturation region, the voltage of M2 drain should be:

$$V_{d2} = V_{GS}$$

$$V_{d4} = V_{d2} + V_{GS} - V_T = 2V_{GS} - V_T$$

Hence we have:

$$V_{o\min} = 2V_{GS} - V_T$$

(3) Minimum input voltage $V_{in\min}$:

$$V_{in\min} = V_{o\min} = 2V_{GS} - V_T$$