

4. The minimum output voltage (V_{MIN}) at $I_{\text{OUT}} = 100\mu\text{A}$ must be at least 1.5V. For the purposes of this design project, V_{MIN} will be considered the output voltage at which I_{OUT} falls to 95% of its nominal value.
5. The layout area of the amplifier must be less than 0.2mm^2 . Use the following formula to determine the circuit area:

$$\text{Total area} = 10 \times (\text{Area of all MOSFET gates})$$

The areas of the R_{LOAD} resistor and the I_{IN} current source should not be considered in the calculation.

2. Design procedure

Obviously this circuit use negative feedback technique to stabilize the output current and boost the output impedance to a higher value, which is called “regulated cascode current mirror”[1]. If transistors M4 is not there, M3 and M5 form the conventional cascode current mirror. With the feedback through M4, the output impedance of this topology is similar to a triple cascode, without the expanse of voltage headroom. The transistors M4 and M5 make up the negative feedback loop, which stabilize I_{out} . If I_{out} were to increase, then since a constant bias of M3 due to the constant input current I_{in} , the voltage at the drain of M3 would rise, which in turn increase the current through M4. Since the current through is also constant, the voltage at the drain, or the gate of M5, would decrease, thereby offsetting the increase in I_{out} by decreasing V_{GS5} .

Now we do some quantitative analysis on this circuit. The small-signal equivalent circuit of transistors M3, M4, M5 and M7 (which is treated as an idea current source), which is used to calculate the output impedance, is shown in Fig.2.

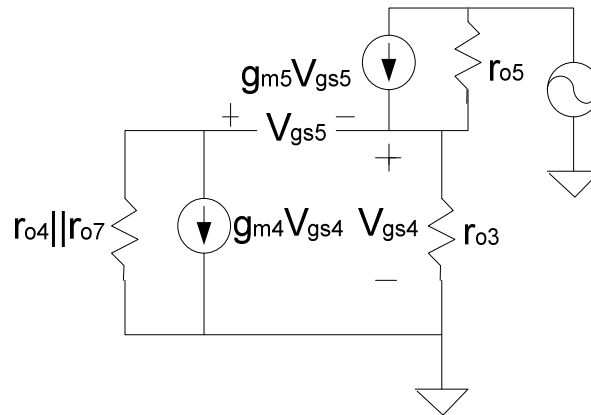


Fig.2 Small-signal test circuit to calculate the output impedance of the regulated cascode current mirror

$$V_{gs4} = i_t \cdot r_{o3} \quad (1)$$

$$V_{gs5} = -V_{gs4} [1 + g_{m4} (r_{o4} \parallel r_{o7})] = -i_t \cdot r_{o3} [1 + g_{m4} (r_{o4} \parallel r_{o7})] \quad (2)$$

$$i_t = g_{m5} V_{gs5} + \frac{v_t - V_{gs4}}{r_{o5}} \quad (3)$$

Fuding Ge, EEE523: Advanced Analog Circuit Design

From (1), (2), (3), we can get:

$$R_{out} = \frac{V_t}{i_t} = g_{m4}(r_{o4} \parallel r_{o7})g_{m5}r_{o3}r_{o5} \quad (4)$$

We can calculate the output impedance in another way. M4 and M7 form the feedback amplifier with gain of:

$$A_{fb} = g_{m4}(r_{o4} \parallel r_{o7}) \quad (5)$$

The output impedance of the cascoded transistor without feedback amplifier is:

$$R_{om3,5} = g_{m5}r_{o3}r_{o5} \quad (6)$$

With the feedback amplifier, the output impedance will be boosted by a factor of A_{fb} , then the output impedance will:

$$R_{out} = A_{fb} \cdot R_{om3,5} = g_{m4}(r_{o4} \parallel r_{o7})g_{m5}r_{o3}r_{o5} \approx \frac{g_m^2 r_o^3}{2} \quad (7)$$

Now let's have a look at the relationship between the output impedance and bias current. We have:

$$r_o = \frac{1}{\lambda I_D} \quad (8)$$

$$g_m = \sqrt{2u_n C_{ox} \frac{W}{L} I_D} \quad (9)$$

Plugging (8) and (9) into (7), we have:

$$R_{out} = \frac{u_n C_{ox} W}{L \lambda^3 I_D^2} \quad (10)$$

We can see that as the bias current (I_{out}) increases, the output impedance actually decreases! It means that if R_{out} meet the requirement at the highest bias current, which in this project is 100uA, then it will meet the requirement at low bias current.

We totally have 7 transistors, 2 PMOS and 5 NMOS. Let $W_p=3W_n$, all the transistors have same channel length, L , all the NMOS have channel width W_n , for PMOS $W_p=3W_n$. Then the total gate area is: $(5W_n+2 \cdot 3W_n)L=11W_nL$. For the upper limit of W_nL , we have:

$$10 \cdot 11W_nL = 0.2mm^2 = 2 \times 10^5 um^2 \quad (11)$$

$$W_nL \leq 1800um^2 \quad (12)$$

Normally for good analog circuit, $L \geq 3L_{min}$, for a 0.6um technology, we can let $L \geq 2\mu m$, for example, $L=3\mu m$. For a large g_m , we would like small L , but if L is very small, second order effects, for example, short channel effects, may play a big role, so r_o begins to decrease.

3. DC and AC simulations results

Following Fig.3 shows the test bench of the current mirror.

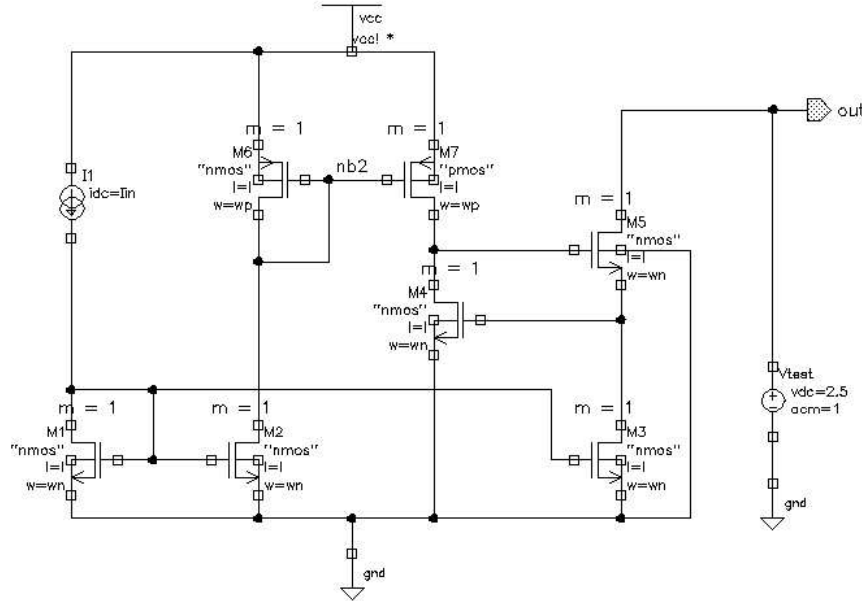


Fig.3 Simulation circuit of the regulated cascode current mirror

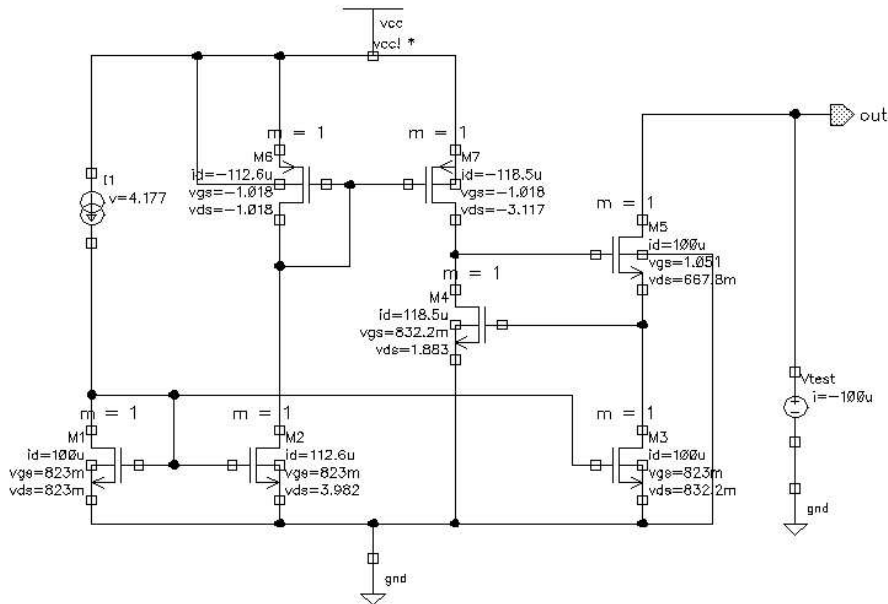


Fig.4 DC operating point of the current mirror

Fuding Ge, EEE523: Advanced Analog Circuit Design

Fig.4 shows the DC operating point of this circuit with a bias current of 100uA. From Fig.4 we can find that all transistors operate in the saturation region, which is a basic requirement of this current mirror. We also can find that the total DC current is about 400uA. The power supply is 5V, so 400uA DC current corresponds to a power dissipation of 2mW, far below the design requirement of 5mW.

Next we test the input output current ratio. We swept the input current from 25uA to 100uA in about 1ms to see the output current. Fig.5 shows the results. It can be see that the current ratio is less than 0.6m, which is below the requirement of 0.01=10m.

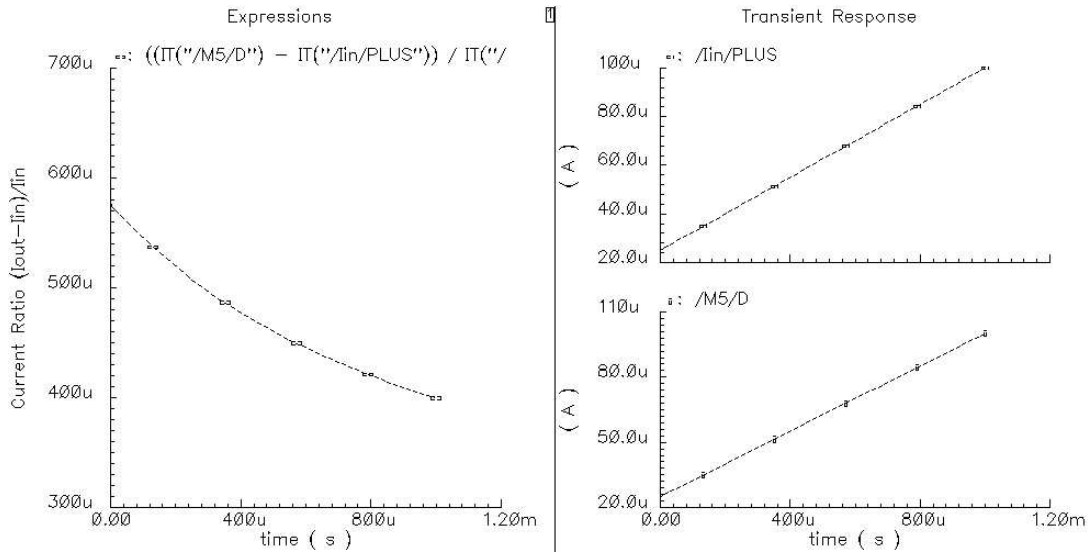


Fig.5 Input output current ratio

Now let's have a look at the output resistance. Fig.6 shows the simulated results using AC analysis with $v_{out}=1.5V$. When $v_{out}=2.5V$, the output resistance is even larger. It can be seen that when the bias current is larger, the output resistance is smaller. For this design, at $I_{in}=100uA$, the (DC) output resistance still can meet the requirement, which is 10GOhms. The -3 dB bandwidth is 36Hz for $I_{in}=25$ and 100Hz for $I_{in}=100uA$.

At last we also checked if the output voltage swing meets the specification or not. Simulations shows even when the output voltage is 1.5V and $I_{in}=100uA$, $I_{out}=100.04uA$, which is still very close to I_{in} .

 


Fig.6 Simulation output impedance R_{out} of the regulated cascode current mirror

4. Schematics with device size, layout area

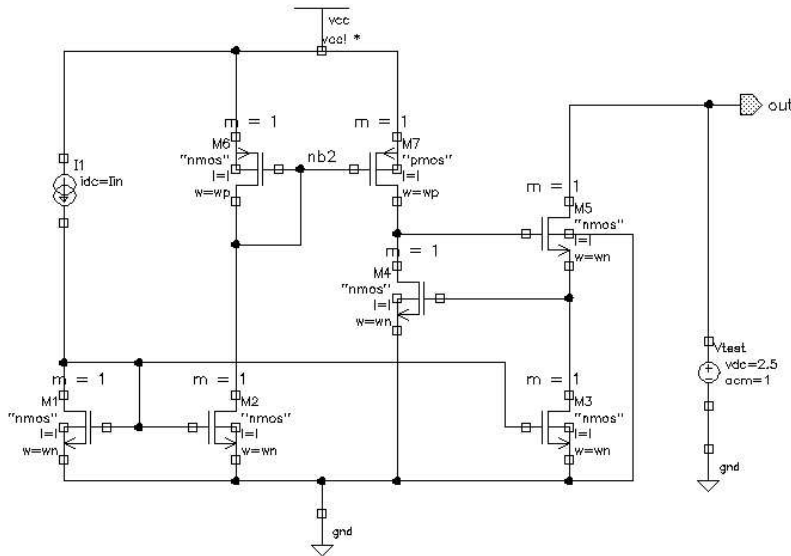


Fig.7 Schematic with device size

Fig.7 shows the device size, which are represented with parameters. All the NMOS transistors are of the same size $L=3\mu\text{m}$ and $W_n=600\mu\text{m}$. The two PMOS transistors are of a size $L=3\mu\text{m}$, and $W_p=1800\mu\text{m}$. With these device sizes, the layout area of the circuitry is around 0.2mm^2 .

5. Summary and Discussion

In this project, we first analyzed regulated cascode current mirror circuitry, derived the necessary equations for the design, and roughly estimated the transistor size. Then following this analysis, we successfully designed a regulated cascode current mirror with all requirements, power, R_{out} , I_{in} and I_{out} mismatch, area, met. See the following table.

Table.1 Summary of the designed regulated cascode current mirror circuitry

Item	Requirement	Design Value	Comments
Transistor size NMOS		$W/L=600\mu/3\mu$	
Transistor size PMOS		$W/L=1800\mu/3\mu$	
Ratio of I_{out} to I_{in}	$<1.00+0.01$	$<1.000+0.001$	
R_{out}	$>10G\ \Omega$	Much larger than $10G\ \Omega$ with all operation conditions	
Area	$<0.2\text{mm}^2$	$<0.2\text{mm}^2$	Depending on the application, the area can be reduced
Power	$<5\text{mW}$	2mV	
-3dB bandwidth	n/a	36 Hz ($I_{out}=25\mu\text{A}$) 100Hz ($I_{out}=100\mu\text{A}$)	Bandwidth can be improved based on application

Every design is a trade off between performance, area, power etc. This design could be modified to meet different application requirements. For example, we could decrease the transistor size to improve the bandwidth at the expense of output resistance. The following figure shows the simulated results with $v_{out}=2.5\text{V}$. We can see that when we decrease the transistor size from $W_n/L=600\mu/3\mu$ to $300\mu/2\mu$ ($W_p=3W_n$), the output resistance decreases too, but with lot of bandwidth improvement.

 


Fig.7 Bandwidth VS Transistor size

Reference

- [1] R. Jacob Baker, Harry W. Wu, David E. Boyce, CMOS circuit design, layout, and simulation, IEEE Press, 1998, New York