

# **PFD-CP Phase Locked Loop Design**

Fuding Ge

© Copyright by Fuding Ge 2001  
All Right Reserved


## Contents

<b>Chapter 1</b>	<b>Introduction.....</b>
1.1	Transfer function between the output phase $\Phi_o$ and the input phase $\Phi_i$
1.2	Values for loop filter components R and C: an example
1.3	Transfer function between phase error $\Phi_e$ and the input phase $\Phi_i$
1.4	Transfer function between $\omega_i$ and $\omega_o$ , $\omega_e$ and $\omega_i$
1.5	PLL operation ranges
1.6	Stead state phase error
1.7	PLL bandwidth and stability analysis
1.8	Noise transfer functions
<b>Chapter 2.</b>	<b>PLL function blocks design</b>
2.1	Project specifications
2.2	PFD design
2.3	Charge pump design
2.4	VCO design
	VCO circuit design
	VCO Phase noise simulation
2.5	Loop filter design
2.6	Frequency divider design
<b>Chapter 3.</b>	<b>PLL simulation results</b>
3.1	Pull-in process
3.2	Frequency step response
3.3	Phase step response
3.4	Noise simulation
	3.4.1 Fourer analysis
	3.4.2 Cycle-to-cycle jitter simulation
<b>Appendix</b>	
	Notes about Laplace transform.....
	MOSFET model used in this project

## Chapter 1

### Introduction
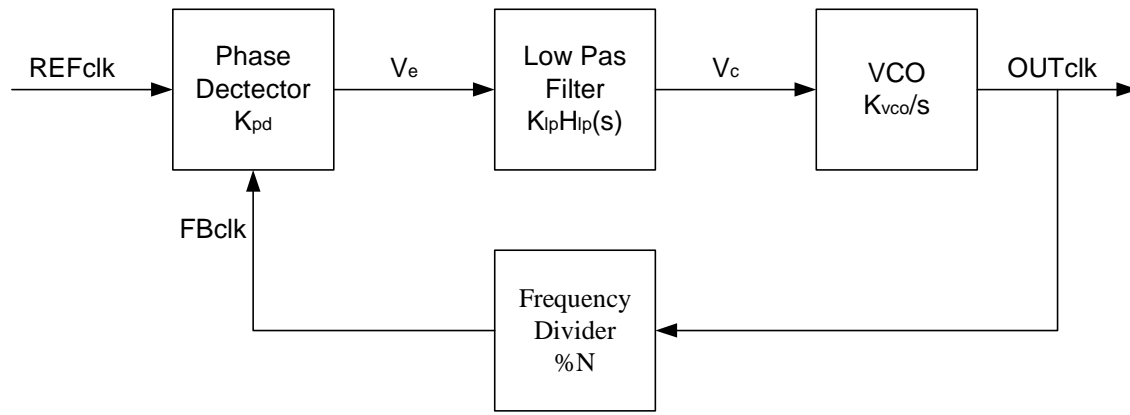
#### 1.1 Closed loop transfer function between the output phase $\Phi_o$ and the input phase $\Phi_i$



A general PLL model

Assume the transfer function of the loop filter is:

$$H_{lp}(s) = K_{lp} F_{lp}(s)$$

Where for passive filter  $K_{LP}=1$ , and for active filter,  $K_{LP}$  can be much larger than 1.

From the feedback control system theory, we know that the closed loop transfer function of the PLL can be generally written as:

$$H(s) = \frac{K_d H_{lp}(s) K_o}{s + K_d H_{lp}(s) K_o / N}$$

where N is the divide down ratio for the output of VCO to the feed back input of the phase detector.

For the system where phase detector is implemented with a PFD followed by a charge pump with a current of  $I_p$ , then followed with a passive filter, which is composed of a resistor R in series with a capacitor C, we have:

$$K_d = \frac{I_p}{2\pi}$$

and:

$$K_d H_{lp}(s) = \frac{I_p}{2\pi} \left( R + \frac{1}{sC} \right)$$

The open-loop forward transfer function is:

$$\left. \frac{\Phi_{out}}{\Phi_{in}} \right|_{openloop} = \frac{I_p}{2\pi} \left( R + \frac{1}{sC} \right) \frac{K_o}{s} = \frac{I_p (1 + sRC) K_o}{2\pi s^2 C}$$

Since the open loop gain has two poles at the origin, this topology is called “type II” PLL. The system has a zero at

$$\omega_z = 1/(RC).$$

The close loop transfer function is:

$$H(s) = \left. \frac{\Phi_{out}}{\Phi_{in}} \right|_{closeloop} = \frac{\frac{I_p}{2\pi} \left( R + \frac{1}{sC} \right) K_o}{s + \frac{I_p}{2\pi} \left( R + \frac{1}{sC} \right) K_o / N}$$

After some mathematical manipulations, we have:

$$H(s) = \frac{\frac{I_p}{2\pi} R \left( s + \frac{1}{RC} \right) K_o}{s^2 + s \frac{I_p K_o R}{2\pi N} + \frac{I_p K_o}{2\pi NC}}$$

This equation is a typical second order system with:

$$\omega_n = \sqrt{\frac{I_p K_o}{2\pi NC}}$$

and:

$$\xi = \frac{\omega_n RC}{2} = \frac{R}{2} \sqrt{\frac{I_p K_o C}{2\pi N}}$$

It is interesting to find out that the natural frequency of the closed loop PLL I is independent of the value of R. It is also helpful to note the damping factor  $\zeta$  is proportional to the value of R. It also should be noted that the both the natural frequency and the damping factor are dependent on the value of N.

Its decay time constant

$$\tau_d = \frac{1}{\zeta\omega_n} = \frac{4\pi N}{I_p K_o R}$$

It can be seen that the decay time constant is independent of capacitor C, only on the resistor R. It makes sense, since an ideal capacitor only charge and discharges but does not dissipate any power, therefore does not contribute to the decay time constant. If the damping factor is smaller than 1,  $\zeta < 1$ , for a step change in the reference input frequency (or phase), the output will response with a sinusoidal component at a frequency of  $\omega_n(1-\zeta^2)^{0.5}$  and approach its final value with the decay time constant  $1/(\zeta\omega_n)$ . Note that if  $\zeta=0.707$  which is usually the case,  $\omega_n(1-\zeta^2)^{0.5} = \zeta\omega_n$ . It should be noted that the decay time constant is proportional to the frequency divide ratio N.

The closed loop transfer function between the output phase  $\Phi_o$  and the input phase  $\Phi_i$  can also be written as:

$$H(s) = \frac{N(2\zeta\omega_n s + \omega_n^2)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Define:

$$K = \frac{K_o I_p R}{2\pi N}$$

$$\tau_z = RC$$

$$\omega_z = 1/\tau_z$$

H(s) can also be written as:

$$H(s) = \frac{N(Ks + K\omega_z)}{s^2 + Ks + K\omega_z}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{K}{\omega_z}}$$

Later we will find that K is approximately equal to the unit gain bandwidth (crossover frequency)  $\omega_c$  of the PLL

## 1.2 Values for loop filter components R and C: an example.

Let's assume the frequency divider ration N is 30. If we use a charge pump current of  $I_p=10\mu A$ , then the gain of the PFD is:

$$K_d=10\mu A/(2\pi)=1.59\mu A/rad.$$

We assume the characteristic of VCO is  $F_{osc} = (-120 \times V_c + 342)$  MHz, so the gain of VCO is:

$$K_o = -120 \text{ MHz/V} = 754 \text{ Mrad/V}$$

The design requires that the instantaneous jumps of VCO control voltage ( $V_c$ ) not exceeding 10mV. For a passive loop filter composed of a resistor R in series with a capacitor C, the instantaneous jumps of  $V_c$  is  $I_p R$ .  $I_p=10\mu A$ , then  $R \leq 1K\Omega$  (for  $V_c$  jumps not exceed 100mV  $R \leq 10K\Omega$ ).

We already know the natural frequency  $\omega_n=251.3$  Krad/s. From  $\omega_n = \sqrt{\frac{I_p K_o}{2\pi N C}}$  (note that in this expression the unit of  $K_o$  is rad/s and the unit of  $\omega_n$  is rad/s too) we can find:

$$C = \frac{I_p K_o}{2\pi N \omega_n^2}$$

and we get  $C = 633$ pF.

Normally the capacitor  $C$  of the loop filter occupies a large silicon area. For a design, the input reference clock signal is given and the natural frequency is set for stability reason. From the equation of  $C$  we can find that a small VCO gain  $K_o$  will help to reduce the area if the frequency range is large enough, also reduce  $K_o$  will improve the noise performance of the loop. Therefore only design  $K_o$  for enough frequency tuning range, never too large. Also note that reduce the charge pump current  $I_p$  helps to reduce  $C$  too. But reduction of  $C$  will increase the noise of the loop filter which is proportional to  $\sqrt{KT/C}$ . So in the design there is a tradeoff between noise and area.

From  $\xi = \frac{\omega_n RC}{2}$ , we get:  $R = \frac{2\xi}{\omega_n C}$ .  $\xi=0.707$ , then  $R=8.87$ K $\Omega$  which is smaller than  $10$ K $\Omega$ , which means that the maximum control voltage  $V_c$  jump is about  $88.7$ mV.

### 1.3. Closed loop transfer function between the error phase $\Phi_e$ and the input phase $\Phi_i$

If we define the loop gain as following:

$$L_p(s) = \frac{K_d H_{lp}(s) K_o}{sN}$$

the phase error transfer function, in a general form, is:

$$H_e(s) = \frac{\Phi_e}{\Phi_i} = \frac{1}{1 + L_p(s)}$$

Which can be written as:

$$H_e(s) = \frac{s^2}{s^2 + s \frac{I_p K_o R}{2\pi N} + \frac{I_p K_o}{2\pi N C}}$$

It can be written in a general form as following:

$$H_e(s) = \frac{s^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

Which shows a high-pass characteristic.

We can derive this equation in another way:

$$H(s) = \frac{\Phi_o}{\Phi_i}$$

$$H_e(s) = \frac{\Phi_e}{\Phi_i} = \frac{\Phi_i - \Phi_o / N}{\Phi_i} = 1 - \frac{H(s)}{N}$$

If  $N=1$ , we have:

$$H_e(s) = 1 - H(s)$$

#### 1.4. Transfer function between $\omega_i$ and $\omega_o$ , $\omega_e$ and $\omega_i$


$$\frac{\omega_e}{\omega_i} = \frac{\Phi_e}{\Phi_i} = H_e(s)$$

$$\frac{\omega_o}{\omega_i} = \frac{\Phi_o}{\Phi_i} = H(s)$$

$$H(s) = \frac{\omega_o}{\omega_i} \Big|_{\text{close loop}} = \frac{\frac{I_P}{2\pi} (R + \frac{1}{sC}) K_o}{s + \frac{I_P}{2\pi} (R + \frac{1}{sC}) K_o / N}$$

$$H_e(s) = \frac{\omega_e}{\omega_i} = \frac{\omega_i - \omega_o / N}{\omega_i} = 1 - \frac{H(s)}{N}$$

#### 1.5. PLL operation ranges

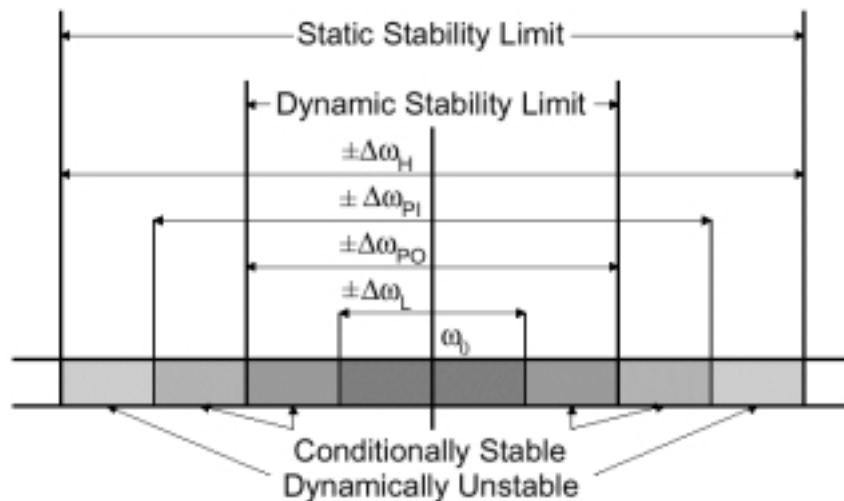

**Hold-in range** (Hold range, Lock range): It is the static stability limit. When the PLL is in the phase-locked state, the maximum frequency range in which the frequency of the input reference signal can slowly be pulled away from the free running frequency of the VCO but the PLL still maintain the phase-locked condition is called the hold-in range.

For a PLL using PFD and charge pump, the hold range is only limited by the VCO output frequency range.

**Pull-in range and pull-in time:** (Pull-in range is also referred as **capture range** in some literatures): It refers to the condition that initially the PLL is not in the phase-locked state, then the reference input signal frequency slowly approaches the free running frequency of the VCO, the maximum frequency range in which the input signal eventually becomes phase-locked is called the lock-in range or capture range.

For a PLL using PFD and charge pump, the hold range is also only limited by the VCO output frequency range.

Both the hold and capture ranges of PFD followed by charge pump type PLL are only limited by the VCO output frequency range. This is one important reason that this type PLL is so popular.

Let  $\omega_{eo}$  to be the initial frequency error, the pull-in (capture) time is

$$T_p = \frac{\omega_{eo}/K_{Forward} - 2N\pi}{N\pi\omega_z}$$

Where:

$$K_{Forward} = \frac{I_p K_O}{2\pi} R = NK$$

So the pull-in time can be written as:

$$T_p = \frac{\omega_{eo}/K - 2\pi}{\pi\omega_z}$$

It can be seen that the pull-in time is proportional to the initial frequency error  $\omega_{eo}$ . We know

$$\omega_z = \frac{1}{RC}$$

So:

$$T_p = \frac{RC(\omega_{eo}/K - 2\pi)}{\pi} = C \left( \frac{2N\omega_{eo}}{I_p K_O} - 2R \right) = \left( \frac{\omega_{eo}}{\omega_n^2} - \frac{2}{\omega_z} \right)$$

It can be seen that as C increases, pull-in time  $T_p$  increases too. Note that the natural frequency  $\omega_n \propto \frac{1}{\sqrt{C}}$ ,

which means the larger the value of C, the smaller the bandwidth, and the longer the pull-in time. Also we can see that increase the value of the resistor R can reduce the pull-in time too.

**Pull-out range:** It is the dynamic stability limit of the PLL. It is the maximum value of a frequency step that applies to the input reference signal of a phase locked PLL and the PLL still maintains the lock state. If the frequency step exceeds the pull-out range, the PLL will not be able to track the input signal and fall out lock. The PLL may acquire lock again through a slow pull-in process.

We already know:



$$\frac{\Phi_e(s)}{\Phi_i(s)} = H_e(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\Phi_i(s) = \frac{\Delta\omega_i(s)}{s}$$

So we have:

$$\frac{\Phi_e(s)}{\Delta\omega_i(s)} = \frac{1}{s} H_e(s) = \frac{s}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

For a step frequency change with a size of  $\Delta\omega$ , we have

$$\omega_i(s) = \frac{\Delta\omega_i(s)}{s}$$

Then:

$$\Phi_e(s) = \frac{1}{s} H_e(s) \cdot \Delta\omega_i(s) = \frac{\Delta\omega}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

For the PLL to keep in lock state,  $\Phi_e < 2\pi$ . Apply the inverse Laplace transform to the above equation, and let  $\Phi_e(t) < 2\pi$ , we can get the pull out range [BEST97]:

$$\Delta\omega_{Po} = 2\pi\omega_n \exp\left(\frac{\zeta}{\sqrt{1-\zeta^2}} \tan^{-1} \frac{\sqrt{1-\zeta^2}}{\zeta}\right), \text{ when } \zeta < 1$$

$$\Delta\omega_{Po} = 2\pi\omega_n e, \text{ when } \zeta = 1$$

$$\Delta\omega_{Po} = 2\pi\omega_n \exp\left(\frac{\zeta}{\sqrt{\zeta^2-1}} \tan^{-1} \frac{\sqrt{\zeta^2-1}}{\zeta}\right), \text{ when } \zeta > 1$$

The least-squares fit gave the linear approximation:

$$\Delta\omega_{Po} = 11.55\omega_n (\zeta + 0.5)$$

Here we gave a few typical values:

$$\Delta\omega_{Po} = 4.38\pi\omega_n, \text{ when } \zeta = 0.707$$

$$\Delta\omega_{Po} = 5.44\pi\omega_n, \text{ when } \zeta = 1$$

Now let's have a look at the physical meaning of the pullout range.

For the case of  $\zeta=1$ , when there is a  $\Delta\omega$  step in the reference clock signal, we have:

$$\Phi_e(t) = \Delta\omega t \exp(-\zeta\omega_n t)$$

It has a peak value of  $0.74\Delta\omega/K$ . In any case if:

$$\frac{\Delta\omega}{K} \leq \Phi_{em} = 2\pi$$

The PLL will keep in lock state [WOLA91].

Where

$$K = \frac{K_o I_p R}{2\pi N}$$

which in our configuration transformed into:

$$\Delta\omega \leq \frac{K_o I_p R}{N}$$

We already know that the decay time constant of the PLL is

$$\tau_d = \frac{1}{\zeta\omega_n} = \frac{4\pi N}{I_p K_o R}$$

So:

$$\Delta\omega_{PO} \leq 4\pi\zeta\omega_n = \frac{K_o I_p R}{N}$$

It is only depends on the value of R.

For a ramp frequency change, PLL keep in locking requires:

$$\Delta\dot{\omega} = \frac{d}{dt}(\Delta\omega_i) < \frac{K_o I_p}{C}$$

It can be seen that the capture frequency change ratio range is independent of the value of R.

**Lock range and lock time:** This range is a subset of pull-in range, It is the offset range between the reference and the scaled-down VCO frequency that the PLL will acquire lock within a single beat between the input reference signal and the feedback signal. The initial state of the PLL is unlock state.

The lock range, according to [BEST97] is:

$$\Delta\omega_L \leq 4\pi\zeta\omega_n$$

It is only depends on the value of R, not dependent on C.

The lock time (settling time), according to [BEST97] is:

$$T_L \approx \frac{2\pi}{\omega_n}$$

We need a detailed inspection of the settling time. In fact PLL is a negative feedback system, theoretically, the output frequency can never be exactly equal to the input reference frequency, but always approaches it asymptotically. Thus **lock time (settling time, switching time)** is usually practically defined to be the time when the output approaches the input reference within a predefined margin. This margin is based on the overall system performance requirement. We know the system asymptotically converge to zero phase (frequency) error in the form of  $\exp(-t\zeta\omega_n)$ , let  $\delta$  to be the frequency tolerance that we can say the PLL is locked, then

$$T_L = -\frac{\ln(\delta)}{\zeta\omega_n} = -\ln(\delta) \cdot \tau_d = -\ln(\delta) \cdot \frac{4\pi N}{I_p K_O R}$$

For  $\delta=1/20000=0.005\%$  and  $\zeta=1$ ,  $T_L=10/\omega_n$ .

The lock time (switching time) is a very important parameter, especially in wireless communication. There are several methods to improve the switch time [TI99]. One is to “pre-tune” the VCO to the desired frequency so that to bring the PLL to lock proximity, then the loop can start settle. Another is to increase the natural frequency  $\omega_n$  for a short time by charging the largest capacitor in the loop filter directly or even increase the charge current in this time. One popular technique is to create a separate port that can charge the capacitor in the transition, another is using a switch that bypass the resistor R and allow charge the capacitor directly [TI99].

### 1.6. Stead state phase error

Stead state phase error (static phase error, or loop stress) is the average value of phase error when the PLL is in lock. Let  $\Delta\omega$  to be the frequency offset between the input signal and the free-running frequency of the VCO. We have [1]:


$$\Phi_{eo} = \frac{2\pi\Delta\omega}{K_o I_p Z_F(0)}$$

It is usually desirable to have static phase error,  $\Phi_{eo}$ , near zero. For the PLL configuration we will use in the projects, i.e., PFD followed by charge pump, followed by passive filter and VCO,  $Z_F(0)=\infty$ , so that the static phase error is zero.

Therefore we can say that from the point view of static phase error, this configuration has the best tracking performance. This is another reason that this type of PLL is popular in practical application.
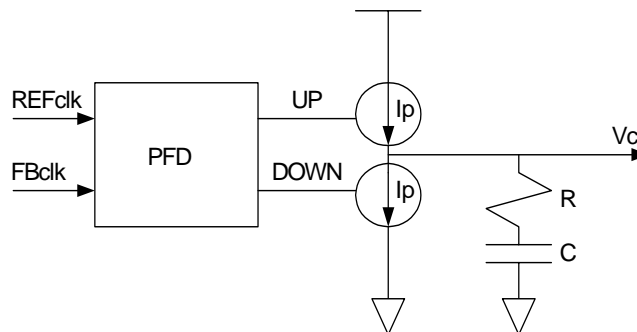
### 1.7 PLL bandwidth and stability analysis

We study the PLL with the following loop filter structure:



Fuding Ge: PLL design

We already know that the open-loop gain is:

$$H(s)|_{openloop} = \frac{I_p}{2\pi} \left( R + \frac{1}{sC} \right) \frac{K_o}{Ns} = \frac{I_p (1 + sRC) K_o}{2\pi s^2 NC}$$

The unit gain bandwidth (crossover frequency) is the value of the frequency when the magnitude of the open loop gain is 1.

$$\left| \frac{I_p (1 + sRC) K_o}{2\pi s^2 NC} \right| = 1$$


Assume  $sRC \gg 1$  we have the unit gain bandwidth  $\omega_c$  as:

$$\omega_c = \frac{I_p}{2\pi} \cdot \frac{K_o}{N} R$$


Note that:

$$\omega_c = 2\zeta\omega_n$$

 Its Bode plot is shown in the following figure. It can be see it is unconditionally stable as long as  $\omega_z$  is smaller than  $\omega_c$ .



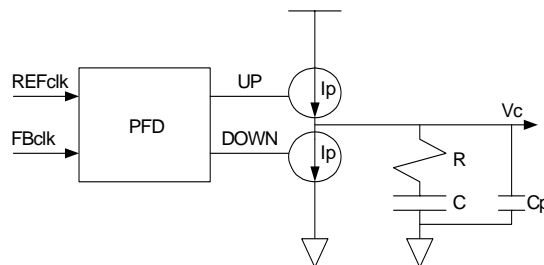For a PLL has the following loop filter structure:




Its open loop gain is:

$$\begin{aligned}
 H(s)|_{openloop} &= \frac{I_p}{2\pi} \frac{\left(R + \frac{1}{sC}\right) \frac{1}{sC_p} K_o}{R + \frac{1}{sC} + \frac{1}{sC_p} Ns} \\
 &= \frac{I_p K_o}{2\pi s N} \cdot \frac{\left(R + \frac{1}{sC}\right)}{1 + \frac{C_p}{C} + sRC_p} = \frac{I_p K_o}{2\pi s N} \cdot \frac{(1 + sRC)}{sC + sC_p + s^2 RC_p C} \\
 &= \frac{I_p K_o}{2\pi s^2 N} \cdot \frac{(1 + sRC)}{(C + C_p)(1 + sR \frac{C_p C}{C_p + C})} = \frac{I_p K_o}{2\pi s^2 N} \cdot \frac{(1 + sRC)}{(C + C_p)(1 + sRC_p \leftrightarrow C)}
 \end{aligned}$$

Where  $C_p \leftrightarrow C$  means  $C_p$  and  $C$  are in series. The value of  $C_p \leftrightarrow C$  is determined by the smaller one.

 Its Bode plot is shown in the following figure:



Its unit gain bandwidth is still about:

$$\omega_c = \frac{I_p}{2\pi} \cdot \frac{K_o}{N} R$$

It has a zero, which is:

$$\omega_z = \frac{1}{RC}$$

and a pole which is at:

$$\omega_p = \frac{1}{RC \leftrightarrow C_p}$$

It can be seen that if  $C_p$  is much smaller than  $C$ , then the pole is almost totally determined by  $C_p$ . Also if  $C_p$  is much smaller than  $C$ , the phase margin is quite large. In practical design,  $C_p$  is usually chosen to be about  $C/10$ . Generally speaking, we can place the loop gain zero  $\omega_z$  a factor  $\alpha$  below the crossover frequency  $\omega_c$  and the 3<sup>rd</sup> pole  $\omega_p$  a factor  $\beta$  above  $\omega_c$ . To guarantee enough phase margin for the PLL to be stable,  $\alpha$  and  $\beta$  are typically at least to 4 or larger, which give a phase margin of 60° or larger.

In the design of a PLL, we may also need to consider the -3dB bandwidth  $\omega_B$ . For the case of damping factor smaller than 1, we have:

$$\omega_B = \omega_n \sqrt{2\zeta^2 + 1 + \sqrt{2\zeta^2 + 1}^2 + 1}$$

When  $\zeta = 0.707$ ,  $\omega_B = 2.06\omega_n$ .

**Example:** We have known the lock-in time is 0.2ms, and is given  $T_s = 16\pi/\omega_n$ , then  $\omega_n = 251.3\text{Krad/s}$ . We chose damping factor  $\zeta$  to be 0.707, which will give the best settling time.

$$\omega_b = 517.7\text{Krad/s and } f_B = 80.0\text{KHz.}$$


The input reference is  $f_{in} = 8\text{MHz}$ ,  $f_B/f_{in} = 1.0\%$ , a quite narrow bandwidth PLL. The loop gain  $L_p$  is defined as

$$L_p = K_d K_F K_O / N$$

$$L_p = \frac{I_p}{2\pi} \left( R + \frac{1}{sC} \right) \frac{K_O}{sN}$$
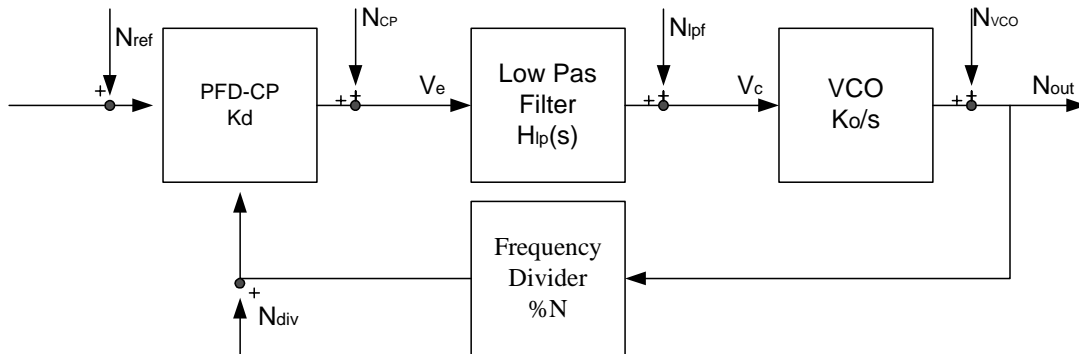
## 1.8 Noise transfer functions

Every building block of the PLL will contribute to the total output noise. The noise sources of the PLL are shown in the following figure.



$N_{ref}$ : noise from the reference signal;

$N_{cp}$ : noise from the charge pump;

$N_{lpf}$ : noise from the loop filter;

$N_{vco}$ : noise from VCO;

## Fuding Ge: PLL design

$N_{div}$ : noise from the frequency divider.

Assume these noise are not correlated, the overall phase noise performance at the output of the PLL depends on the terms described above.

$$N_{total}^2 = N_{ref,out}^2 + N_{CP,out}^2 + N_{lpf,out}^2 + N_{VCO,out}^2 + N_{div,out}^2$$

Where  $N_{xxx,out}^2$  is the noise power at the output due to noise source Nxxx.

The transfer function of  $N_{ref}$ ,  $N_{div}$  to the output is same as the closed-loop transfer function of the PLL, which is:

$$H(s) = \frac{N_{out}}{N_{ref}} = \frac{N(2\zeta\omega_n s + \omega_n^2)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

and has a low pass characteristic.

The transfer function of the noise from charge pump  $N_{CP}$  to the output has the same form as  $N_{ref}$  and  $N_{div}$  if we reference NCP to the input of PFD by

$$N_{cp,in} = N_{cp} / K_d$$

Where  $K_d$  is the gain of the PFD, and can be written as

$$K_d = \frac{I_p}{2\pi}$$

So it shows low pass characteristics too.

In order to reduce the output noise due to input noise sources from frequency divider, the reference signal and PFD, the bandwidth of the PLL should be as small as possible. Note that these noises are amplified by a factor of the divider ratio N, so if these noises are concerns, N should be small.

Now let's have a look at the transfer function of the noise due to the loop filter. Assume the noise can be written as a voltage source  $V_{nlpf}$ , we have:

$$H(s) = \frac{\Phi_{out}}{V_{nlpf}} = \frac{K_o / s}{1 + \frac{I_p}{2\pi} (R + \frac{1}{sC}) \frac{K_o}{sN}} = \frac{K_o}{s + \frac{I_p}{2\pi} (R + \frac{1}{sC}) \frac{K_o}{N}} = \frac{sK_o}{s^2 + \frac{I_p}{2\pi} (sR + \frac{1}{C}) \frac{K_o}{N}}$$

This is of a bandpass filter characteristic. We can simply verify by let  $\omega=0$  and  $\omega=\infty$ , at both cases, the output is zero. Otherwise the output is large than zero.

The transfer function from VCO noise to output can be written as:

$$H(s) = \frac{\Phi_{out}}{V_{nVCO}} = \frac{1}{1 + \frac{I_p}{2\pi} (R + \frac{1}{sC}) \frac{K_o}{sN}} = \frac{s^2}{s^2 + \frac{I_p}{2\pi} (sR + \frac{1}{C}) \frac{K_o}{N}}$$

which has a high-pass characteristic.

## Fuding Ge: PLL design

From above results, we can see that if the noise of VCO is the dominant noise source, a large PLL bandwidth should be used, which is in conflict with the requirement of the reference noise. So the bandwidth of the PLL is a tradeoff between noise from reference and noise from VCO, and the speed requirement.



## Chapter 2. PLL function blocks design

### 2.1 Project specifications

The purpose of this project is to design a phase-locked loop clock synthesizer that will be able to generate a 200MHz clock from an reference clock of 8MHz.

The settling time or lock-in time  $T_s$  for the PLL is less than 0.15ms. Also, the settling time for the PLL is given by  $T_s = 16\pi/\omega_n$ .

The maximum value of the instantaneous jumps of the VCO control voltage should be less 100mV.

The charge pump current is  $I_p = 10\mu\text{A}$ .


This PLL clock synthesizer includes a divide-by-N circuit, which will determine the multiplicity of the oscillator clock.

In project#1 we will design the phase-frequency detector (PFD) accompanied by the charge-pump, and the passive loop filter.


1. Derive the values for the natural frequency  $\omega_n$ , the damping factor  $\zeta$ , the loop bandwidth  $\omega_B$  and the loop gain  $L_p$ .
2. Design the PFD so that during the lock condition, the narrow pulse at the rising edges of the input and output clocks to be around 2ns at room temperature (27°C) and typical processing conditions.
3. Design the charge pump as explained in class to charge and discharge  $I_p$  as calculated in part 5.
4. Design the voltage-to-current and the VCO to generate 200MHz at a value of the control voltage  $V_c$  close to  $V_{dd}/2$ .
5. Design a programmable divider, which accepts a register value in order to change the divide down ration N.
6. From your simulation plot the VCO generated frequency  $F_{osc}$  versus the control voltage  $V_c$ . Determine the VCO gain at 200MHz.
7. Build the schematic and run simulation for the whole PLL and plot the VCO control voltage for  $N=25$ ,  $N=15$  and  $N=35$ . In this part you need to observe the PLL lock condition by observing and plotting the VCO control voltage.
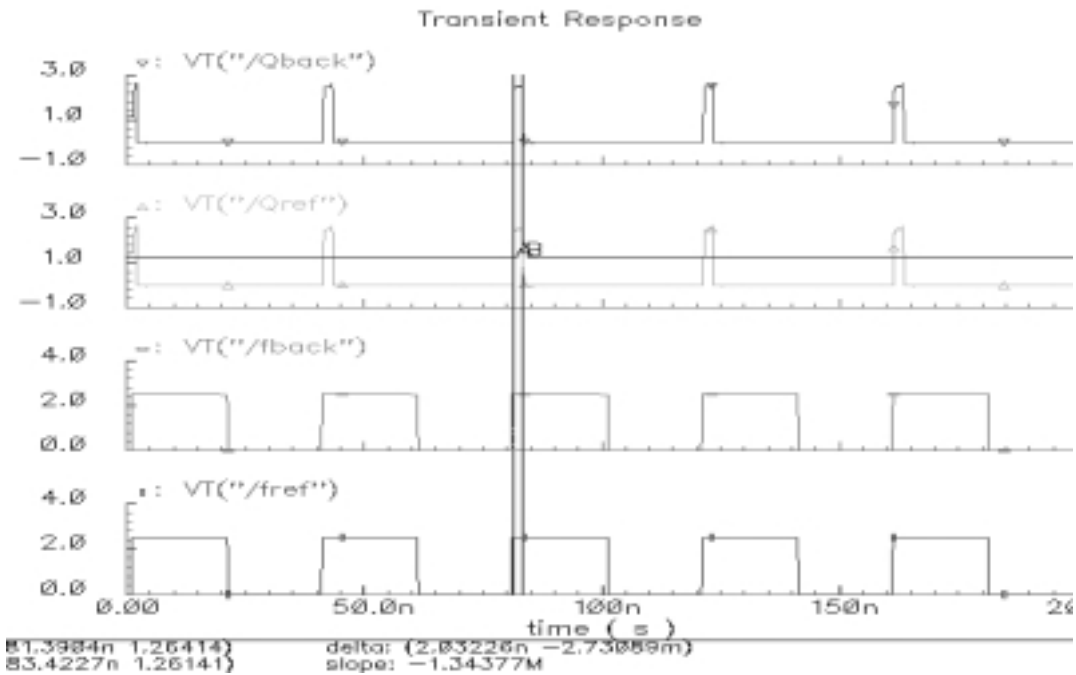
## 2.2 PFD design


In order to eliminate the PFD dead zone, we require the pulse width of the DFF output to be about 2ns when the PLL is in lock state. In this way the up and down signal are long enough to reach a valid logic level and turn on the switches in the charge pump. This pulse width should not be very large, since a large pulse width will introduce jitter due to the unmatched UP and DOWN current. It should also be long enough to fully turn the UP and DOWN switches. The simulation result is shown in the following figure. Note that right now we only test the function of the blocks, in order to save simulate time, the input clock signal is not 8Mhz, but much larger.



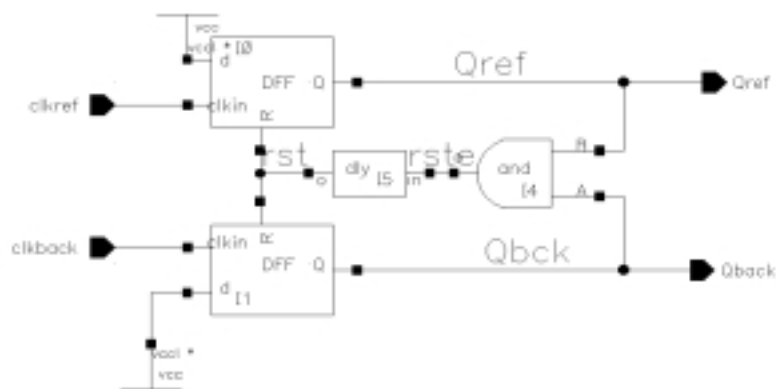This pulse width is tuned by the delay block, which is showed in the following figure as “dly”.




Fuding Ge: PLL design

 


Schematics of DFF used in the PFD block

 The “dly” block is shown in the following figure. In this design some transistors (5uX5u) used as capacitors to increase the delay is used. The size of the inverter is: P: 1.25u/0.25u; N:0.5u/0.25u. The last one is 3x larger to drive large load.




 In order to get the “UP”, “DOWN” signals and their complementary, we used a block named “PFDbuf” which consists some inverters as shown below.




Other gates **transistor sizes**: NAND gate: NMOS: 0.5u/0.25u; PMOS: 0.5u/0.25u; NOR gate: NMOS: 1u/0.25u; PMOS: 4u/0.25u.

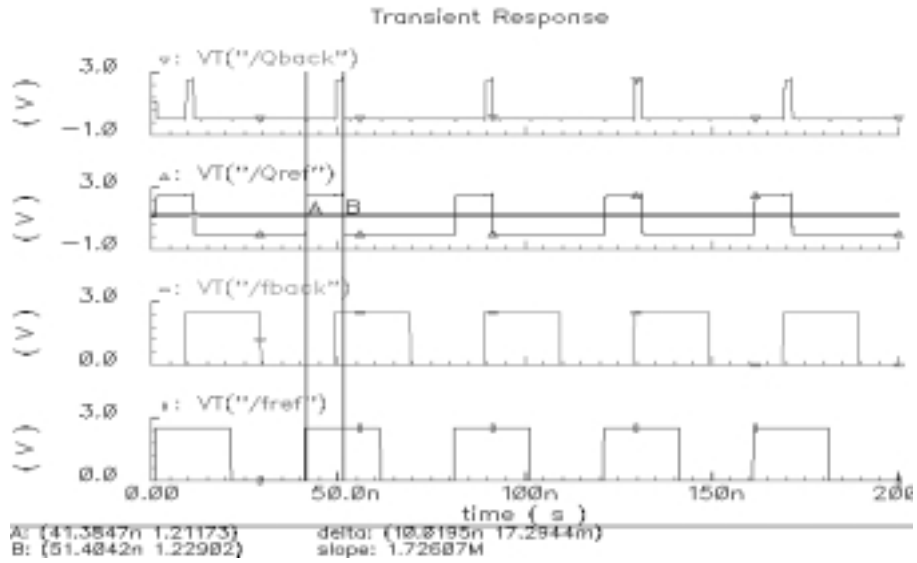The simulation results of the PFD are shown in the following figures.



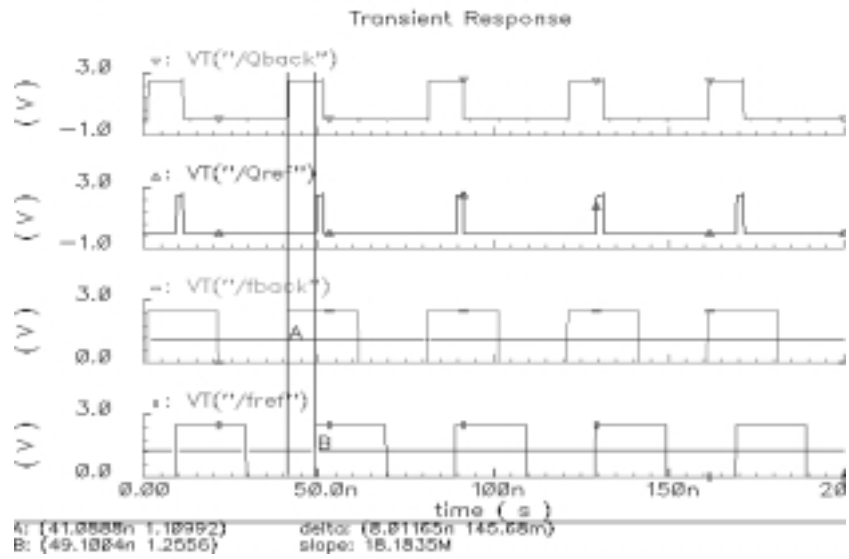The  $f_{ref}$  signal leads  $f_{back}$  signal




The  $f_{ref}$  signal lags  $f_{back}$  signal

From these simulation results we find the PFD functions correctly.

 
### 2.3 Charge pump design

In this design, we use a current steering configuration for the charge pump. The schematics and the transistor sizes are shown in the following figure.




Current steering charge pump

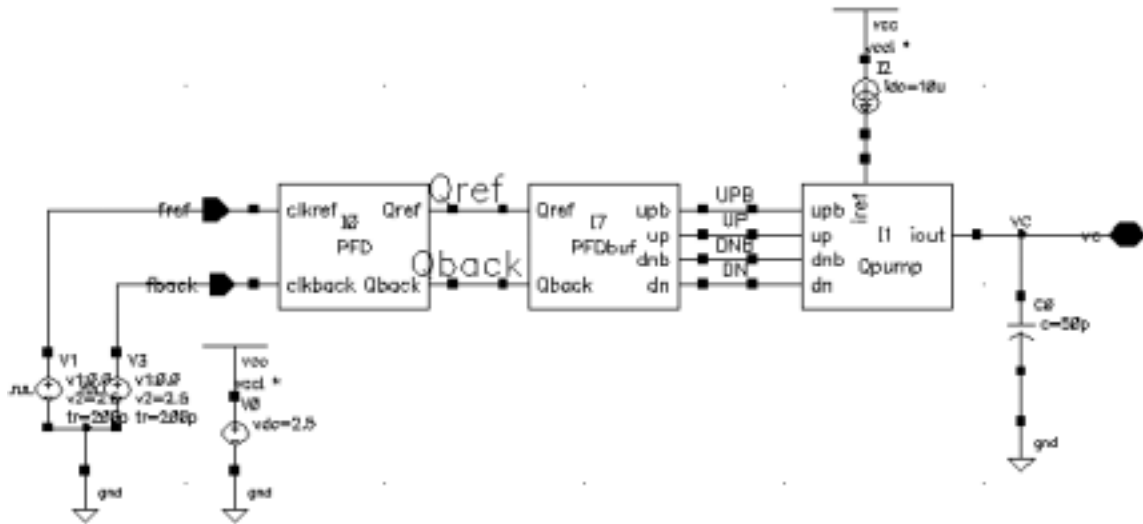The following circuit is the test bench for the charge pump, this test bench is used to verify the function of charge pump. Note that in order to test the function, only a capacitor is used in place of the filter.




Test bench for the charge pump.

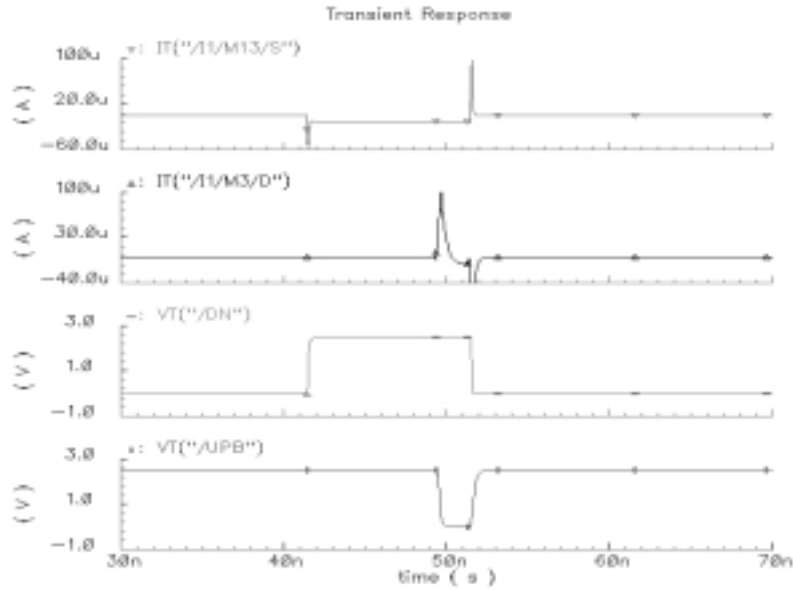The following figure shows the simulation result for the charge pump. The transistor M3 and M13 are the switches control the charge current (see above figure).




Transistor current

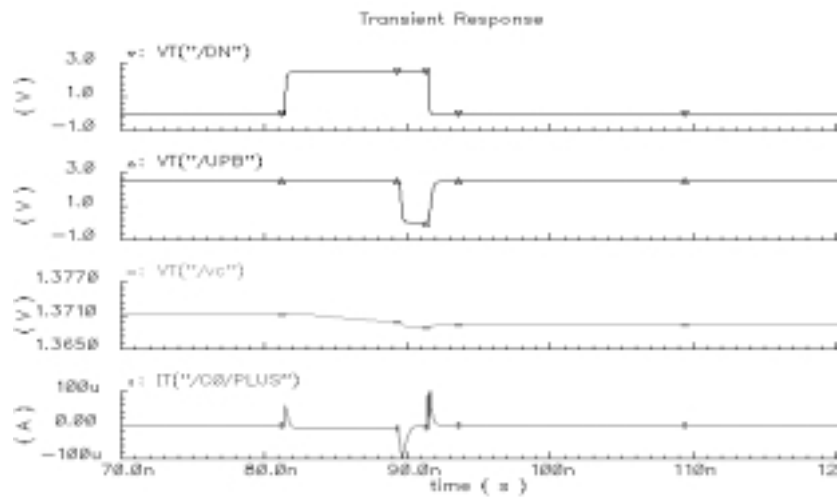


Current and voltage at the loop filter capacitor

 From the above two figures we find that the function of charge pump is correct. We also can see large charge injection when the switches change state. In order to reduce the charge injection, dummy switches are used in this design as shown in the following figures.



Charge pump with dummy switches.

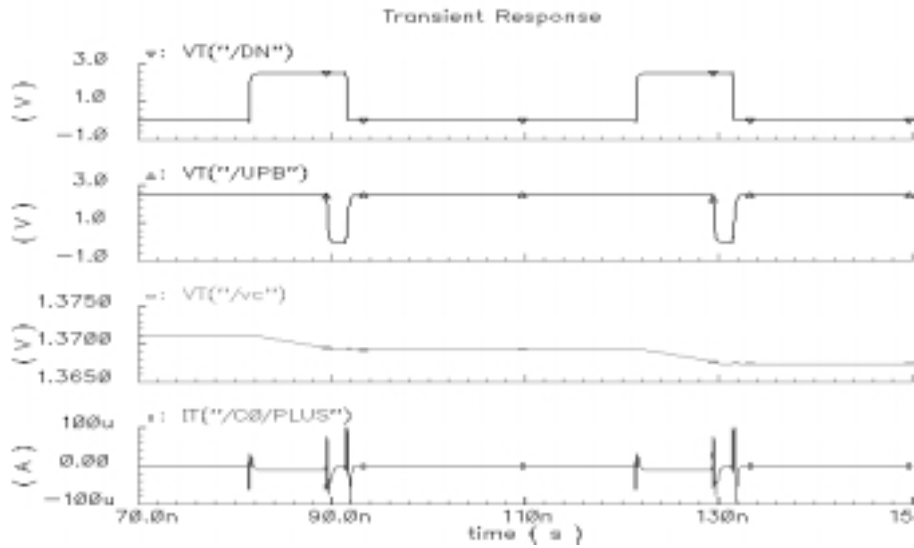


Simulation results for the charge pump with dummy switches.

Though we used the dummy transistor to reduce the charge
 
### Relationship between phase error and VC

The input clock is fixed at 8MHz. Force the feedback output clock to be 8MHz. Select a reference voltage  $V_c$  at which the input and output clocks are aligned, then run a series of simulations in order to plot VC verse  $\Phi_e = \Phi_i - \Phi_o/N$ .


The test bench we used is shown following:



Note that the filter has been implemented using the values calculated above.

We force the two clock signals into PFD as 8MHz but let the feedback one to be lag or lead the reference. Then run the simulation for 10 cycles, then measure the Vc value. The following table and figure shows the relationship between phase error and Vc. From the figure we can find that the linearity of this design is quite good.


Output clock lags the input clock (ns)	Corresponding phase error $\Phi_e$ (rads)	After 10 cycles measured Vc
20	0.16	1.25352
15	0.12	1.25262
10	0.08	1.25173
5	0.04	1.25083
0	0	1.24998
-5	-0.04	1.24917
-10	-0.08	1.24833
-15	-0.12	1.2475
-20	-0.16	1.24666

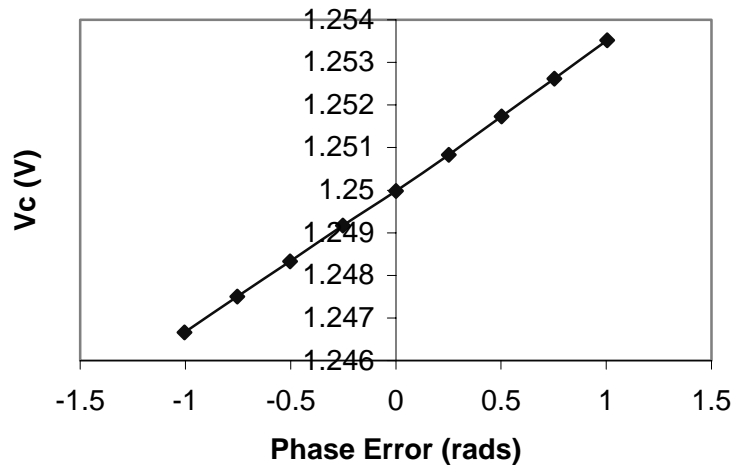

 
### Discussion and conclusions

Due to the nonideality of the charge pump, PFD (charge injection, the delay between UP and its complementary signal, DOWN and its complementary, etc), there are large Vc spike even in the lock state, shown in the following figure.






 The spike is quite large (about 480mV peak to peak in the figure). Fortunately, the output of the filter drives the VCO, which always shows some load capacitor. BUT this load capacitor has a big effect on the voltage jump. We now model this load capacitor to be about 0.3pF, as show in the following test bench:



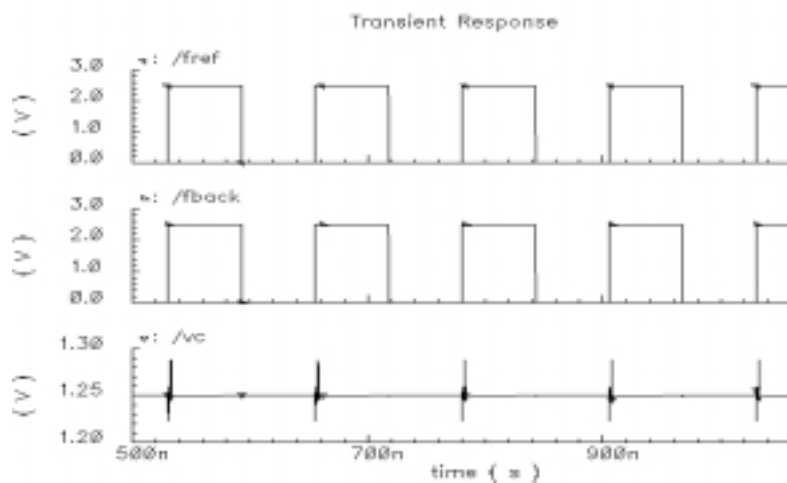Then the  $V_c$  spikes become much smaller, as shown in the following, the peak-to-peak value is about 65mV.



In other words, this design should meet the maximum 100mV  $V_c$  jump requirement. If the VCO input load capacitance is not large enough to solve the  $V_c$  jump problem, a capacitor can be added intentionally. Actually the nonideality of the charge will also introduce phase noise, it should be reduced through both good design (a better charge pump, for example better match between the UP current and DOWN current).


**Conclusion:** the function of the PFD and charge pump are tested and the results show that their function are correct.

## 2.4 Self-biased VCO design [MANE96]
 
### 2.4.1 VCO circuit design


If a precise 50% duty cycle clock is required, a VCO runs at twice the desired frequency is used in the PLL then this twice-frequency signal is divided by 2 using D flip-flop. In this design we did not do this.

The schematic of the VCO is shown in the following figure. It consists of three parts: bias generation circuit, current controlled oscillator and a circuit transfer the small swing differential output from oscillator to a single ended CMOS rail-to-rail clock signal.



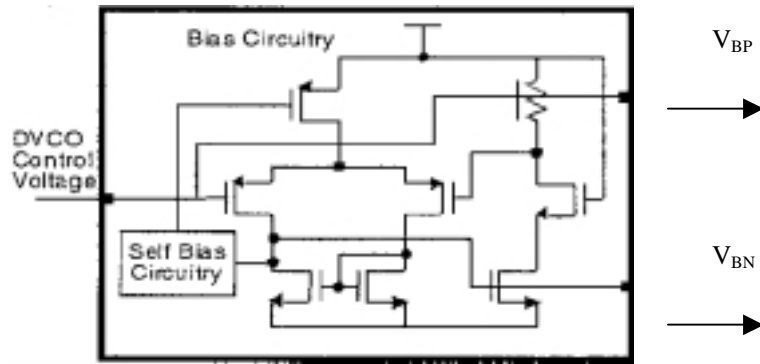
#### Bias generation circuit

Because the delay cell is current controlled and the VCO frequency is proportional to the bias current, we need a V-I converter to convert the control voltage  $V_c$  from the low-pass filter to a current whose value is proportional to  $V_c$ . The function block can be shown as following:




 It can be implemented by the following schematic.



Fuding Ge: PLL design

 
Because this bias generation circuit is self-biased, it needs an initial circuit which can be implemented as shown below:



Note that the channel length of M1 is very large which means it is a weak transistor.

 
**Oscillator circuit**

The conventional current delay elements (shown following) are power supply sensitive. In this design we did not use this sort of delay elements.




In this design we use differential current-controlled delay element.

The following figure shows the delay cell. It is based on a P-MOSFET source-coupled pair (N-MOSFET source coupled pair can also be used in the design) with voltage-controlled resistor (VCR) load element. By controlling signal  $R_{control}$  to VCR, the voltage swing is held constant and independent on power supply voltage. Then the delay is only dependent on  $I_{source}$  so that VCO frequency is directly proportional to  $I_{source}$ .

 


Fuding Ge: PLL design

 
The following figure shows a N-MOSFET source coupled pair delay cell. The symmetric load acts as the VCR and  $V_{BP}$  is the control voltage  $R_{control}$ . Signal  $V_{BN}$  is the bias voltage controls the  $I_{source}$ .



 In our design it is implemented as shown in the following figure.




 In our design there are 4 delay stages in the oscillator. The four stages are connected as shown in the following figure.



The circuit that transfers the small swing differential output from oscillator to a single ended CMOS rail-to-rail clock signal is shown in the following figure.

Fuding Ge: PLL design


 


$$F = \frac{1}{2nt} = \frac{\sqrt{\mu C_{ox} (W/L) I_D}}{C_{Load}}$$

$$K_{vco} = \frac{\mu C_{ox}}{2} \left(\frac{W}{L}\right)_{vcr} \frac{1}{C_{load}}$$

Here  $I_D$  is the bias current of the delay stages and  $C_{load}$  is the total buffer output capacitance for all stages. The following figure shows the frequency of the VCO versus the control voltage.

  The following figure shows the VCO test circuit.



## Fuding Ge: PLL design

From the figure we can find that its gain is as:

$$K_v = 366 \text{ MHz/V (From } V_c = 0.7 \text{ V to } 1.5 \text{ V)}$$


Some of its output frequency and the corresponding control voltage are as follows:

Fo=1.33 MHz @ Vc=0.5V
Fo=16.6 MHz @ Vc=0.667V
Fo=62.7 MHz @ Vc=0.833V
Fo=122.5 MHz @ Vc=1.0V
Fo=184.0 MHz @ Vc=1.167V
Fo=214.0 MHz @ Vc=1.25V
Fo=243.8 MHz @ Vc=1.33V
Fo=304.4 MHz @ Vc=1.495V
Fo=332.8 MHz @ Vc=1.664V
Fo=341.8 MHz @ Vc=1.833V
Fo=347.2 MHz @ Vc=2.0V

We use some variables to optimize the VCO. The following table shows the final results we used in the design.

W1/L1	4.5/1.5
Win/Lin	1.0/0.8
Wbs/Lbs	3.0/3.0

 
With the same size of delay cell and bias generation circuits, we test the VCO with different delay stages. The following figure shows the results of three-stage VCO:



From the figure we can find that gain of this 3-stage VCO is:

$$K_v = 478 \text{ MHz/V (From } V_c = 0.8 \text{ V to } 1.6 \text{ V)}$$

Fuding Ge: PLL design


 


$K_v=275\text{MHz/V}$  (From  $V_c=0.8\text{ V}$  to  $1.6\text{ V}$ )




 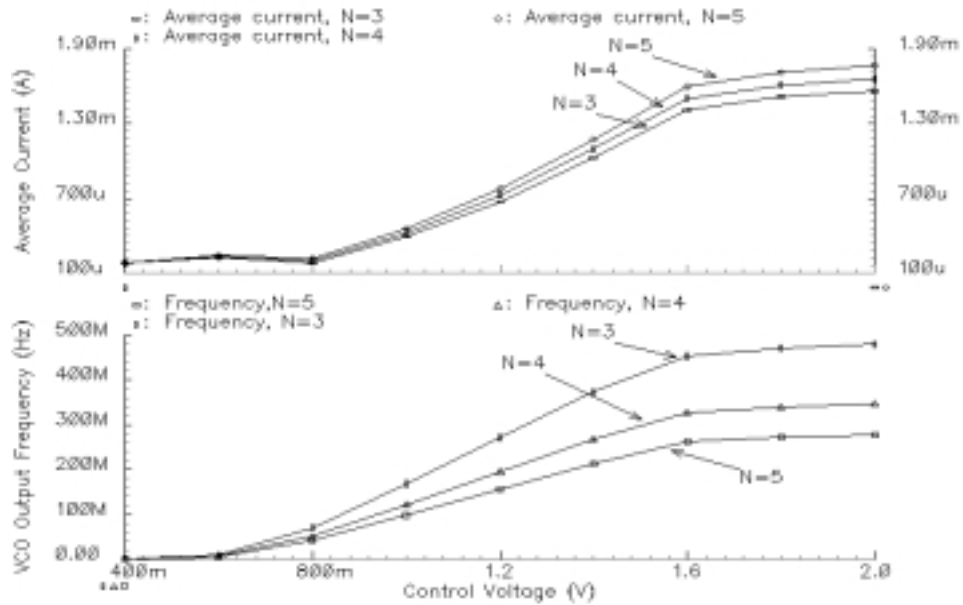
### VCO output frequency, power VS number of delay stages




In the following simulations, we keep the bias generation circuit and the circuit transfer the small swing differential output from oscillator to a single ended CMOS rail-to-rail clock signal to be identical. The delay stage itself also keeps the same. We only change the number of delay stages in the current control oscillator block.


  
### VCO output frequency, power VS size of load transistor



   
### VCO output frequency, power VS size of the input transistor



 
## 2.4.2 VCO Phase noise simulation results


The following figures show the simulation results using SpectreRF Periodic Steady-State (PSS) analysis and Periodic Noise (PNoise) analysis tools.



Phase noise VS delay stage number

 

 Phase noise VS load transistor size. Number of delay stages keeps the same.



Phase noise VS input transistor size. Number of delay stages keeps the same, in this case it is 4.  
From Win=1um to Win=5um, there is a 3.67dB noise reduction.  
From Win=5um to Win=10um, there is a 2.5dB noise reduction.

Some conclusions about the noise of ring oscillator: The jitter resulting from the device intrinsic noise generally decreases as the power consumption increases. The effect of power supply and substrate noise on the total noise of a given oscillator topology is relatively independent of the power consumption [HERZ98].

## 2.5 Loop filter design

We have known the lock-in time is 0.15ms, and is given  $T_s=16\pi/\omega_n$ , then

$$\omega_n=335\text{Krad/s or }53\text{KHz}$$

We chose damping factor  $\zeta$  to be 0.707, which will give the best settling time. Here loop bandwidth  $\omega_b$  is the -3dB bandwidth, and which is:

$$\omega_b = \omega_n \sqrt{2\zeta^2 + 1 + \sqrt{(2\zeta^2 + 1)^2 + 1}}$$

When  $\zeta = 0.707$ ,  $\omega_b=2.06\omega_n$ . So

$$\omega_b = 670\text{Krad/s and }f_b=106\text{KHz.}$$

The input reference is  $f_{in}=8\text{MHz}$ ,  $f_b/f_{in}=1.25\%$ , is still a quite narrow bandwidth PLL.

The divide down ratio should be the ratio between the desired output frequency and the input reference frequency, in this project, it is:

$$N=200\text{MHz}/8\text{MHz}=25.$$

If we use a charge pump current of  $I_p=10\mu\text{A}$ , then the gain of the PFD is:

$$K_d=10\mu\text{A}/(2\pi)=1.59\mu\text{A/rad.}$$

We have design a VCO with a gain of:

$$K_o = 365 \text{ MHz/V} = 2,293 \text{ Mrad/V}$$

The design requires that the instantaneous jumps of VCO control voltage ( $V_c$ ) not exceeding 10mV (later the instructor changed this value to 100mV). For a passive loop filter composed of a resistor  $R$  in series with a capacitor  $C$ , the instantaneous jumps of  $V_c$  is  $I_p R$ .  $I_p=10\mu\text{A}$ , then  $R \leq 1\text{K}\Omega$  (for  $V_c$  jumps not exceed 100mV  $R \leq 10\text{K}\Omega$ ).

We already know the natural frequency  $\omega_n=335\text{Krad/s}$ . From  $\omega_n = \sqrt{\frac{I_p K_o}{2\pi N C}}$  we can find:

$$C = \frac{I_p K_o}{2\pi N \omega_n^2}$$

$$C = \frac{10 \times 10^{-6} \times 2\pi \times 365 \times 10^6}{2\pi \times 25 \times (335 \times 10^3)^2} = 1.3\text{nF}$$

From  $\zeta = \frac{\omega_n R C}{2}$ , we get:  $R = \frac{2\zeta}{\omega_n C}$ .  $\zeta=0.707$ , then  $R=3.25\text{K}\Omega$ . The value of  $R$  is smaller than  $10\text{K}\Omega$ ,

which means that the maximum  $V_c$  jump is about 33 mV.

### Summary:

$$\begin{aligned} I_p &= 10\mu\text{A}; \\ K_o &= 365\text{KHz/V} \\ R &= 3.25\text{Kohms}; \end{aligned}$$


$$C=1.3\text{Nf}$$

$$f_n=53\text{KHz.}$$

 
## 2.6 High-speed programmable divider design [LARS96]

From the point view of skew, it simply masks out the clock cycles, dose not introduce any additional delay in the feedback clock. One important requirement for the divider is that the divider should be able work at the **maximum** VCO output frequency. This design requirement is not trivial for modern high frequency system. For our VCO designed in this project the maximum output frequency is about 400MHz. For a 0.25um CMOS process, it is not difficulty to meet this requirement.


But when we design the divider, our goal is a high speed (above GHz), general purpose programmable and high portable divider. TSPC DFF is a very popular high speed dynamic circuit. The following figure shows a rising edge triggered TSPC DFF and its simulation results. It can be seen that this DFF can run at a input clock frequency of about 4GHz .




A rising edge triggered TSPC DFF.

 


TSPC DFF running at 4GHz input clock.

 

A falling edge triggered TSPC DFF

 


Divide by 2 circuit using TSPC DFF

 


Simulation results for the divide-by-2 TSPC DFF.



Fuding Ge: PLL design

 


 Schematic of the 6-bit programmable divider



Static loadable DFF used for the divider

 This divider can work with a input frequency of 1GHz, as shown in the following figure.



## VerilogA modeling of the divider


During the simulations of the whole PLL, the divider consumes a lot of computing time. In order to save the simulation time when checking the PLL in a system level, we can use the build-in verilogA function of Cadence Analog Artist Mixed signal simulation environment. The following is a verilogA code for a divide-25 divider:

```
-----  
// VerilogA for pll, DIV_va, veriloga  
  
`include "constants.h"  
`include "discipline.h"  
  
module DIV_va (in,out);  
input in; output out; electrical in, out;  
  
parameter real vlo=0, vhi=2.5;  
parameter integer ratio=25 from [2:inf);  
  
parameter integer dir=1 from [-1:1] exclude 0;  
        //dir=1 for positive edge trigger  
        //dir=-1 for negative edge trigger  
  
parameter real tt=100p from (0:inf);  
parameter real td=10p from (0:inf);  
parameter real ttol=1p from (0:td/5);  
  
integer count,n;  
real dt;  
  
analog begin  
  
        //Phase /frequency detector state machine  
        @(cross (V(in)-(vhi+vlo)/2, dir, ttol)) begin  
            count = count+1;  
            if (count >= ratio)  
                count=0;  
            n=(2*count >= ratio);  
  
        end  
  
V(out) <+ transition(n? vhi: vlo, td, tt);  
  
end  
endmodule
```

---
 
## Chapter 3. PLL simulation results

The following figure shows the whole PLL.




Schematic of the whole PLL

### Results for divide ratio $N=25$

 
#### Pull-in process

In the simulation, we initialize the voltage of  $V_c$  to be 2V which means the VCO is in a low frequency. The frequency of the reference clock is 8MHz.




$V_c$  versus time, initial value is 2 V

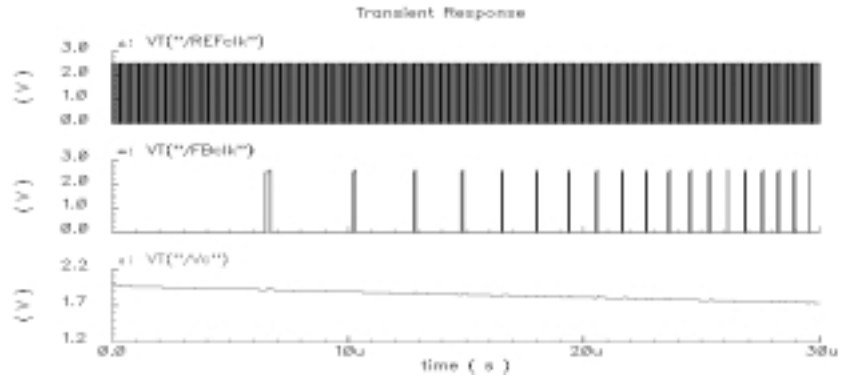
It can be seen that the control voltage stabilized after 120  $\mu$ s, which means the PLL is in lock state. This is a typical pull-in process.




The PLL is not in lock state at first

 

 
There are some ripples in Vc when it approaches lock state



 
Much detailed Vc. The smallest ripple is due to the time-discrete nature of the PFD. The longer ripple is due to the finite bandwidth of the PLL



 It is interesting to notice that lower point of the  $V_c$  ripple corresponding to the rising edge of the feedback clock signal and the upper point corresponding to the rising edge of the reference clock signal.



 This figure just shows that the two clocks are aligned.



This figure shows the control voltage versus time with an initial value of 1.25 V.

### Frequency step response

The hold range of frequency step is:

$$\omega_H = 2\pi N K_F = K_o I_p R$$


For this design,  $K_o=366\text{MHz}$ ,  $I_p=10\ \mu\text{A}$ ,  $R=3.25\text{Kohms}$ ,  $f_H=11.9\text{MHz}$ .

The lock range is:


$$\omega_L = 4\pi\zeta\omega_n$$

For this design,  $\zeta=0.707$ ,  $\omega_n=53\text{KHz}$ ,  $f_L=0.47\text{MHz}$ .


#### Case I: large frequency step

 

 
Control voltage  $V_c$  VS time: The PLL is initially in lock state with a 8MHz reference clock. At time=30 $\mu\text{S}$ , the reference increase to 10MHz with a step frequency change of 2MHz.



 The PLL is initially in lock state with a 8MHz reference clock. At time=30 $\mu$ S, the reference clock frequency increase from 8MHz to 10MHz with a step frequency change of 2MHz



 
Control voltage  $V_c$  VS time: The PLL is initially in lock state with a 8MHz reference clock. At time=30 $\mu$ S, the reference increase to 9MHz with a step frequency change of 1MHz.




Control voltage  $V_c$  VS time for PLL with different damping factors but the same natural frequency: The PLL is initially in lock state with an 8MHz reference clock. At time=30 $\mu$ S, the reference increase to 9MHz with a step frequency change of 1MHz.

### Case II: small frequency step

## Fuding Ge: PLL design

 


 Control voltage  $V_c$  VS time: The PLL is initially in lock state with a 8MHz reference clock. At time= $30\mu$ S, the reference increase to 8.5MHz with a step frequency change of 0.5MHz.




The PLL is initially in lock state with a 8MHz reference clock. At time= $30\mu$ S, the reference increase to 8.5MHz with a step frequency change of 0.5MHz.

## Phase step response

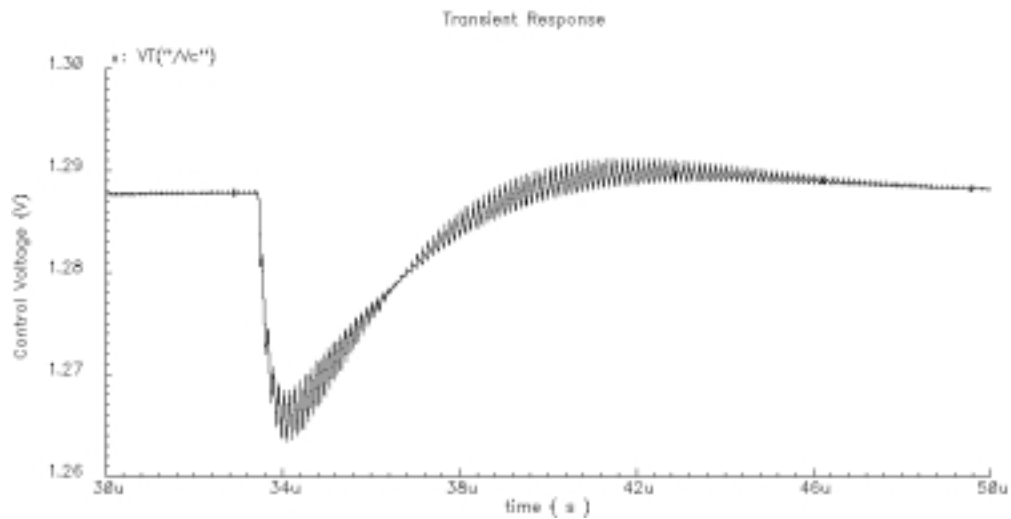


 Control voltage VS time in the case of a 50ns phase step 90ns.








 
Input reference clock with a phase step of 90ns.




Results for divide ratio N=15

 

  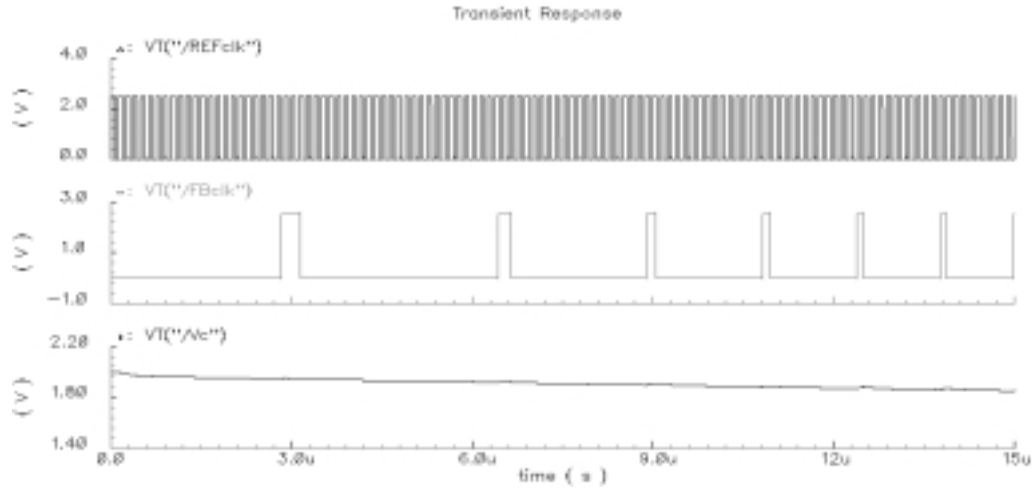Compared to the case of N=25, the case of N=15 need less time to lock. This is due to different initial condition.



 

### Check the instantaneous frequency of VCO output

In order to observe the instantaneous frequency of VCO output, I built a VerilogA model which transform the instantaneous period of the VCO output to frequency using  $\text{frequency} = 1/\text{period}$ . The following are the code I used:

```
-----
////////////////////////////////////
// Instantaneous Frequency Meter ///
////////////////////////////////////

// This verilogA model will output the frequency of the input
// based on the instantaneous period of input clock signal

// You need to change the value of hlfvcc to match the power supply
// of the clock signal. In this version vcc=2.5 and hlfvcc=1.25
// The time of the first transition is unknown, so it is discarded
// and the frequency always begin at 0 Hz

`include "constants.h"
`include "discipline.h"

nature Frequency
  abstol = 1m;
  access = FF;
  units = "Hz";
  blowup = 1.0e10;
endnature

discipline freq_current
  potential Frequency;
  flow Current;
enddiscipline

module Fremeter(vin,fout);

  input vin;
  output fout;

  freq_current fout;
  electrical vin;

  real latest;
  real tearly;
  real fout_val;

```

## Fuding Ge: PLL design

```
real hlfvcc;
integer counter;


analog begin

    @ ( initial_step ) begin
        tearly=0;
        tlatest=1.0;
        hlfvcc=1.25;    //Change your hlfvcc here !
        counter =0;
    end

    @ ( cross ((V(vin)-hlfvcc),+1 )) begin
        tlatest = $realtime;
        fout_val = 1/(tlatest-tearly);
        tearly = tlatest;
        counter = counter +1;
    end

    if (counter == 1)
        FF(fout) <+ 0.0;
    else
        FF(fout) <+ fout_val;
    end

endmodule
```

 

From this figure we can see that by watching  $V_c$ , we do observe the change of VCO output frequency. Damping factor is 0.303.

### 3.4 Noise simulation


#### 3.4.1 Fourier analysis

Phase noise is defined as in the following equation [HAJI99]:


$$L\{\Delta\omega\} = 10 \cdot \log \left[ \frac{P_{\text{sideband}}(\omega_0 + \Delta\omega, 1\text{Hz})}{P_{\text{carrier}}} \right]$$
 
## Fuding Ge: PLL design


Where  $P_{\text{sideband}}(\omega_0 + \Delta\omega, 1\text{Hz})$  is the single sideband power at a frequency offset,  $\Delta\omega$ , from the carrier in a measurement bandwidth of 1 Hz, and  $P_{\text{carrier}}$  is the total power under the power spectrum. It includes both amplitude and phase fluctuations.



 This shows the VCO output spectrum. The input reference is an ideal clock with a frequency of 8 MHz. Power supply is 2.5 V. The magnitude of the 200 MHz signal is 1.57595 V and the 192 MHz spurious signal is 2.499 mV.  $20\log(2.499\text{mV}/1.57595\text{V}) = -56\text{dB}$ .



 This figure shows the control voltage when the PLL is in lock stage. This figure shows a largest change in  $V_c$  is about 0.6 mV, the VCO gain is about 360 MHz/V, then the frequency is about 200 kHz.



This figure shows the time distribution of jitter, which is defined as instantaneous period minus the average of period when the PLL is in lock state. The time from A to B is about 20uS, roughly about the natural frequency.

### 3.4.2 Cycle-to-cycle jitter simulation

The cycle-to-cycle jitter of a clock signal is defined as the r.m.s. variation (standard deviation) in the period, which can be described by the following equation:

$$\sigma_{CTC} = \sqrt{\frac{1}{M} \sum_{i=1}^{M, M \rightarrow \infty} (t_i - t_{avg})^2}$$

Where  $t_i$  is the instantaneous period of the signal and  $t_{avg}$  is the average period value of the clock signal<sup>1</sup>. Using the so-called short-cut formula we can rewrite the above equation as:

$$\sigma_{CTC} = \sqrt{\frac{1}{M} \sum_{i=1}^{M, M \rightarrow \infty} t_i^2 - (t_{avg})^2} = \sqrt{\frac{1}{M} \sum_{i=1}^{M, M \rightarrow \infty} t_i^2 - \left(\frac{1}{M} \sum_{i=1}^{M, M \rightarrow \infty} t_i\right)^2}$$

We use this equation and transformed it into a VerilogA module to calculate the cycle-to-cycle jitter. The VerilogA code is shown in the following:

```

-----
// ////////////////////////////////////////
// Cycle-to-cycle jitter meter          //
// Copyright by Fuding Ge, All right reserved //
// ////////////////////////////////////////

// This verilogA model output the rms cycle-to-cycle jitter of the input
// clock signal. The definition of the cycle-to-cycle jitter is the rms
// variation in itd period.

```

<sup>1</sup> Here we divide the sum by M instead of more formal mathematical definition:

$$\sigma_{CTC} = \sqrt{\frac{1}{M-1} \sum_{i=1}^{M, M \rightarrow \infty} (t_i - \bar{t})^2}$$

## Fuding Ge: PLL design

```
// JitCTC=sqrt((sum(ti-tavg)**2)/M) where M is the number of periods of test.
// M should be as large as possible. ti is the instantaneous and tavg
// is the average of the periods: tavg=(t1+t2+...+tM)/M

// In this model we use the following equation:
////////////////////////////////////
// JitCTC=sqrt((sum(ti)**2)/M-(tavg)**2)    //
////////////////////////////////////

// You need to change the value of hlfvcc to match the power supply
// of the clock signal. In this version vcc=2.5 and hlfvcc=1.25

`include "constants.h"
`include "discipline.h"

nature Time
    abstol = 1e-25;
    access = TT;
    units = "ps";
    blowup = 1.0e10;
endnature

nature Number
    abstol = 1e-3;
    access = NUM;
    units = "";
    blowup = 1.0e200;
endnature

discipline time_current
    potential Time;
    flow Current;
enddiscipline

discipline number_current
    potential Number;
    flow Current;
enddiscipline

////////////////////////////////////

module Jittermeter(vin,jitter,num_period);
input vin;
output jitter,num_period;

electrical vin;
time_current jitter;
number_current num_period;

    real tlatest;
    real tearly;
    real period_early, period_latest;

    real period_square;
    real period_square_sum;
    real period_square_avg;

    real period_total;
    real period_avg;
    real period_avg_square;

    real jitter_val;
    real hlfvcc;
    integer counter;
    integer counter_begin;

////////////////////////////////////
    analog begin
```

## Fuding Ge: PLL design

```
//////// initialize the parameters//////////
@ ( initial_step ) begin
    tearly=0.0;
    tlatest=0.0;
    hlfvcc=1.25;          //Change your hlfvcc here !
    counter =0;
    counter_begin=20000;
    period_early=0.0;
    period_latest=0.0;

    period_square=0.0;
    period_square_sum=0.0;
    period_square_avg=0.0;

    period_total=0.0;
    period_avg=0.0;
    period_avg_square=0.0;
end

////////////////////////////////////////
@ ( cross ((V(vin)-hlfvcc),+1 ) ) begin
    tlatest = $realtime*1e12;
    period_latest = tlatest-tearly; //Current period value
    tearly = tlatest;
    period_early = period_latest;
    counter = counter +1;

if (counter >= counter_begin+2) begin

    period_square = period_latest*period_latest;
    period_square_sum = period_square_sum + period_square;
    period_square_avg = period_square_sum/(counter-counter_begin-1);

    period_total = period_total + period_latest;
    period_avg = period_total/(counter-counter_begin-1);
    period_avg_square = period_avg*period_avg;

    jitter_val = period_square_avg - period_avg_square;
end
end

////////////////////////////////////////

//// output jitter value and number of measure periods ////
if (counter-counter_begin < 10000)
    begin
        TT(jitter) <+ 0;
        NUM(num_period) <+ 0;
    end
else
    begin
        TT(jitter) <+ sqrt(jitter_val);
        NUM(num_period) <+ counter-counter_begin;
    end
end

end
endmodule
-----
```

Herzel [HERZ98] defined the cycle-to-cycle jitter as the variance between successive periods:

$$\sigma_{\text{CTC,CC}} = \sqrt{\frac{1}{M} \sum_{i=1}^{M, M \rightarrow \infty} (t_{i+1} - t_i)^2}$$




Fuding Ge: PLL design

For white noise source, two successive periods are uncorrelated, and since adjacent cycle jitter represents the difference between two periods, it is twice as large as the variance of one period, so:


$$\sigma_{CTC,CC} = \sqrt{2}\sigma_{CTC}$$

We can also use this equation to implement jitter simulation.




The following figure shows the simulation results of the cycle-to-cycle jitter using Spectre. It can be seen that the accuracy of the transient analysis is very important. If the accuracy is set to be liberal, the jitter is about 5 ps, but if the accuracy is set to be conservative or moderate, the jitter is only about 0.3 ps. It can also be seen that there are not much difference between moderate and conservative accuracy.

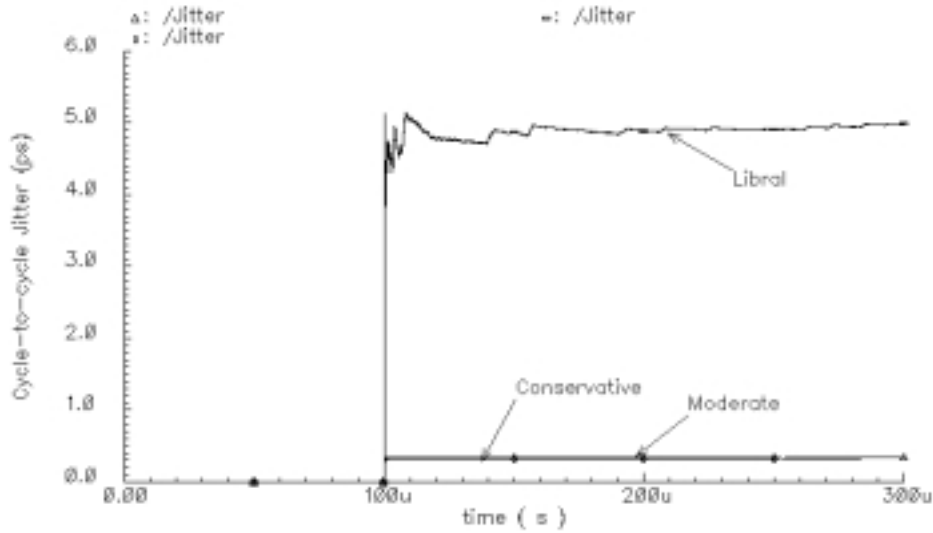

**Results for N=35**

 

Vc versus time, Vc stabilized at 1.0698

   

## Notes about Laplace Transform

Laplace transform:

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

Inverse Laplace transform:

$$f(t) = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s)e^{st} dt$$

Delay in time domain:

$$L\{f(t - \tau)\} = F(s)e^{-s\tau}$$

Differentiation in time domain:

$$L\left\{\frac{df(t)}{dt}\right\} = sF(s)$$

Integration in time domain:

$$L\left\{\int_0^t f(t)dt\right\} = \frac{F(s)}{s}$$

Initial value theorem:

$$f(t = 0) = \lim_{s \rightarrow \infty} sF(s)$$

Final value theorem:

$$f(t = \infty) = \lim_{s \rightarrow 0} sF(s)$$

**MOSFET model used in this project**

In this and next projects, we will use the TSMC 0.25 $\mu$ m process. The power supply is about 2.5V. We download the model files from MOSIS web page then modified to support the Cadence Spectre mixed signal simulation tools.

The typical transistor parameters for BSIMV3V are shown in the following. The gate oxide thickness is 57A. The threshold voltage of NMOS is about 0.412V and about -0.58V for PMOS.

```

model nch bsim3v3 type=n
+ tnom          =27              version = 3.1          tox          = 5.7E-9
+ xj            = 1E-7           nch          = 2.3549E17       vth0         = 0.4122189
+ k1            = 0.4555302      k2           = 5.728531E-3   k3           = 1E-3
+ k3b          = 2.9233592      w0           = 1.816641E-7   nlx          = 2.10175E-7
+ dvt0w        = 0              dvt1w        = 0              dvt2w        = 0
+ dvt0         = 0.4608679      dvt1         = 0.5163149   dvt2         = -0.5
+ u0           = 318.8665069     ua           = -9.32302E-10    ub           = 2.162432E-18
+ uc           = 3.868128E-11    vsat         = 1.458598E5   a0           = 1.626434
+ ags          = 0.3003966      b0           = -4.103132E-7  b1           = 5E-6
+ keta         = -4.297464E-4    a1           = 0              a2           = 0.4274964
+ rdsw         = 116            prwg         = 0.5          prwb         = -0.2
+ wr           = 1              wint         = 0              lint         = 1.056485E-8
+ xl           = 3E-8           xw           = -4E-8         dwg          = -1.833849E-8
+ dwb          = 2.423085E-9     voff         = -0.1085255   nfactor      = 1.6188811
+ cit          = 0              cdsc         = 2.4E-4          cdscd        = 0
+ cdsb         = 0              eta0         = 4.244913E-3       etab         = 5.001973E-4
+ dsub         = 0.0551518      pclm         = 1.9563343     pdiblc1     = 1
+ pdiblc2      = 7.485749E-3     pdiblc      = -0.0349745   drout       = 0.8869937
+ psbcl        = 7.999904E10     pscbe2      = 5E-10         pvag        = 0
+ delta        = 0.01           rsh          = 4.4           mobmod       = 1
+ prt          = 0              ute          = -1.5            kt1          = -0.11
+ kt1l         = 0              kt2          = 0.022         ual         = 4.31E-9
+ ub1          = -7.61E-18      uc1          = -5.6E-11         at           = 3.3E4
+ wl           = 0              wln          = 1              ww           = 0
+ wwn          = 1              ww1          = 0              ll           = 0
+ lln          = 1              lw           = 0              lwn          = 1
+ lwl          = 0              capmod       = 2              xpart       = 0.5
+ cgdo         = 6.08E-10        cgso         = 6.08E-10       cgbo         = 1E-12
+ cj           = 1.758361E-3     pb           = 0.99          mj           = 0.4595413
+ cjsw         = 3.984847E-10    pbsw        = 0.99          mjsw        = 0.3488353
+ cjswg        = 3.29E-10        pbswg       = 0.99          mjswg       = 0.3488353
+ cf           = 0              pvth0        = -0.01          prdsw       = -10
+ pk2          = 2.330213E-3     wketa        = 7.327459E-3   lketa       = -6.323718E-3

model pch bsim3v3 type=p
+ tnom          = 27              version = 3.1          tox          = 5.7E-9
+ xj            = 1E-7           nch          = 4.1589E17       vth0         = -0.5806205
+ k1            = 0.6160845      k2           = 6.878321E-3   k3           = 0
+ k3b          = 12.103096      w0           = 1E-6          nlx          = 1E-9
+ dvt0w        = 0              dvt1w        = 0              dvt2w        = 0
+ dvt0         = 3.0107968      dvt1         = 0.7196372   dvt2         = -0.1087959
+ u0           = 113.5280395     ua           = 1.428339E-9       ub           = 1E-21
+ uc           = -1E-10         vsat         = 2E5            a0           = 0.8190934
+ ags          = 0.1198761      b0           = 1.300549E-6     b1           = 5E-6
+ keta         = 0.0159086      a1           = 7.587589E-4     a2           = 0.5038746
+ rdsw         = 826.8966468     prwg         = 0.3121607     prwb         = -0.335727
+ wr           = 1              wint         = 0              lint         = 3.708011E-8
+ xl           = 3E-8           xw           = -4E-8         dwg          = -4.149242E-8
+ dwb          = 5.696148E-9     voff         = -0.127106       nfactor      = 1.154513
+ cit          = 0              cdsc         = 2.4E-4          cdscd        = 0
+ cdsb         = 0              eta0         = 0.8298199       etab         = -0.3400479
+ dsub         = 1.2581086      pclm         = 1.175511         pdiblc1     = 6.170092E-3
+ pdiblc2      = -3.886687E-9    pdiblc      = -1E-3         drout       = 0.0670916

```

## Fuding Ge: PLL design

+ pscbe1	= 7.623894E9	pscbe2	= 1.944679E-9	pvag	= 0.6564436
+ delta	= 0.01	rsh	= 3.4	mobmod	= 1
+ prt	= 0	ute	= -1.5	kt1	= -0.11
+ kt11	= 0	kt2	= 0.022	ual	= 4.31E-9
+ ub1	= -7.61E-18	uc1	= -5.6E-11	at	= 3.3E4
+ wl	= 0	wln	= 1	ww	= 0
+ wwn	= 1	wwl	= 0	ll	= 0
+ lln	= 1	lw	= 0	lwn	= 1
+ lwl	= 0	capmod	= 2	xpart	= 0.5
+ cgdo	= 6.51E-10	cgso	= 6.51E-10	cgbo	= 1E-12
+ cj	= 1.893794E-3	pb	= 0.99	mj	= 0.4672189
+ cjsw	= 3.253221E-10	pbsw	= 0.5596564	mjsw	= 0.2788539
+ cjswg	= 2.5E-10	pbswg	= 0.5596564	mjswg	= 0.2788539
+ cf	= 0	pvth0	= 5.588398E-3	prdsw	= 3.2881861
+ pk2	= 3.613465E-3	wketa	= 0.0252565	lketa	= -0.0108543

## Reference

- [GARD80] F.M. Gardner, "Charge-pump phase-lock loops", IEEE Trans. Comm., Vol.COM-28, pp.1849-1858, Nov 1980.
- [HERZ99] Frank Herzl and Behzad Razavi, "A study of oscillator jitter due to supply and substrate noise", IEEE Trans. Circuit and system – II, Vol46 (1), PP56-62, 1999.
- [WOLA91] D.H. Wolaver, "Phase-locked loop circuit design", Prentice Hall, Englewood Cliffs, NJ, 1991.
- [MANE96] J. G. Maneatis, "Low jitter process-independent DLL and PLL based on self-biased techniques", IEEE J. SSC, Vol. 31, No.11, pp1723-1732, Nov, 1996
- [LARS96] P. Larsson, "High-speed architecture for a programmable frequency divider and a dual-modulus prescaler", IEEE J. SSC, Vol. 31, No.5, pp744-748, May, 1996
- [BEST97] R.E. Best, "Phase-locked loops, design, simulation and applications", McGraw-Hill, New York, 1997, 3<sup>rd</sup> Edition
- [TI99] Texas Instruments, "Fractional/integer-N PLL basics", SWRA029, edited by Curtis Barrett, wireless communication business unit, 1999
- [HAJI99] Ali Hajimiri, Thomas H. Lee, "The design of low noise oscillators", Kluwer Academic, Boston, 1999