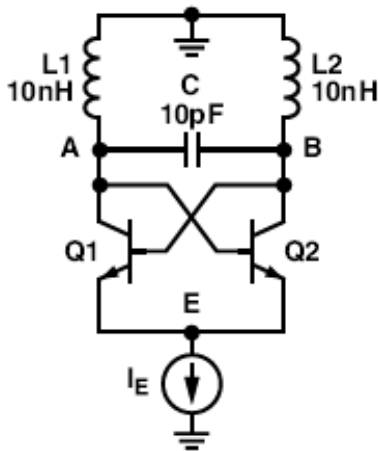


[http://www.geocities.ws/glene77is/GC\\_Alpha\\_RG\\_pdf\\_files/DrLeif\\_2\\_Fourth-Dee-Oscillator-example.gif](http://www.geocities.ws/glene77is/GC_Alpha_RG_pdf_files/DrLeif_2_Fourth-Dee-Oscillator-example.gif)



TO MINIMIZE THE INTRODUCTION OF DISTRACTING COMPLICATIONS OF THE KIND FREQUENTLY ENCOUNTERED IN PRACTICAL OSCILLATORS, Q1 AND Q2 ARE INITIALLY ALLOWED TO BE "IDEAL"; THAT IS,  $BF = BR = VAF = VAR = \text{INF.}$  AND THE DEVICE RESISTANCES AND CAPACITANCES ARE ZERO;  $\tau_f = 10\text{ps.}$

LIKewise, FOR THE INITIAL EXPERIMENTS, THE TANK IS ASSUMED TO BE LOSS-LESS AND WITHOUT A LOAD.

$I_E$  IS TURNED ON VERY RAPIDLY, AND THE CONSEQUENCES ARE OBSERVED FOR A VARIETY OF CONDITIONS, WHICH WILL BE ELABORATED ON IN DETAIL DURING FURTHER DISCUSSIONS WITH DR. LEIF.