

D-Day (continued) [The Wit and Wisdom of Dr. Leif—5]

By Barrie Gilbert [barrie.gilbert@analog.com]

Niku's Daedalus Day presentation began in Volume 40, Number 3. The complete series can be found online at www.analog.com/library/analogdialogue/leif1.html.

"This next study will show some results comparing the relative effects of mismatches and noise. Such comparisons can never be precise, for reasons I gave earlier. Not only are mismatches just *interesting cases*; the onset of strong oscillations—the start-up trajectory—also depends on such controllable factors as the rise-rate of the tail current, I_T ; the overdrive beyond the critical value, I_{CRIT} ; and the load resistance, determining the tank's effective Q . Once these have been chosen, we can compare start-up times, defined as the time from when the tail current crosses I_{CRIT} to the time the oscillations reach 90% of their final amplitude.

"I'm sure all of you appreciate that, frequently, the potency of simulation in gaining insights does not necessitate the use of accurate parameter values, or reliable process statistics, such as are essential in predicting the performance of a production microsym. Rich insights are to be gained from pursuing a well-planned set of comparative studies using relative values that are just as valuable as the *confirmation* of an original design using absolute parameter values ..."

Dr. Leif raised his hand politely. Niku caught the gesture and invited his comments. "Yes, sir? Do you have a little song for us?" she teased.

"Perhaps we ought to say '*far more* valuable,' since we should never forget that learning is as much a part of an engineer's job as getting new products to market—and this is as important for our Fusers as for Originators. We must always set aside time in our busy lives to think about those Fundaments, and ceaselessly ask ourselves those vital questions: 'What If?', 'How About?', 'Why does *that* Happen?'. You need to be acutely aware that, while your latest, thoroughly robust, high-yielding, and trend-setting product, which you have managed to get to market in a competitive time-frame, and yet meets every one of its highly challenging performance specifications and goes on to make us all fabulously rich ..." (Leif grins as the audience groans, and he takes a brief sip from his water glass) "... while all that is very important, it is the *new insights* that you gained throughout the experience, as well as from the time you put into facing up to *independent, self-assigned* challenges—of the sort that Niku is urging you to undertake—they will be the *foundation stones* of your career. New product development frequently requires the use of several distinctively clever ideas. But that is a one-time event. On the other hand, the *new insights* that opened to you, during the experience, become the precious gems you'll add to your own unique treasure trove of tools. These diamond-hard gems of insight will never be far from you, waiting in your subconscious to illuminate and inform the creative work of a long and productive career. I ..."

Leif stopped abruptly, as suddenly as he had apparently felt the need to make these interlineal observations. Returning to his front-row seat, he seemed uncharacteristically self-conscious. What next thought that he decided to suppress was in his mind?

"*War das eu'r lied?*" Niku again teased, with a little quote from *Die Meistersinger*—as asked by Hans Sachs, the humble cobbler, of Sextus Bessemer, the town clerk of 16th-century Nuremberg who was attempting to serenade the heroine Eva. From the chats they frequently enjoyed over at Galaxybux, Niku knew that Leif

would be in on the joke, and both smiled together at its poignant appropriateness. But the bulk of the audience was perplexed by this unfamiliar four-word exchange, yet increasingly aware of the unusual rapport and the spirited give-and-take between these two. Had they been more informed about widowed Hans Sachs and the young Eva, the parallel would have been evident.

Breaking eye-contact, and seeming to suddenly remember she was in the middle of a lecture, Niku blushed deeply and visibly for the second time in an hour.

"Thank you, Dr. Leif. So ... uh, back to our little friend, Oscar. A few minutes ago ..." (Or was it a week? Or a century?) "I showed that its internal noise—and the enormous noise-amplification factor—reduce this time to just a few cycles. So, comparisons of start-up time are much too close to be of any use as a source of insight. In fact, for even tiny amounts of [stochastic] noise, the very notion of a *start-up trajectory* becomes moot. Rather, the modulation envelope during startup, which can be seen in this slide" (Micha-2, which had remained frozen on the screen) "is determined by the particular L , C , and R of the tank.

"However, to complicate matters further, the *effective* loading of this tank, embedded in the active circuit—the *in-situ* value—is *not* the value that is conventionally deduced from measurements of the tank alone—the *ex-situ* value. And here, I'm not referring to any incidental, parasitic effects, for example, as caused by the shunt loading imposed by the incremental output resistance of the differential pair. In fact, as I believe I mentioned earlier, to remove all such complicating factors, the transistors are assigned Early voltages (VAF and VAR) of 10^9 volts, and the classical dc beta-modeling factors (BF and BR) are similarly 10^9 .

"This is not as fanciful as it might at first seem, because the core properties of the BJT do not depend on these parameters having moderately low values. Indeed, they represent *defects*—rather than *assets*—of the transistor. We long ago gave up thinking of the BJT as a current-controlled current source (CCCS); rather, just like field-effect devices, they are more properly viewed as voltage-controlled current-sources (VCCS). The finite output resistance of a VCCS never did anything *useful* for it; neither does the base current of a BJT, unless you were foolish enough to actually depend on the need for some finite base current.

"Likewise, the depletion capacitances (CJE, CJC, CJS) are just useless baggage, as are the ohmic resistances (RE, RB-RBC, RC), and should not be *depended on* for any specific circuit behavior. Between them, they only increase the *inertia* of a circuit, and the ohmic parts contribute *thermal noise*. They are defects of a BJT. By the way, don't confuse the diffusion capacitance with those parasitics. It is a *direct measure* of the base charge needed to establish a given collector current.

"This perspective—and the practice of stripping the BJT model of all nonuseful attributes during preliminary investigations of new and unfamiliar topologies—is called 'Foundation Design' by Dr. Leif. When every nuance of the cell has been thoroughly understood and accounted for, using what he calls this 'Level 0' model, it is permissible to move forward to a 'Level 1' model, which, for example, might first add in more realistic values of the dc betas and Early voltages, the consequences of quasistatic depletion-layer modulation by the terminal voltages ..."

Some in the audience, listening to what was beginning to sound more like philosophy, were manifesting spaced-out expressions; but most were working hard to follow the convoluted contour of Niku's thinking. Leif again wanted to comment and again was polite enough to signify this by raising his hand.

"Dr. Leif?"

“Ah, well, let’s see now. First, if you’ll forgive me Niku, you’re running a little short on time, and I know you have some really interesting discoveries to share with us, about Oscar. I suspect you didn’t plan to digress so deeply into these peripheral ideas at the expense of the main theme, did you? Secondly, neither the term ‘Foundation Design’ nor its principles are mine, although I admit I am a passionate advocate of them. They go *way* back to the last century, and the lectures given by a long-departed ADI Fellow, of whom we hear very little these days. When I get back to my office, I’ll issue a cy-mail, and include a reference to his lectures, for the engineering community. Okay. That’s it.”

“Oh, yes; now I recall, you did tell me that Foundation Design came from a long time back. I’m sorry I got that mixed up. And you’re right: I got a bit carried away with some incidental ideas. I was about to explain that another approach to tracing the start-up trajectory is to disable the modeling, and run the simulations in the old SPICE-like mode, when they *didn’t* model noise as a time-process. Then, using a variety of representative mismatches we can simply observe how the start-up times compare to the noise-driven case.

“In fact, now that we have seen how very short this delay can be, provided that noise mechanisms are fully modeled, we need to extract some other insights from these studies. To be candid, that was the only reason for starting down this path. I was pretty sure from the outset that noise had to be the driver—in both senses: ‘was bound to be’ and ‘had better be,’ and that in all cases where this wasn’t so it would be due to unplanned mismatches. But never due to *glitches*! Any oscillator that needs to be started by such gross influences is, as a matter of practical definition, a poor design, since this very sensitivity is almost bound to degrade the phase noise after it reaches its periodic steady state.”

“Dr. Yeng?” It was a rather mature lady’s voice from two rows back. “That’s not quite true. There are times when one wishes to preserve a very high effective Q in a different class of oscillator, which would indeed eventually start up because of noise, and in a certain sense *right away*, but would reach its cyclostationary state only after perhaps tens of thousands of cycles; whereas its services are needed immediately following a logic edge that defines $t = \text{zero}$. So one needs to introduce a particularly well-managed start-up strategy to do this; and with it, the oscillator not only starts up instantly, but at exactly its final amplitude.”

“That’s really interesting!” said Niku, clearly genuinely pleased to learn of something that sounded so close to her own recent discoveries. “Can you say a little more about this?”

“I can, although I don’t wish to steal too much of your time. I have a couple of visuals prepared. By the way, I’m Hjørdis Björklund. May I open my Michaday channel to the screen?”

“Oh ... yes, of course,” said Niku, slightly flustered by having forgotten that her own access to the GE°E had been suspended, in its capacity as a surrogate presenter.

“Michaday, this is Björklund. Show 101.37.01.255.”

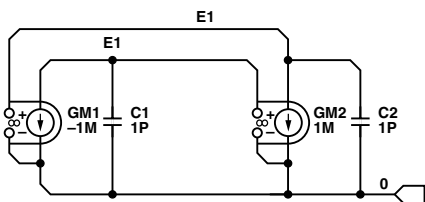


Figure 1. The mysterious Dr. Björklund’s first visual.

With no chummy banter, of the sort that Niku always expected from Micha, but just a curt “Certainly, Dr. Björklund”—which suggested to Niku that this lady was no newcomer to Solna and

was all business—a simple schematic instantly appeared. She wondered why she’d never met this individual; and why Dr. Leif was apparently suppressing his mirth. What was going on?

“This is just an illustrative example I prepared. It’s nothing more than two ideal gm/C integrators in a loop, forming a sine/cosine oscillator, of the sort one might need in an I/Q demodulator. The rapid start-up is essential because such a subsystem is shut down between active time-slots, until valid data is available. When this happens, the phase-locked loop, of which this is a part, needs to acquire the carrier within a few cycles. On the other hand, a high effective Q is essential to minimize phase noise; and normally that would result in the oscillator’s start-up process being far too sluggish. So it appears there’s a basic conflict, here.

“Now, keep in mind,” continued the mysterious Dr. Björklund, “that this is an *illustrative* circuit. Practical integrators used in a loop as basic as this will cause the amplitude of the oscillations to either decay—if their poles move off the imaginary axis into the left side of the s -plane, due to the shunting of the capacitors by the finite incremental output resistance of the gm cells—or the amplitude will rise exponentially when there is some additional hidden phase lag in the gm cells causing the resonant poles to move into the right plane.

“Such practical details are taken care of by regulating means on top of what I’m showing here. But they are not germane to the key idea that, sometimes, one does use a sort of glitch to get the ball rolling; though that would be a particularly inept description of the elegant way in which this start-up means is implemented. Michaday, show *.256.”

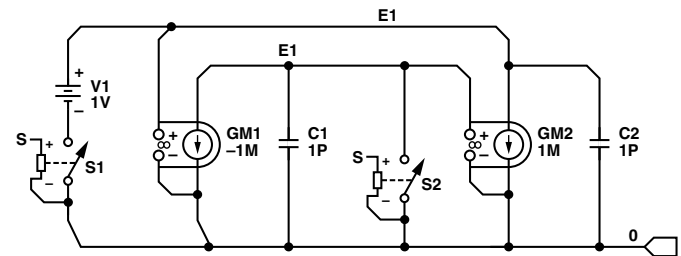


Figure 2. Dr. Björklund’s second visual.

“Here’s the key idea. Notice the two switches, one connecting a dc voltage source, which I am showing as 1 V, to the output E_2 , while the other simply connects the output E_1 to ground. These switches remain closed right up to the moment we wish to start the oscillations. Now, Miku, what happens when we suddenly release the initial conditions of this describing function?”

$$\int E_1(gm/C) dt = -\int E_2(gm/C) dt$$

“It’s *Niku*, ma’am.” This was not fair! She had allowed this lady a moment or two, to show a sort of quick example of something or another that had admittedly sounded relevant to her own talk, and a bit interesting. But now, here was this ... this *lady*, calling her ‘Miku,’ and putting her on the spot, in *her* time! Fortunately, while Niku might show her inexperience, and *was* perhaps being a bit too familiar with Leif, and *did* play cheeky with Michaday (Gosh! Can a GE°E get *embarrassed* in public, she suddenly wondered)—for all that, *she* was a warrior, too (for she knew that Hjørdis means ‘Sword Goddess’).

“Well, that’s trivial ...” (whoa, *careful*, girl) “uh ... Dr. Björklund” (that’s better; don’t let her see you’re rattled). “When the initial values are released this equation will execute a harmonic pair, of stable peak amplitude (E_1, E_2) = 1 V, at an angular frequency of $\omega = gm/C$, which, with the values shown, will be at 159.155 MHz.”

“Yes ... that’s ... right,” said Björklund, who promptly sat down.

“Dr. Leif,” said Niku with a coy grin, “may I please have Micha back on my team?”

“He has been waiting for you for some time, Niku.” Was that a trace of empathetic tenderness in Leif’s voice, she wondered, now kicking herself for probably looking foolish in front of all those guys, or appearing to be angling for brownie points from the old fellow. Well, old is a matter of degree. Leif carried his 79 years remarkably well. His bronzed features, athletic form, white casual shirt and slacks, and the upscale gold watch gave him the appearance of one having just sailed up from Monte Carlo.

“Thank you, sir. Okay, Micha, you must have heard what was just discussed. Please take that equation and show us how this way of starting an I/Q oscillator plays out.”

That part of the GE^oE currently servicing Dr. Björklund—her still-open channel—though operating within the one framework, was not in any sort of loyalty clash to the channel assigned to Niku. These machines shared at least that much with the old digital juggernauts. Micha probably had no idea what it meant to be “fair” or “even handed” in its dealings with those who used it. But, in the time since these latest models had arrived, it was becoming clearly evident—a surprise even to Neuromorphix, Inc.—that they developed a closer rapport with some users than others. It didn’t affect the speediness of their service, even less the accuracy of the results they produced. But it was almost as if they enjoyed working with some more than others. Leif had been made especially aware of this phenomenon during the past few minutes. It was evident that Micha was acting like ... well, a *pal* to Niku, while merely a coolly efficient servant to Björklund. In the few seconds Leif had been pondering this, the requested solution had been generated and the screen showed the result.

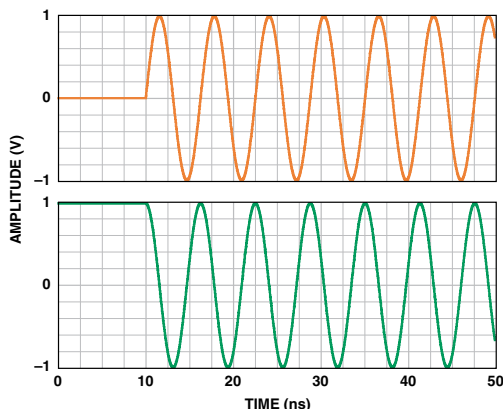


Figure 3. The instant start-up and exactly-sustained amplitude of Dr. Björklund’s “illustrative” oscillator.

“Thank you very much, Micha. Yes, that’s a useful technique to remember for relatively low-frequency oscillators. Of course, it is not usually as easy to preset the initial conditions in a resonant-tank RF oscillator, but in fact, that is one of the slides I will show in a few moments. So, after that little detour, let’s first get back to the start-up trajectory of the basic Oscar oscillator.”

Standing, Dr. Leif once again found he needed to intervene.

“Niku, I’m quite sure this audience could listen to you all day; I know *I* could,” he quipped. “But you may not have noticed that we’ve exceeded the allocated one hour by a generous margin, and I have yet to pose the traditional teaser. So, may I suggest that you open-access the rest of your work on Michaday, so that interested engineers can check in from time to time at the same address, for the final pages of this interesting story? I suspected you would have too much material to cram into one hour, but even though you didn’t get to the best part I don’t think anybody here today will feel their time was ill-spent. Am I right?”

To Niku’s delight, the audience’s applause was generous. The hand-clapping—at first a random noise—quickly phase-locked into the rhythmic foot-stomping common in Europe, no less in Scandinavia. She thought, “How apt a metaphor for how little Oscar struggles up from the noise floor!” Still standing, Dr. Leif was the last to cease clapping. It was abundantly evident that he was very pleased with how Niku had progressed since he hired her, only a few months ago. Her determination to track down the root causes of observed effects, in a manner that went far beyond the mediocre, shallow, repetitive, and unsatisfying explanations so often found in textbooks, gave him the strong assurance that this young woman was destined to become a major innovator in the coming years.

“Well, that’s it for another D-Day. Now we can all get back to some serious invention-making! And Dr. Björklund, I’d like to see you in my office, please.” With that the audience dispersed, and Leif approached Niku, who listened for a moment, smiled, and then two sets of eyes twinkled conspiratorially. But their brief resonance was lost in the noise floor.

Barrie Gilbert, the first-appointed ADI Fellow, has “spent a lifetime in pursuit of analog excellence.” Barrie was born in Bournemouth, England, in 1937. Before joining ADI, he worked with first-generation transistors at SRDE in 1954. At Mullard, Ltd., in the late ’50s, he pioneered transistorized sampling oscilloscopes, and in 1964 became a leading ‘scope designer at Tektronix. He spent two years as a group leader at Plessey Research Labs before joining Analog Devices in 1972, where he is now director of the Northwest Labs in Beaverton, Oregon. Barrie is a Life Fellow of the IEEE and has received numerous service awards. He has about 70 issued patents, has authored some 50 papers, is a reviewer for several professional journals, and is a co-author or co-editor of five books. In 1997, he was awarded an honorary doctorate of engineering from Oregon State University.



PRODUCT INTRODUCTIONS: VOLUME 40, NUMBER 4

Data sheets for all ADI products can be found by entering the model number in the Search box at www.analog.com

| | |
|---|--|
| October | |
| Accelerometer, 2-axis, ±3-g range | ADXL323 |
| Converter, Synchronous Buck, 2-/3-phase, 8-bit VID code | ADP3193 |
| Converter, Synchronous Buck, 2-/3-/4-phase, 8-bit VID code | ADP3198 |
| Multiplexers, iCMOS, 4-/8-channel, low-capacitance, ±15-V operation | ADG1408/ADG1409 |
| Temperature Sensor, Digital, 2-channel, over-/under-temperature alarms | ADT7482 |
| Temperature Sensor, Digital, 1-wire data interface | ADT7484A |
| Temperature Sensor, Digital, 2-channel, 1-wire data interface | ADT7486A |
| Transceivers, RS-485/RS-422, ESD protected | ADM307xE |
| Transceivers, RS-485/RS-422, ESD protected | ADM3486E/ADM3490E/ADM3491E |
| November–December | |
| ADC, Pipelined, 8-channel, 12-bit, 40-/50-MSPS, LVDS outputs | AD9222 |
| ADC, Successive-Approximation, 16-bit, 750-kSPS, ±1.5-LSB max INL | AD7612 |
| Controllers, Hot Swap, monitor supply voltage and current | ADM1175/ADM1176/ADM1177/ADM1178 |
| Converter, Synchronous Buck, 2-/3-phase, 8-bit VID code | ADP3199 |
| Detector, Signal-Power, 50-MHz to 4-GHz | ADL5501 |
| Front-End, Mixed-Signal, broadband modems | AD9857 |
| Monitors, Digital Power, over-current alert | ADM1191/ADM1192 |
| Regulators, Low-Dropout, 500-mA loads | ADP1715/ADP1716 |
| Switch, HDMI/DVI, 4:1, equalization and pre-emphasis | AD8191 |
| Temperature-Sensor/Voltage-Monitor, Digital, one-wire data interface | ADT7488A |
| Transmitter, HDMI/DVI, high-performance | AD9889A |
| Transceiver, RS-485, high-speed, isolated, ESD protected | ADM2490E |