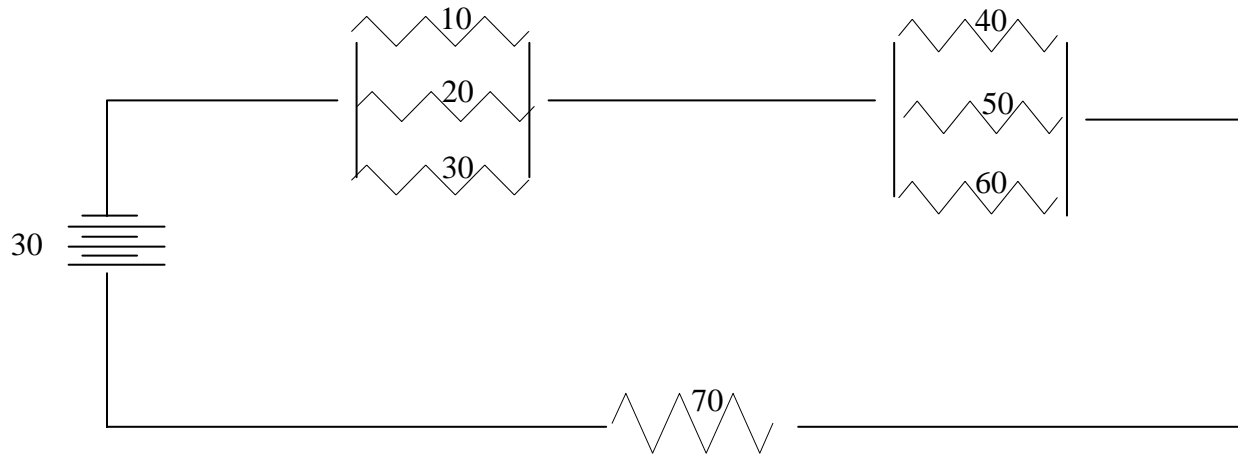
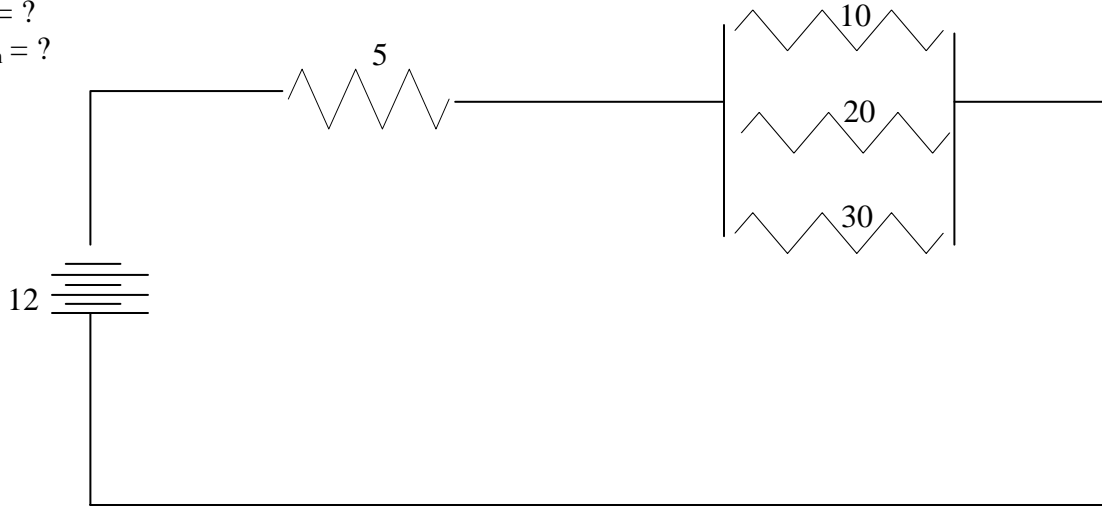


1. $R_{eq} = ?$
2. $I_T = ?$
3. $V_{5\text{ ohm}} = ?$
4. $V_{\text{para}} = ?$
5. $I_{30\text{ ohm}} = ?$



6. $R_{eq} = ?$
7. $I_T = ?$
8. $V_{10-20-30\text{ para}} = ?$
9. $I_{60\text{ ohm}} = ?$