


Inter American University of Puerto Rico  
Bayamón Campus  
School of Engineering  
Department of Electrical Engineering

ELEN 3301 – Electric Circuits I

Problem Set 2 Solutions

*Due Wednesday, September 1*

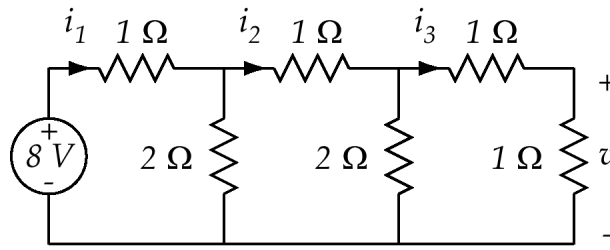
**Problem 1:** Find currents  $i_1$ ,  $i_2$ ,  $i_3$  and voltage  $v$  in the following circuit:



Note that all the resistances from the voltage source can be combined to form a  $2\ \Omega$  equivalent resistance. Thus, the total current leaving the voltage source  $i_1 = 8V/2\Omega = 4A$ . This current can flow down the first resistor or continue down the ladder. If we combine the resistors down the ladder, we see an equivalent resistance of  $2\ \Omega$ . Thus, using current divider, the current will split evenly into  $2\ A$  down the  $2\ \Omega$  resistor and  $i_2 = 2A$  down the ladder. In the final section, the  $2\ A$  must again divide, and it is easy to see in this case that both legs have a  $2\ \Omega$  resistance. Thus, the  $2\ A$  will again divide into  $1\ A$  down the  $2\ \Omega$  resistor and  $i_3 = 1A$ . Using Ohm's law,  $v = i_3 \cdot 1\Omega = 1V$ .

**Problem 2:** Find node voltages  $e_1$ ,  $e_2$  and  $e_3$  for the networks shown below using the node method (Note that the ground node has been chosen):

(A)

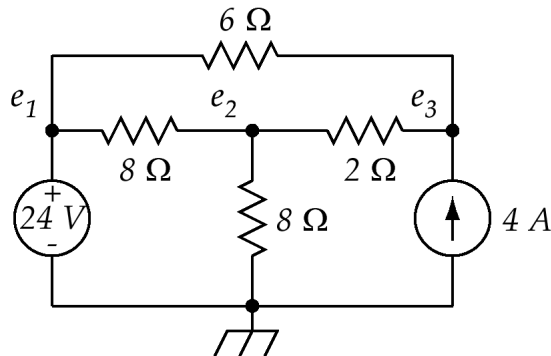

$$\text{Node } e_1: e_1 = 24V$$

$$\text{Node } e_2: \frac{e_3 - e_2}{2\Omega} = \frac{e_2}{8\Omega} + \frac{e_2 - 24V}{8\Omega}$$


$$\text{Node } e_3: 4A = \frac{e_3 - e_2}{2\Omega} + \frac{e_3 - 24V}{6\Omega}$$

Solving these two equations for  $e_2$  and  $e_3$  yields:

$$e_2 = 24V$$

$$e_3 = 30V$$

(B)

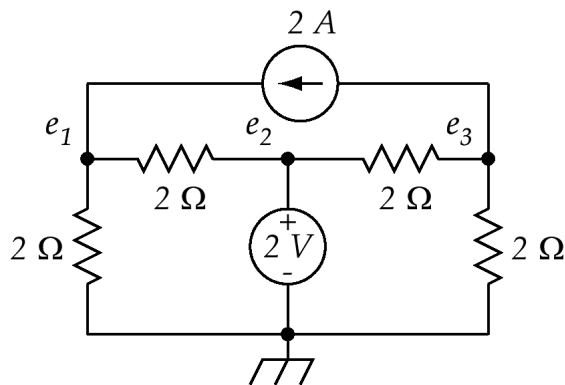

$$\text{Node } e_1: 2 = \frac{e_1 - 2V}{2\Omega} + \frac{e_1}{2\Omega}$$


$$\text{Node } e_2: e_2 = 2V$$

$$\text{Node } e_3: \frac{2V - e_3}{2\Omega} + \frac{-e_3}{2\Omega} = 2A$$

Solving these two equations for  $e_1$  and  $e_3$  yields:

$$\begin{aligned} e_1 &= 3V \\ e_3 &= -1V \end{aligned}$$

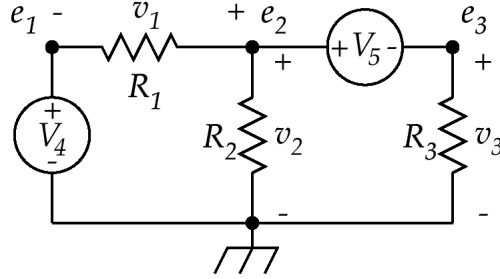**Problem 3:** Find voltages  $v_1$ ,  $v_2$  and  $v_3$  in the following circuit using the node method:



$$\text{Node } e_1: e_1 = V_4$$

Nodes  $e_2$  and  $e_3$  are joined by a voltage source; we must treat them together as a supernode where  $e_3 = e_2 - V_5$ :

$$\text{Supernode } \{e_2, e_3\}: \frac{e_2 - V_4}{R_1} + \frac{e_2}{R_2} + \frac{e_2 - V_5}{R_3} = 0$$

Solving this equation for  $e_2$  yields:

$$e_2 = \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_4 + \frac{R_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_5$$

Finally,

$$\begin{aligned} v_2 = e_2 &= \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_4 + \frac{R_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_5 \\ v_1 = e_2 - V_4 &= \frac{R_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_5 - \frac{R_1 R_2 + R_1 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_4 \\ v_3 = e_2 - V_5 &= \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_4 - \frac{R_1 R_3 + R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_5 \end{aligned}$$