


Inter American University of Puerto Rico  
Bayamón Campus  
School of Engineering  
Department of Electrical Engineering

**ELEN 3301 – Electric Circuits I**

**Problem Set 7 Solutions**

*Due Wednesday, October 20*

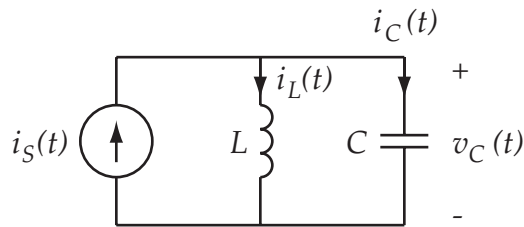**Problem 1:** For the circuit below,  $v_C(0) = 0$  and  $i_L(0) = 0$ .



(A) Let  $i_S(t) = I_S u(t)$ . Find an algebraic expression and sketch  $i_L(t)$  for  $-\pi\sqrt{LC} < t < 2\pi\sqrt{LC}$ .

To derive the differential equation, use KCL in the top node:

$$i_S = i_C + i_L$$

Note that  $i_C = C \frac{dv_C}{dt}$  and  $v_C = v_L = L \frac{di_L}{dt}$ . Substituting these expressions yields

$$i_S = C \frac{dv_C}{dt} + i_L = LC \frac{d^2 i_L}{dt^2} + i_L$$

Divide by  $LC$  to leave the equation in standard form

$$\frac{d^2 i_L}{dt^2} + \frac{i_L}{LC} = \frac{i_S}{LC}$$

For  $t < 0$ ,  $i_S = 0$  and  $i_L = 0$ . For  $t > 0$ ,  $i_S = I_S$ . The differential equation in this period is

$$\frac{d^2 i_L}{dt^2} + \frac{i_L}{LC} = \frac{I_S}{LC}$$

By now, it should be fairly obvious that the particular solution is  $i_L = I_S$ , which corresponds to a steady state as  $t \rightarrow \infty$  where the inductor acts as a short, the capacitor as an open, and all the current  $I_S$  flows through the inductor. From Problem Set 6, recall that the homogeneous solution for  $i_L$  is of the form

$$i_{L, Homogeneous}(t) = A \sin(\omega_0 t) + B \cos(\omega_0 t)$$

where  $\omega_0 = \frac{1}{\sqrt{LC}}$ . The general solution is

$$i_L(t) = I_S + A \sin(\omega_0 t) + B \cos(\omega_0 t)$$

The initial condition  $i_L(0) = 0$  yields


$$i_L(0) = I_S + B = 0 \Rightarrow B = -I_S$$

The initial condition  $v_C(0) = 0$  implies that  $\frac{di_L}{dt} = 0$  since  $\frac{di_L}{dt} = \frac{v_C}{L}$ . In order to apply this initial condition, the derivative of  $i_L$  is computed and evaluated at zero:

$$\left. \frac{di_L}{dt} \right|_{t=0} = A\omega_0 = 0 \Rightarrow A = 0$$

Thus, the solution is
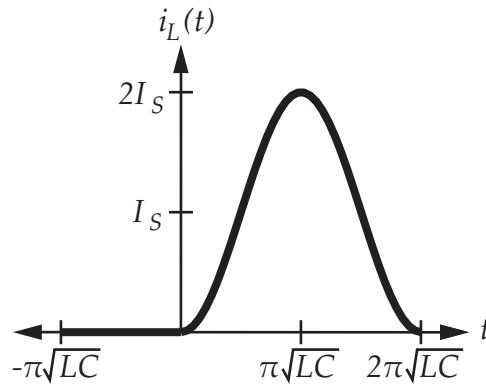
$$\begin{aligned} i_L(t) &= 0 & t < 0 \\ i_L(t) &= I_S[1 - \cos(\omega_0 t)] & \omega_0 = \frac{1}{\sqrt{LC}} & t > 0 \end{aligned}$$




- (B) Let  $i_S(t) = I_S u(t)$ . Find an algebraic expression and sketch  $i_C(t)$  for  $-\pi\sqrt{LC} < t < 2\pi\sqrt{LC}$ .  
*Hint: Use KCL and the expression for  $i_L(t)$  found in part (A).*

Note that  $i_C = i_S - i_L$ . Thus,

$$i_C(t) = 0 \quad t < 0$$
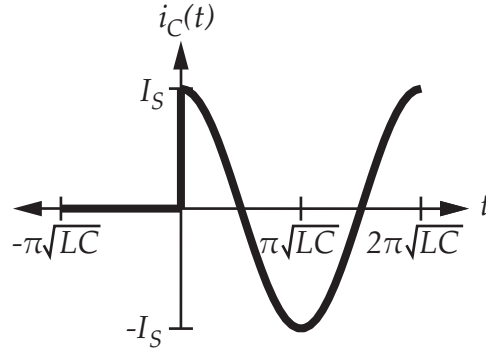
$$i_C(t) = I_S - I_S[1 - \cos(\omega_0 t)] = I_S \cos(\omega_0 t) \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad t > 0$$




- (C) Let  $i_S(t) = I_S u(t)$ . Find an algebraic expression and sketch  $v_C(t)$  for  $-\pi\sqrt{LC} < t < 2\pi\sqrt{LC}$ .  
*Hint: Use KVL and the expression for  $i_L(t)$  found in part (A).*

Note that  $v_C = v_L = L \frac{di_L}{dt}$ . Thus,

$$v_C(t) = 0 \quad t < 0$$

$$v_C(t) = L \frac{d}{dt} (I_S[1 - \cos(\omega_0 t)]) = LI_S \omega_0 \sin(\omega_0 t) = I_S \sqrt{\frac{L}{C}} \sin(\omega_0 t) \quad t > 0$$

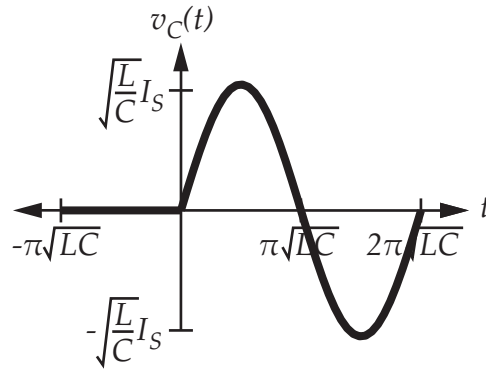where  $\omega_0 = \frac{1}{\sqrt{LC}}$ .



- (D) Let  $i_S(t) = Q\delta(t)$ . Repeat parts (A), (B) and (C) using this new input. Remember to sketch all three responses.

Note that

$$Q\delta(t) = \frac{Q}{I_S} \frac{d}{dt} I_S u(t)$$


Therefore, because of linearity, the application of the same operator to the answers obtained in the previous three parts yields the responses to the new input:

$$i_L(t) = \frac{Q}{I_S} \frac{d}{dt} I_S [1 - \cos(\omega_0 t)] = Q\omega_0 \sin(\omega_0 t) = \frac{Q}{\sqrt{LC}} \sin(\omega_0 t)$$


$$i_C(t) = \frac{Q}{I_S} \frac{d}{dt} I_S \cos(\omega_0 t) = -\frac{Q}{\sqrt{LC}} \sin(\omega_0 t)$$

$$v_C(t) = \frac{Q}{I_S} \frac{d}{dt} I_S \sqrt{\frac{L}{C}} \sin(\omega_0 t) = \frac{Q}{C} \cos(\omega_0 t)$$

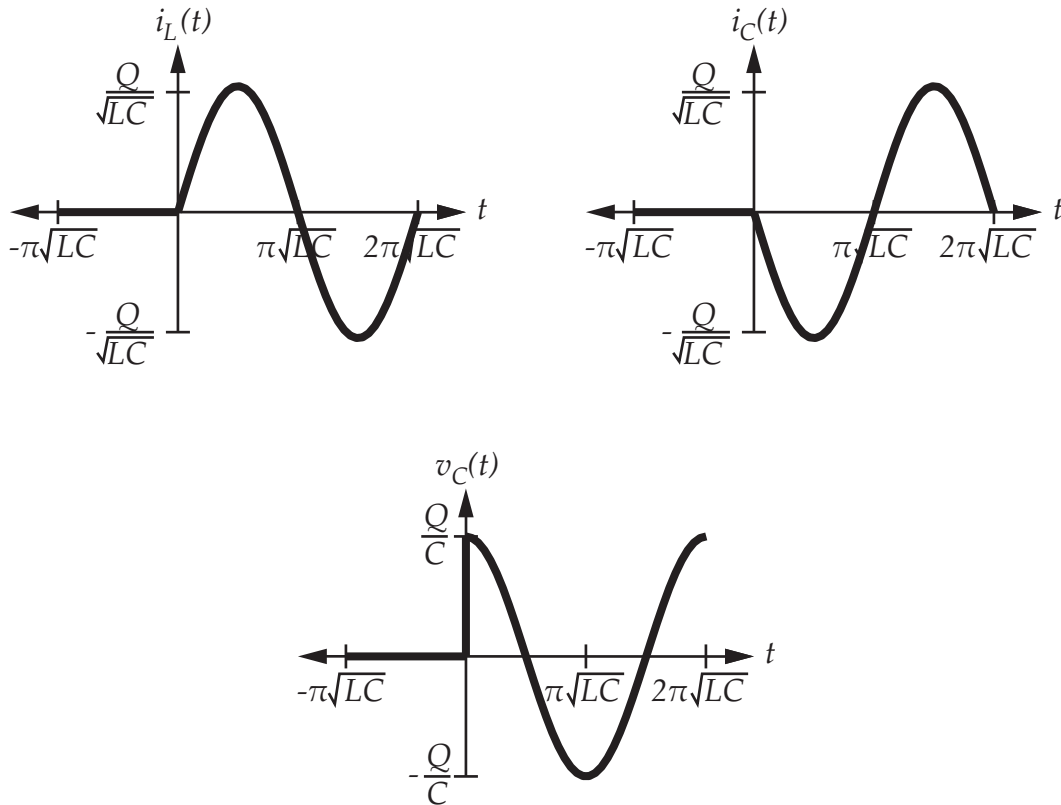where  $\omega_0 = \frac{1}{\sqrt{LC}}$  in all cases.



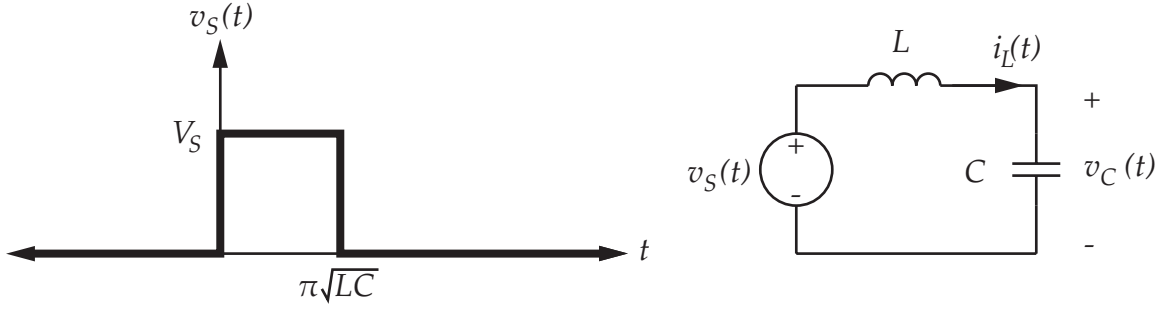**Problem 2:** For the circuit below,  $v_C(0) = 0$  and  $i_L(0) = 0$ . If  $v_S(t)$  is as shown in the figure below, find an algebraic expression and sketch  $v_C(t)$  for  $-\pi\sqrt{LC} < t < 3\pi\sqrt{LC}$ .



To derive the differential equation, use KVL:

$$v_S = v_L + v_C$$

Note that  $v_L = L \frac{di_L}{dt}$  and  $i_L = C \frac{dv_C}{dt}$ . Substituting these expressions yields

$$v_S = L \frac{di_L}{dt} + v_C = LC \frac{d^2v_C}{dt^2} + v_C$$

Divide by  $LC$  to leave the equation in standard form

$$\frac{d^2v_C}{dt^2} + \frac{v_C}{LC} = \frac{v_S}{LC}$$

For  $t < 0$ ,  $v_S = 0$  and  $v_C = 0$ . For  $0 < t < \pi\sqrt{LC}$ ,  $v_S = V_S$ . The differential equation in this period is

$$\frac{d^2v_C}{dt^2} + \frac{v_C}{LC} = \frac{V_S}{LC}$$

The particular solution is  $v_C = V_S$ , which corresponds to a steady state as  $t \rightarrow \infty$  where the inductor acts as a short, the capacitor as an open, and all the voltage  $V_S$  shows across the capacitor. From Problem Set 6, recall that the homogeneous solution for  $v_C$  is of the form

$$v_{C,Homogeneous}(t) = A \sin(\omega_0 t) + B \cos(\omega_0 t)$$

where  $\omega_0 = \frac{1}{\sqrt{LC}}$ . The general solution is

$$v_C(t) = V_S + A \sin(\omega_0 t) + B \cos(\omega_0 t)$$

The initial condition  $v_C(0) = 0$  yields

$$v_C(0) = V_S + B = 0 \Rightarrow B = -V_S$$

The initial condition  $i_L(0) = 0$  implies that  $\frac{dv_C}{dt} = 0$  since  $\frac{dv_C}{dt} = \frac{i_L}{C}$ . In order to apply this initial condition, the derivative of  $v_C$  is computed and evaluated at zero:

$$\left. \frac{dv_C}{dt} \right|_{t=0} = A\omega_0 = 0 \Rightarrow A = 0$$

Thus, the solution for  $0 < t < \pi\sqrt{LC}$  is

$$v_C(t) = V_S[1 - \cos(\omega_0 t)] \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad 0 < t < \pi\sqrt{LC}$$

For  $t > \pi\sqrt{LC}$ ,  $v_S = 0$ . The differential equation in this period is

$$\frac{d^2 v_C}{dt^2} + \frac{v_C}{LC} = 0$$

The initial conditions must be obtained by evaluating the expression obtained for  $v_C(t)$  at  $t = \pi\sqrt{LC}$ . Thus,

$$\begin{aligned} v_C(\pi\sqrt{LC}) &= 2V_S \\ \frac{dv_C}{dt} &= \frac{i_L(t)}{C} = V_S\omega_0 \sin(\omega_0 t) \\ \left. \frac{dv_C}{dt} \right|_{t=\pi\sqrt{LC}} &= \frac{i_L(\pi\sqrt{LC})}{C} = 0 \end{aligned}$$

The particular solution is  $v_C = 0$  for this period. Thus, the general solution reduces to the homogeneous solution:

$$v_C(t) = A \sin(\omega_0 t) + B \cos(\omega_0 t)$$

The initial condition  $v_C(\pi\sqrt{LC}) = 2V_S$  yields

$$v_C(\pi\sqrt{LC}) = -B = 2V_S \Rightarrow B = -2V_S$$

In order to apply the initial condition  $\left. \frac{dv_C}{dt} \right|_{t=\pi\sqrt{LC}} = 0$ , the derivative of  $v_C$  is computed and evaluated at zero:

$$\left. \frac{dv_C}{dt} \right|_{t=\pi\sqrt{LC}} = -A\omega_0 = 0 \Rightarrow A = 0$$

Thus, the solution for  $t > \pi\sqrt{LC}$  is

$$v_C(t) = -2V_S \cos(\omega_0 t) \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad t > \pi\sqrt{LC}$$

The complete solution is

$$v_C(t) = 0$$

$$t < 0$$

$$v_C(t) = V_S[1 - \cos(\omega_0 t)] \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$0 < t < \pi\sqrt{LC}$$

$$v_C(t) = -2V_S \cos(\omega_0 t) \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$t > \pi\sqrt{LC}$$

