

Inter American University of Puerto Rico
Bayamón Campus
School of Engineering
Department of Electrical Engineering

ELEN 3302 – Electric Circuits II

Problem Set 2 Solutions

Due Wednesday, September 1

Problem 1: Find the particular solution of $x(t)$ in

$$a \frac{d^2}{dt^2} x(t) + b \frac{d}{dt} x(t) + cx(t) = \cos \omega t$$

assuming as a solution:

(A) $x(t) = K \cos(\omega t + \phi)$, where K and ϕ are real.

Start by calculating the derivatives:

$$\begin{aligned} x(t) &= K \cos(\omega t + \phi) \\ \dot{x}(t) &= -K\omega \sin(\omega t + \phi) \\ \ddot{x}(t) &= -K\omega^2 \cos(\omega t + \phi) \end{aligned}$$

Using the angle addition formulas:

$$\begin{aligned} x(t) &= K \cos \phi \cos \omega t - K \sin \phi \sin \omega t \\ \dot{x}(t) &= -K\omega \cos \phi \sin \omega t - K\omega \sin \phi \cos \omega t \\ \ddot{x}(t) &= K\omega^2 \cos \phi \cos \omega t + K\omega^2 \sin \phi \sin \omega t \end{aligned}$$

We introduce these expressions into the differential equation and equate sines and cosines. This yields two algebraic equations:

$$\text{cosine equation: } cK \cos \phi - aK\omega^2 \cos \phi - bK\omega \sin \phi = 1$$

$$\text{sine equation: } -c \sin \phi + a\omega^2 \sin \phi - b\omega \cos \phi = 0$$

The sine equation yields:

$$\tan \phi = \frac{b\omega}{a\omega^2 - c}$$

Thus,

$$\sin \phi = \frac{b\omega}{\sqrt{(a\omega^2 - c)^2 + (b\omega)^2}}$$

$$\cos \phi = \frac{a\omega^2 - c}{\sqrt{(a\omega^2 - c)^2 + (b\omega)^2}}$$

Substituting these expressions into the cosine equation yields:

$$K = -\frac{1}{\sqrt{(a\omega^2 - c)^2 + (b\omega)^2}}$$

Thus, the particular solution is:

$$x(t) = -\frac{1}{\sqrt{(a\omega^2 - c)^2 + (b\omega)^2}} \cos(\omega t + \tan^{-1} \frac{b\omega}{a\omega^2 - c})$$

(B) $x(t) = Ke^{j\omega t} + K^*e^{-j\omega t}$, where K and K^* are complex and K^* denotes the complex conjugate of K .

Again, start by calculating the derivatives:

$$x(t) = Ke^{j\omega t} + K^*e^{-j\omega t}$$

$$\dot{x}(t) = j\omega Ke^{j\omega t} - j\omega K^*e^{-j\omega t}$$

$$\ddot{x}(t) = -\omega^2 Ke^{j\omega t} - \omega^2 K^*e^{-j\omega t}$$

We introduce these expressions into the differential equation, express $\cos \omega t$ as $1/2e^{j\omega t} + 1/2e^{-j\omega t}$, and equate $e^{j\omega t}$ and $e^{-j\omega t}$ terms. This yields two complex algebraic equations:

$$e^{j\omega t} \text{ equation: } cK + bj\omega K - a\omega^2 K = 1/2$$

$$e^{-j\omega t} \text{ equation: } cK^* - bj\omega K^* - a\omega^2 K^* = 1/2$$


Note that one equation is the complex conjugate of the other, as expected. Solving for K and K^* :

$$K = \frac{1/2}{c - a\omega^2 + bj\omega} \quad K^* = \frac{1/2}{c - a\omega^2 - bj\omega}$$

The particular solution is:

$$x(t) = \frac{1/2}{c - a\omega^2 + bj\omega} e^{j\omega t} + \frac{1/2}{c - a\omega^2 - bj\omega} e^{-j\omega t}$$

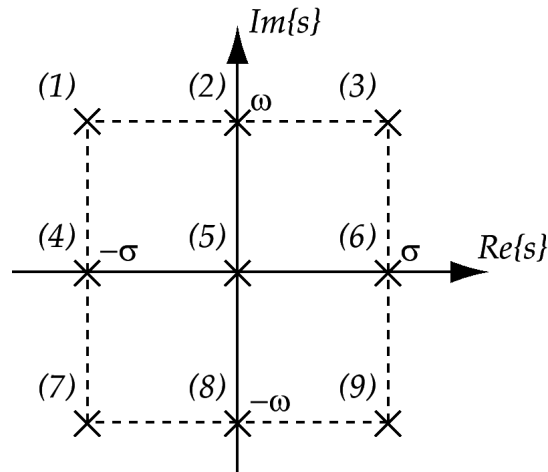Problem 2: Provide an algebraic expression and a qualitative sketch of the real part of the complex time function for each of the complex frequencies marked with an $\times$ in the s -plane shown below:




Note that each $s = \sigma + j\omega$ represents a complex time function of the form e^{st} . Since we are interested in the real part only, let's compute it and then substitute the different values of σ and ω :


$$\begin{aligned}
 \text{Re}\{e^{st}\} &= \text{Re}\{e^{(\sigma+j\omega)t}\} \\
 &= \text{Re}\{e^{\sigma t}e^{j\omega t}\} \\
 &= \text{Re}\{e^{\sigma t}(\cos \omega t + j \sin \omega t)\} \\
 &= \text{Re}\{e^{\sigma t} \cos \omega t + j e^{\sigma t} \sin \omega t\} \\
 &= e^{\sigma t} \cos \omega t
 \end{aligned}$$

Therefore,

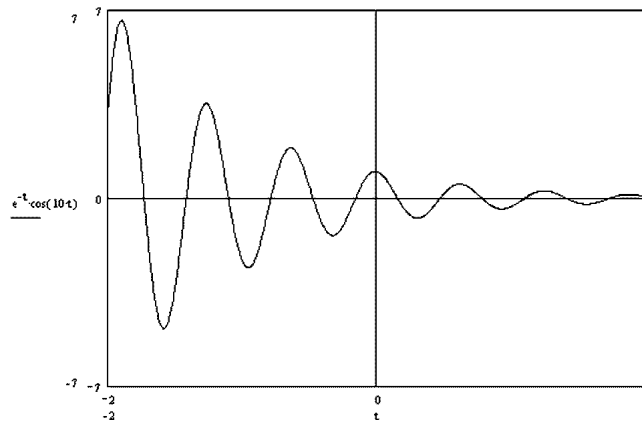
(1) $\text{Re}\{e^{st}\} = e^{-\sigma t} \cos \omega t$, exponentially decaying oscillation



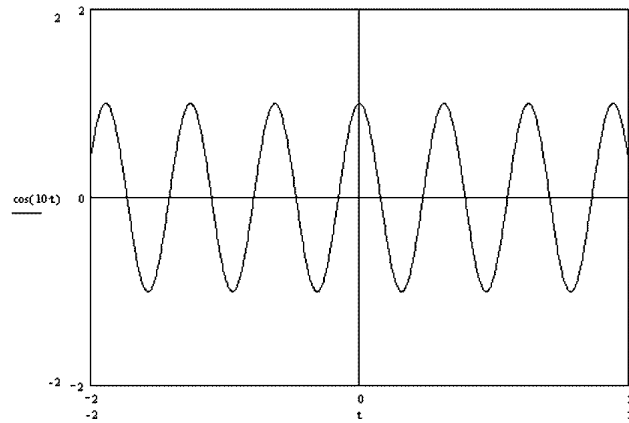
(2) $Re\{e^{st}\} = \cos \omega t$, constant oscillation



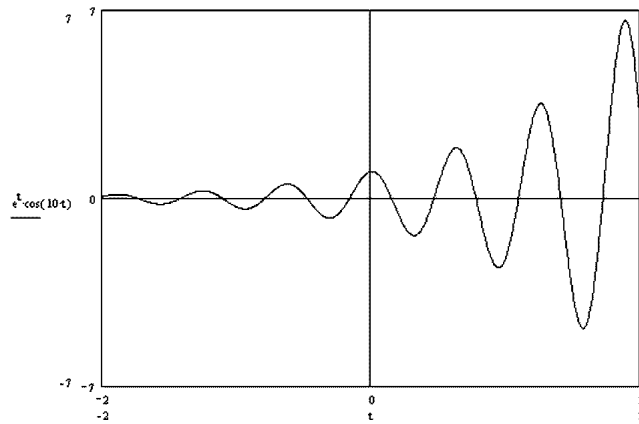
(3) $Re\{e^{st}\} = e^{\sigma t} \cos \omega t$, exponentially increasing oscillation



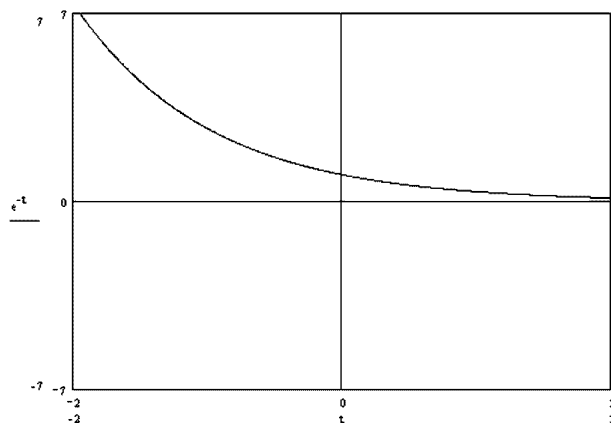
(4) $Re\{e^{st}\} = e^{-\sigma t}$, exponential decay



(5) $Re\{e^{st}\} = 1$, constant

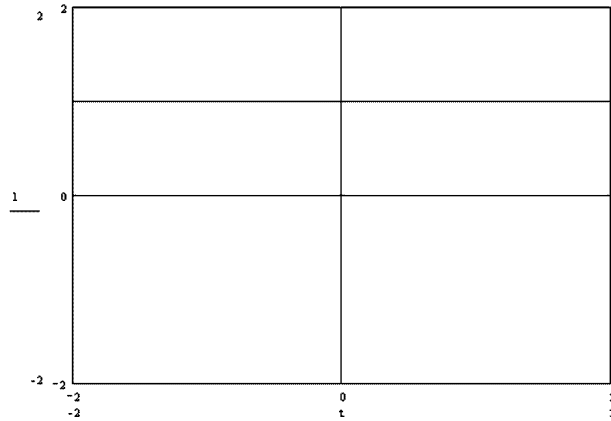


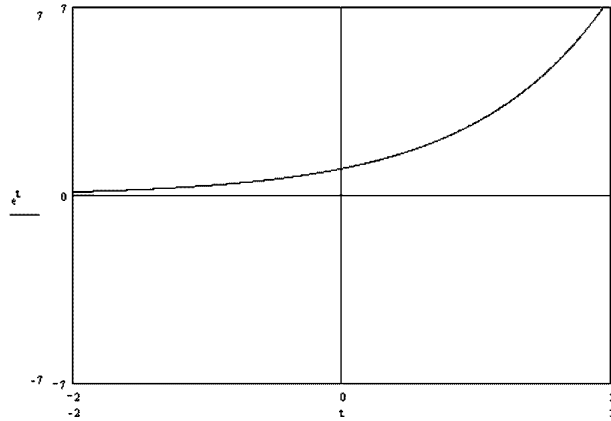(6) $Re\{e^{st}\} = e^{\sigma t}$, exponential increase



The frequency ω shows inside a cosine. Thus, the real part of a negative frequency will be exactly the same as the real part of the same positive frequency. Therefore, (7), (8) and (9) are identical to (1), (2) and (3), respectively.

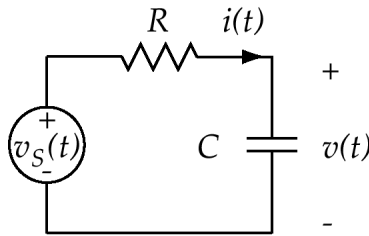Problem 3: Provide an algebraic expression for the sinusoidal steady-state of $i(t)$ and $v(t)$ if $v_S(t) = V_S \sin \omega t$.



Recall that the impedance of a resistor is R and a capacitor is $\frac{1}{Cj\omega}$. The relation between V and V_S is a voltage divider:

$$\begin{aligned} \frac{V}{V_S} &= \frac{\frac{1}{Cj\omega}}{R + \frac{1}{Cj\omega}} = \frac{1}{RCj\omega + 1} \\ \left| \frac{V}{V_S} \right| &= \frac{1}{\sqrt{1 + (RC\omega)^2}} \quad \angle \frac{V}{V_S} = -\tan^{-1} RC\omega \\ v(t) &= V_S \frac{1}{\sqrt{1 + (RC\omega)^2}} \sin(\omega t - \tan^{-1} RC\omega) \end{aligned}$$

The current I can be found dividing V_S by the total impedance of the circuit:

$$\begin{aligned} \frac{I}{V_S} &= \frac{1}{R + \frac{1}{Cj\omega}} = \frac{Cj\omega}{RCj\omega + 1} \\ \left| \frac{I}{V_S} \right| &= \frac{C\omega}{\sqrt{1 + (RC\omega)^2}} \quad \angle \frac{I}{V_S} = \frac{\pi}{2} - \tan^{-1} RC\omega \\ i(t) &= V_S \frac{C\omega}{\sqrt{1 + (RC\omega)^2}} \sin\left(\omega t + \frac{\pi}{2} - \tan^{-1} RC\omega\right) \end{aligned}$$