


Inter American University of Puerto Rico
 Bayamón Campus
 School of Engineering
 Department of Electrical Engineering

ELEN 3311 – Electronics I


Final Exam Review Problems

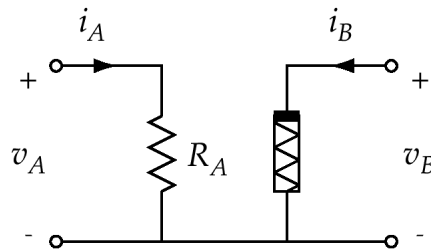Problem 1: The nonlinear resistor inside the three-terminal device shown below is characterized by the equations:


$$\begin{array}{lll} v_B = ri_A & i_B \geq \frac{r}{R_B}i_A & \text{Region I} \\ i_B = \frac{v_B}{R_B} & v_B \leq ri_A & \text{Region II} \end{array}$$



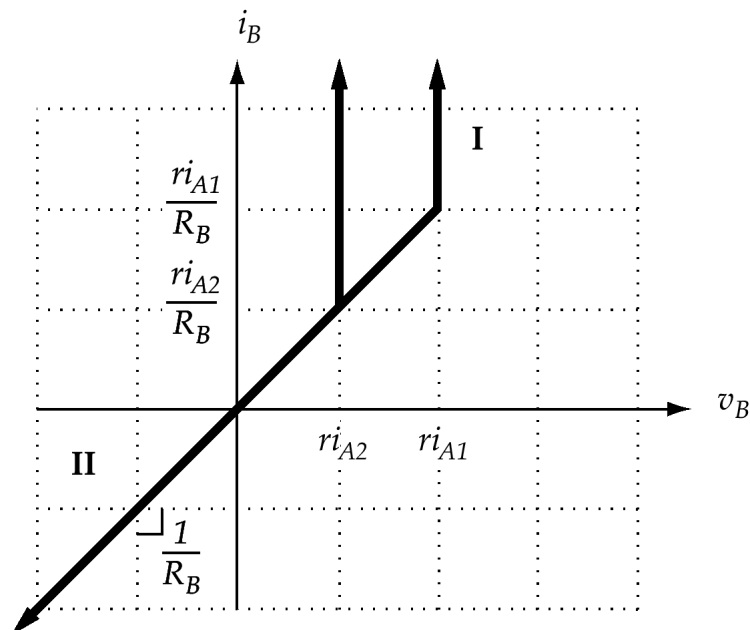These equations trace the following curves in the v_B - i_B plane for $i_{A1} > i_{A2} > 0$:



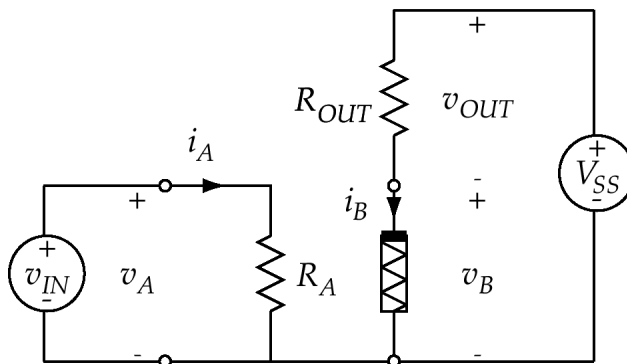
The three-terminal resistor is placed inside the circuit shown below:




- Find an algebraic equation for the v_B - i_B constraint imposed by the external circuit and graph this load line in the v_B - i_B plane. Mark the points corresponding to solutions of the circuit.
- Find an algebraic expression for the v_{IN} - v_{OUT} relation in each region. Find the small-signal gain $\frac{v_{out}}{v_{in}}$ for each region using these expressions.
- Find the range of v_{IN} for which the circuit is operating in each region independently and verify that the regions complement each other.
- Find the value of v_{OUT} at each transition between regions of operation independently and verify that the values of v_{OUT} are the same.
- Plot the v_{IN} - v_{OUT} relation showing clearly all transition values, any intercepts and/or any asymptotes.
- Draw the small-signal circuit diagram for each region and find the small-signal gain. Verify that each gain is the same as the one found before. Remember that all elements in the small-signal circuit must be linear.

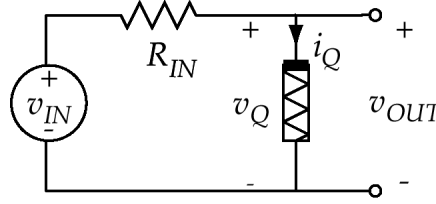Problem 2: The nonlinear resistor inside the circuit shown below is characterized by the equations:

$$\begin{aligned}
 i_Q &= \alpha(v_Q - V_1)^2 + I_1 & v_Q &\geq V_1 & \text{Region I} \\
 i_Q &= I_1 \sin\left(\frac{\pi v_Q}{2 V_1}\right) & -V_1 &\leq v_Q \leq V_1 & \text{Region II} \\
 i_Q &= -I_1 & v_Q &\leq -V_1 & \text{Region III}
 \end{aligned}$$



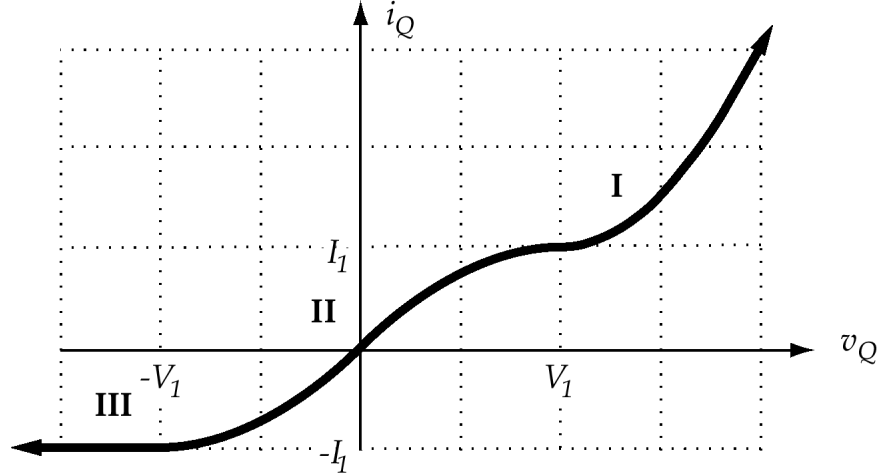These equations trace the following curve in the v_Q - i_Q plane:



- Find an algebraic equation for the v_Q - i_Q constraint imposed by the external circuit and graph these load lines in the v_Q - i_Q plane for $v_{IN} > 0$ and $v_{IN} < 0$. Mark the points corresponding to solutions of the circuit.
- Find an algebraic expression for the v_{IN} - v_{OUT} relation in each region. Do not solve the equations for v_{OUT} (for some regions, you can't!). Find the small-signal gain $\frac{v_{out}}{v_{in}}$ for each region using these expressions. Remember that $\frac{v_{out}}{v_{in}} = \left[\frac{v_{in}}{v_{out}}\right]^{-1}$, but $\frac{dv_{OUT}}{dv_{IN}} \neq \left[\frac{dv_{IN}}{dv_{OUT}}\right]^{-1}$!
- Draw the small-signal circuit diagram for each region and find the small-signal gain. Verify that each gain is the same as the one found before. Remember that all elements in the small-signal circuit must be linear.