

ELECTROMAGNETICS THEORY
BEKP3553
1-2006/2007

Tutorial 7


Transmission Line

- 1) Calculate the line parameter R' , L' , G' and C' for a coaxial line with the inner conductor diameter of 0.5cm and an outer conductor diameter of 1cm, filled with insulating material where $\mu = \mu_0$, $\epsilon_r = 2.25$ and $\sigma = 10^{-3} S/m$. The conductors are made of copper with $\mu_c = \mu_0$ and $\sigma_c = 5.8 \times 10^7 S/m$. The operating frequency is 1GHz.

- 2) Find α and Z_0 of a distortionless line when whose $R' = 4 \text{ ohm/m}$ and $G' = 4 \times 10^{-4} S/m$.

- 3) A $50\text{-}\Omega$ lossless transmission line is terminated in a load with impedance $Z_L = (30 - j60)\Omega$. The wavelength is 5cm. Find:
 - (i) The reflection coefficient at the load.
 - (ii) The standing-wave ratio on the line.
 - (iii) The position of the voltage maximum nearest the load.
 - (iv) The position of the current maximum nearest the load.

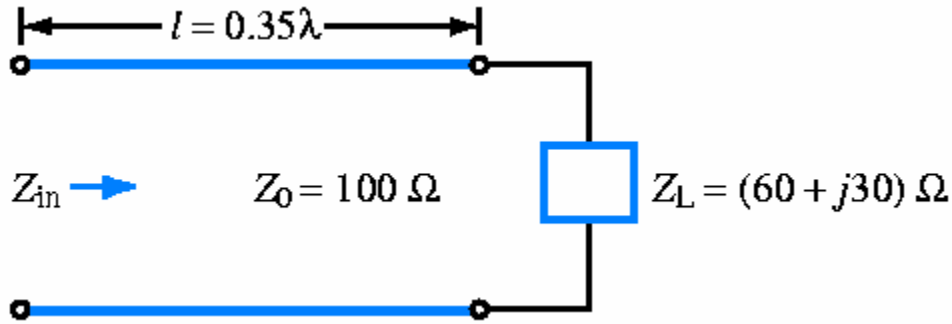- 4) A lossless transmission line of electric length $l = 0.35\lambda$ is terminated in a load impedance as shown in Figure 5. Find:
 - (i) Γ
 - (ii) S
 - (iii) Z_{in}



- 5) A 6-m section of 150Ω lossless lines is driven by a source with

$$v_g(t) = 5 \cos(8\pi \times 10^7 t - 30^\circ) \text{ (V)}$$

and $Z_g = 150 \Omega$. If the line, which has a relative permittivity $\epsilon_r = 2.25$, is terminated in a load $Z_L = (150 - j50) \Omega$, find the following:

- Wavelength (λ) on the line.
 - The reflection coefficient at the load.
 - The input impedance.
 - The input voltage \tilde{V}_i .
 - The time-domain input voltage $v_i(t)$.
- 6) A 50Ω lossless lines of length $l = 0.375 \lambda$ connects a 200 MHz generator with $\tilde{V}_g = 150V$ and $Z_g = 50 \Omega$ to a load Z_L . Determine the time-domain current through the load for:
- $Z_L = (50 - j50) \Omega$
 - $Z_L = 50 \Omega$
 - $Z_L = 0$ (short circuit)