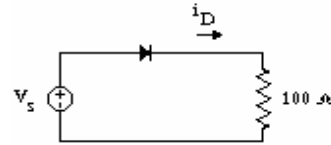



- 1) The source voltage $v_s = 1.1 + 0.1 \sin 1000t$ is placed across a series combination of a diode and a 100Ω load resistance, as shown in figure find the current i_D if

$$\eta V_T = 40 \text{ mV}$$


$$V_\gamma = 0.7 \text{ V}$$



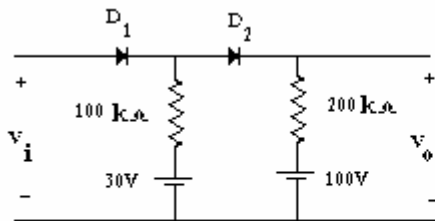- 2) Sketch transfer function of each clipper circuit shown in figure. Assume ideal diodes.




(a)

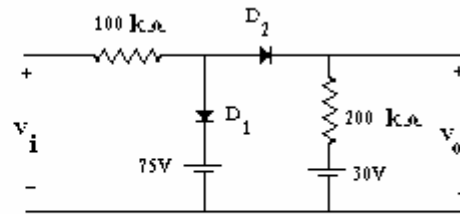

(b)

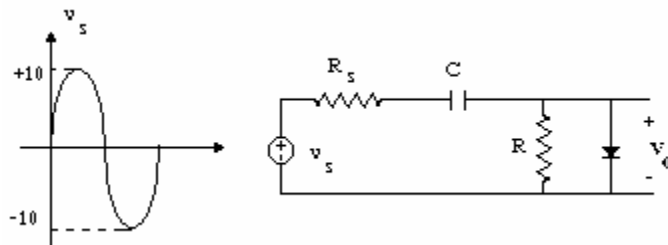- 3) An ideal diode 10KHz sinusoidal voltage source whose peak excursions are $\pm 10V$ with respect to ground is applied to the diode clamping circuit of the figure below, Assume $R = \infty, R_s = 0, C = 1\mu F$, the diode has $R_r = \infty, R_f = 0, V_\gamma = 0$. Sketch output waveform.




- 4) The signal shown in the figure problem (3) with a frequency of 1KHz is applied to the circuit, with values $R = 10k\Omega, R_s = 0, C = 1\mu F, R_r = \infty, R_f = 0, V_\gamma = 0$.


a) Sketch the output waveform, v_o .

b) Repeat part (a) if $R = 1K\Omega$ and $C = 0.1\mu F$.

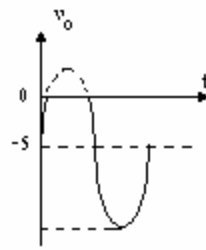
- 5) What type of clipper is needed to obtain the waveforms shown in below? Assume the input is $10\sin t$ volts. Draw the circuits.




(a)

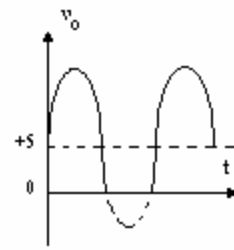

(b)

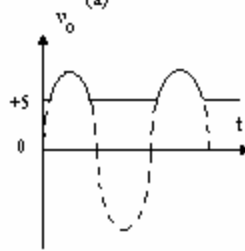

(c)

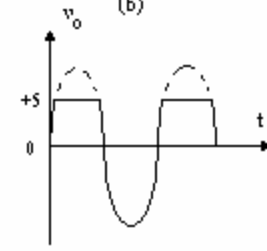

(d)