

Chapter 6 Test Generation for Sequential Circuits

Sequential Circuit Testing

- ☞ Exhaustive testing requires $> 2^n$ tests (sensitive to the order of tests).
- ☞ Testing requires a *sequence* of test vectors.
- ☞ Still has all the complexity of C/L ATPG.
- ☞ Requires initialization of the machine, which may be difficult:
 - ⇒ Long initialization sequence.
 - ⇒ Simulator limitations.
 - ⇒ Invalid state justification.
- ☞ Faults may cause the number of internal states to grow.
- ☞ Have to cope with the harder-to-detect delay faults (timing errors).

General Case:

- ☞ Make no assumption about internal state.
- ☞ Apply test sequence T_α for a fault α and observe the response sequence R_α . If R_α is disjoint from the set of normal response sequences starting from any possible state, then T_α *strongly detects* α .
- ☞ NOT doable in practice!

Restricted Case (Static Testing):


- ① With the circuit output stable, apply the next input vector.
- ② Wait for new output to stabilize, and then observe.
- ③ Do ① & ② for all $t \in T_\alpha$.



ATPG Approaches:

- ① *Time-frame expansion* (unrolling the feedback path): convert time domain into space domain, and use combinational ATPG—Extended D-algorithm, Sequential 9V, EBT, BACK, etc.
- ② *Simulation-based approach*: search for test vectors guided by cost functions and simulations—CONTEST.
- ③ *Checking experiment*: formal approach to derive test sequence for FSMs (useful only for small circuits).
- ④ *Scan*: modify the circuit to facilitate combinational ATPG.
- ⑤ *Functional test*: testing that a (part of a) system operates correctly in a functional sense (i.e., each module is realization & fault independent—fault model is at functional level).

 
Time-Frame Expansion (Iterative Array Conversion)



Sequence of inputs in time: $x(0), x(1), \dots, x(n)$.


Sequence of outputs in time: $z(0), z(1), \dots, z(n)$.

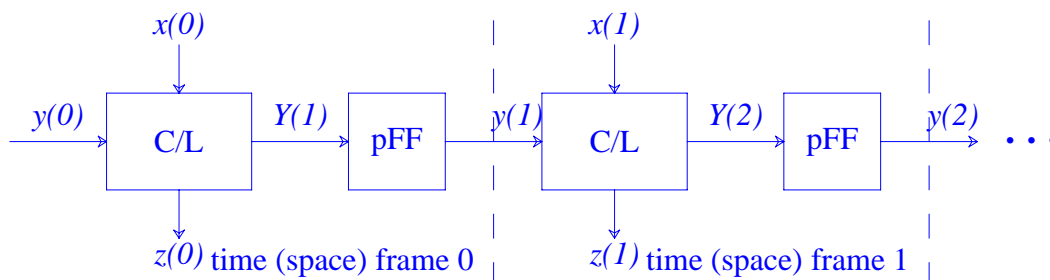Sequence of internal states in time: $y(0), y(1), \dots, y(n)$.



- ☞ For synchronous sequential circuits (FSMs).
- ☞ Transforming FSMs to iterative logic arrays by unrolling the Huffman model.
- ☞ Applying D-alg (or PODEM, path sensitizer, etc.) to the ILA.
- ☞ Pseudo flip-flop (pFF) is a combinational circuit mapping its excitation function onto its output, e.g., a pseudo T-FF can be constructed by an XOR gate as shown below.



T	Y	y
0	0	0
0	1	1
1	0	1
1	1	0

 

- ☞ When a single stuck fault is present in the real sequential circuit, it will appear as a multiple fault, existing in each unfolded iteration (time frame).

 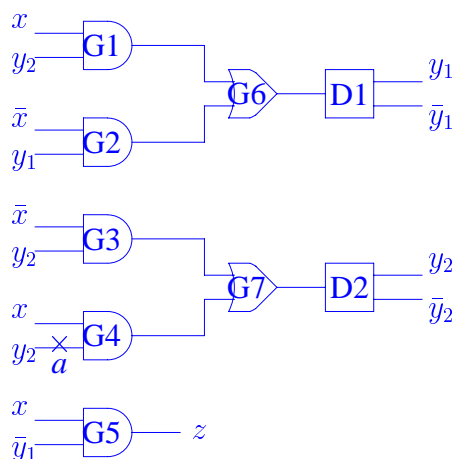Example 1

We use the unrolling method to derive a test sequence for the fault $\alpha \equiv a/1$ of the following circuit. Assume that the initial state of the sequential circuit is $(y_1, y_2) = (0, 0)$.



t_0 : Initial state $y_1 = y_2 = 0$.

$\therefore y_2 = 0$ and $a/1 \therefore a = \bar{D}$.

Set $x(0) = 1 \Rightarrow y_2(1) = \bar{D}$ and $z(0) = 1$.

$\therefore z \neq D$ or \bar{D} . \therefore Continue!

t_1 : Cannot propagate D or \bar{D} to z yet

\therefore Set $x(1) = 1 \Rightarrow y_1(2) = y_2(2) = \bar{D}$ and $z(1) = 1$.

t_2 : On $G5$, let $x(2) = 1$

$\therefore y_1(2) = \bar{D}$. $\therefore z(2) = D$.

\therefore Test sequence $X = 111$. □

Termination rules

★ If $z = D$ or \bar{D} then a test sequence is found.

★ If $k > 4^n$, where n is the number of FFs of the original circuit (\neq number of time frames = k), then the circuit is redundant and no test sequence exists.

☞ \therefore 4 possibilities (0, 1, D , & \bar{D}) for each y_i (FF).

Extended D-algorithm [Kubo, NEC R&D, 10/1968] [Putzolu & Roth, IEEE TC, 6/1971]

1. Select a target fault α .
2. Create a copy of C/L; time-frame = 0.
3. Generate a test for α by D-algorithm for time-frame 0.
4. If fault effect is propagated to FFs, continue propagation in the next time-frame.
5. If there are values required in FFs, continue justification in the previous time-frame.

☞ It is incomplete, because a fault effect may be propagated to a faulty line in a subsequent time-frame, and 5 values are insufficient for such a situation.



- ☞ It is complete if 9 values (instead of 5 values) is used [Muth, IEEE TC, 6/1976]: 0/0, 0/1, 0/*u*, 1/0, 1/1, 1/*u*, *u*/0, *u*/1, *u*/*u* (implementation is very complex, however).
- ☞ Going both forward and backward in time requires maintaining a large number of time-frames during test generation, and it is hard to identify *cycles*. ∴ Impractical.

Extended BackTrace (EBT) Algorithm [Marlett, DAC-78 & 86]

1. Select a path from the fault site to a PO. /* May involve several time-frames. */
 2. Sensitize the path backwards from the PO to the fault site. /* Justification is done in the same direction. */
 3. If it fails, select another path;
if there is no path left, select another PO;
go to 2.
 4. Justify the required value at the fault site.
- ☞ Only 2 time-frames need to be maintained: present time-frame and previous time-frame.
 - ☞ Easier to identify *cycles*.
 - ☞ Only a single path is selected each time.
 - ☞ Number of possible paths from fault site to POs can be large.

Exercise 1

Show that EBT is complete, or prove that it is not by giving a counter example.

Definition 1

Drivability is a measure associated with a signal that estimates the effort of propagating a D or \bar{D} from the fault site to the signal.



Back Algorithm [Cheng, ICCD-88]

1. Calculate controllability measures for the fault-free circuit.
2. Pick a target fault;
Calculate controllability measures for the faulty circuit.
3. Derive drivability measures.
4. Assign a D/\bar{D} to a PO;
time-frame = 0;
if all POs with finite drivability have been considered, go to 2 (fault undetectable).
5. Justify all values—use drivability to guide the backward search (implication), i.e., select the gate input with the smallest drivability.
 - ☞ May involve several time-frames backwards.
 - ☞ May need backtracking on the decisions.
 - ☞ May need backtracking on the time-frames.
 - ☞ May need to back up to step 4.
 - ☞ Sensitized paths are created implicitly.

Other Time-Frame Expansion Algorithms

- ★ ESSENTIAL [Schulz & Auth, ITC-89].
- ★ FASTEST [Kelsey & Saluja, ICCAD-89].
- ★ HITEC [Niermann & Patel, EDAC-91].
- ★ Lee-Reddy [Lee & Reddy, ICCAD-91].



Simulation-Based Test Generation

CONTEST [Agrawal, Cheng, & Agrawal, IEEE TCAD, 2/1989]

- ☞ A concurrent test generator for sequential circuits—using a concurrent fault simulator which automatically analyzes races and oscillations.

Initialization:

- ```
{1. Start with an arbitrary vector and all FFs in
 unknown state;
 2. Generate new vectors to reduce cost by 1-bit changes
 in the present vector; /* only true-value sim */
 /* cost = number of FFs in unknown state */
 3. Stop when cost drops below desired value; }
```

Tests for concurrent targets:

- ```
{1. Start with initialization vectors;
  2. Fault simulate vectors and remove detected faults;
  3. Compute cost function for the last vector;
   /* cost(undetected f.)=min dist of its effect from a PO */
   /* cost(vector)=sum of costs of all undetected faults */
  4. New vectors = those 1-bit changes that reduce cost; }
```

Tests for remaining undetected single faults:

- ```
{1. Revise the cost function (a dynamic testability measure);
 /* cost = K x activation cost + propagation cost */
 /* activation cost = dynamic CY of faulty line */
 /* propagation cost = min dynamic OY of faulty line */
 /* K is a large weighting factor */
 2. Generate a test for a single fault; }
```

- ☞ Timing is considered, and asynchronous circuits can be handled.
- ☞ Can easily be implemented by modifying an existing fault simulator.
- ☞ Cannot identify untestable faults.



☞ Coverage for hard-to-detect faults can be low.

### Checking Experiments [Hennie, 1964]

Given the state table of an FSM, find an I/O sequence pair  $(X, Z) \ni$  the response of the machine to  $X$  will be  $Z$  iff the machine is operating correctly.

#### Definition 2

An *adaptive experiment* is an experiment in which the choice of the present input is based on the earlier outputs, while a *preset experiment* is one in which the entire input sequence  $X$  is specified in advance.

☞ A measure of efficiency: length of (i.e., # of symbols in)  $X$ .

#### Assumptions on the FSM:

- Fully specified and deterministic.
- Reduced, i.e.,  $q_i \neq q_j, \forall i \neq j$ .
- Strongly connected, i.e.,  $\forall i, j, \exists X \ni q_i \rightarrow q_j$ .
- No fault will increase the number of states.
- Has a distinguishing sequence.

#### Definition 3

A *homing sequence* (HS) for an FSM is an input sequence  $\ni$  the corresponding output sequence uniquely determines its final state (regardless of the initial state).

#### Definition 4

A *distinguishing sequence* (DS) for an FSM is an input sequence  $\ni$  given different initial states it produces different output sequences.

☞ Every DS is an HS.

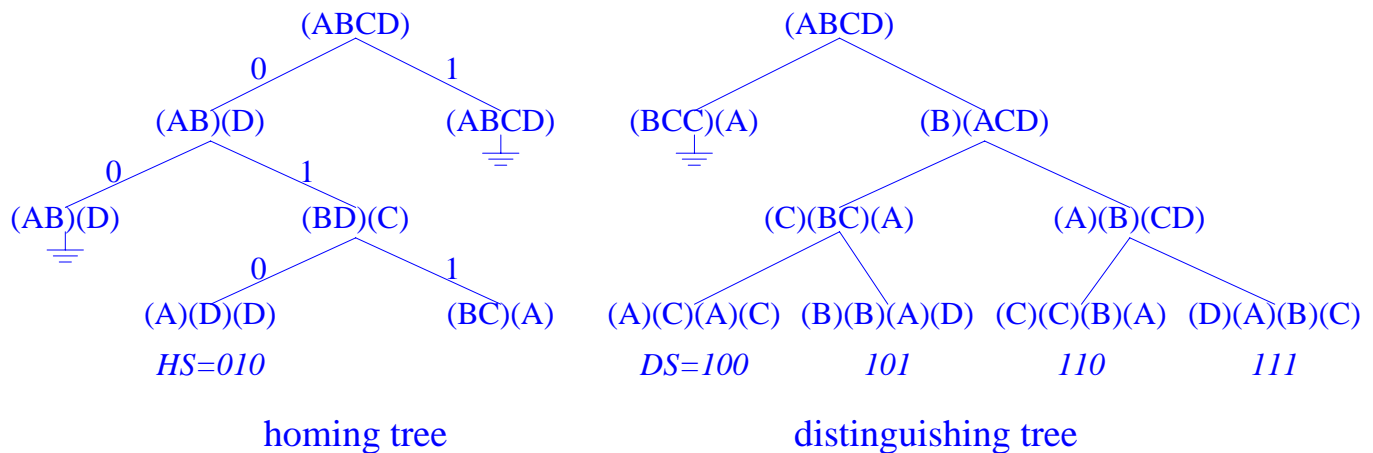
☞ The DS is a necessary tool for performing a checking experiment; it provides a way of identifying the state of a machine.



**Example 2**

For the following two state transition tables representing two different FSMs, a homing sequence for the FSM shown on the left and a distinguishing sequence for the one shown on the right are derived below by using a *homing tree* and a *distinguishing tree*, respectively.  $\square$

| PS | $x = 0$ | $x = 1$ | PS | $x = 0$ | $x = 1$ |
|----|---------|---------|----|---------|---------|
| A  | B,0     | D,0     | A  | C,0     | D,1     |
| B  | A,0     | B,0     | B  | C,0     | A,1     |
| C  | D,1     | A,0     | C  | A,1     | B,0     |
| D  | D,1     | C,0     | D  | B,0     | C,1     |

**Definition 5**

A *synchronizing sequence* (SS) for an FSM is an input sequence which takes the machine to a specified final state regardless of the output sequence or the initial state.

☞ Not every FSM has an SS (or DS).

☞ An HS with a length  $\leq n(n-1)/2$  exists for every reduced FSM of  $n$  states.

**Exercise 2**


Prove the above two statements.



**Example 3**

A synchronizing sequence for the following FSM can be derived by using a *synchronizing tree* as shown below.  $\square$

| PS | $x = 0$ | $x = 1$ |
|----|---------|---------|
| A  | B,1     | C,0     |
| B  | A,0     | D,1     |
| C  | B,0     | A,0     |
| D  | C,1     | A,1     |

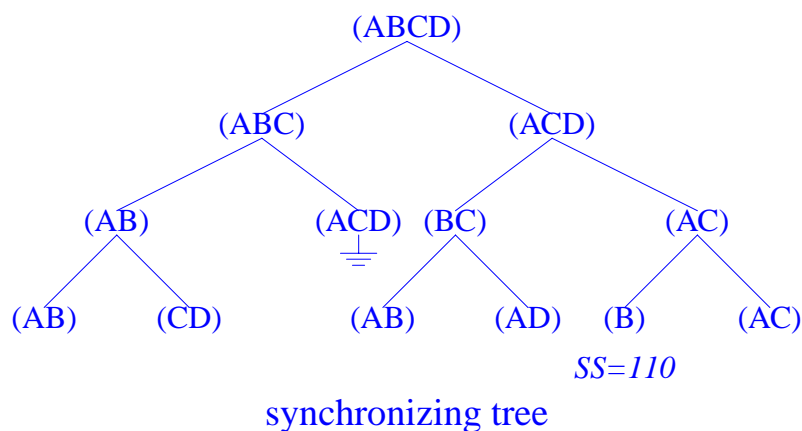

*Sketch of a Checking Experiment:*

- ① (Initialization) Initialize the state, using an SS or HS.
- ② (State identification (A-seq)) Visit each state to assure its existence. DS must be applied twice to each state of the machine.
- ③ (Transition verification (B-seq)) Verify every state transition using the DS.

$\rightarrow$  The result for  $X$  takes the form:  $X_1X_2X_3$ , where  $X_1$  is an SS or HS,  $X_2$  the A-seq, and  $X_3$  the B-seq, where A-seq & B-seq may be mixed up whenever appropriate to shorten  $|X|$ .

|         |       |                   |       |                   |       |
|---------|-------|-------------------|-------|-------------------|-------|
| input:  |       | DS                |       | DS                |       |
| state:  | $q_i$ | $\longrightarrow$ | $q_j$ | $\longrightarrow$ | $q_k$ |
| output: |       | $z_i$             |       | $z_j$             |       |




- ☞ Observation of  $z_i$  identifies  $q_i$  and establishes  $q_j$ .
- ☞ The A-seq starts with a repetition of DS until a previously visited state occurs as  $q_i$ . The DS is applied once more to identify  $q_i$ . Further repetition of DS would continue looping through already visited states. Use a *transfer sequence*, i.e., a shortest input sequence  $\ni q_i \rightarrow q_j$ , to place the machine in a new state, and continue until all states have been verified.
- ☞ Not every FSM has a DS. If not, we must modify it to have one [Kohavi].

#### Example 4

We will find a DS for the following FSM, and use it to design a test sequence (checking experiment) for the machine. Assume that the machine is initialized to state  $A$  before the experiment.

| PS | $x = 0$ | $x = 1$ |
|----|---------|---------|
| A  | C,0     | D,1     |
| B  | B,0     | A,1     |
| C  | A,1     | B,0     |
| D  | B,0     | C,0     |

 

The result is shown in the next page. Note that in the A-seq, we have  $A \xrightarrow{1} D \xrightarrow{1} C$ . Therefore, if  $A \xrightarrow{1} D$  is verified in the B-seq, then  $D \xrightarrow{1} C$  is already verified in the A-seq.  $\Rightarrow$  The experiment length can be reduced.  $\square$



|      |                 |     |                |     |    |     |    |     |   |    |           |
|------|-----------------|-----|----------------|-----|----|-----|----|-----|---|----|-----------|
| i/p: | $\frac{DS}{11}$ | 11  | $\frac{TS}{1}$ | 11  | 11 | 11  | 11 |     |   |    |           |
| q:   | A               | C   | A              | D   | B  | D   | B  |     |   |    |           |
| o/p: | 10              | 01  | 1              | 00  | 11 | 00  |    |     |   |    | end A-seq |
| i/p: | 0               | 11  | 0              | 11  | 1  | 11  | 0  | 11  | 0 | 11 |           |
| q:   | B               | → B | D              | → B | D  | → C | A  | → C | A |    |           |
| o/p: | 0               | 11  | 0              | 11  | 0  | 01  | 0  | 01  |   |    |           |
| i/p: | 1               | 11  | 1              | 11  | 0  | 11  | 1  | 11  |   |    |           |
| q:   | A               | → D | B              | → A | C  | → A | C  | → B | D |    |           |
| o/p: | 1               | 00  | 1              | 10  | 1  | 10  | 0  | 00  |   |    | end B-seq |

- ☞ Checking experiment can be considered as a form of functional test; it is realization independent and fault independent.
- ☞ Limit: it requires the generation of the state table, which is impractical for large circuits or for circuits obtained by high-level synthesis.

### Definition 6

A *unique input-output sequence* (UIOs) for an FSM is an input-output (IO) sequence  $\exists$  given different initial states it has different IO sequences [Sabnani & Dahbura, 1988].

### Exercise 3

How do we use UIOs instead of DS for checking experiments? Discuss the advantages and/or disadvantages.

## Functional Testing

Select tests which will validate the functional operation of the CUT.

- ☞ For example, the functional test for a FF may consists of
  1. Validating that the FF can be set and reset.
  2. Validating that the FF can hold its state.
- ☞ The testing of RAMs (and PLAs) are usually functional. Checking experiments are impossible for them.
- ☞ There is a growing need for functional-level ATPG due to increasing circuit complexity and synthesis.

