


ECE 201: Linear Circuit Analysis I:

Chapter 4: Mesh Analysis

MATLAB EXAMPLES

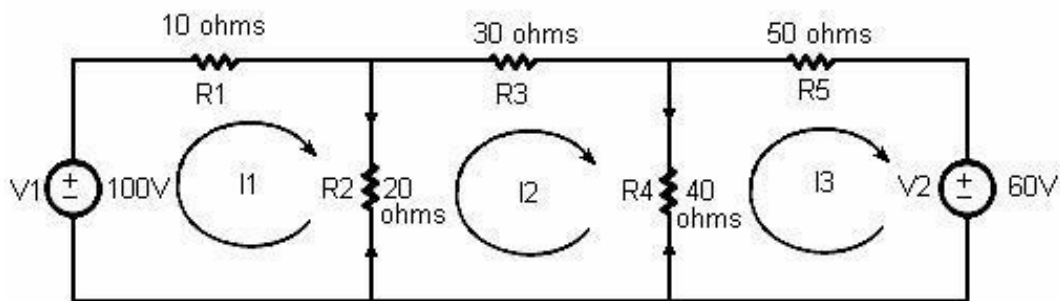Example 1

Below is a particular circuit that you decide to solve using Mesh Analysis. We can write the equations for the circuit, but so far, we don't know how to solve them. One way is using Cramer's rule, another way is using your TI Calculator. However, we are going to use MATLAB to solve this circuit.



Mesh Analysis

KVL & Ohms' Law @ Loop 1

$$-V_1 + i_1 R_1 + R_2(i_1 - i_2) = 0$$

$$-100 + 10i_1 + 20(i_1 - i_2) = 0$$

KVL & Ohms' Law @ Loop 2

$$R_2(i_2 - i_1) + i_2 R_3 + R_4(i_2 - i_3) = 0$$

$$20(i_2 - i_1) + 30i_2 + 40(i_2 - i_3) = 0$$

KVL & Ohms' Law @ Loop 3

$$R_4(i_3 - i_2) + i_3 R_5 + V_2 = 0$$

$$40(i_3 - i_2) + 50i_3 + 60 = 0$$



$$\begin{bmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ 0 & -R_4 & R_4 + R_5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ -V_2 \end{bmatrix}$$

$$\begin{bmatrix} (10 + 20) & -20 & 0 \\ -20 & 20 + 30 + 40 & -40 \\ 0 & -40 & 40 + 50 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ -60 \end{bmatrix}$$

$$\begin{bmatrix} 30 & -20 & 0 \\ -20 & 90 & -40 \\ 0 & -40 & 90 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ -60 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 3.79 \\ 0.679 \\ -0.3647 \end{bmatrix}$$

```

% ECE 201 Linear Circuit Analysis I
% Lecture Notes MATLAB Program
% Circuit Example 1

% Initializing given variables
v1 = 100.0;           % Volts
v2 = 60.0;           % Volts
r1 = 10.0;           % Ohms
r2 = 20.0;           % Ohms
r3 = 30.0;           % Ohms
r4 = 40.0;           % Ohms
r5 = 50.0;           % Ohms

% Assign appropriate values to row 1 of Matrix A
%      * using equation AX = B
A(1,1) = r1 + r2;     % 1st column of A
A(1,2) = ( - r2 );   % 2nd column of A
A(1,3) = 0.0;        % 3rd column of A

% Assign appropriate values to row 2 of Matrix A
A(2,1) = ( - r2 );   % 1st column of A
A(2,2) = r2 + r3 + r4; % 2nd column of A
A(2,3) = ( - r4 );   % 3rd column of A

% Assign appropriate values to row 3 of Matrix A
A(3,1) = 0.0;        % 1st column of A
A(3,2) = ( - r4 );   % 2nd column of A
A(3,3) = r4 + r5;    % 3rd column of A

% Assign appropriate values to column 1 of Matrix B
B(1,1) = v1;         % 1st row of B
B(2,1) = 0;          % 2nd row of B
B(3,1) = ( - v2 );   % 3rd row of B

% Calculate matrix X by solving AX = B for X
X = inv(A) * B;

% Assign appropriate values of Matrix X to their
% respective currents
i1 = X(1,1);
i2 = X(2,1);
i3 = X(3,1);


% Display results
fprintf('\n');
fprintf('i1 = %f A\n', i1);
fprintf('i2 = %f A\n', i2);
fprintf('i3 = %f A\n', i3);

% Output
%
%   i1 = 3.786164 A
%   i2 = 0.679245 A
%   i3 = -0.364780 A

```

Figure 1: Program for Above Circuit

Example 2:

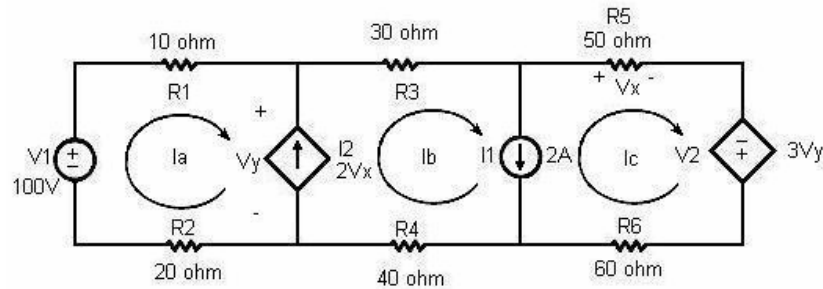

```

% ECE 201 Linear Circuit Analysis I
% Lecture Notes MATLAB Program
% Circuit Example 2

% Initializing given variables
v1 = 100.0;           % Volts
i1 = 2.0;            % Amps
r1 = 10.0;           % Ohms
r2 = 20.0;           % Ohms
r3 = 30.0;           % Ohms
r4 = 40.0;           % Ohms
r5 = 50.0;           % Ohms
r6 = 60.0;           % Ohms
v2 = 0.0;            % Volts
i2 = 0.0;            % Amps
mult_v2 = 3.0;       % Constant Multiplier
mult_i2 = 2.0;       % Constant Multiplier

% Assign appropriate values to row 1 of Matrix A
% * using equation AX = B
A(1,1) = -1.0;       % 1st column of A
A(1,2) = 1.0;       % 2nd column of A
A(1,3) = - ( r5 * mult_i2 ); % 3rd column of A

% Assign appropriate values to row 2 of Matrix A
A(2,1) = 0.0;       % 1st column of A
A(2,2) = 1.0;       % 2nd column of A
A(2,3) = - 1.0;    % 3rd column of A

% Assign appropriate values to row 3 of Matrix A
A(3,1) = r1 + ( mult_v2 * r1 ); % 1st column of A
A(3,1) = A(3,1) + ( mult_v2 * r2 ) + r2; % 1st column of A cont..
A(3,2) = r3 + r4;    % 2nd column of A
A(3,3) = r5 + r6;    % 3rd column of A

% Assign appropriate values to column 1 of Matrix B
B(1,1) = 0.0;       % 1st row of B
B(2,1) = i1;        % 2nd row of B
B(3,1) = ( mult_v2 * v1 ) + v1; % 3rd row of B

% Calculate matrix X by solving AX = B for X
X = inv(A) * B;

% Assign appropriate values of Matrix X to their respective currents
i_a = X(1,1);
i_b = X(2,1);
i_c = X(3,1);

```

```
% Calculate necessary voltages
v_y = v1 - ( ( r1 + r2 ) * i_a ); % Calculate v_y using KVL
v_x = r5 * i_c; % Calculate v_x using Ohm's Law
```

```
% Display results
fprintf('\n');
fprintf('i_a = %f A\n', i_a);
fprintf('i_b = %f A\n', i_b);
fprintf('i_c = %f A\n', i_c);
fprintf('v_x = %f V\n', v_x);
fprintf('v_y = %f V\n', v_y);
```

```
% Output
```

```
%
% i_a = 2.169231 A
% i_b = 1.998291 A
% i_c = -0.001709 A
% v_x = -0.085470 V
% v_y = 34.923077 V
```

 


Figure 2: Program for Circuit in Example 2