

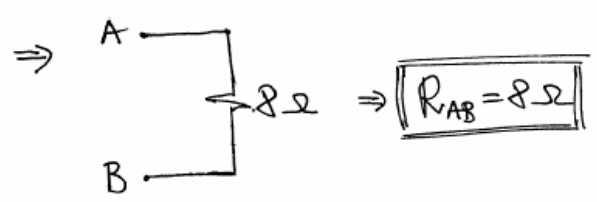
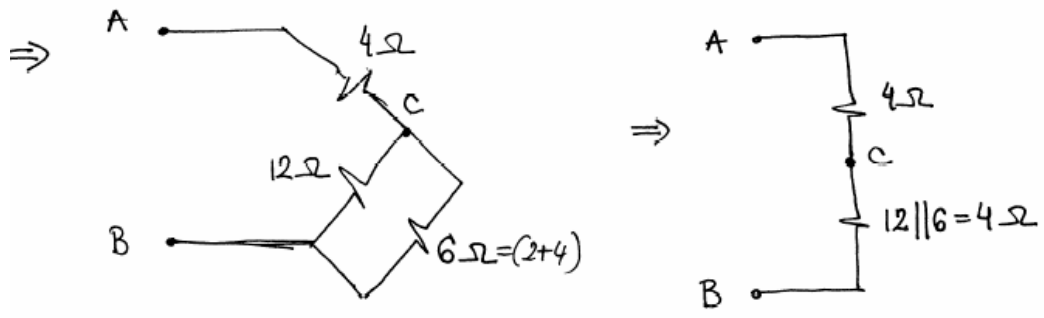
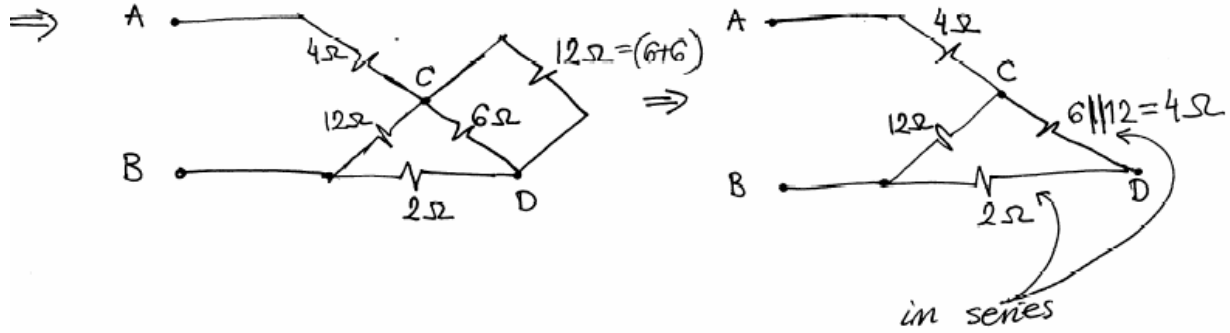


PRACTICE FINAL EXAM: PART I SOLUTIONS

Find the equivalent resistance R_{AB} .

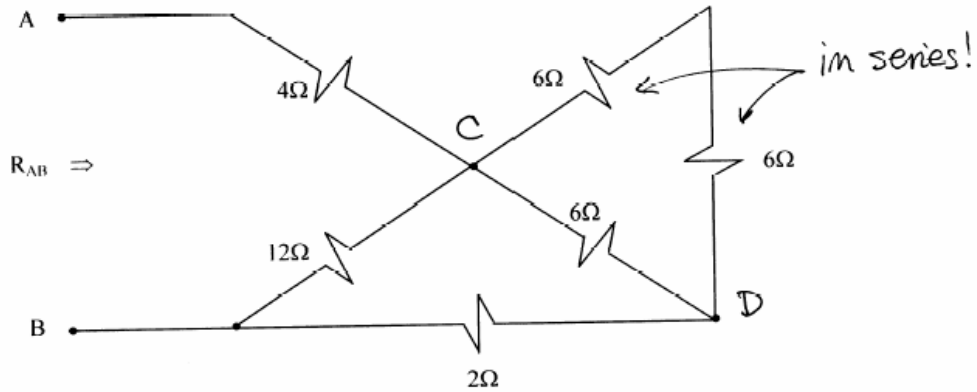

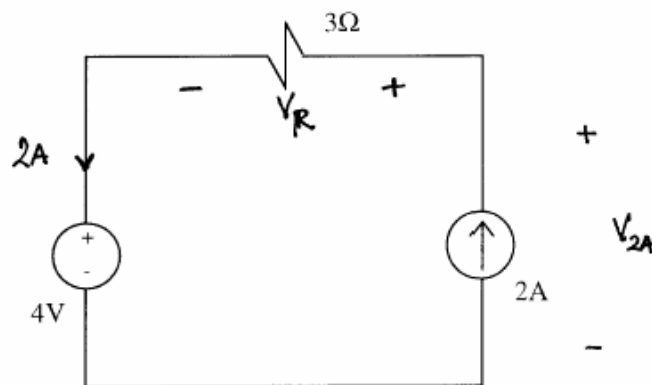Find the power absorbed or supplied by each element.




$$P_R = V_R \cdot 2A = (3\Omega \cdot 2A) \cdot 2A = \underline{12\text{ W} - \text{absorbed}}$$

$$P_{4V} = 4V \cdot 2A = \underline{8\text{ W} - \text{absorbed}}$$

$$P_{2A} = V_{2A} \cdot 2A = (4V + V_R) \cdot 2A = (4V + 3\Omega \cdot 2A) \cdot 2A = 10V \cdot 2A = \underline{20\text{ W} - \text{supplied}}$$

Use mesh analysis to **find the current I_0** in the circuit below.

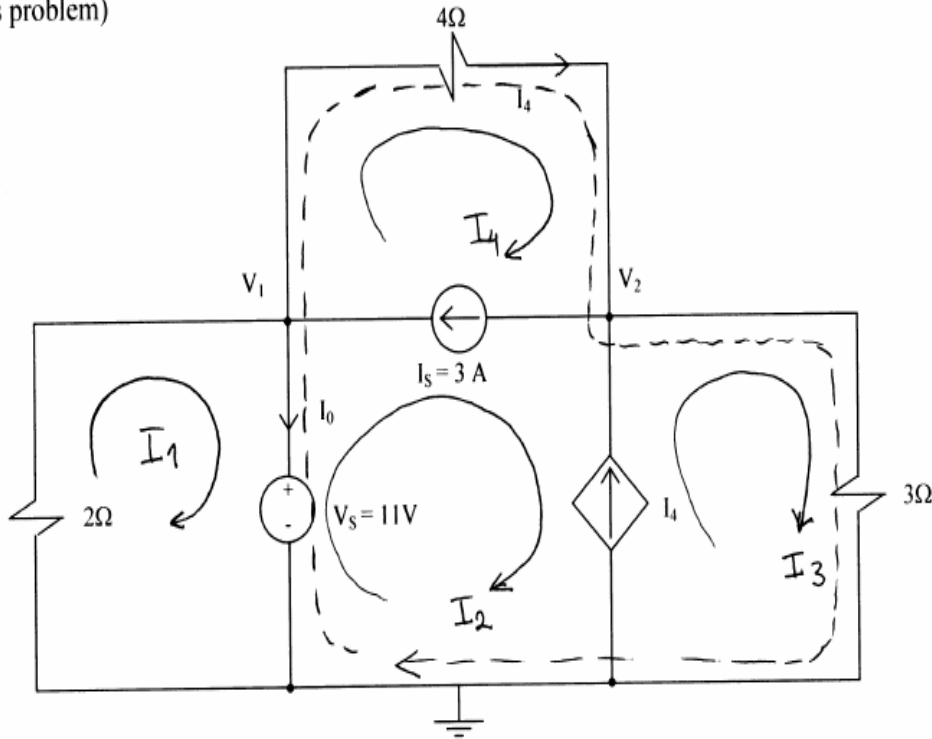(Note: This is the same circuit as in problem 4. You may use results from problem 4 to check your answers but you must write and solve mesh analysis equations to get credit for this problem)



$$\text{mesh 1: } -V_s - 2I_1 = 0 \dots (1) \Rightarrow I_1 = -\frac{11}{2} = -5.5 \text{ A}$$

$$\text{supermesh: } V_s - 4I_4 - 3I_3 = 0 \dots (2)$$

$$\text{source } I_s : I_s = I_4 - I_2 \dots (3) \Rightarrow I_2 = I_4 - 3 \dots (5)$$

$$\text{dep. source } I_4 : I_4 = I_3 - I_2 \dots (4)$$

$$(5) (4) : I_4 = I_3 - I_4 + 3 \Rightarrow I_3 = 2I_4 - 3 \dots (6)$$

$$(6) (2) : 11 - 4I_4 - 3(2I_4 - 3) = 0 \Rightarrow 11 - 4I_4 - 6I_4 + 9 = 0 \\ \Rightarrow 20 - 10I_4 = 0 \Rightarrow \underline{I_4 = 2 \text{ A}}$$


$$(5) \Rightarrow I_2 = 2 - 3 \Rightarrow \underline{I_2 = -1 \text{ A}}$$

$$I_0 = I_1 - I_2 = -5.5 + 1 \Rightarrow \boxed{I_0 = -4.5 \text{ A}}$$

Write nodal analysis equations for V_1 , V_2 and V_3 in standard form:

$$\begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix}$$

Do not solve the equations.

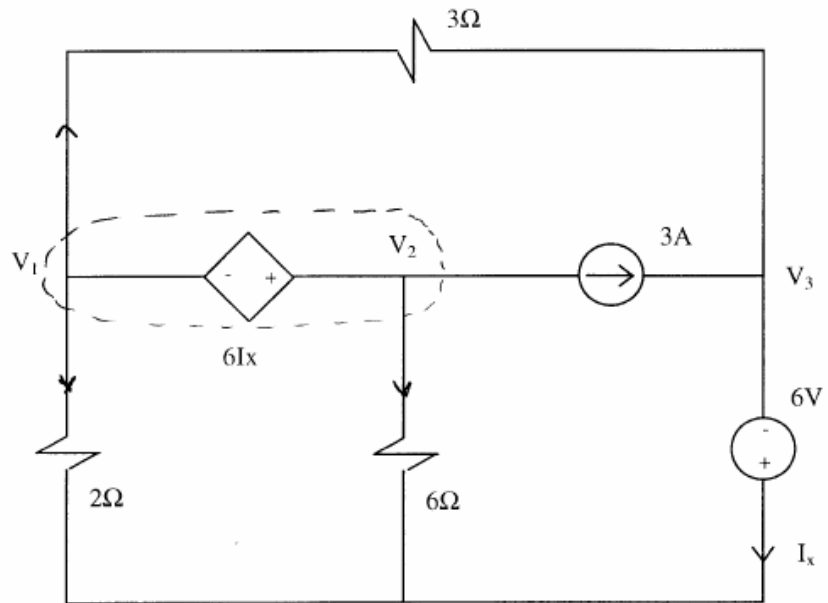

Supermode: $\left\{ \begin{array}{l} \frac{V_1}{2} + \frac{V_1 - V_3}{3} + \frac{V_2}{6} + 3 = 0 \quad / \cdot 6 \Rightarrow 3V_1 + 2V_1 - 2V_3 + V_2 = -18 \dots (1) \\ V_2 - V_1 = 6I_x \end{array} \right. \Rightarrow V_2 - V_1 = 6\left(3 + \frac{V_1 - V_3}{3}\right) = 18 + 2(V_1 - V_3)$



@ V_3 : $\left\{ \begin{array}{l} V_3 = -6 \dots (2) \\ I_x = 3 + \frac{V_1 - V_3}{3} \end{array} \right.$

$V_2 - V_1 = 18 + 2V_1 - 2V_3$

$3V_1 - V_2 - 2V_3 = -18 \dots (3)$

$$\begin{bmatrix} 5 & 1 & -2 \\ 0 & 0 & 1 \\ 3 & -1 & -2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -18 \\ -6 \\ -18 \end{bmatrix}$$

Use superposition to find V_0 .

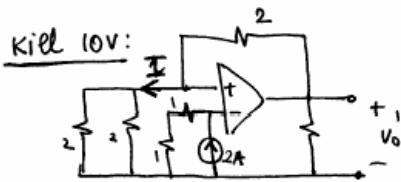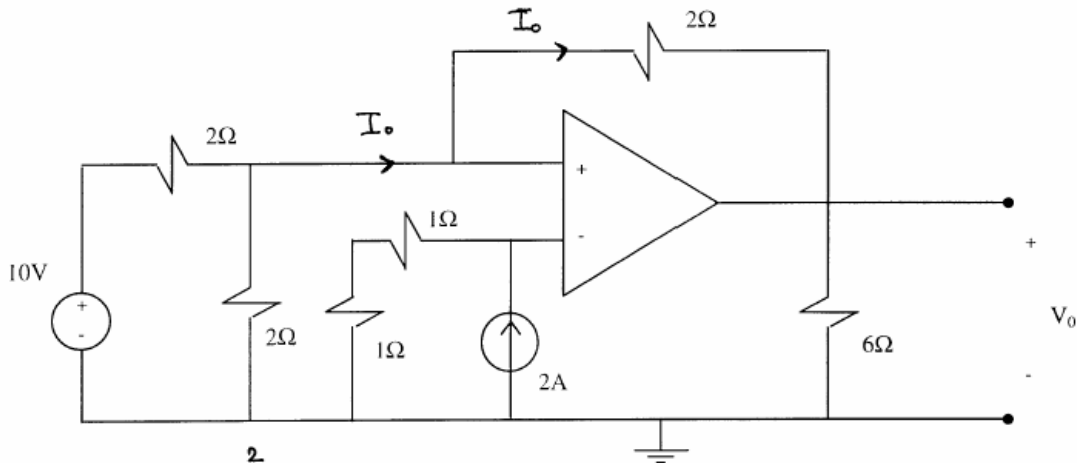


$$V_- = 2A(1+1) = 4V$$

$$V_+ = V_- = 4V$$

$$I = \frac{V_+}{2 \parallel 2} = \frac{4V}{1\Omega} = 4A$$
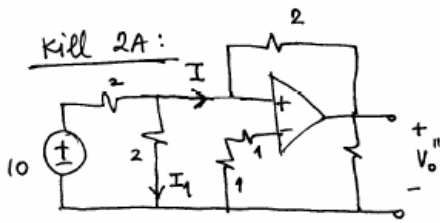
$$V_0' = V_+ + 2 \cdot I = 4V + 2\Omega \cdot 4A = \underline{12V}$$



$$V_- = 0 \Rightarrow V_+ = 0 \Rightarrow I_1 = 0$$

$$\Rightarrow I = \frac{10 - V_+}{2} = 5A$$

$$V_0'' = V_+ - I \cdot 2\Omega = 0 - 5A \cdot 2\Omega = \underline{-10V}$$

$$\text{Total: } V_0 = V_0' + V_0'' = 12V - 10V = \underline{2V}$$


Check by analyzing original circuit:

$$V_- = 2A(1+1) = 4V \Rightarrow V_+ = 4V$$


$$I_0 = \frac{10 - V_+}{2} - \frac{V_+}{2} = \frac{10 - 4}{2} - \frac{4}{2} = 3 - 2 = 1A$$

$$V_0 = V_+ - 2 \cdot I_0 = 4 - 2 \Rightarrow \underline{V_0 = 2V} \checkmark$$

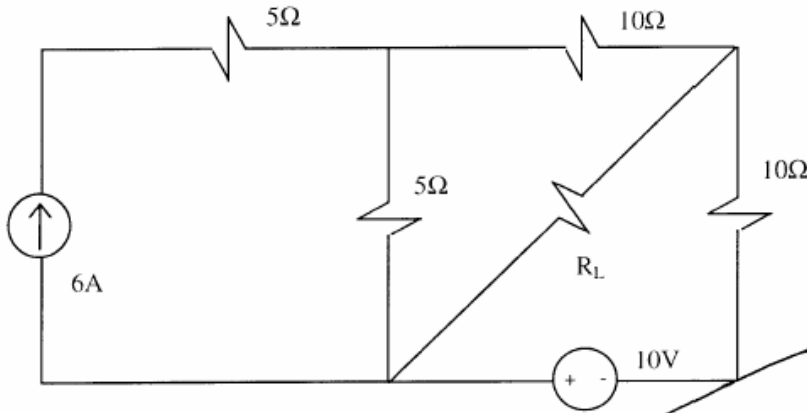- a) Use source transformation to find the value of R_L for maximum power transfer.
 b) What is the maximum power that can be transferred to R_L ?
 NOTE: Repeat source transformation steps until R_L can be found without using any current or voltage division.



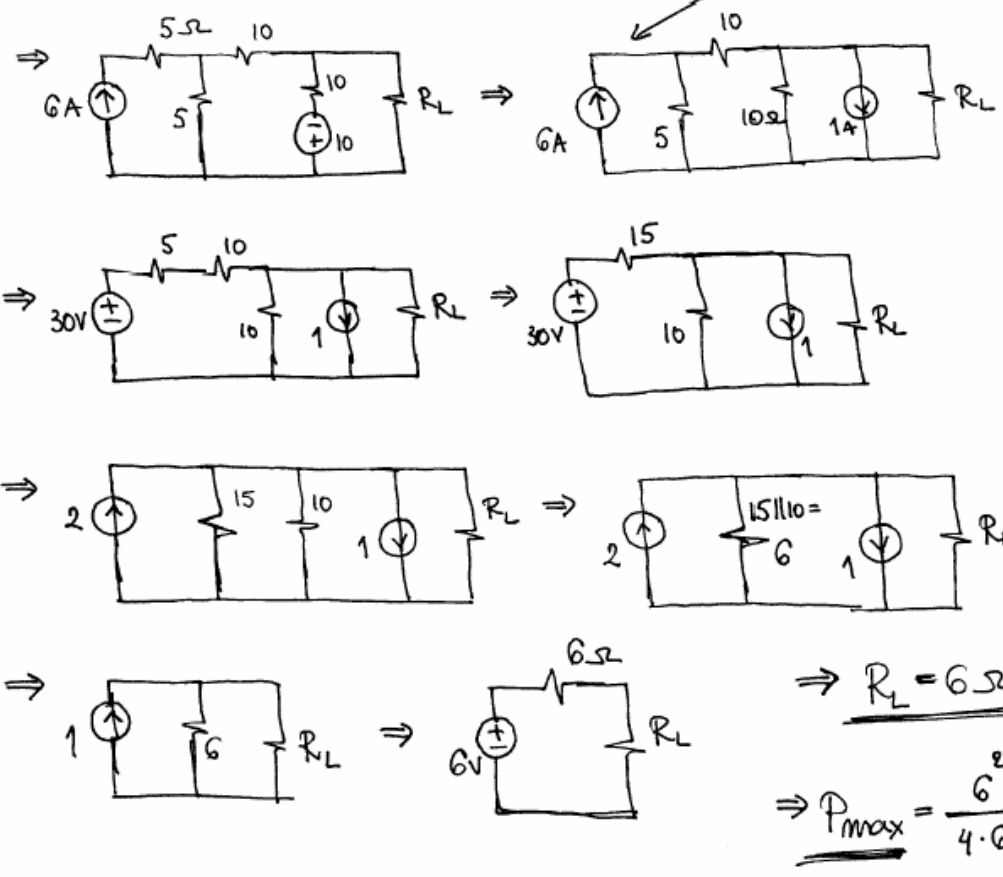5Ω can be ignored since it is in series with a current source.





$\Rightarrow \underline{R_L = 6\Omega}$ for maximum power transfer

$\Rightarrow \underline{P_{max} = \frac{6^2}{4 \cdot 6} = 1.5W}$

Use Thevenen's theorem to find V_o .

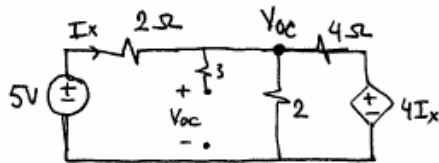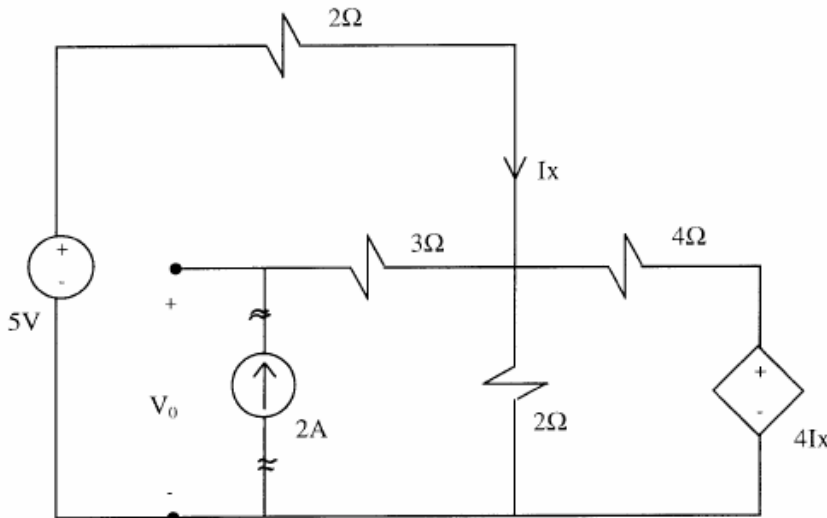HINT: Cut the circuit at the terminals of the 2A current source.




$$\text{KCL @ } V_{oc}: \frac{5 - V_{oc}}{2} = \frac{V_{oc}}{2} + \frac{V_{oc} - 4I_x}{4}$$

$$I_x = \frac{5 - V_{oc}}{2}$$

$$\Rightarrow \frac{5 - V_{oc}}{2} = \frac{V_{oc}}{2} + \frac{V_{oc}}{4} - \left(\frac{5 - V_{oc}}{2}\right) \Rightarrow 5 - V_{oc} = V_{oc} \left(\frac{1}{2} + \frac{1}{4}\right) = V_{oc} \cdot \frac{3}{4}$$

$$\Rightarrow 5 = V_{oc} + \frac{3}{4} V_{oc} = \frac{7}{4} V_{oc} \Rightarrow \underline{V_{oc} = \frac{20}{7}}$$

For R_{TH} we need I_{sc} :

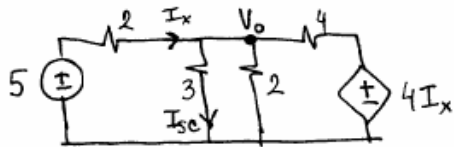


$$\text{KCL @ } V_o: \frac{5 - V_o}{2} = \frac{V_o}{3} + \frac{V_o}{2} + \frac{V_o - 4I_x}{4}, \quad I_x = \frac{5 - V_o}{2}$$

$$\Rightarrow \frac{5 - V_o}{2} = V_o \left(\frac{1}{3} + \frac{1}{2} + \frac{1}{4}\right) - \frac{5 - V_o}{2}$$

$$\Rightarrow 5 - V_o = V_o \cdot \frac{4+6+3}{12} \Rightarrow 5 = V_o \cdot \frac{13}{12} + V_o = \frac{25}{12} V_o \Rightarrow V_o = \frac{12 \cdot 5}{25} \Rightarrow V_o = \frac{12}{5}$$

$$I_{sc} = \frac{V_o}{3} = \frac{12}{3 \cdot 5} \Rightarrow \underline{I_{sc} = \frac{4}{5}}$$

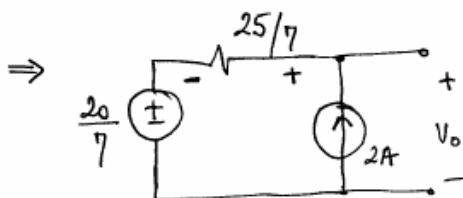
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{20}{7}}{\frac{4}{5}} = \frac{100}{28} = \frac{25}{7} = R_{TH}$$




$$V_o = V_{TH} + 2 \cdot R_{TH} = \frac{20}{7} + 2 \cdot \frac{25}{7} = \frac{20}{7} + \frac{50}{7} = \frac{70}{7}$$

$$\Rightarrow \boxed{V_o = 10 \text{ V}}$$

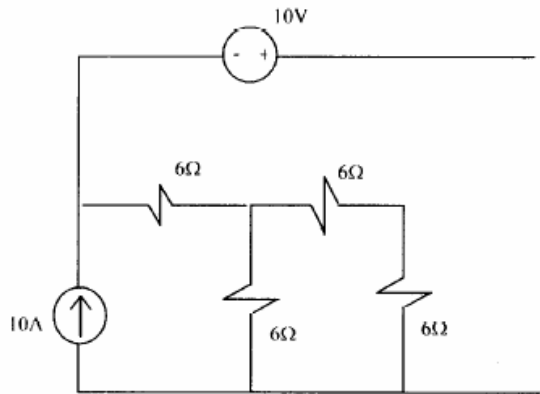
1. Find both Thevenen's and Norton's equivalent of the following circuit.



Find R_{TH} :

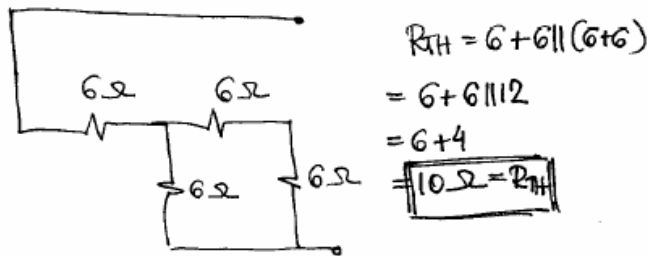

Find V_{TH}

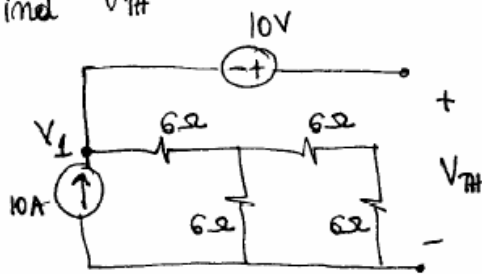


$$V_1 = 10A \cdot (6 + 6 \parallel (6 + 6))$$

$$= 10A \cdot 10\Omega = 100V$$


$$V_{TH} = V_1 + 10V \Rightarrow V_{TH} = 110V$$

$$I_{NT} = \frac{V_{TH}}{R_{TH}} = \frac{110V}{10\Omega} \Rightarrow I_{NT} = 11A$$

Norton's Equivalent

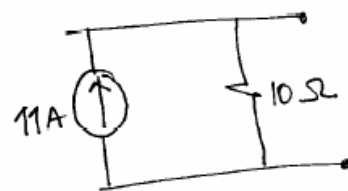


Thevenen's Equivalent

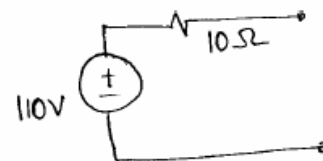

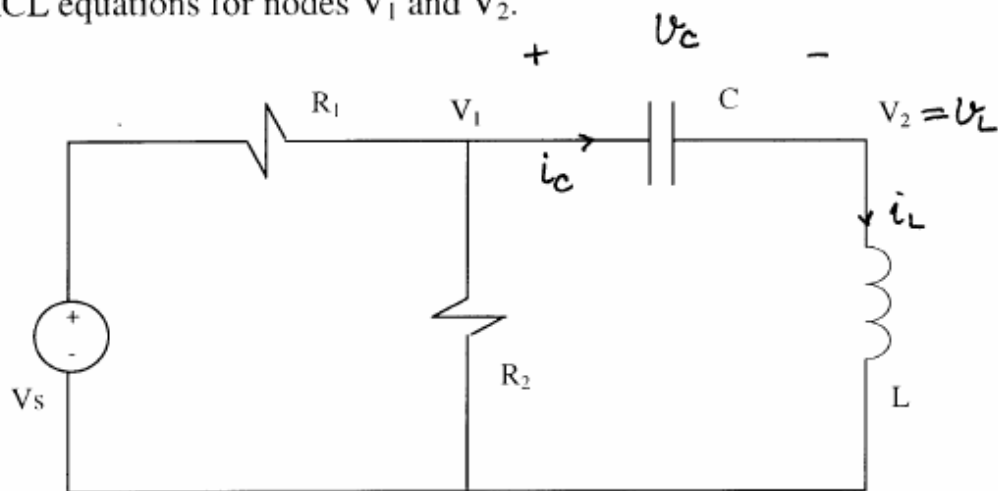2. If the load is $R_L = 1K\Omega$, does this circuit behaves more like a current or a voltage source?

$R_g = 10\Omega \Rightarrow R_g \ll R_L \Rightarrow$ This circuit behaves more like a voltage source.

Write KCL equations for nodes V_1 and V_2 .



$$\textcircled{V_1}: \frac{V_s - V_1}{R} = \frac{V_1}{R} + i \quad ; \quad i = i_c = i_L \quad ; \quad i_L = \frac{1}{L} \int v_L dt$$






$$\Rightarrow \frac{V_s - V_1}{R} = \frac{V_1}{R} + \frac{1}{L} \int v_1 dt \quad \dots (1)$$

$$\textcircled{V_2}: \quad i_c = i_L$$

$$i_c = C \cdot \frac{d}{dt} \cdot v_c = C \cdot \frac{d}{dt} (v_1 - v_2) = C \frac{dv_1}{dt} - C \frac{dv_2}{dt}$$


$$\Rightarrow C \frac{dv_1}{dt} - C \frac{dv_2}{dt} = \frac{1}{L} \int v_1 dt \quad \dots (2)$$

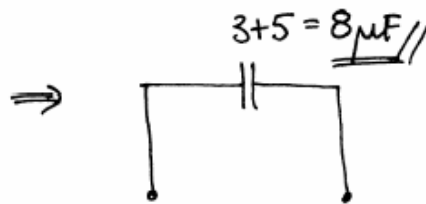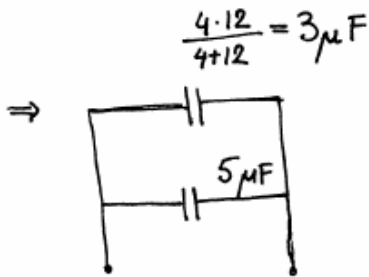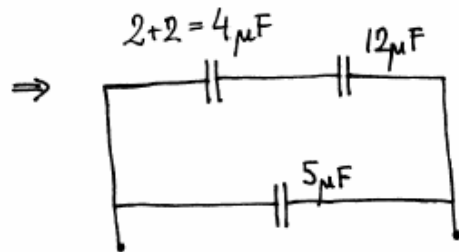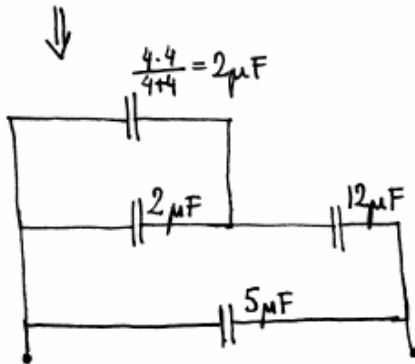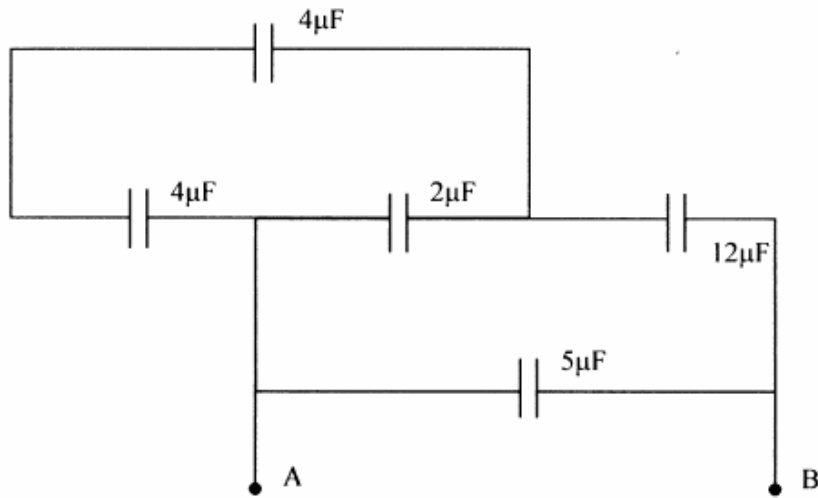Find the equivalent capacitance between points A and B.




⇒ $C_{eq} = 8\mu\text{F}$

Find $i_o(0^+)$.

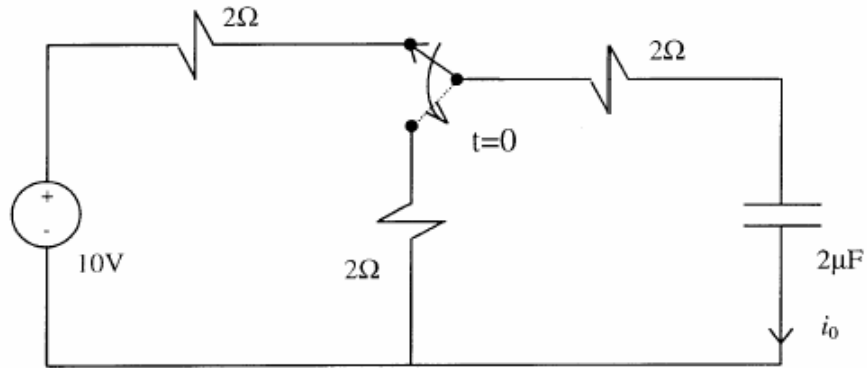


@ $t=0^-$: STEADY STATE :

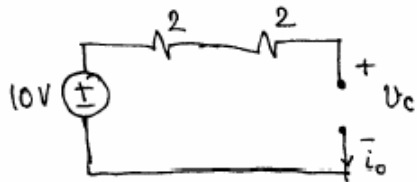

$$i_o(0^-) = 0$$

$$v_c(0^-) = 10V$$

@ $t=0^+$

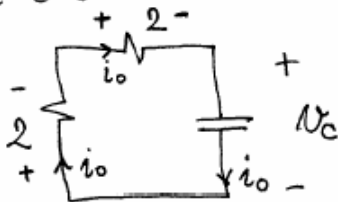


$$\text{KVL: } 2i_o(0^+) + 2i_o(0^+) + v_c(0^+) = 0$$


$$\Rightarrow i_o(0^+) = -\frac{v_c(0^+)}{4} = -\frac{v_c(0^-)}{4} = -\frac{10}{4}$$

$$\Rightarrow \underline{\underline{i_o(0^+) = -2.5A}}$$

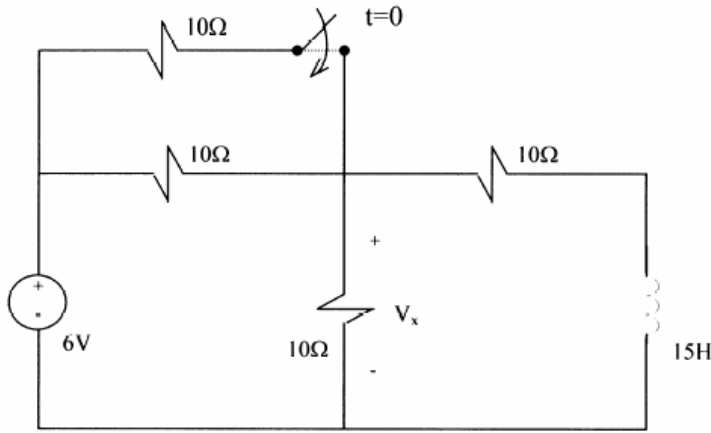Find voltage $V_x(t)$, for $t > 0$ s. Sketch $V_x(t)$, for $t > -1$ s.




@ $t = 0^-$: STEADY STATE :

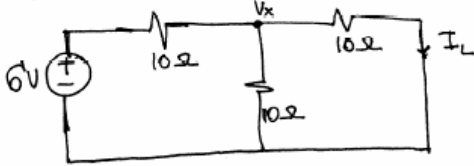

$$V_x(0^-) = \frac{10 \parallel 10}{10 + 10 \parallel 10} \cdot 6V = \frac{5}{15} \cdot 6 = \underline{2V}$$

$$I_L(0^-) = \frac{V_x}{10} = 0.2A$$

@ $t = 0^+$:

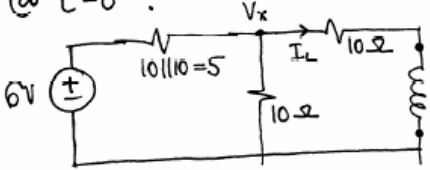

a) non-discontinuity condition for inductor:

$$I_L(0^+) = I_L(0^-) = 0.2A$$


b) KCL @ V_x :

$$\frac{6 - V_x}{5} = \frac{V_x}{10} + I_L \Rightarrow 12 - 2V_x = V_x + 10I_L$$

$$\Rightarrow V_x = \frac{1}{3}(12 - 10I_L)$$

$$\Rightarrow \underline{V_x(0^+) = \frac{10}{3}V}$$


time constant: $\tau = \frac{L}{R_{TH}}$

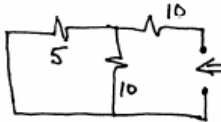

$$R_{TH} = 10 + 5 \parallel 10 = 10 + \frac{50}{15} = 10 + \frac{10}{3} = \frac{40}{3}$$

$$\Rightarrow \tau = \frac{15 \cdot 3}{40} = \frac{45}{40} \Rightarrow \underline{\tau = \frac{9}{8}}$$


@ $t \rightarrow \infty$: STEADY STATE

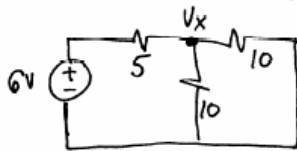

$$V_x = \frac{10 \parallel 10}{5 + 10 \parallel 10} \cdot 6$$

$$= \frac{5}{10} \cdot 6$$

$$\underline{V_x = 3V}$$

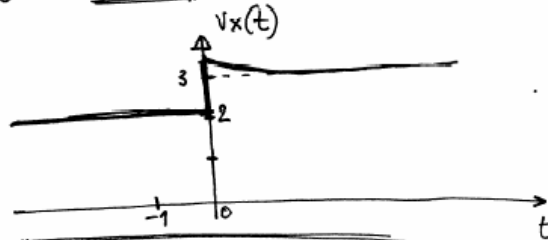

$$\Rightarrow V_x(t) = V_x(\infty) + [V_x(0^+) - V_x(\infty)] e^{-t/\tau} \Rightarrow \underline{V_x(t) = 3 + \frac{1}{2} e^{-8t/9}, t > 0}$$