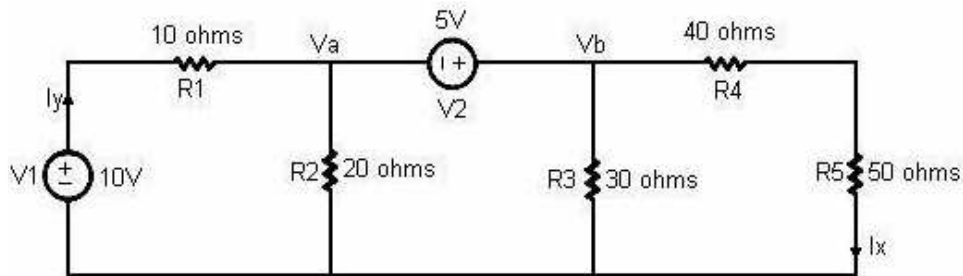



# ECE 201: Linear Circuit Analysis I:

## Chapter 4: Superposition Principle

1. Find  $i_x$  using superposition and any other analysis techniques you have acquired up until this point.



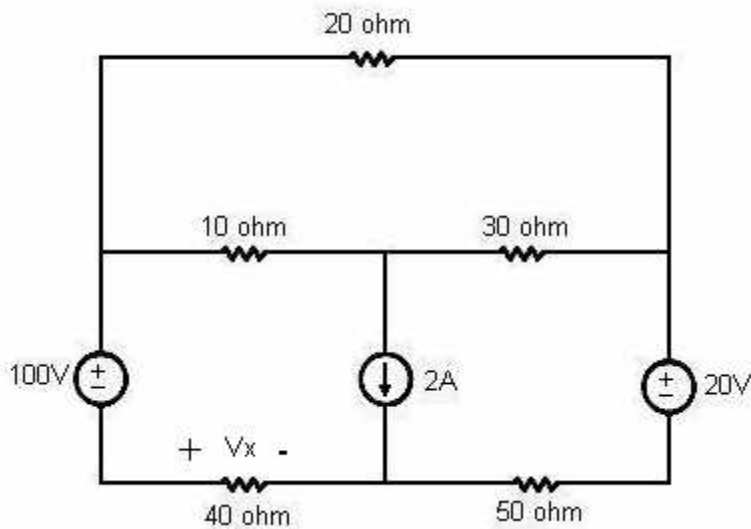2. Find  $v_x$  using superposition and any other analysis techniques you have acquired up until this point.



3. Find  $i_x$  using superposition and any other analysis techniques you have acquired up until this point.

