

ECE 370: Digital Systems-Logic Design

Sample Test: Chapter 2

Spring 2005

1. Is the following equality valid? Determine using Boolean algebra and check yourself using a truth table.

$$\bar{A}\bar{C} + BC + A\bar{B} = \bar{A}B + AC + \bar{B}C$$

2. What is the simplest sum-of-products expression for the following function? (*Hint: Use the consensus theorem* $AB + BC + AC = AB + AC$)

$$f(A, B, C, D) = B\bar{C}D + ACD + A\bar{B}D$$

3. What is the most simplified minimum-cost POS for the following function?

$$f(A, B, C, D) = \sum m(0, 2, 4, 5, 6, 7, 8, 10, 12, 14, 15)$$

4. A circuit that controls a given digital system has three inputs: X, Y, and Z. It has to recognize three different conditions:

- Condition A is true if Z is true and either X is true or Y is false
- Condition B is true if X is true and either Y or Z is false
- Condition C is true if Y is true and either X is true or Z is false

The control circuit must produce a logic HIGH output if at least two of the conditions A, B, and C are true. What is the simplest circuit that can be designed for this purpose?

5. Given the following digital logic network, answer the following questions:

- a) What is the un-simplified Boolean function for $f(w, x, y, z)$?
- b) What is complete truth table that describes $f(w, x, y, z)$?
- c) What given the following waveforms for $w, x, y,$ and $z,$ what is the waveform for $f(w, x, y, z),$



