

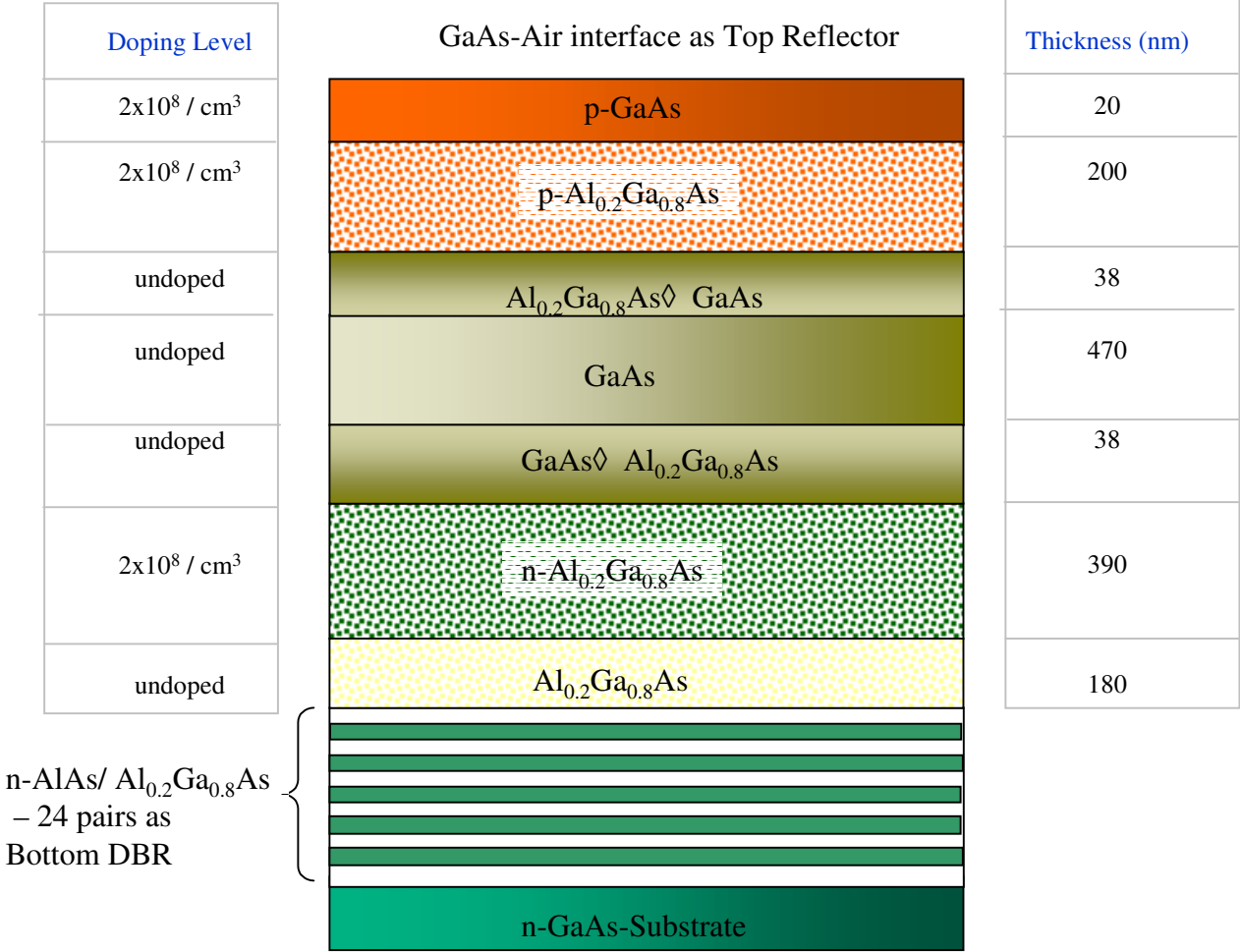


# 50 GHz *p-i-n* Photodiode

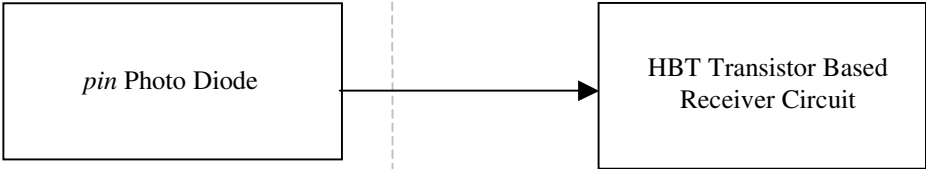

1. <http://www.fen.bilkent.edu.tr/~ozbay/Papers/34-99apl-ozbaypin.pdf>
2. Electronics Letters, Oct, 1994, pp 1796
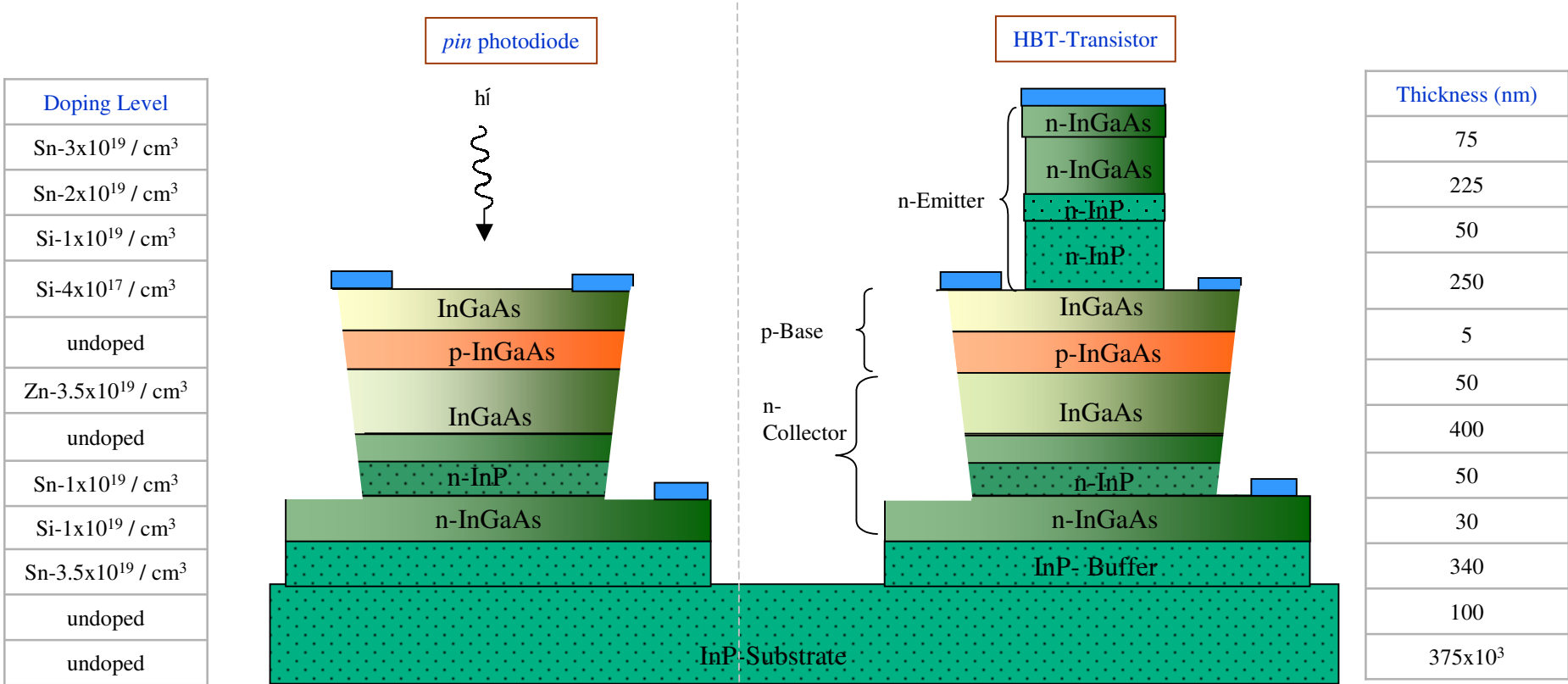
# InP–InGaAs Single HBT Technology for Photoreceiver OEIC's at 40 Gb/s




HBT – Heterojunction Bipolar Transistor

1. Huber, IEEE Journal. Light Wave Tech. Vol 18, July 2000, 992
2. Razavi, Design of Integrated Circuits for optical communications

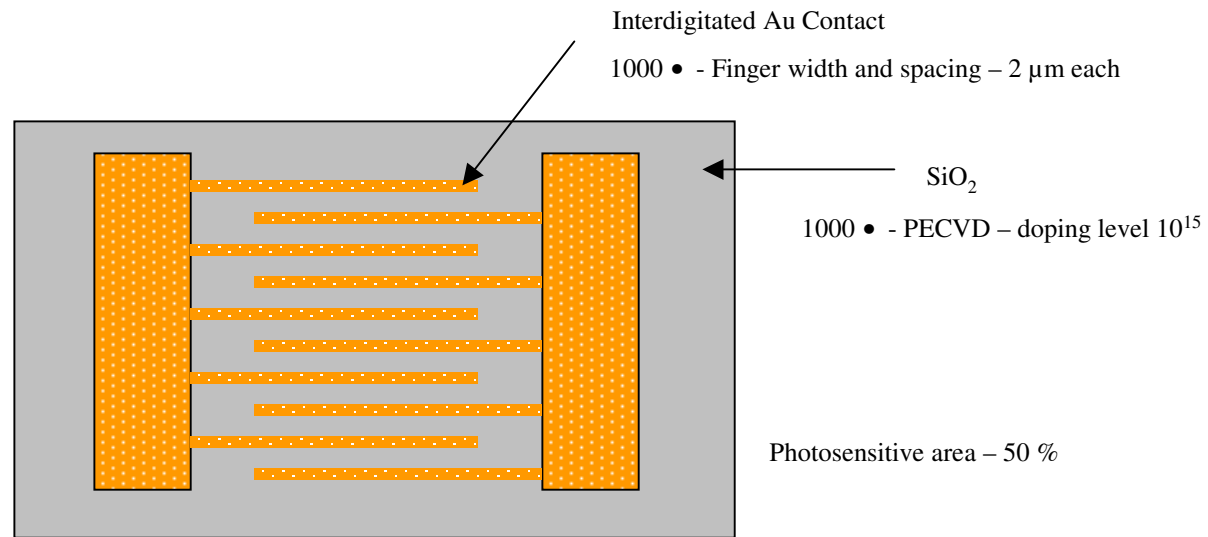
# Metal-Semiconductor-Metal (MSM) Photo detector

- Formation of two schottky contacts on a undoped semiconductor layer, either single or interdigitated



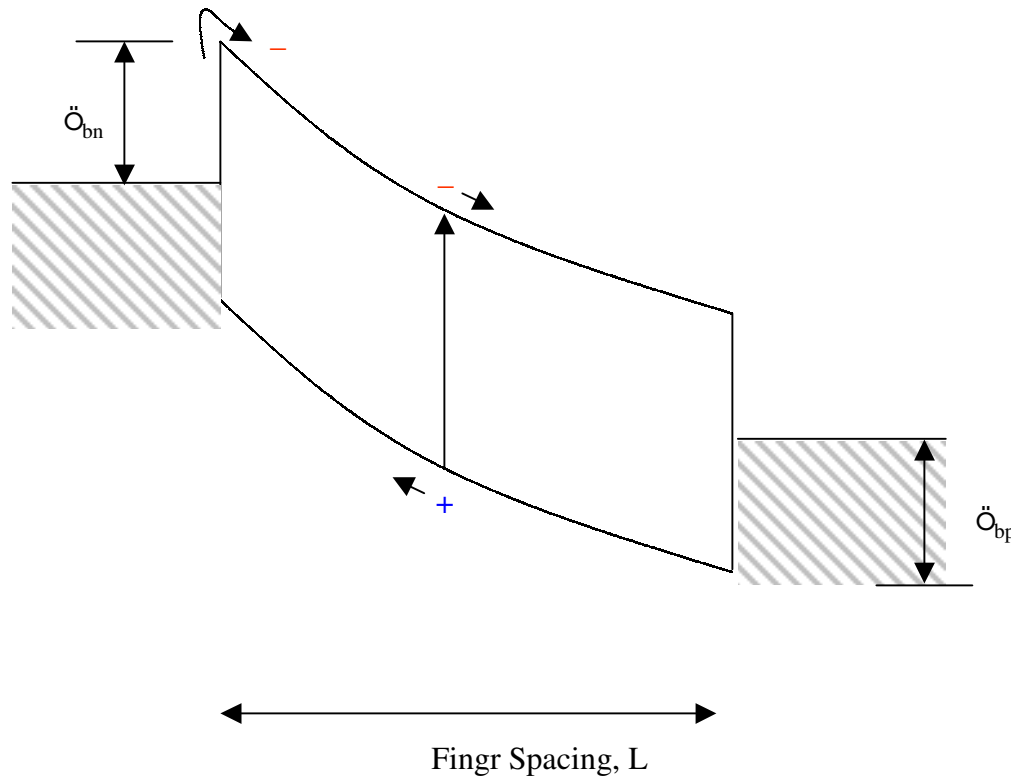
## Energy Band Diagram of MSM detector under Bias


- Adjacent metal/ semiconductor/ metal interfaces are schottky barriers, which serve as two back to back diodes
- When Bias is applied across fingers, one junction becomes FB and other RB
- Photo generated electron-hole pairs in the bulk are swept away by the electric field



# Bandwidth Calculation

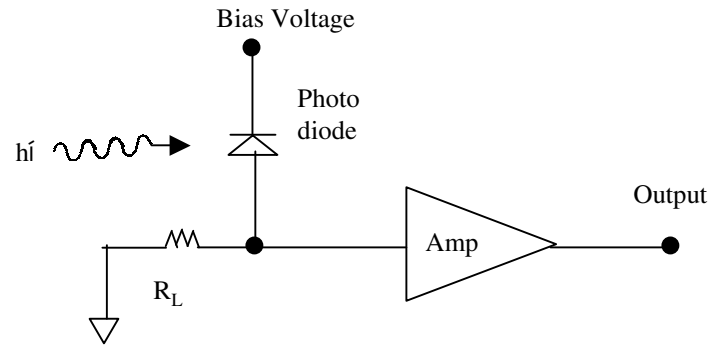

## Equivalent Circuit

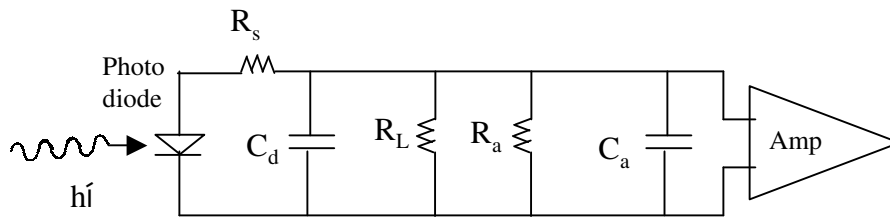

$C_d$  = Junction + Packaging Capacitance

$R_L$  = Bias Resistor

$R_s$  = Series Resistance of photodiode (small and can be neglected)

$R_a$  = Amplifier Input Resistance

$C_a$  = Amplifier Input Capacitance

## Bandwidth Calculation

$$C_T = \text{Total Capacitance} = C_D \parallel C_a$$

$$R_T = \text{Total Resistance} = R_D \parallel R_a$$

$$\text{Bandwidth} = \frac{1}{2\pi R_T C_T}$$

## Example

$$C_D = 3\text{pf}$$

$$C_a = 4\text{pf}$$

$$R_L = 1\text{K}\Omega$$


$$R_a = 1\text{M}\Omega$$

$$R_T = R_L \parallel R_a \approx 1\text{K}\Omega$$

$$C_T = C_D \parallel C_a = 7\text{pf}$$

$$\text{Bandwidth} = \frac{1}{2\pi \times 1 \times 10^3 \times 7 \times 10^{-12}} = 23\text{MHz}$$

## Bandwidth

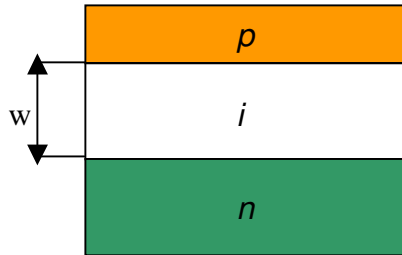

Bandwidth,

$$BW = \frac{0.44}{\tau_r}$$

Where  $\tau_r$  is the transit time

$$\tau_r = \frac{w}{v_d}$$

$v_d$  is the saturated carrier drift velocity

## Example<sup>1</sup>

Let

$$v_d = 8 \times 10^6 \text{ cm/s}$$


$$w = 20 \times 10^{-4} \text{ cm}$$

$$\tau_r = \frac{w}{v_d} = \frac{20 \times 10^{-4}}{8 \times 10^6} = 0.25 \text{ ns}$$

Bandwidth,

$$BW = \frac{0.44}{0.25 \times 10^{-9}} = 1.76 \text{ GHz}$$

## Working Principle of pin diode

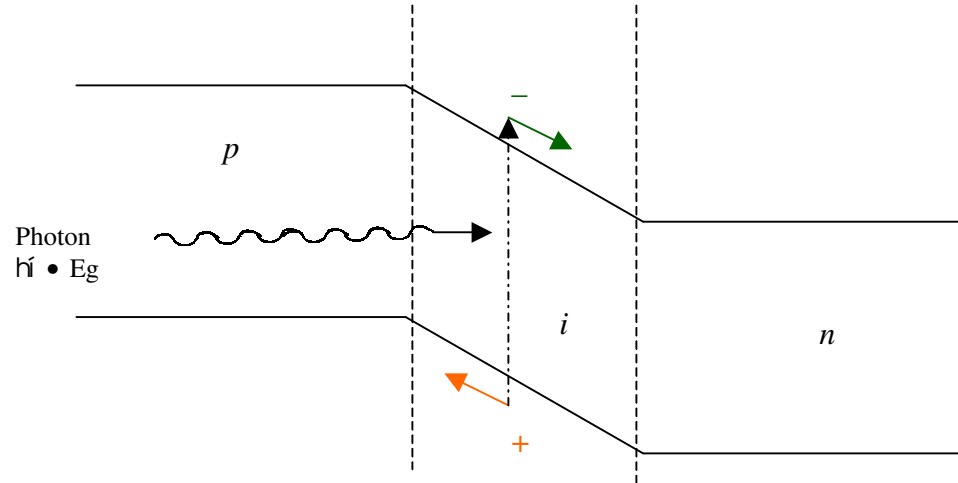

Simple Energy Band diagram for a pin diode

- Photons with an energy greater than or equal to the bandgap energy  $E_g$ , generates e-h pairs which act as photocurrent carriers
- Wavelength corresponding to  $E_g$  is the cut off wavelength which is upper limit of wavelength range

Cutoff Wavelength,

$$\lambda_c = \frac{hc}{E_g} = \frac{1240}{E_g \text{ (eV)}} \text{ in nm}$$

### Example


Bandgap of GaAs at 300K is 1.43 eV

Cutoff Wavelength,

$$\lambda_c = \frac{hc}{E_g} = \frac{1240}{1.43} = 867 \text{ nm}$$

Hence GaAs photodiode will not operate for photons of wavelength greater than 867 nm

# Photodiode Pulse Response

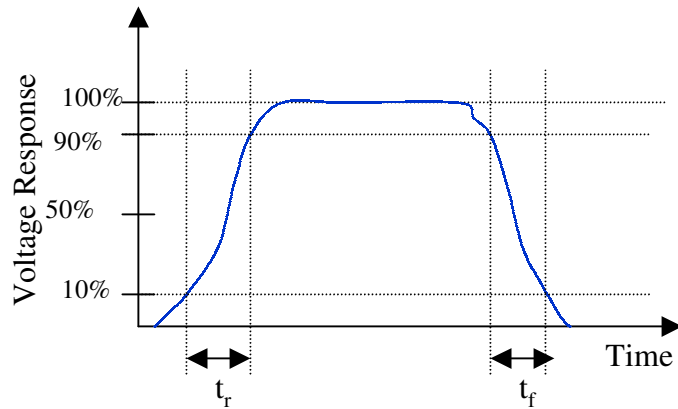


$t_r$ -Rise Time  
 $t_f$ -Fall Time

Both depends on carrier drift velocity,  
 intrinsic region width  $w$  and junction  
 capacitance  $C_j$


Input Pulse




$w \gg 1/\alpha$   
 small  $C_j$

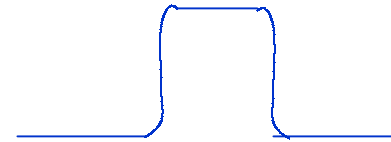

$w \gg 1/\alpha$   
 Large  $C_j$

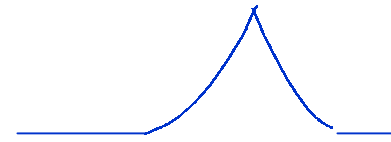


$w \bullet 1/\alpha$   
 small  $C_j$

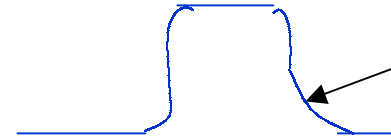

Diffusion component



# Simple Receiver Circuit

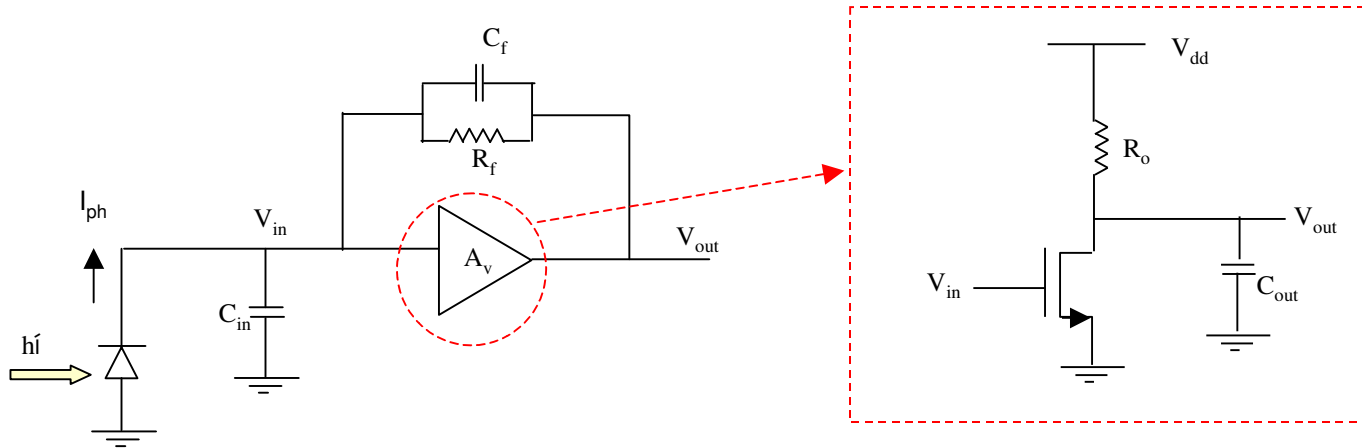

Transimpedance Amplifier with CS Voltage Amplifier


Transimpedance function of the receiver circuit

$$H_r(f) = \frac{v_{out}}{i_{in}} = \frac{R_f \left( \frac{A_v}{1 - A_v} \right)}{1 + j2\pi f \left( C_f + \frac{C_{in}}{1 - A_v} \right)}$$

Voltage gain of CS stage with feedback loading

$$A_v = \frac{-g_m + \frac{1}{R_f} + j2\pi f C_f}{\frac{1}{R_o} + \frac{1}{R_f} + j2\pi f (C_{out} + C_f)}$$



# Wide Bandwidth Preamplifier Circuits

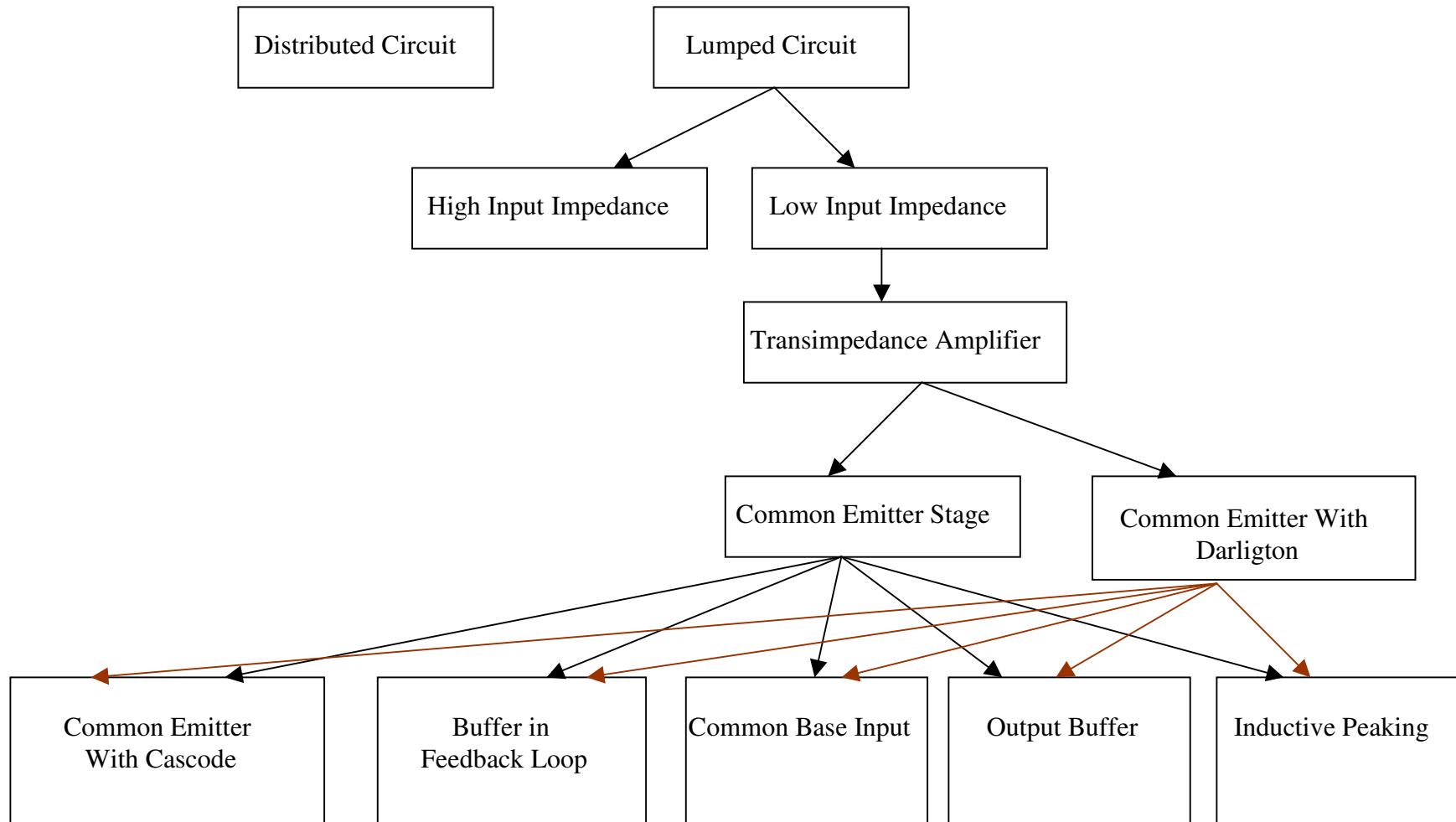

Huber, Dieter



[InP/InGaAs single hetero-junction bipolar transistors for integrated photoreceivers operating at 40 Gb/s and beyond](#)
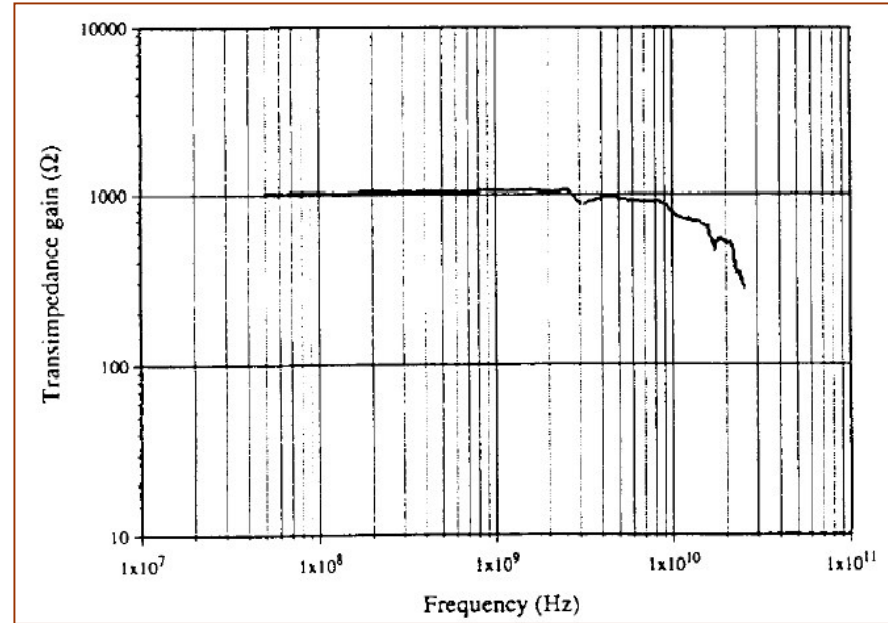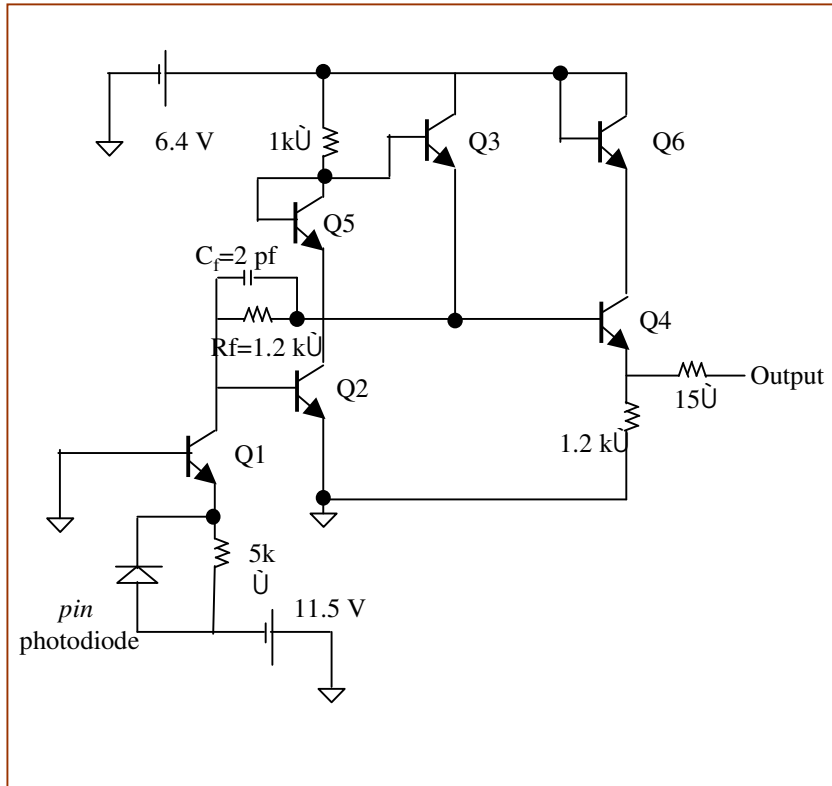
# Common Base HBT Based Preamplifier Circuit



Measured Frequency Response

# First pass Amplifier (CS)

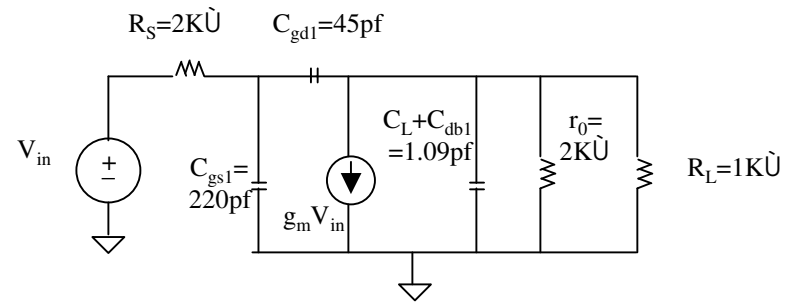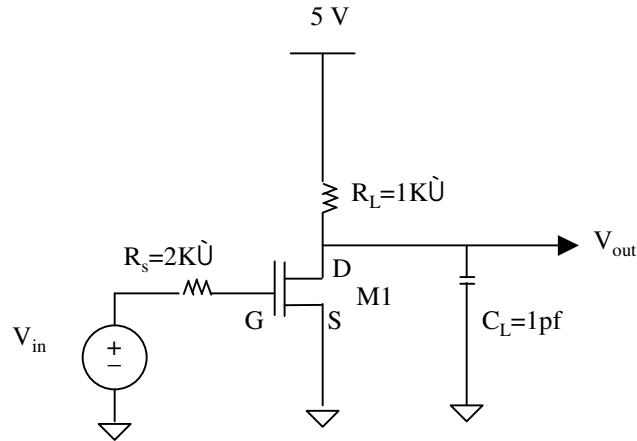

Small Signal Equivalent Circuit at High Frequencies

## Example<sup>1</sup>

$$\tau_{gs1} = C_{gs1} r_{gs1} = C_{gs1} R_s = 220 \times 10^{-15} \times 2000 = 0.44 \text{ ns}$$


$$\tau_{gd1} = C_{gd1} r_{gd1} = C_{gd1} (R_s + R_L + g_m \cdot \frac{1}{1 + g_m R_E} \cdot R_s \cdot R_L) = 45 \times 10^{-15} \times \left( 2000 + 1000 + \frac{12 \times 10^{-3} \times 2000 \times 1000}{1 + 0} \right) = 1.215 \text{ ns}$$

$$\tau_{gb1} = C_{gb1} r_{gb1} = C_{gb1} (R_L \parallel r_o) = 0.09 \times 10^{-12} \times (1000 \parallel 2000) = 0.06 \text{ ns}$$



$$\tau_L = C_L (R_L \parallel r_o) = 1 \times 10^{-12} \times (1000 \parallel 2000) = 0.67 \text{ ns}$$

$$\text{Bandwidth} = \frac{1}{\tau_{gs1} + \tau_{gd1} + \tau_{gb1} + \tau_L} = \frac{10^9}{0.44 + 1.215 + 0.06 + 0.67} = 419.28 \text{ MHz}$$


# Second pass Cascode Amplifier (CS)

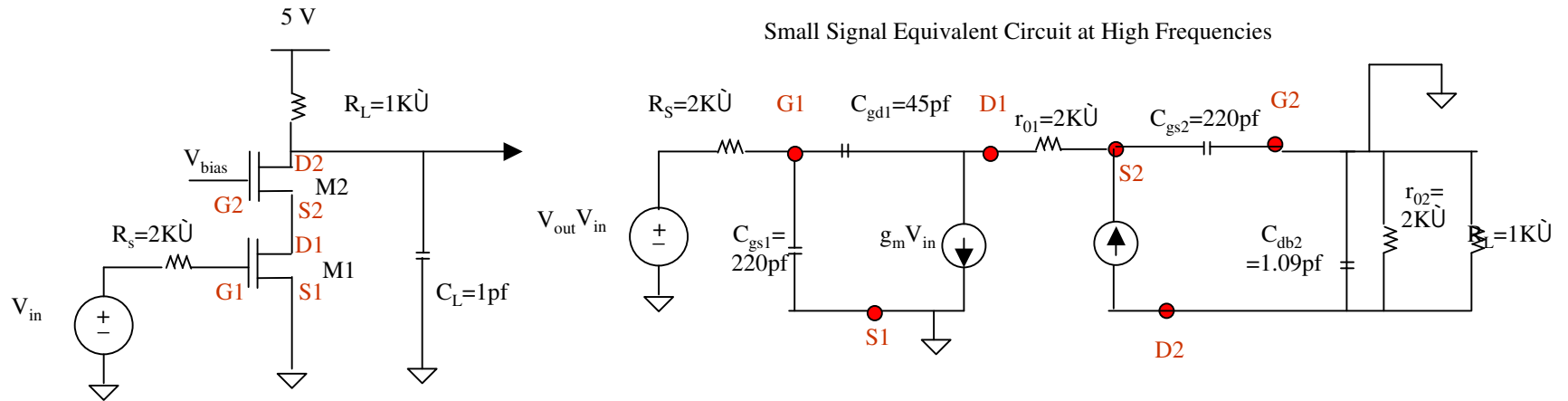

# Current Mirror

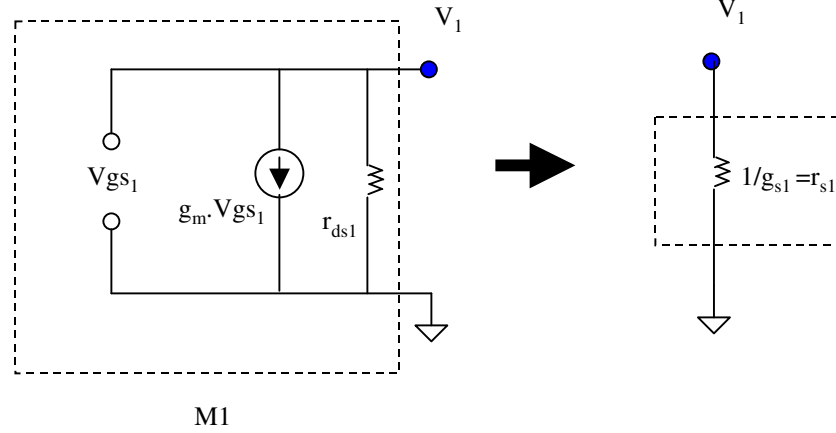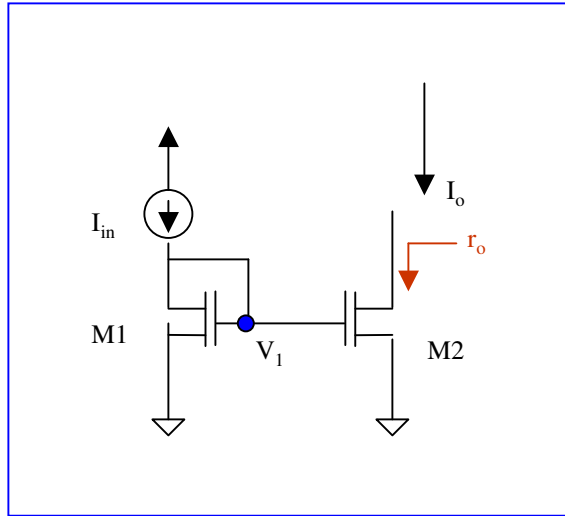
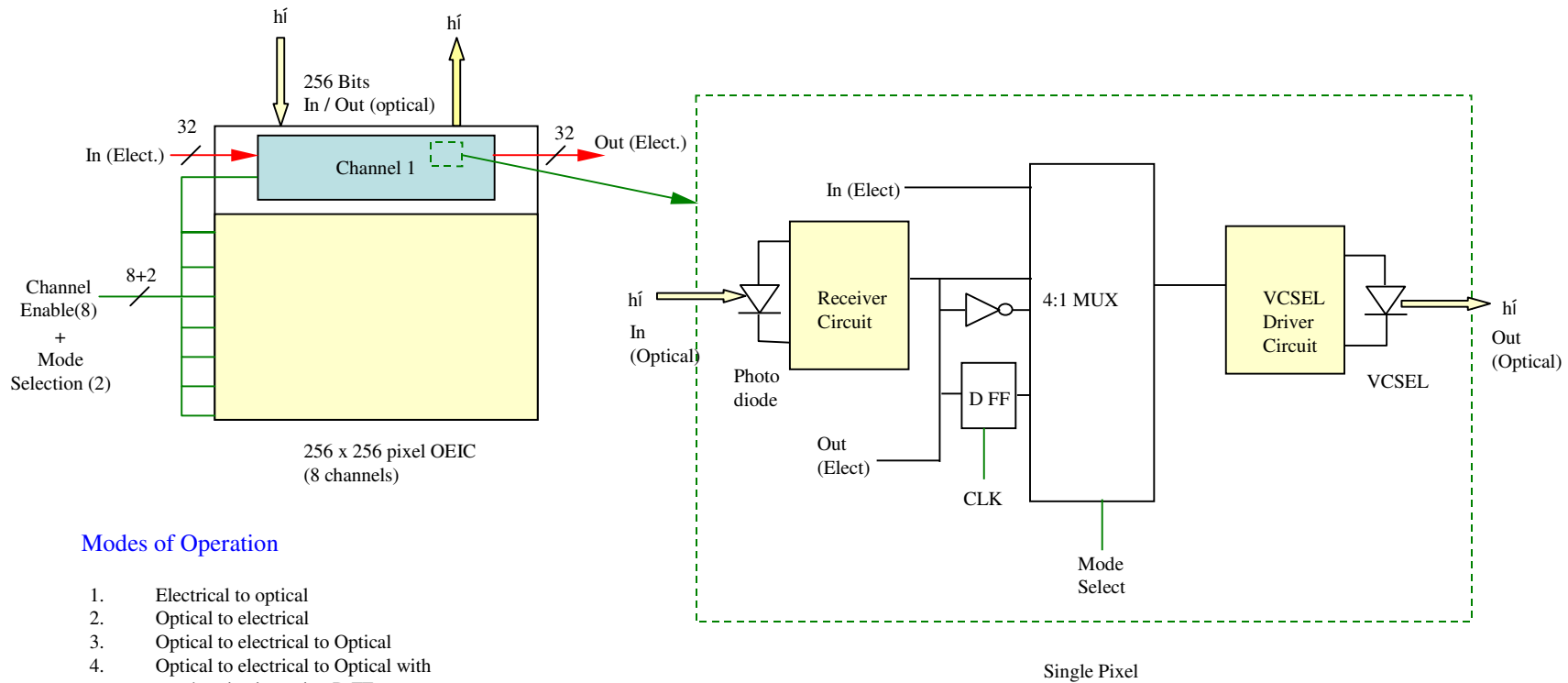
# 32 bit 8 Channel Bidirectional OEIC<sup>1</sup>



## Modes of Operation

1. Electrical to optical
2. Optical to electrical
3. Optical to electrical to Optical
4. Optical to electrical to Optical with synchronization using D FFs