
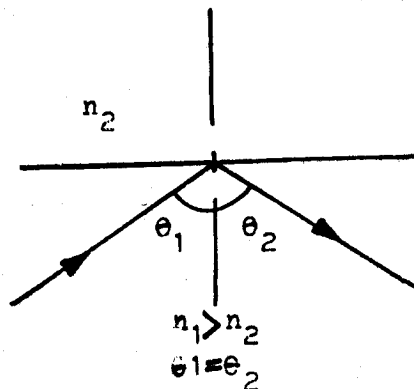
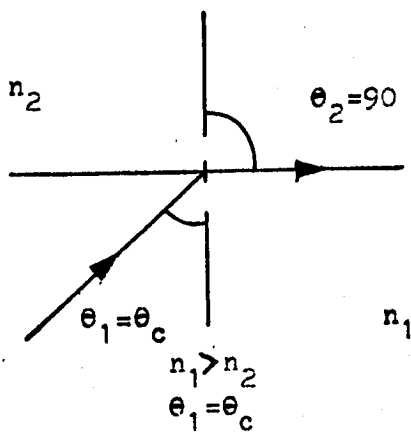



SEQUENCE OF PRESENTATION

1. INTRODUCTION TO OPTICAL FIBERS
2. INTRODUCTION TO DATA TRANSMISSION
3. MANCHESTER CODE MODULATOR
4. MULTIPLEXING
5. MANCHESTER CODE DEMODULATOR
6. DEMULTIPLEXING
7. ERROR DETECTION
8. INTERFACING THE OPTICAL EQUIPMENT
9. CONCLUSIONS

TOTAL INTERNAL REFLECTION

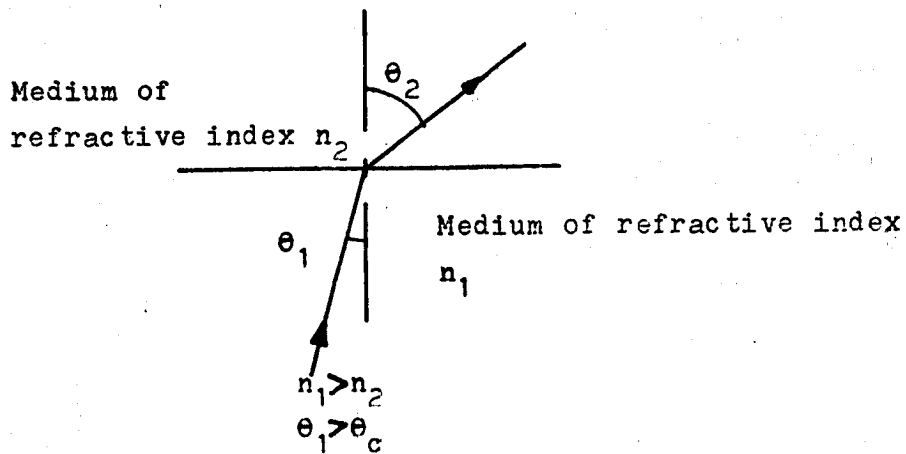


OPTICAL FIBER

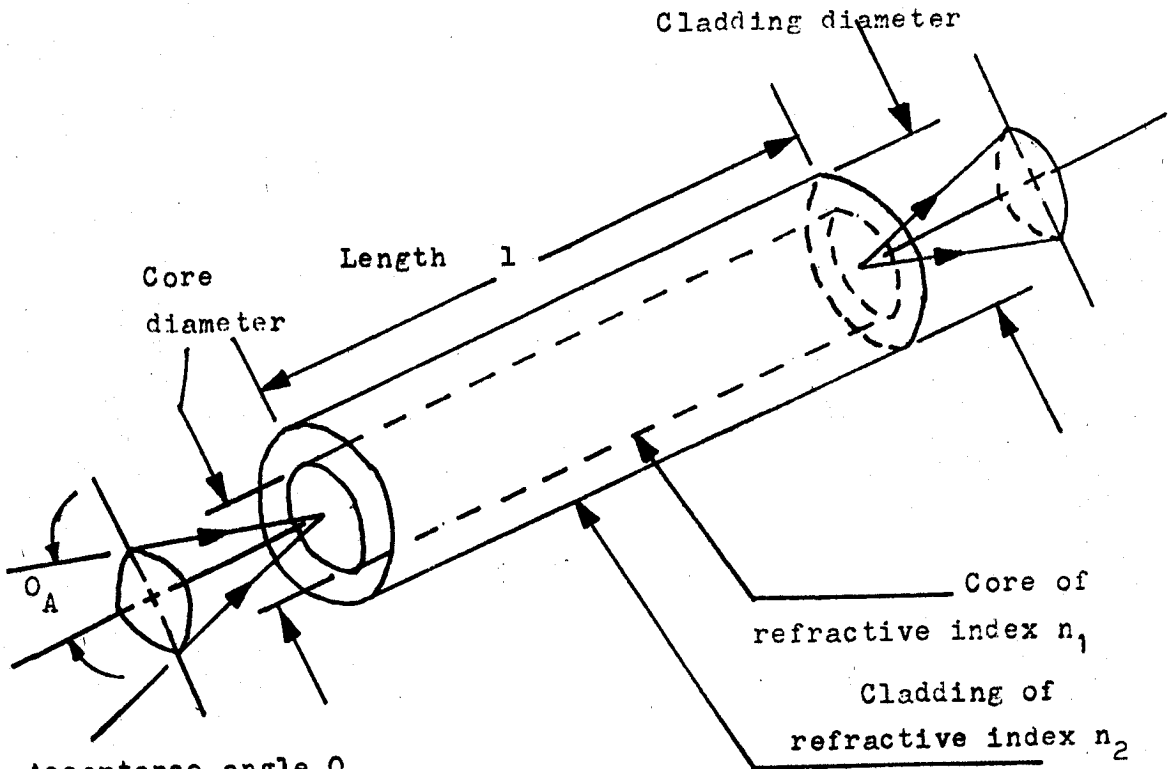

Acceptance angle θ_A
Numerical aperture N.A. = $\sin \theta_A$

Transmission loss = αl

MODES OF PROPAGATION IN OPTICAL FIBER

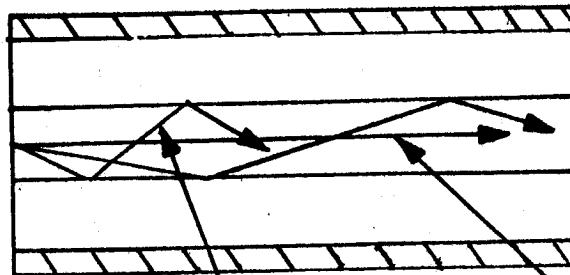

Slowest mode


Fastest mode

DATA COMMUNICATION CODES

Codes used in data communication are divided in two major categories:

1. NON-SELF CLOCKING

(a) NRZ

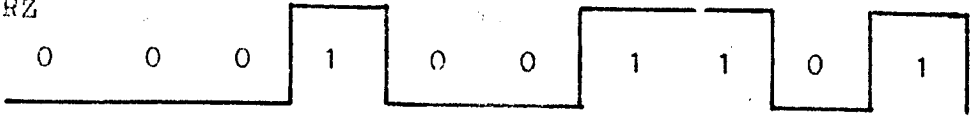

(b) RZ




2. SELF CLOCKING

(a) MANCHESTER CODE




(b) BI-PHASE MARK CODE

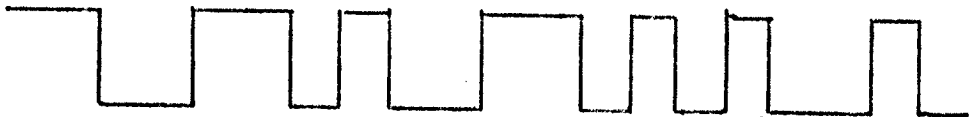

(c) BI-PHASE SPACE CODE




DATA COMMUNICATION SYSTEM

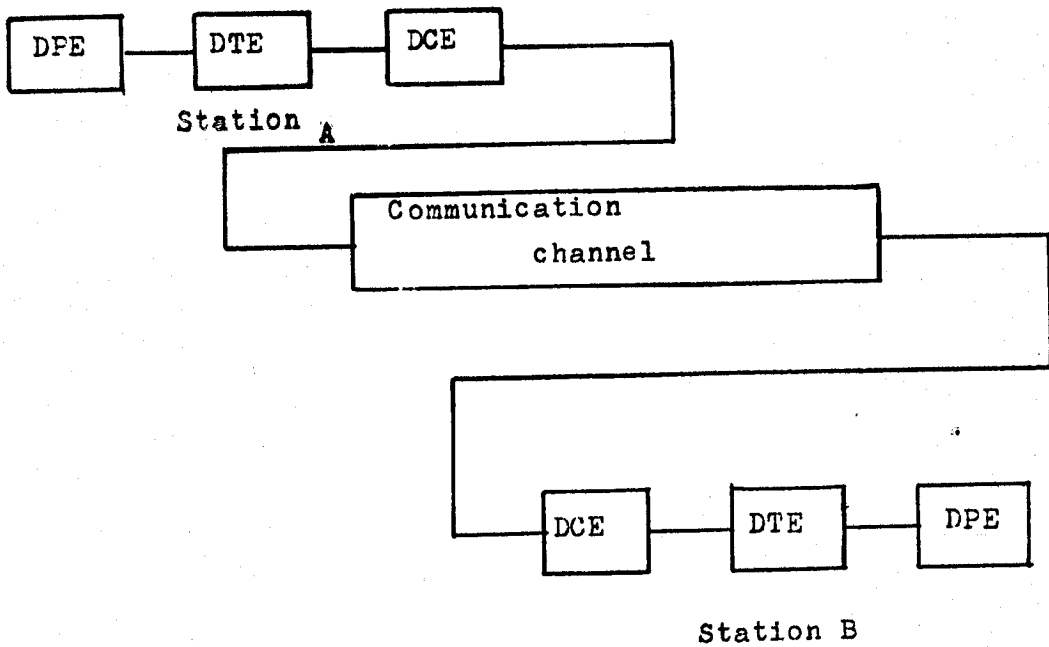

- DPE- Data Processing Equipment
- DTE- Data Terminal Equipment
- DCE- Data Communication Equipment

MANCHESTER CODE MODULATOR

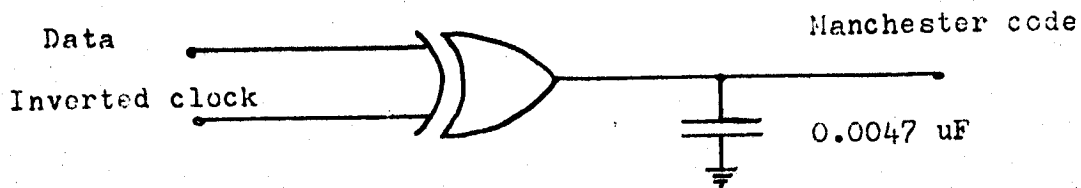

WAVEFORMS

Inverted clock




Data




Manchester code



MULTIPLEXER

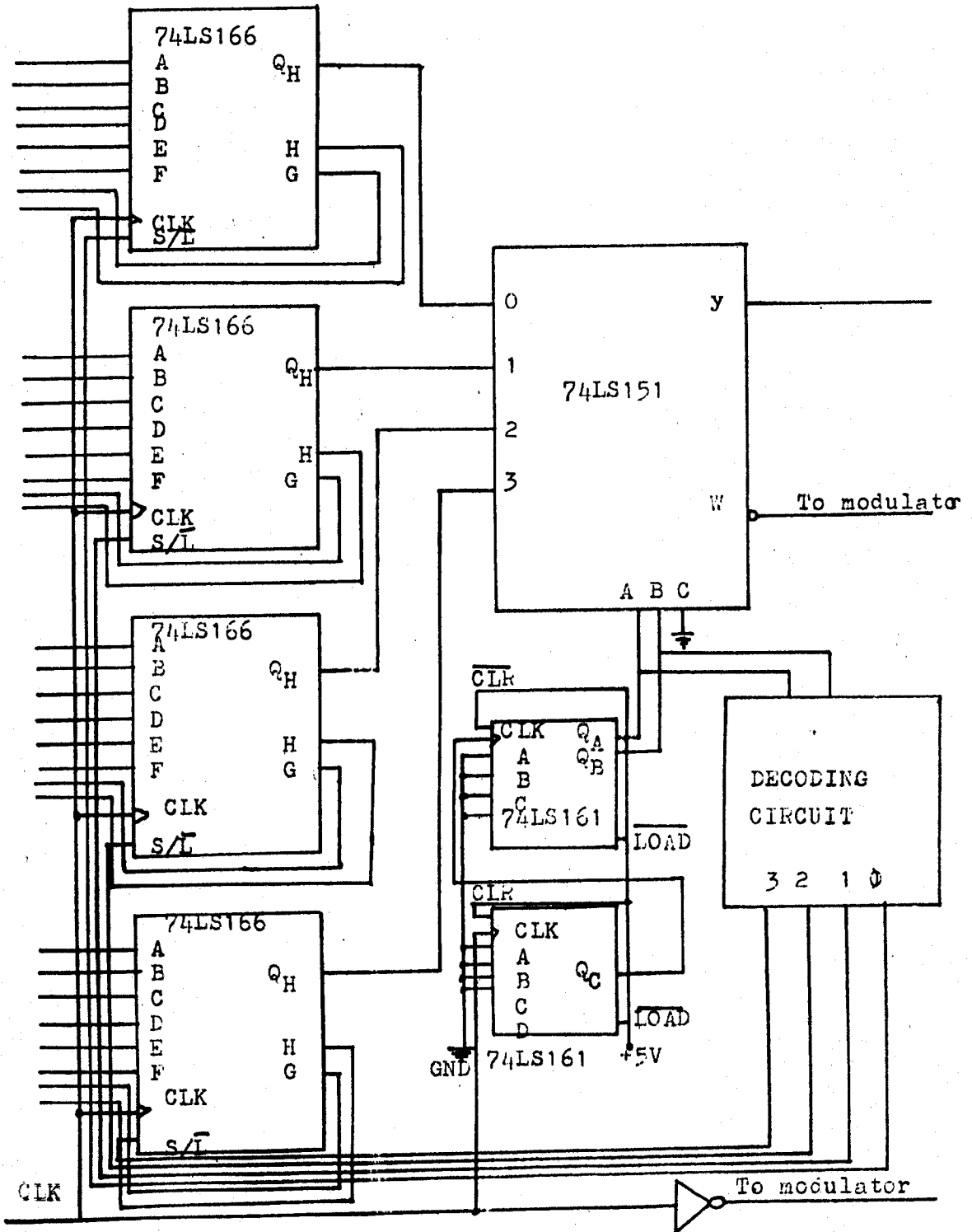

DECODING CIRCUIT

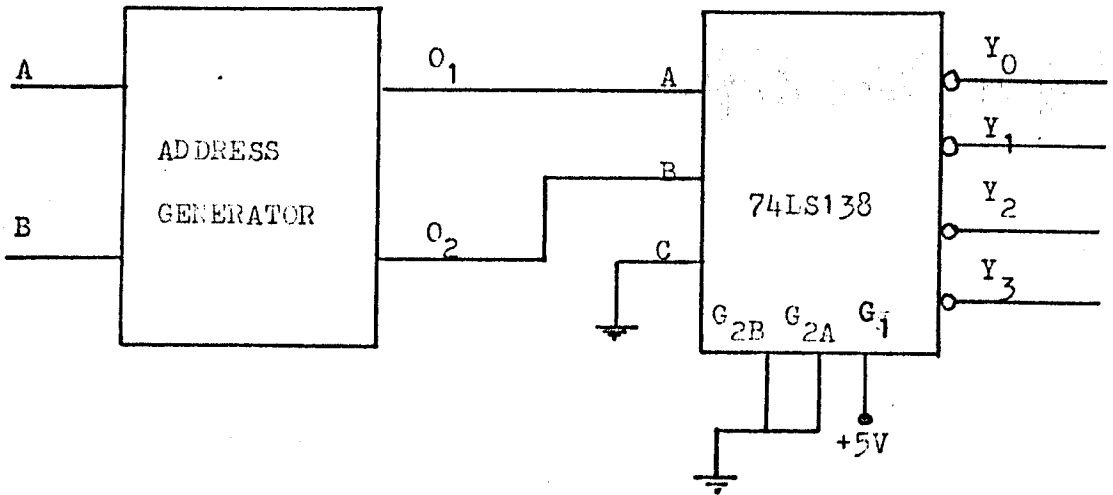


ADDRESS GENERATOR

TRUTH TABLE

INPUTS		OUTPUTS	
B	A	O ₁	O ₂
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

BLOCK DIAGRAM

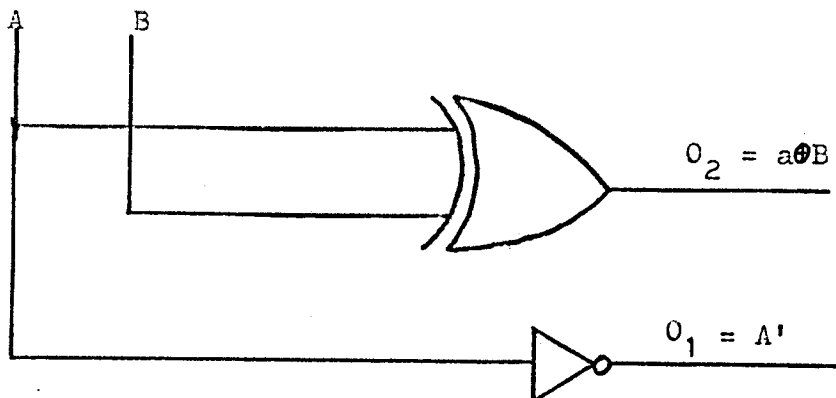

DEMODULATION TECHNIQUES

Demodulation can be performed in two ways;

1. XORing the data with the Manchester code to extract the clock

2. XORing the clock with the Manchester code to extract the data


MANCHESTER CODE




DATA



CLOCK

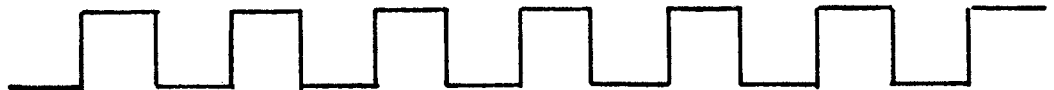

XORING THE CLOCK WITH THE CODE

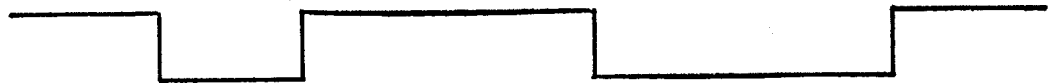


XORING THE DATA WITH THE CODE




MANCHESTER CODE DEMODULATOR

MODULATED
DATA
INPUT

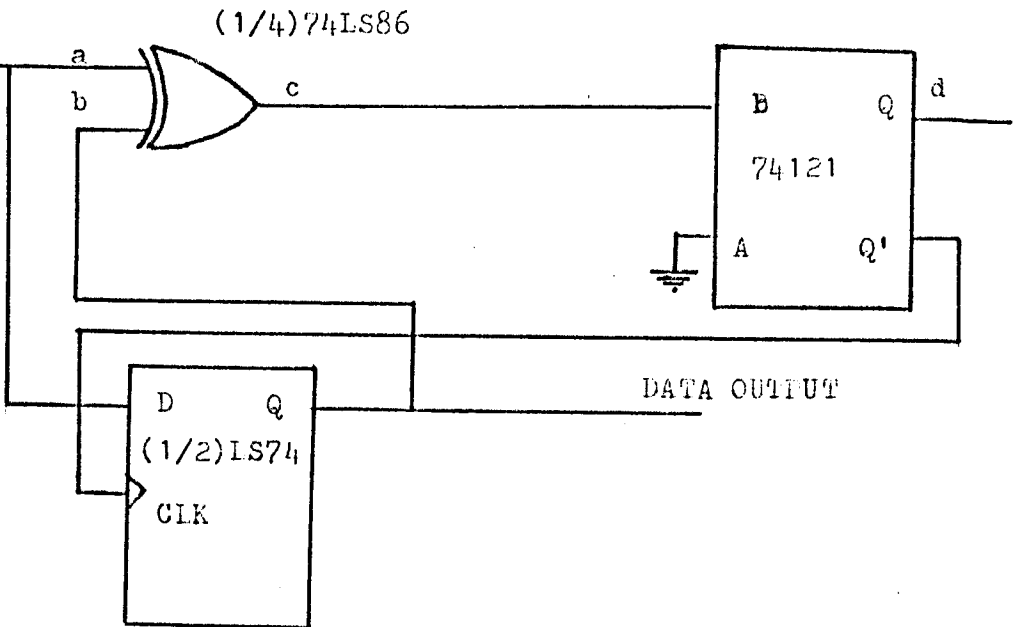


WAVEFORMS

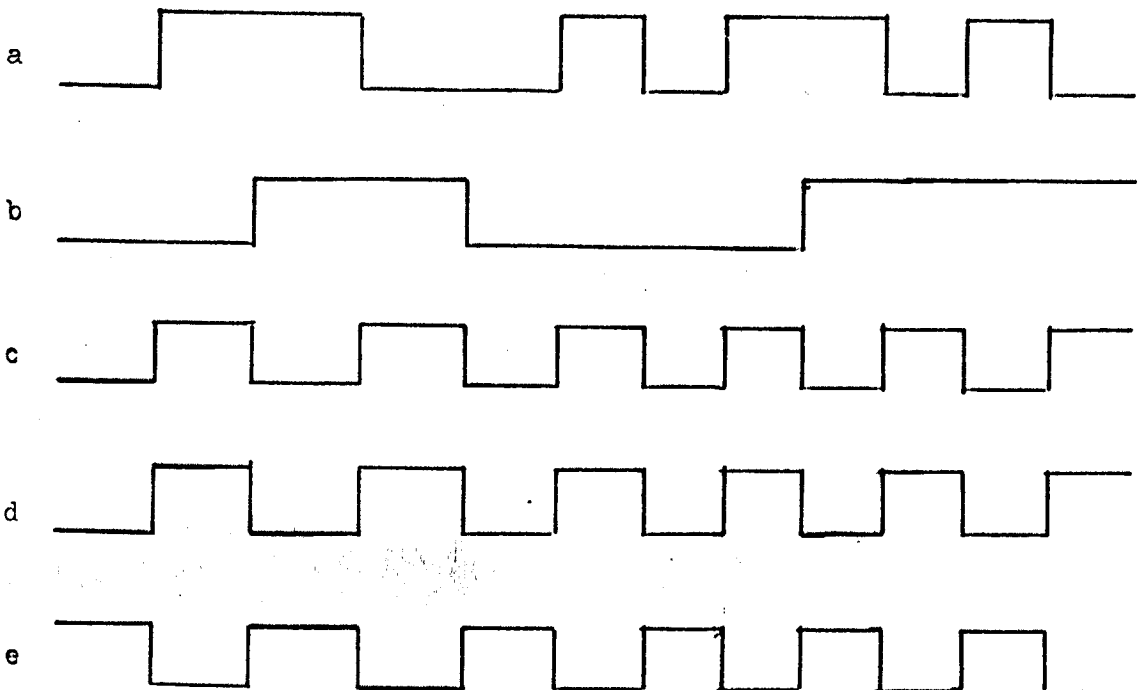


DEMULTIFLEXER

INVERTED DATA

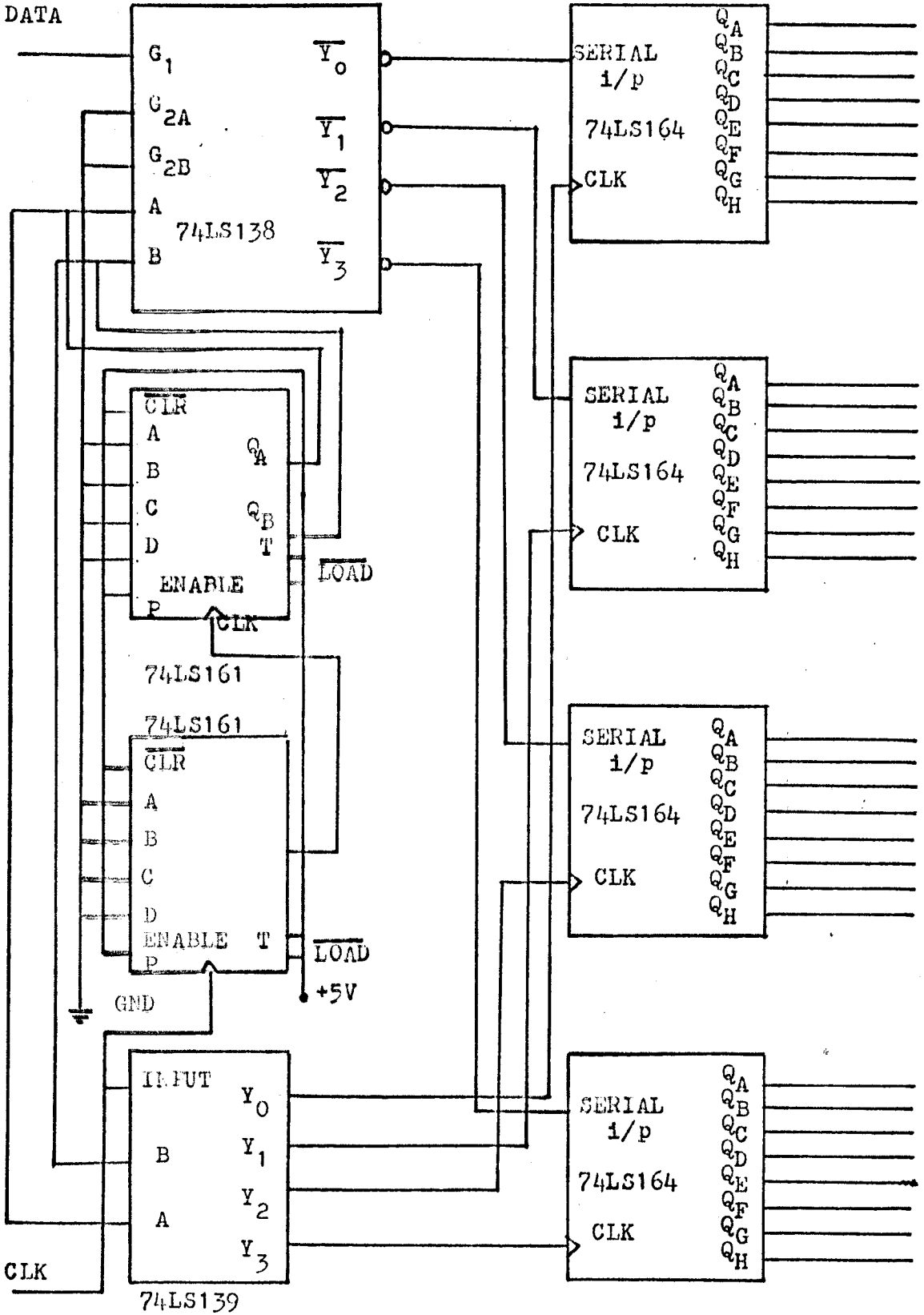

DATA STORAGE CIRCUIT

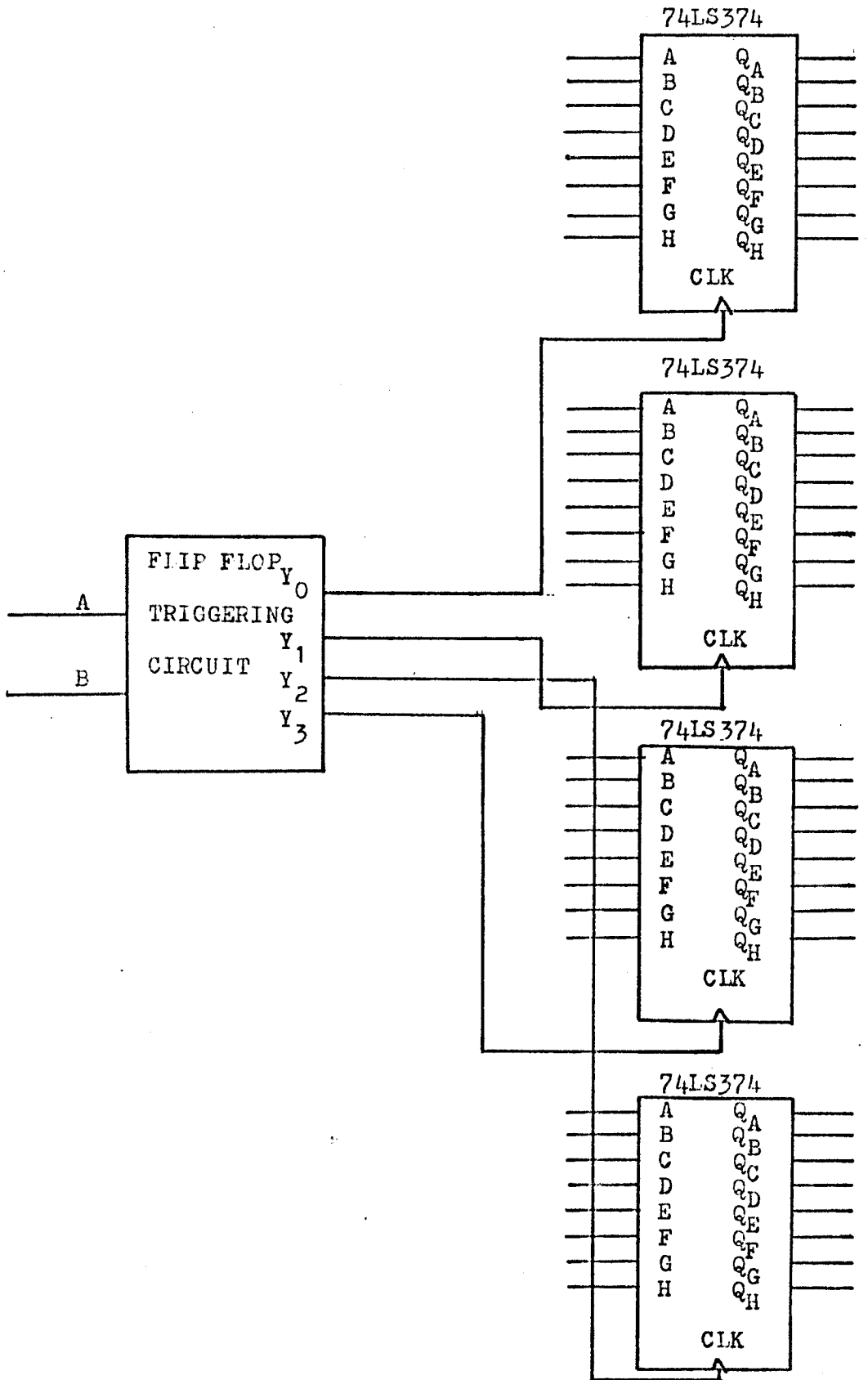


FLIP FLOP TRIGGERING CIRCUIT


TRUTH TABLE

INPUTS		OUTPUTS			
B	A	Y_0	Y_1	Y_2	Y_3
0	0	0	0	0	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	1	0


BLOCK DIAGRAM

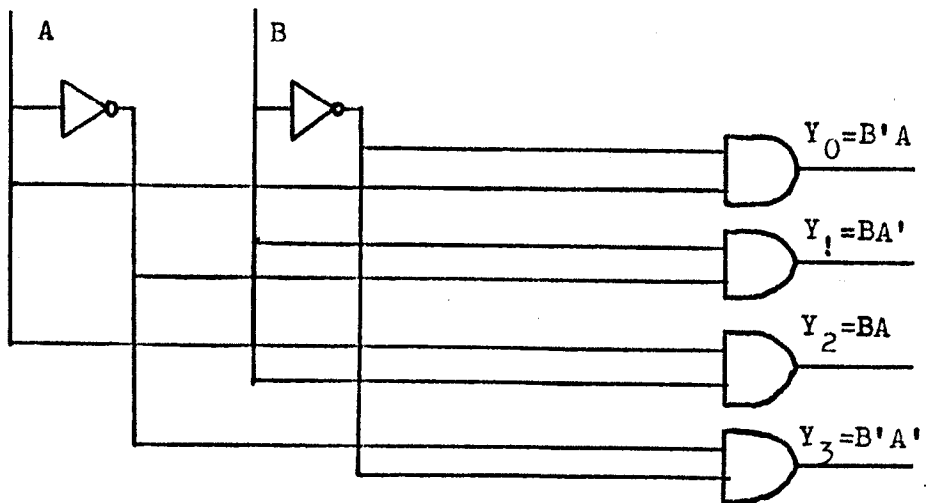


PARITY GENERATION AT THE TRANSMITTER

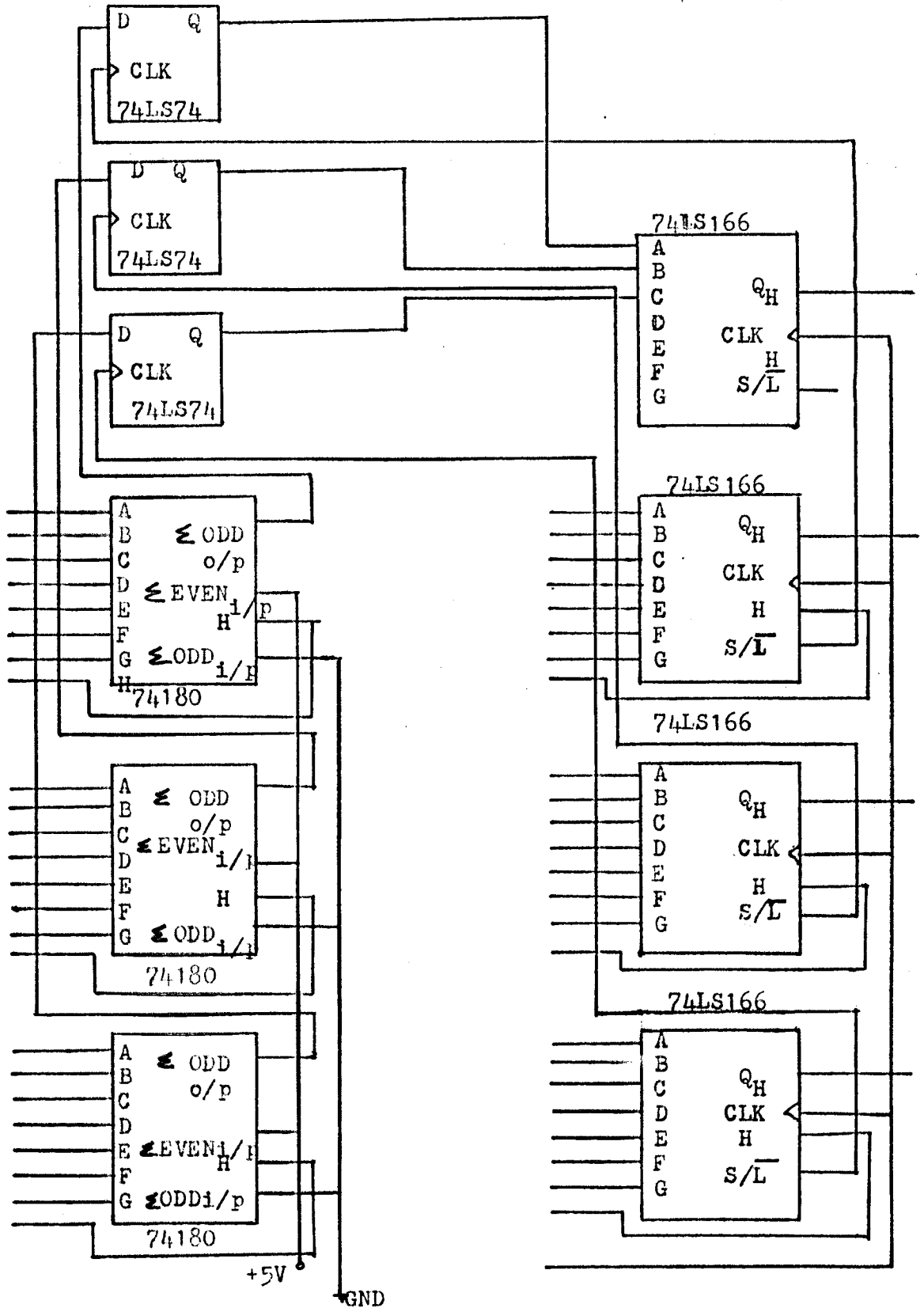

ERROR DETECTION AT THE RECEIVER

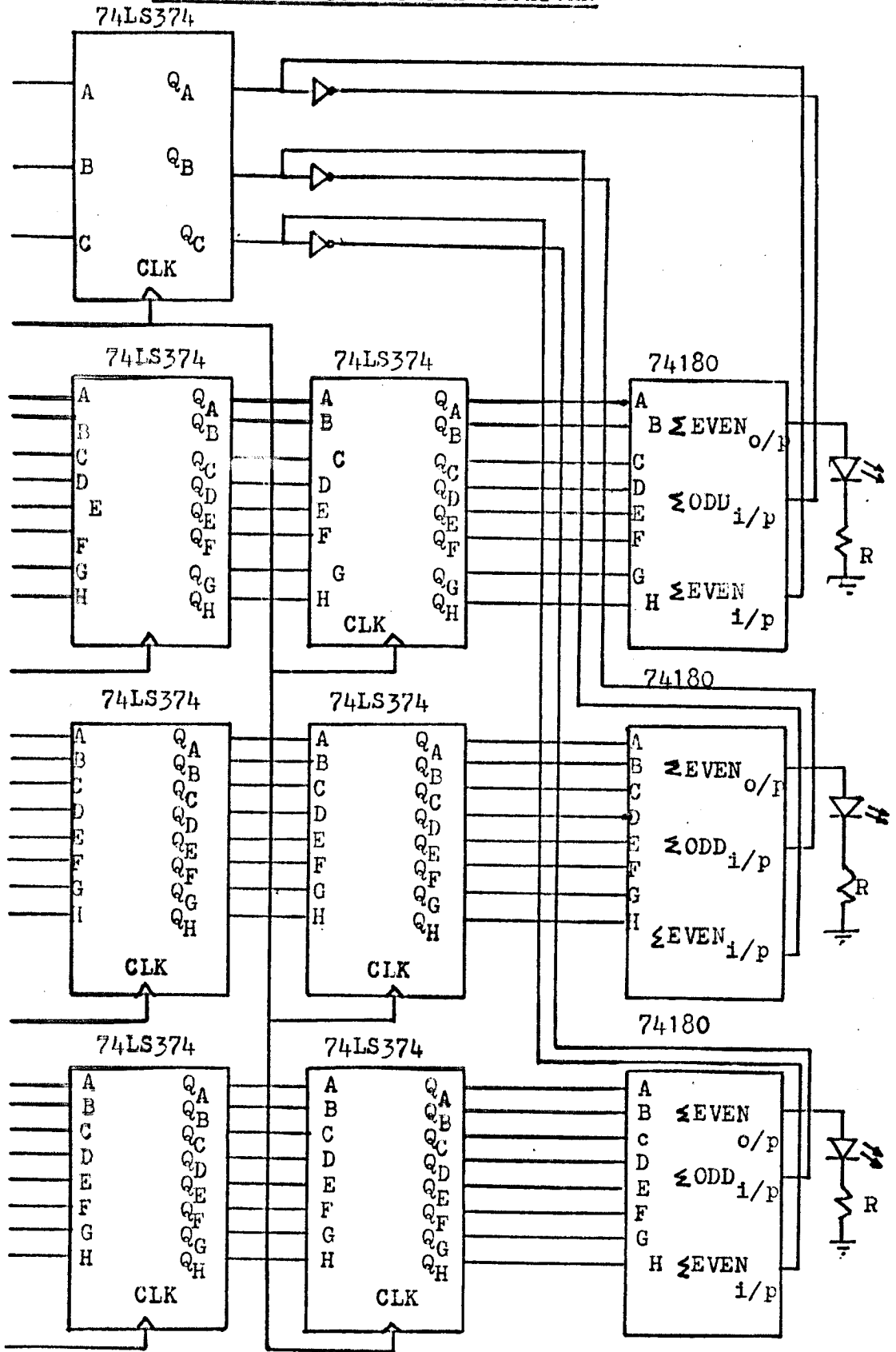

INTERFACING THE EMITTER

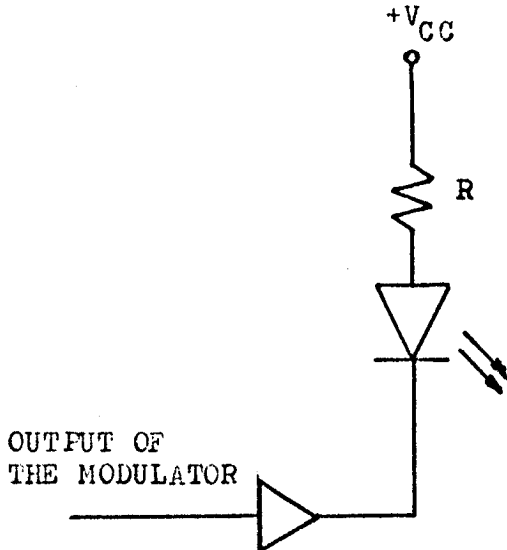

$$I_{FMAX} = 100 \text{ mA}$$

Operating at 70% of the maximum ratings

$$V_F (\text{typ}) = 1.6 \text{ V}$$

$$R = (V_{CC} - V_F - V_{CESAT}) / I_F$$

$$R = (5 - 1.6 - 0.2) / 70 \text{ mA}$$

$$= 45.71 \Omega$$

INTERFACING THE DETECTOR

