



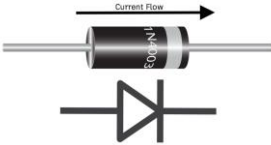


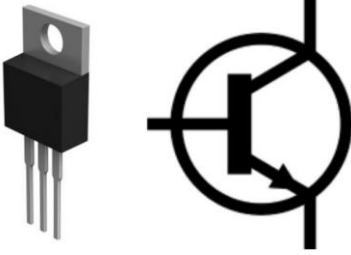

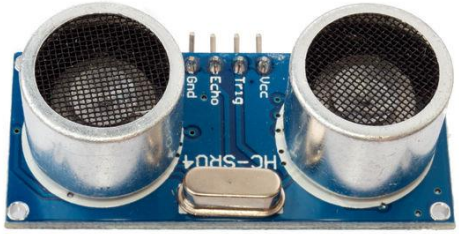
1. What is Electronics?

Electronics is the study and use of **electricity to control the flow of electrons** in circuits to make devices work.

- Think of electricity as **water flowing in pipes**.
- Electronics is like **valves, taps, and pumps** that control how water flows.

2. Basic Components of Electronics

Component	Symbol	Function	Simple Example
Battery / Power Supply		Provides voltage (energy)	9V battery in a toy car
Resistor		Limits current flow	Makes an LED safe from burning
LED		Emits light when current passes	Indicator light on a device
Capacitor		Stores electrical charge	Helps smooth power supply in phones
Diode		Allows current in one direction	Protects circuits from reverse polarity

Component	Symbol	Function	Simple Example
<p>Transistor</p>	 <p>Transistor Symbol</p>	<p>Acts like a switch or amplifier</p>	<p>Turns a small signal into a bigger one</p>
<p>Switch</p>		<p>Turns circuit on/off</p>	<p>Light switch in your room</p>
<p>Sensor</p>		<p>Detects something (light, distance, temp)</p>	<p>HC-SR04 for distance, LDR for light</p>

3. Voltage, Current, and Resistance

1. **Voltage (V)** – Pushes electrons through a circuit.
 - Like water pressure in a pipe.
 - Example: 5V from Arduino can power an LED.
2. **Current (I)** – Flow of electrons (measured in Amperes, A).
 - Like water flowing through the pipe.
 - Example: LED draws 20 mA (0.02 A) to glow.
3. **Resistance (R)** – Limits current flow (measured in Ohms, Ω).
 - Like a narrow section in the pipe slowing water.
 - Example: Using 220 Ω resistor to limit current to LED.

Ohm's Law:

$$V=I \times R \quad V = I \times R$$

- **Example:** 5V supply, 220 Ω resistor $\rightarrow I = 5 / 220 \approx 0.023$ A (23 mA)