

EE 437 HARDWARE PROJECT

II

PART 1: 4TH ORDER BUTTERWORTH LOW PASS FILTER

MELTEM DOGANER
ÖMER RAGIP ÖZKAN

4th Order Butterworth Low Pass Filter:

Cascaded Design

The filter asked for to design was a low pass filter with $f_c=2$ kHz. In the look up table this line below is shown.

F_{01}	Q_1	F_{02}	Q_2
1	0.541	1	1.306

$$F_0 = f_{0(\text{table})} \times f_c$$

$$\text{So } F_{01} = 1 \times 2 = 2 \text{ kHz}$$

$$F_{02} = 1 \times 2 = 2 \text{ kHz}$$

It was known that to avoid loss of dynamic range and filter accuracy due to possible signal clipping in the high Q sections, the sections are cascaded in order of ascending Q's. In this design two unity gain Sallen-Key sections are used.

Design Procedures:

i) For $Q_1 = 0.541$

1) C is chosen **10nF**,

2) $4Q^2 = 4 \times (0.541)^2 = 1.171$ let $n=2.2$ so $nC=$ **22nF**

3) $k = \frac{n}{2Q^2} - 1 = 2.758$

$$m = k + \sqrt{(k^2 - 1)} = 5.328$$

4) $R = \frac{1}{\sqrt{(mn)} \cdot 2\pi \cdot f_0 \cdot C} = 2324 \Omega$ for a 1% value it is chosen **2,32 kW**,

mR is also chosen as $5.328 \times 2324 = 12382 \Omega$ for a 1% value it is chosen

$$mR = \mathbf{12.4 kW}$$

ii) For $Q_2 = 1.306$

1) C is chosen **10nF**,

2) $4Q^2 = 4 \times (1.306)^2 = 6.822$ let $n = 10$ so $nC =$ **100nF**


$$3) \quad k = \frac{n}{2Q} - 1 = 1.931$$

$$m = k + \sqrt{(k^2 - 1)} = 3.583$$


$$4) \quad R = \frac{1}{\sqrt{(mn) \cdot 2p \cdot f_0 \cdot C}} = 1329 \, \Omega \text{ for a 1\% value it is chosen } \mathbf{1.33 \, kW}$$

mR is also chosen as $3.583 \times 1329 = 4762 \, \Omega$ for a 1% value it is chosen

mR = **4.75 kW**

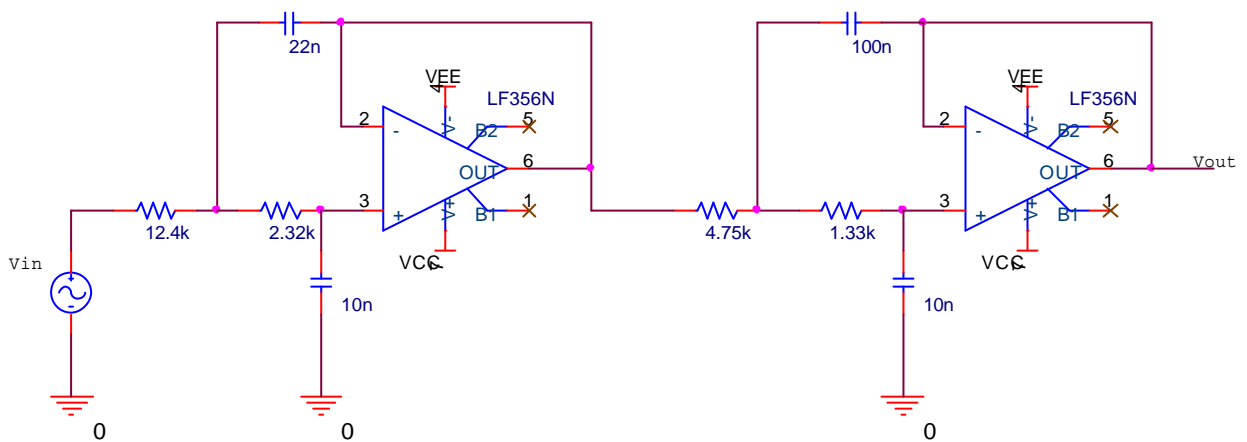

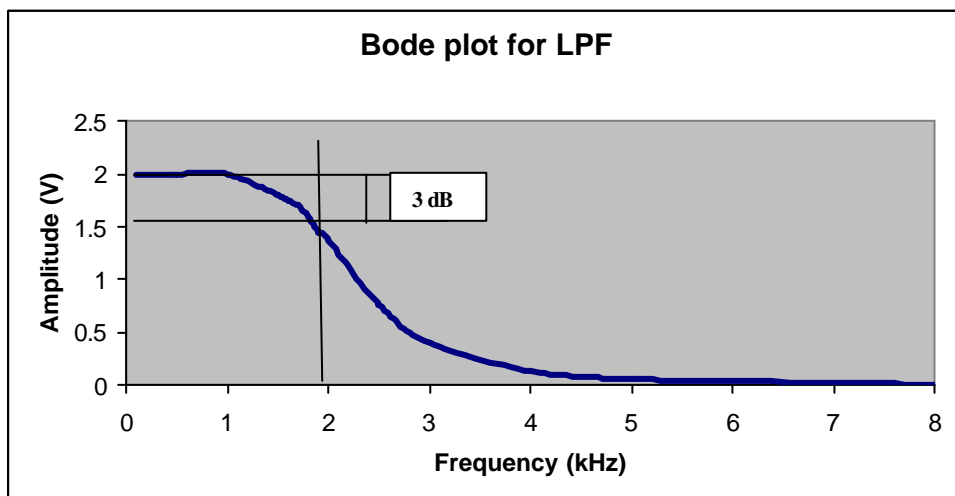According to design values and circuit diagram above the bode plot below is obtained.



1.97 kHz was measured as the cut off frequency point for our low pass filter design.

EE 437 HARDWARE PROJECT

II

PART 2: 3rd ORDER CHEBYSHEV HIGH PASS FILTER

MELTEM DOGANER
ÖMER RAGIP ÖZKAN

3rd Order Chebyshev (1.0 dB Ripple) High Pass Filter

Direct Design

The filter asked for to design was a high pass filter with $f_c=1$ kHz. In the look up table this line below is shown.

L_1	C_2	L_3
2.0236	0.9941	2.0236

In conversion we would like to obtain $C_{1(new)} = \mathbf{10\ nF}$

$$C_{1(new)} = \frac{1}{(k_z \omega_c L_{1(old)})} \text{ so } k_z = 7865$$

$R_{new} = k_z/R_{old}$ for $R_{old} = 1\Omega$, $R_{new} = 7865\ \Omega$ In this design with 1% sensitivity

7.87 kW is used.


$$C_{3(new)} = C_{1(new)} = \mathbf{10\ nF}$$

$$L_{2(new)} = \frac{k_z}{\omega_c C_{2(old)}} = \frac{7865}{2\pi \cdot 1000 \cdot 0,9941} = 1.2592H$$


In order to find GIC realization of L;

$C_2 = \mathbf{10\ nF}$ is chosen and all R values are assumed to be equal.

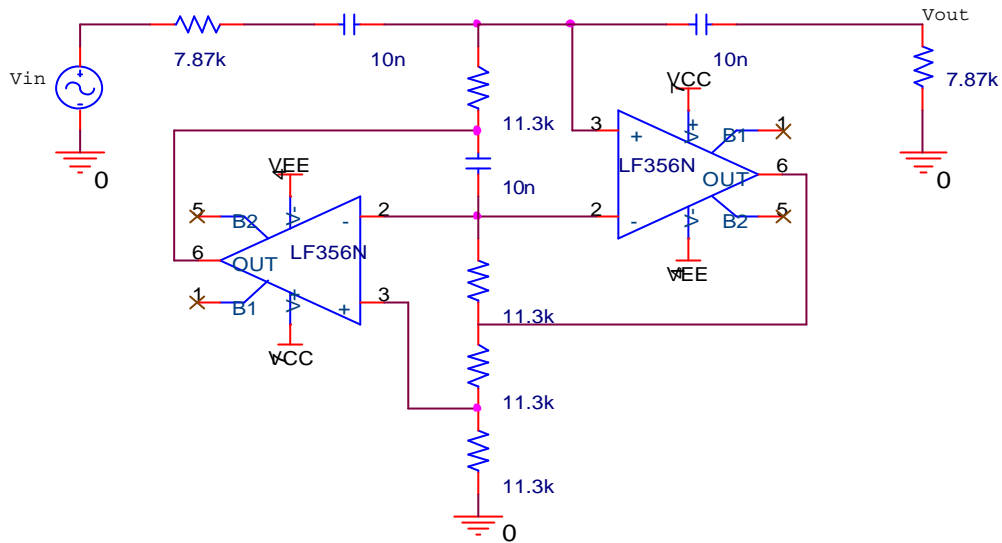$L = R^2 \times C$ so $1.2592 = R^2 \times 10 \times 10^{-9}$ R is found to be 11221Ω . In this design with 1% sensitivity, it is used as **11.3 kW**



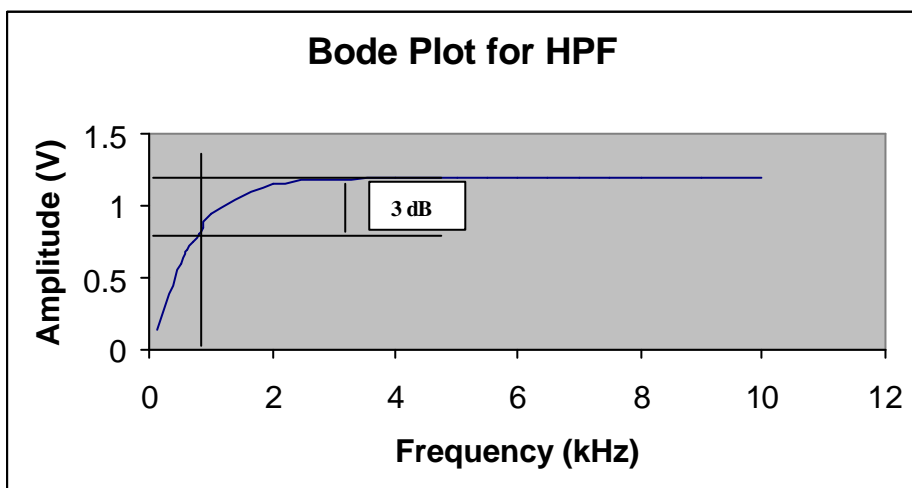According to design values and circuit diagram above the bode plot below is obtained.



870 Hz was measured as the cut off frequency point for our high pass filter design.