



CALEDONIAN COLLEGE OF ENGINEERING, OMAN

Session : 2003 – '04

DIET :

Level : II

Module Leader :

Jan 2004

Duration : TWO Hours

**Analogue Electronics
(ENGE 254)**

CANDIDATES SHOULD ATTEMPT ANY FOUR FULL QUESTIONS

PLEASE READ THE QUESTIONS CAREFULLY

MATERIALS TO

BE SUPPLIED/ALLOWED:

Question paper (Supplied)

Blank Examination Script (Supplied)

Non-programmable calculator (Allowed)

- Q1 (a) Explain the characteristics and functions of Emitter, Base and Collector regions of a BJT transistor. [6]
- (b) (i) Derive the relation between β_{DC} and α_{DC} . [4]
- (ii) For a BJT, $I_B = 40\mu A$, and $I_C = 2.65mA$. Determine β_{DC} , and α_{DC} . [4]
- (c) The common emitter short circuit current gain (β_{DC}) of the transistor shown in Fig.Q1-c is 150.

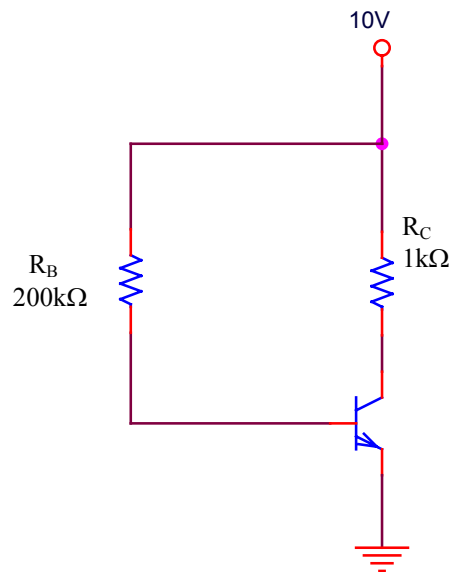


Fig. Q1-c

Determine

- (i) the values of I_B , I_C and V_{CE} . [9]
- (ii) the region of operation. [2]

- Q2 (a) Explain with the aid of equations why the base bias circuit is considered an unstable biasing condition. [10]
- (b) (i) Sketch the circuit diagram of a tuned amplifier and explain its operation. [4]
- (ii) State why a tuned amplifier is not used for audio applications. [4]
- (c) With the aid of diagrams explain the operation of an N-channel D-MOSFET. [7]

- Q3 (a) For the oscillator circuit block diagram shown in fig. Q3-a the feedback factor is $1/29$ and the phase shift around the closed loop is 0° . What should be the gain of amplifier for sustained oscillation? [3]

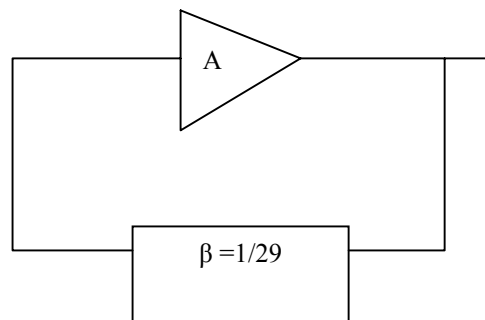


Fig.Q3-a

- (b) For the oscillator circuit shown in Fig.Q3-b, identify its type and find the gain required to sustain oscillation. Determine the value of R_f required to sustain this gain. Find the frequency of oscillation. [10]

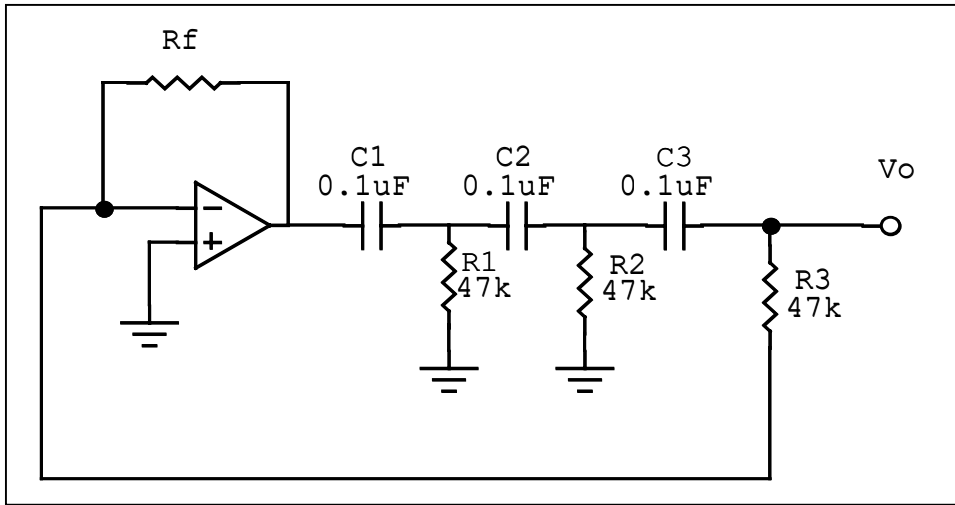


Fig.Q3-b

- (c) Sketch a crystal oscillator circuit and explain its operation. [5]
- (d) Design a Hartley oscillator to operate on frequency of 45kHz. Sketch the circuit diagram of the oscillator. [7]

- Q4 (a) Explain with the aid of equations common mode rejection ratio and slew rate. [5]
- (b) For the circuit shown in Fig.Q4-b, calculate the magnitude of the output voltage, assuming ideal operational amplifiers. [10]

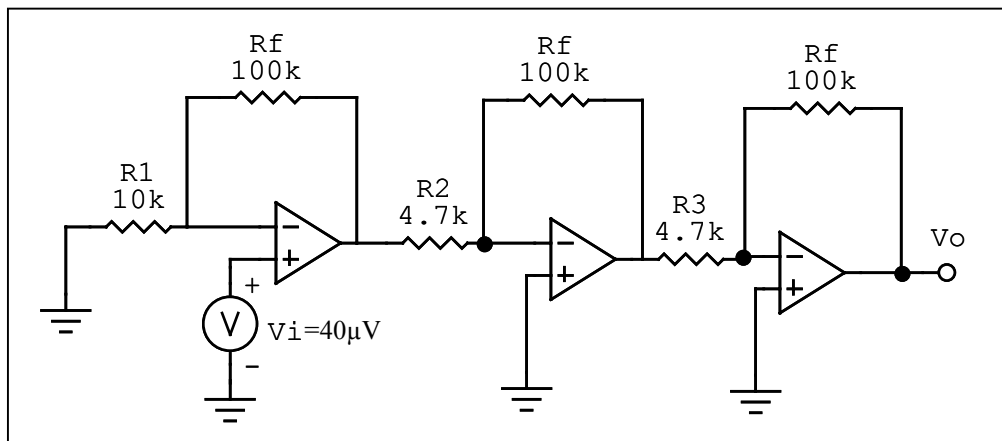


Fig.Q4-b

- (c) State the important features and application of the Voltage follower. [5]
- (d) Sketch the circuit diagram and the output waveform of the zero level comparator. [5]

- Q5 (a) State the advantages of active filters over passive filters. [3]
- (b) Design a 2nd order LPF with cutoff frequency equal to 15kHz and gain equal to 1.586. Sketch the filter circuit and frequency response. [9]
- (c) Sketch the general frequency response curve for a band pass filter. [5]
- (d) With the aid of block diagrams explain the operation of a band stop filter and sketch the frequency response. [8]
- Q6 (a) Identify the circuit shown in Fig.Q6-a. Find the values of T_{on} , T_{off} , the frequency of oscillation and the duty cycle. [10]

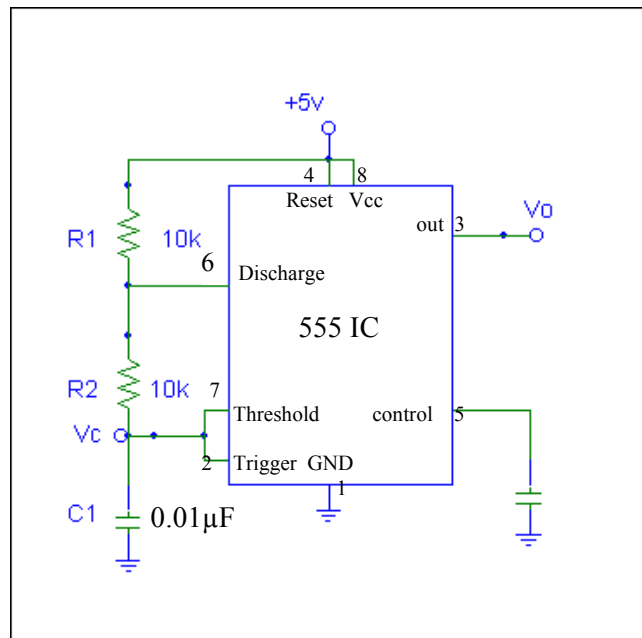


Fig.Q6-a

- (b) Sketch the waveforms at pin 2 and pin 3 for the circuit shown in Fig.Q6-a. [4]
- (c) Briefly explain how light is conducted through an optical fiber. [5]
- (d) State the advantages of using optical fibers over traditional copper wires in communication systems. [6]

END OF QUESTION PAPER

