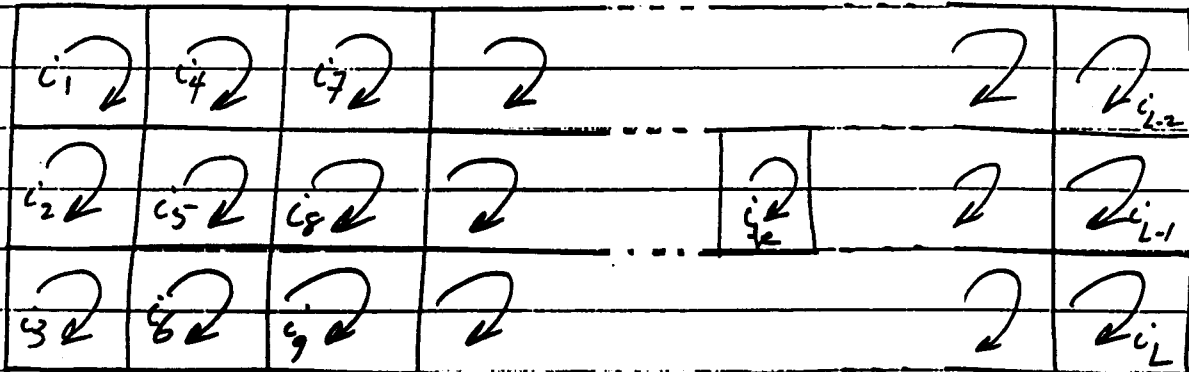


# ENEL 341 Circuits I

## Loop Variable Analysis

Consider a complex network with  $L$  independent loops, as shown in the graph below:



Each of the above  $L$  loops may contain  $R, L$  and  $C$  in any one or all the branches that make up the loop.

Let us consider the  $k$ th loop and define:

$R_{kk}$  to be the total resistance in loop  $k$ ;

$L_{kk}$  " " " " inductance " " " ";

$D_{kk}$  " " " " elastance " " " ";

$R_{kj}$  " " " " resistance common between loops  $k$  and  $j$ ;

$L_{kj}$  " " " " inductance " " " ";

$D_{kj}$  " " " " elastance " " " ";

Note that  $D_{kk} = D_1 + D_2 + \dots = \frac{1}{C_1} + \frac{1}{C_2} + \dots = \frac{1}{C_{kk}}$

Writing KVL at loop  $k$  yields,

$$\left[ R_{kk} + L_{kk} \frac{d}{dt} + D_{kk} \int dt \right] i_k(t) - \sum_{\substack{j=1 \\ j \neq k}}^L \left[ R_{kj} + L_{kj} \frac{d}{dt} + D_{kj} \int dt \right] i_j(t) = \pm V_k$$

Voltage drop in loop  $k$  produced by current in loop  $k$

Voltage drops in loop  $k$  produced by currents flowing in all other neighbouring loops

voltage sources in loop  $k$ .

(+) if  $V_k$  force current in the

same direction

as  $i_k$

(-) if otherwise.

$$k = 1, 2, \dots, L$$

$$\sum_{j=1}^L a_{kj} i_j(t) = V_k, \quad k = 1, 2, \dots, L$$

where  $a_{kj} = \left[ R_{kj} + L_{kj} \frac{d}{dt} + D_{kj} \int dt \right]$

$$a_{kk} = R_{kk} + L_{kk} \frac{d}{dt} + D_{kk} \int dt$$


"OR"

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_k \\ \vdots \\ V_L \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} & \dots & a_{1L} \\ a_{21} & a_{22} & \dots & a_{2L} \\ \vdots & \vdots & \ddots & \vdots \\ a_{L1} & a_{L2} & \dots & a_{LL} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_L \end{bmatrix}$$

"OR"  $\underline{V} = \underline{A} \underline{i}$

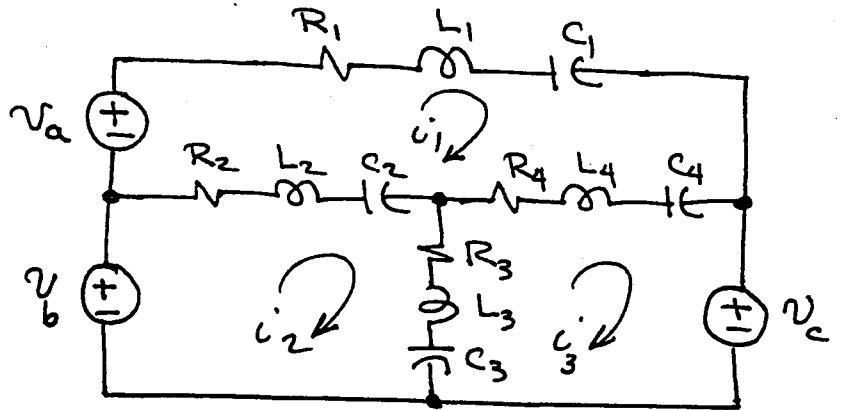Examples: (1) Passive R, L, C circuits.

$$a_{11} = (R_1 + R_2 + R_4) + (L_1 + L_2 + L_4) \frac{d}{dt} + (D_1 + D_2 + D_4) \int dt$$



$$a_{22} = (R_2 + R_3) + (L_2 + L_3) \frac{d}{dt} + (D_2 + D_3) \int dt$$

$$a_{33} = (R_3 + R_4) + (L_3 + L_4) \frac{d}{dt} + (D_3 + D_4) \int dt.$$

$$a_{12} = -R_2 - L_2 \frac{d}{dt} - D_2 \int dt = a_{21}$$

$$a_{13} = -R_4 - L_4 \frac{d}{dt} - D_4 \int dt = a_{31}$$

$$a_{23} = -R_3 - L_3 \frac{d}{dt} - D_3 \int dt = a_{32}$$


$$V_1 = v_a, \quad V_2 = v_b \quad \text{and} \quad V_3 = -v_c$$

Note that if the voltage source <sup>(drives)</sup> the current in a loop in the same direction then the plus sign is used, otherwise, the (-) sign is used.

Note that in the above example  $A$  is symmetric; i.e.,  
 $a_{ij} = a_{ji}$ .

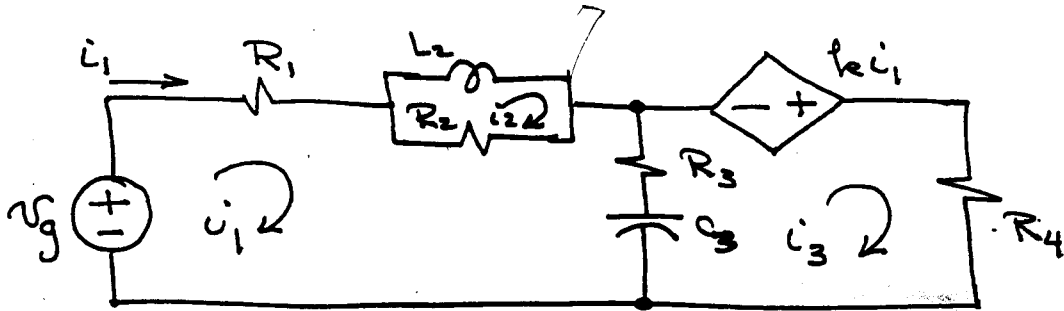Example (2): Active circuits:

Write a set of equilibrium equations on the loop basis to describe the network in the fig. below. Note that the Net. contains one controlled source. Collect terms in your formulation so that your equations have the general form  $A\underline{i} = \underline{V}$ .



Controlled sources:

$v = k i_x$  CCVS

$v = k v_x$  VCVS (Opamp)

$i = k i_x$  CCCS Bipolar

$i = k v_x$  VCCS Fet



Controlled Voltage Source



Controlled current source

- (a) diamond shape
- (b) dot physically exist.

$a_{11} = (R_1 + R_2 + R_3) + D_3 \int dt$

$a_{12} = -R_2 = a_{21}$

$a_{13} = -R_3 - D_3 \int dt = a_{31}$

$a_{22} = R_2 + L_2 \frac{d}{dt}$

$a_{23} = 0 = a_{32}$

$a_{33} = (R_3 + R_4) + D_3 \int dt$

$v_1 = v_g$

$v_2 = 0$

$v_3 = k i_1$

$$a_{11}i_1 + a_{12}i_2 + a_{13}i_3 = v_1$$

$$a_{21}i_1 + a_{22}i_2 + a_{23}i_3 = v_2$$

$$a_{31}i_1 + a_{32}i_2 + a_{33}i_3 = v_3$$

In matrix form:

$$\begin{bmatrix} R_1 + R_2 + R_3 + \frac{1}{C_3} \int dt & -R_2 & -R_3 - \frac{1}{C_3} \int dt \\ -R_2 & R_2 + L_1 \frac{d}{dt} & 0 \\ -R_3 - \frac{1}{C_3} \int dt & 0 & R_3 + R_4 + \frac{1}{C_3} \int dt \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_a \\ 0 \\ v_{b1} \end{bmatrix}$$

"OR"

$$\begin{bmatrix} R_1 + R_2 + R_3 + \frac{1}{C_3} \int dt & -R_2 & -R_3 - \frac{1}{C_3} \int dt \\ -R_2 & R_2 + L_1 \frac{d}{dt} & 0 \\ -R_3 - \frac{1}{C_3} \int dt & 0 & R_3 + R_4 + \frac{1}{C_3} \int dt \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_a \\ 0 \\ 0 \end{bmatrix}$$

$$A i = V$$


Note that A is not symmetric.

Comments:

In Loop analysis all current sources in loops should be converted to voltage sources. In this case the variables will be the loop's currents.
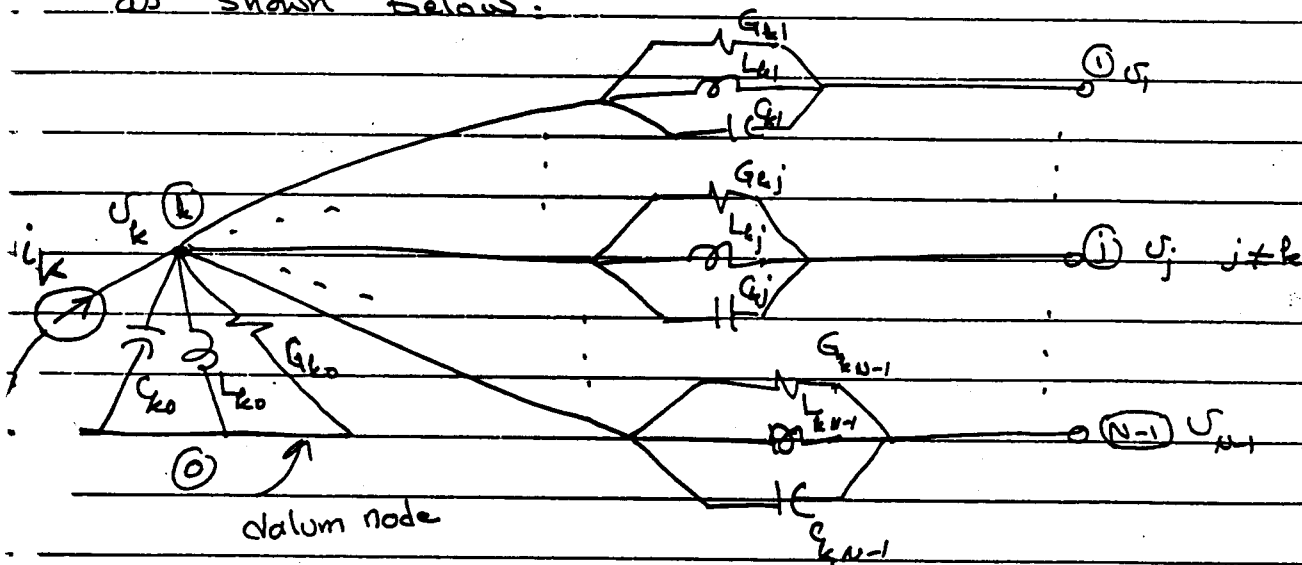
## Node Variables Analysis

Let us consider a net. with  $N$  nodes and only one part. Assign a node to be a reference node (datum) node. In this case the variables are the  $(N-1)$  node-datum voltages  $(V_1, V_2, \dots, V_{N-1})$  as shown below:



Define =

$$G_{kj} = \text{sum of all conductance bet. nodes } k \text{ and } j$$

$$\frac{1}{L_{kj}} = \text{sum of the reciprocal of inductance bet. nodes } k \text{ and } j$$

$$C_{kj} = \text{sum of all cap. bet. nodes } k \text{ and } j$$

Writing KCL @  $k$  yields

$$i_k = \left( G_{k0} + C_{k0} \frac{d}{dt} + \frac{1}{L_{k0}} \int dt \right) V_k + \sum_{\substack{j=1 \\ j \neq k}}^{N-1} \left[ G_{kj} + C_{kj} \frac{d}{dt} + \frac{1}{L_{kj}} \int dt \right] (V_k - V_j)$$

$\uparrow$  note  $i_k > 0$  in (entering)  
 $i_k < 0$  out (leaving)

$k = 1, 2, \dots, N-1$

"OR"

$$i_k = \sum_{j=1}^{N-1} b_{kj} V_j, \quad k = 1, 2, \dots, N-1$$

where  $b_{kj} = \begin{cases} G_{kj} - C_{kj} \frac{d}{dt} - \frac{1}{L_{kj}} \int dt, & k \neq j \\ G_{kk} + C_{kk} \frac{d}{dt} + \frac{1}{L_{kk}} \int dt, & k = j \end{cases}$



"OR"

$$\underline{I} = \underline{B} \underline{U}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_k \\ \vdots \\ i_{N-1} \end{bmatrix} = \begin{bmatrix} b_{11} & b_{12} & \dots & b_{1,N-1} \\ b_{21} & b_{22} & \dots & b_{2,N-1} \\ \vdots & \vdots & \ddots & \vdots \\ b_{N-1,1} & b_{N-1,2} & \dots & b_{N-1,N-1} \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \\ \vdots \\ U_{N-1} \end{bmatrix}$$

$$i_{kk} = \sum_{j=1}^N \frac{V_j}{L_{jk}} \quad \text{and} \quad i_{kk} = \sum_{j=1}^N \frac{V_j}{L_{jk}}$$

Example: (1)

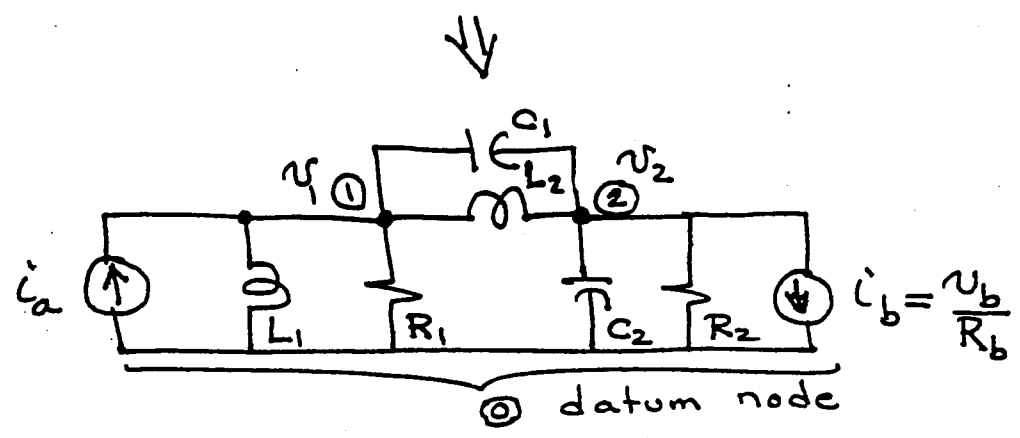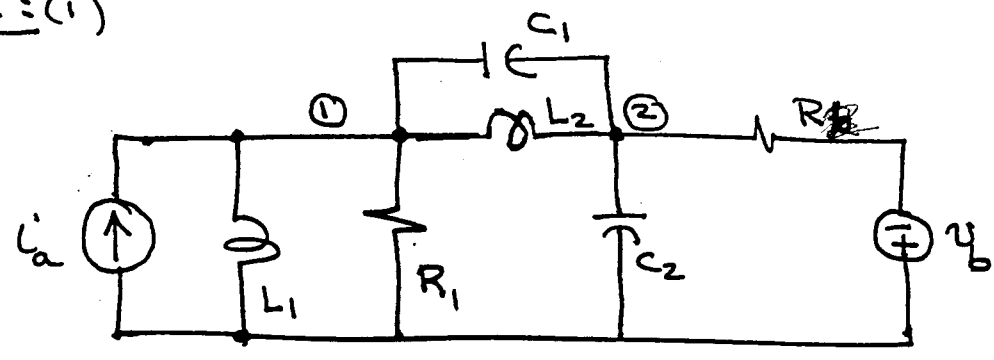

$N = 3 \quad (0, 1, 2)$

$$\left. \begin{aligned} i_1 &= \sum_{j=1}^2 b_{1j} v_j \\ i_2 &= \sum_{j=1}^2 b_{2j} v_j \end{aligned} \right\} \text{"OR"} \quad \begin{aligned} i_1 &= b_{11} v_1 + b_{12} v_2 \\ i_2 &= b_{21} v_1 + b_{22} v_2 \end{aligned}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad \text{OR} \quad i = B v$$

where,  $i_1 = i_a$ ,  $i_2 = -i_b$  and

Note that  $i$  is pos. if entering a node and neg. otherwise.

$$b_{11} = G_1 + C_1 \frac{d}{dt} + \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \int dt$$

$$b_{12} = b_{21} = -C_1 \frac{d}{dt} - \frac{1}{L_2} \int dt, \text{ and}$$



$$b_{22} = G_2 + (C_1 + C_2) \frac{d}{dt} + \frac{1}{L_2} \int dt$$

Thus,

$$\begin{bmatrix} i_a \\ -i_b \end{bmatrix} \begin{bmatrix} G_1 + C_1 \frac{d}{dt} + \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \int dt & -G_2 dt - \frac{1}{L_2} \int dt \\ -C_1 \frac{d}{dt} - \frac{1}{L_2} \int dt & G_2 + (C_1 + C_2) \frac{d}{dt} + \frac{1}{L_2} \int dt \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Note that B in this ex. is symmetric.


Example (2):

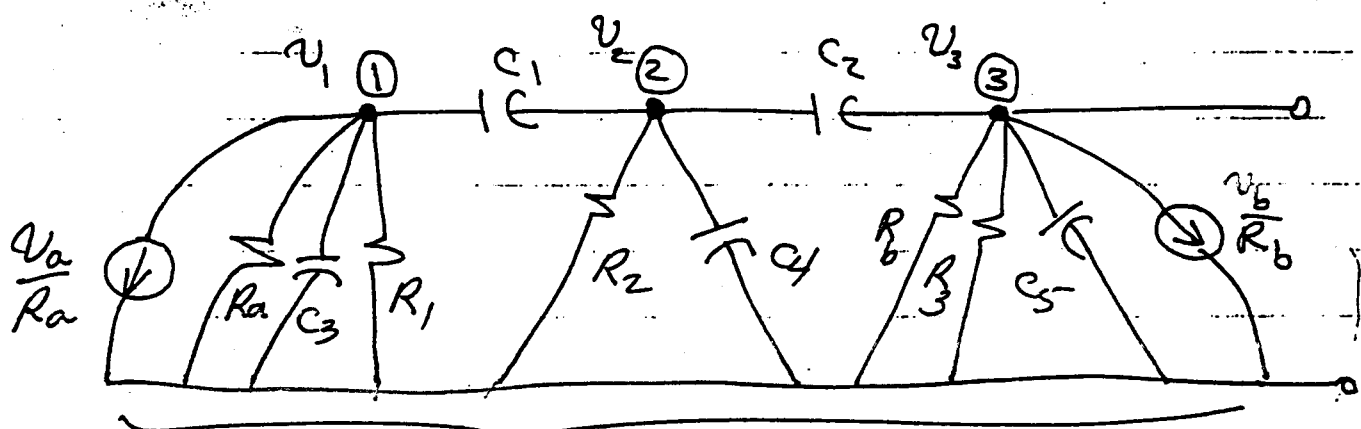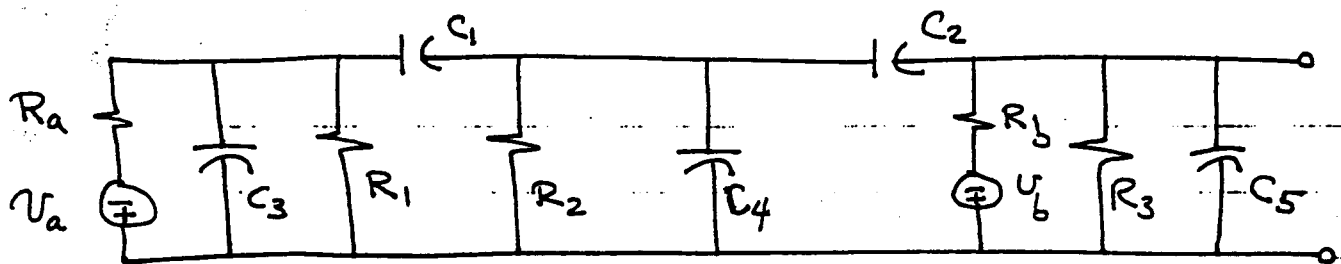


Datum Node

$$\text{Symmetric } \underline{\underline{B}} \begin{bmatrix} G_a + G_1 + (C_1 + C_3) \frac{d}{dt} & -C_1 \frac{d}{dt} & 0 \\ -C_1 \frac{d}{dt} & G_2 + (C_1 + C_2 + C_4) \frac{d}{dt} & -C_2 \frac{d}{dt} \\ 0 & -C_2 \frac{d}{dt} & (G_b + G_3) + (C_2 + C_3) \frac{d}{dt} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -\frac{v_a}{R_a} \\ 0 \\ -\frac{v_b}{R_b} \end{bmatrix}$$

Example (3)

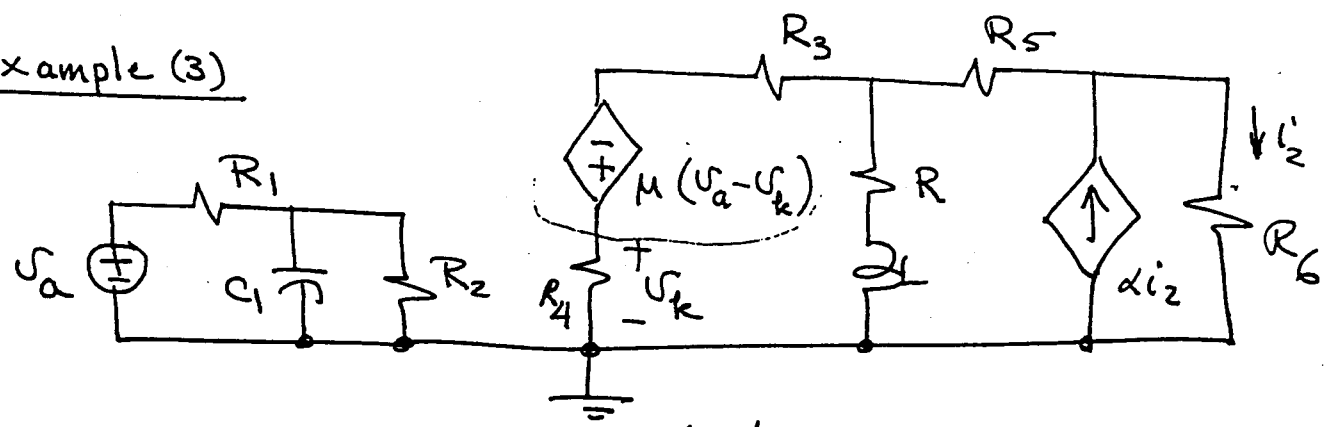

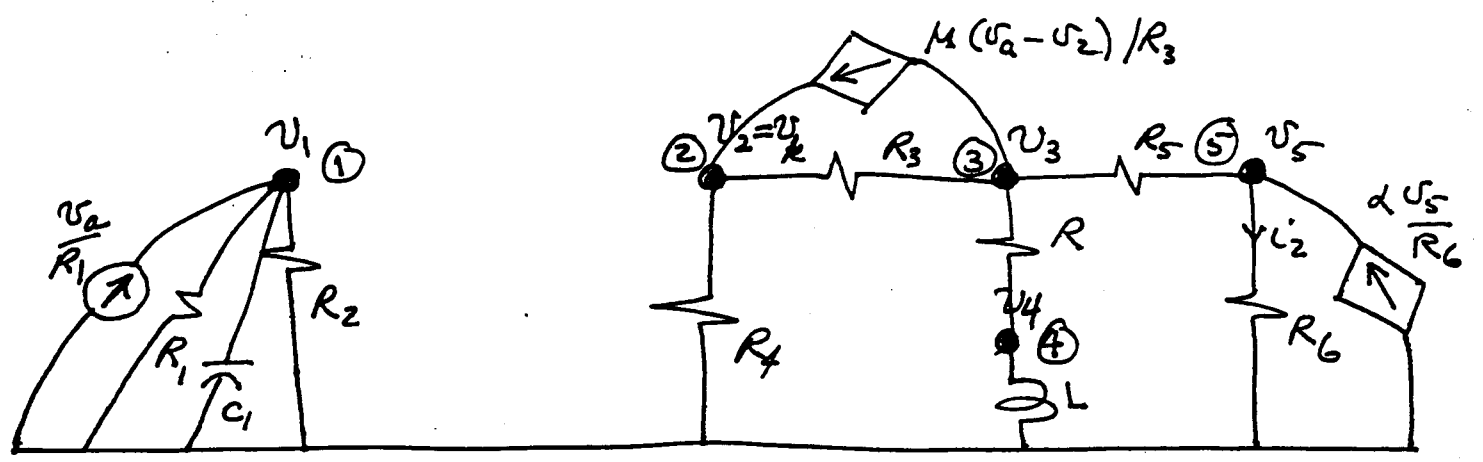Explain why  $R_3$  and  $V_{VS}$  (instead of  $R_4$  and  $V_{VS}$ ) are converted to current source.



$$b_{11} = (G_1 + G_2) + C_1 \frac{d}{dt}, \quad b_{12} = 0, \quad b_{13} = 0, \quad b_{14} = 0, \quad b_{15} = 0$$

$$b_{21} = 0, \quad b_{22} = G_3 + G_4, \quad b_{23} = -G_3, \quad b_{24} = 0, \quad b_{25} = 0$$

$$b_{31} = 0, \quad b_{32} = -G_3, \quad b_{33} = (G + G_3) + G_5, \quad b_{34} = -G, \quad b_{35} = -G_5$$

$$b_{41} = 0, \quad b_{42} = 0, \quad b_{43} = -G, \quad b_{44} = G + \frac{1}{L} \int dt, \quad b_{45} = 0$$

$$b_{51} = 0, \quad b_{52} = 0, \quad b_{53} = -G_5, \quad b_{54} = 0, \quad b_{55} = G_5 + G_6$$

$$i_1 = \frac{U_a}{R_1}, \quad i_2 = \mu(U_a - U_2)/R_3, \quad i_3 = -\mu(U_a - U_2)/R_3$$

$$i_4 = 0, \quad i_5 = \alpha \frac{U_5}{R_6}$$