

EE 1291

Electrical Engg (PART A)

D.ELANGOVAN

Chapter 2

Single phase circuits

Lecture 3



Single-phase Circuits

2.1 Basic definition

Single Phase Circuit

Review

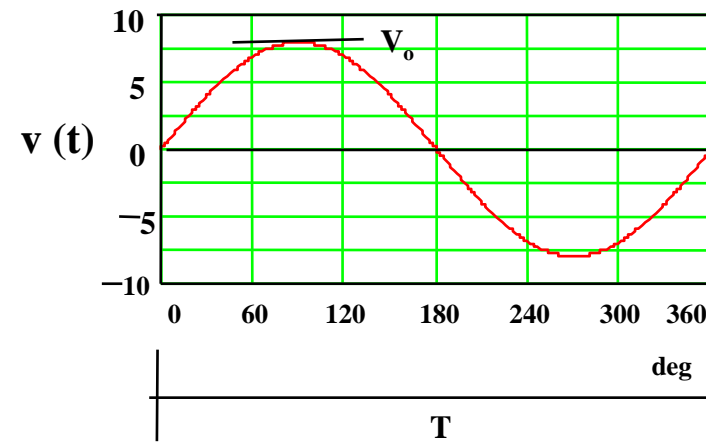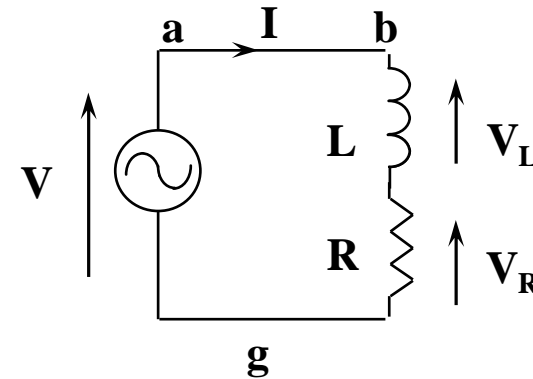- Single phase circuit components:
- Voltage or current sources
- Impedances (resistance, inductance, and capacitance)
- The components are connected in series or in parallel.
- The figure shows a simple circuit where a voltage source (generator) supplies a load (resistance and inductance in series).



Single Phase Circuit

Review

- **The voltage source produces a sinusoidal voltage wave**

$$v(t) = \sqrt{2} V_{rms} \cos(\omega t + \delta)$$

where: V_{rms} is the rms value of the voltage (volts)

ω is the angular frequency (rad/sec)

$$\omega = 2\pi f = \frac{2\pi}{T} \text{ rad/sec} \qquad f = \frac{1}{T} \text{ Hz}$$

f is the frequency (60 Hz in USA, 50 Hz in Europe).

T is the time period (seconds).

Single Phase Circuit

Review

The rms value is calculated by:

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

The peak value (max value) of the voltage is:

$$V_0 = \sqrt{2} V_{\text{rms}}$$

Single Phase Circuit

Review

- **The current is also sinusoidal**

$$i(t) = \sqrt{2} I_{\text{rms}} \sin(\omega t - \phi)$$

where: I_{rms} is the rms value of the current.

ϕ is the phase-shift between current and voltage.

- **The rms current is calculated by the Ohm's Law:**

where: Z is the impedance

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

Single Phase Circuit

Review

Complex Notation

- Voltage phasor:

$$\mathbf{V} = |\mathbf{V}| e^{j\delta} \quad \text{or}$$

$$\mathbf{V} = |\mathbf{V}| \angle \delta = |\mathbf{V}| \cos \delta + j|\mathbf{V}| \sin \delta$$

where : V is the rms value, and δ is the phase angle

Note: The supply voltage phase angle is often selected as the reference with $\delta = 0$

Single Phase Circuit

Review

Complex Notation

- Current phasor

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{|V| e^{j\delta}}{|Z| e^{j\phi}} = \left| \frac{V}{Z} \right| e^{j(\delta-\phi)} = \left| \frac{V}{Z} \right| [\cos(\delta-\phi) + j\sin(\delta-\phi)]$$

Single Phase Circuit

Review

- The sinusoidal current, voltage is expressed in complex form:

$$V_O = I_{\text{rms}} \cdot e^{j \cdot \delta} = V_{\text{rms}} \cdot (\cos(\delta) + j \cdot \sin(\delta))$$

$$I_O = I_{\text{rms}} \cdot e^{j \cdot \Phi} = I_{\text{rms}} \cdot (\cos(\Phi) + j \cdot \sin(\Phi))$$

2.2 Impedances

Single Phase Circuit

Review

- **The Ohm law states:** $V_o = I_o \cdot Z_o$

$$\cdot Z_o = \frac{V_o}{I_o} = \frac{V_{\text{rms}}}{I_{\text{rms}}} \cdot e^{j(\delta - \Phi)} = \frac{V_{\text{rms}}}{I_{\text{rms}}} \cdot e^{j(\theta)}$$

$$Z_o = |Z| \cdot (\cos(\theta) + 1j \cdot \sin(\theta))$$

Zo is the impedance

Single Phase Circuit

Review

- The impedance has resistive and reactive part,
- The reactance depend on the frequency:

$$\dot{Z}_O = R_O + j X_O(\omega)$$

- The absolute value and phase angle is:

$$|Z_O| = \sqrt{R_O^2 + X_O(\omega)^2} \quad \Phi = \text{atan}\left(\frac{X_O}{R_O}\right).$$

Single Phase Circuit


Review

Fig 2.02 Impedance Triangle

$$\mathbf{Z} = |\mathbf{Z}| e^{j\phi}$$

$$\mathbf{Z} = \sqrt{R^2 + X^2}$$
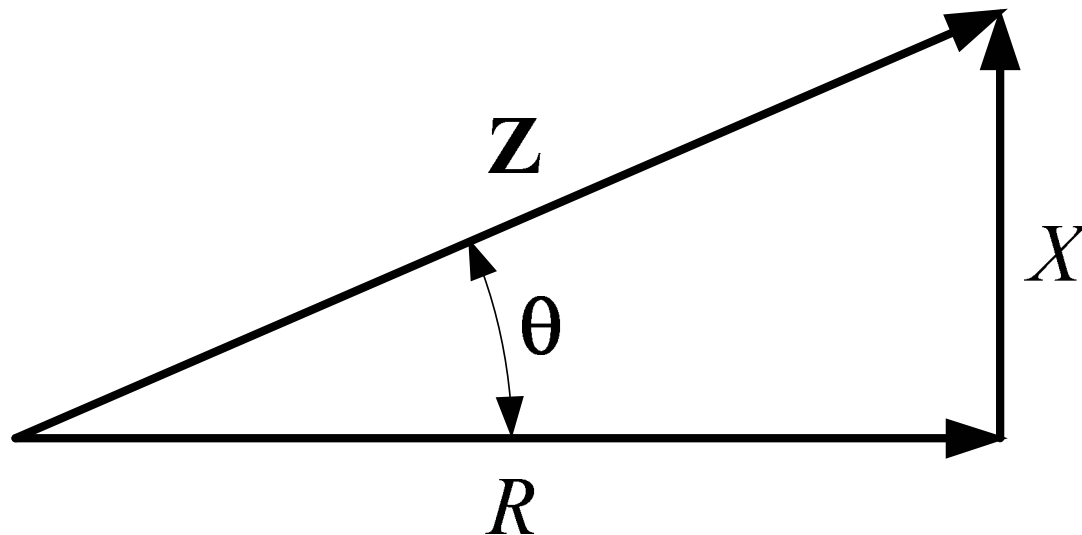
$$\phi = \tan^{-1} \left(\frac{X}{R} \right)$$



Single Phase Circuit

Review

- The impedances (in Ohms) are :

- a) **Resistance (R)**

- b) **Inductive reactance**

$$X_L = j \cdot \omega \cdot L_{ind}$$

- c) **Capacitive reactance**

$$X_c = \frac{1}{j \cdot \omega \cdot C_{cap}}$$

Single Phase Circuit

Review

Series connection

$$Z_e = \sum_{k=1}^N Z_k$$

Single Phase Circuit

Review

Series connection Example: (resistance, capacitor, and inductance connected in series)


$$\begin{aligned}\mathbf{Z}_e &= \mathbf{Z}_R + \mathbf{Z}_L + \mathbf{Z}_C = R + j\omega L_{ind} + \frac{1}{j\omega C_{cap}} \\ &= |\mathbf{Z}| e^{j\theta} = |\mathbf{Z}| [\cos(\theta) + j \sin(\theta)]\end{aligned}$$

$$|\mathbf{Z}| = \sqrt{R^2 + \left(\omega L_{ind} - \frac{1}{\omega C_{cap}} \right)^2} \quad \theta = \arctan \left(\frac{\omega L_{ind} - \frac{1}{\omega C_{cap}}}{R} \right)$$

Single Phase Circuit

Review

Fig 2.3 Parallel connection

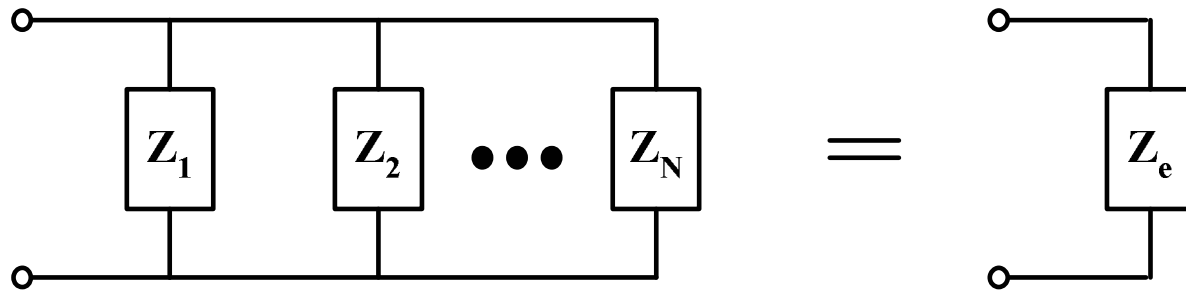

$$Z_e = \frac{1}{\sum_{k=1}^N \frac{1}{Z_k}}$$

Single Phase Circuit

Review

Parallel connection

Impedance phasor: (resistance, capacitor, and inductance connected in parallel)

$$\mathbf{Z} = \frac{1}{\mathbf{Y}} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + \frac{1}{j\omega C}} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C}$$


Two impedances connected in parallel

$$\mathbf{Z} = \frac{1}{\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2}} = \frac{\mathbf{Z}_1 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}$$

Single Phase Circuit

Review

Fig 2.10 Delta-wye transformation

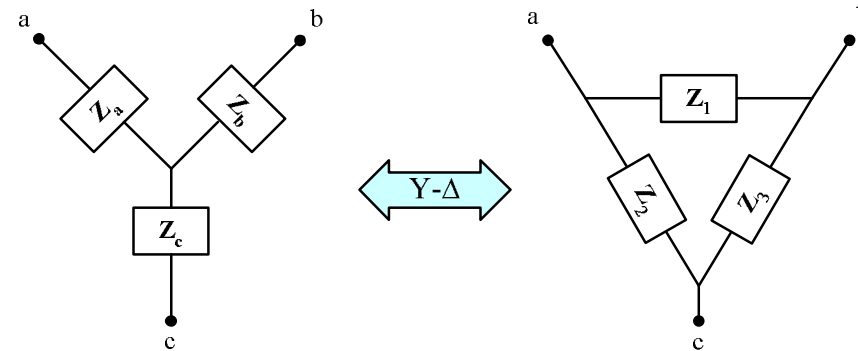

$$Z_a = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_b = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_c = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$

Reverse

$$Z_1 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c}$$

$$Z_2 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_b}$$

$$Z_3 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_a}$$

Same values $Z_{\Delta} = 3 Z_Y$

Single Phase Circuit

Review



Example: Fig 2.4: Calculate the impedance of a compensated line

$$R_{\text{mi}} := 0.32 \frac{\Omega}{\text{mi}}$$

$$X_{\text{mi}} := 0.75 \frac{\Omega}{\text{mi}}$$

$$d_{\text{line}} := 3\text{mi}$$

$$C_{\text{comp}} := 1572\mu\text{F}$$

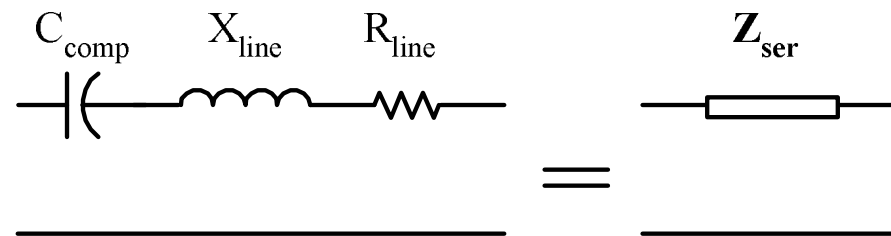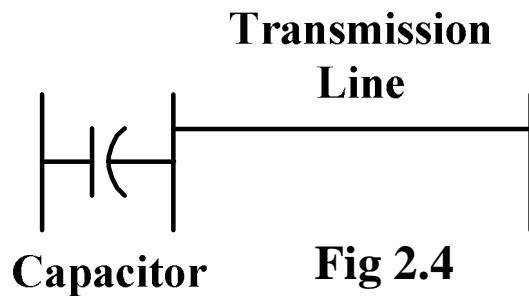

Single Phase Circuit

Review

Example: Fig 2.4: Calculate the impedance of a compensated line

The three impedances are connected in series

$$R_{mi} := 0.32 \frac{\Omega}{mi} \quad X_{mi} := 0.75 \frac{\Omega}{mi} \quad d_{line} := 3mi$$

$$C_{comp} := 1572\mu F \quad f := 60Hz \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 376.991 \text{ Hz}$$

$$Z_{line} := R_{mi} \cdot d_{line} + 1j \cdot X_{mi} \cdot d_{line} + \frac{1}{1j\omega \cdot C_{mi} \cdot d_{line}}$$

$$Z_{line} = 0.96 + 1.688i \Omega \blacksquare$$

Single Phase Circuit

Review

Example: Fig 2.4: Calculate the impedance of a motor and capacitor conncted in parallel

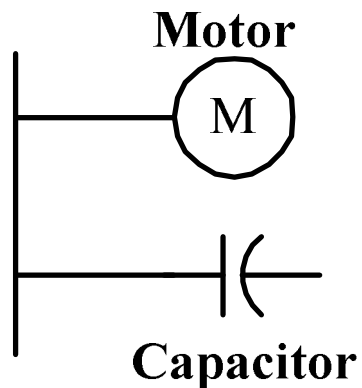


Fig 2.6

$$X_{\text{mot}} := 23\Omega$$

$$R_{\text{mot}} := 20\Omega$$

$$C_{\text{comp_M}} := 500\mu\text{F}$$

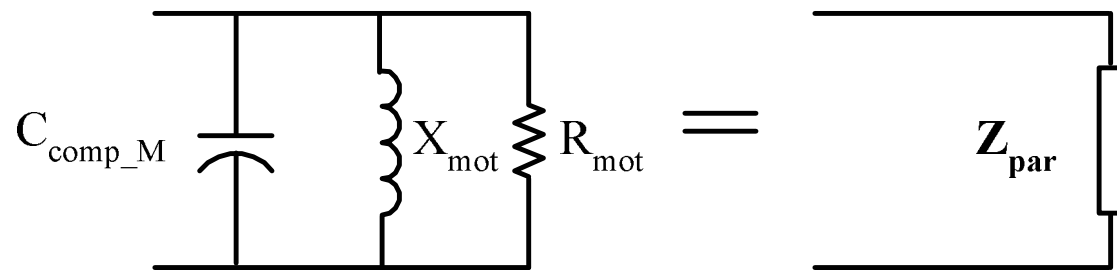


Fig. 2.7

Single Phase Circuit

Review

Example: Fig 2.4: Calculate the impedance of a motor and capacitor connected in parallel

$$X_{\text{mot}} := 23\Omega \quad R_{\text{mot}} := 20\Omega \quad C_{\text{comp}_M} := 500\mu\text{F}$$

$$f := 60\text{Hz} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 376.991\text{Hz}$$

$$X_{\text{mot}_C} := \frac{1}{1j \cdot \omega \cdot C_{\text{mot}_C}} \quad X_{\text{mot}_C} = -5.305i \Omega \blacksquare$$

$$Z_{\text{mot}} := \frac{1}{\frac{1}{1jX_{\text{mot}}} + \frac{1}{R_{\text{mot}}} + \frac{1}{X_{\text{mot}_C}}} \quad Z_{\text{mot}} = 2.125 - 6.163i \Omega.$$

Single Phase Circuit

Review

2.3 Power

Single Phase Circuit

Review

Instantaneous power is the product of the instantaneous voltage and current

$$p(t) = v(t) i(t) = \sqrt{2} V_{rms} \cos(\omega t + \delta) \sqrt{2} I_{rms} \cos(\omega t + \phi)$$

Using the trigonometric identity

$$\cos(\alpha) \cos(\beta) = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$

The instantaneous power is:

$$p(t) = V_{rms} I_{rms} \left[\cos(\delta - \phi) + \cos(2\omega t + \delta + \phi) \right]$$

Single Phase Circuit

Review

The average or active power is the integral

$$P = \frac{1}{T} \int_0^T p(t) dt = V_{rms} I_{rms} \cos(\delta - \phi)$$

Apparent power $\mathbf{S} = \mathbf{V}_{rms} * \mathbf{I}_{rms}$

Complex power:

$$\begin{aligned} \mathbf{S} &= \mathbf{V}_{rms} \mathbf{I}_{rms}^* = V_{rms} e^{j\delta} I_{rms} e^{-j\phi} \\ &= V_{rms} I_{rms} \cos(\delta - \phi) + j V_{rms} I_{rms} \sin(\delta - \phi) \\ &= P + jQ \end{aligned}$$


Single Phase Circuit

Review

Power Factor , Should be more than 0.8

$$pf = \frac{P}{V_{rms} I_{rms}} = \frac{P}{|S|} = \cos(\delta - \phi)$$


Fig 2.11 Power triangle

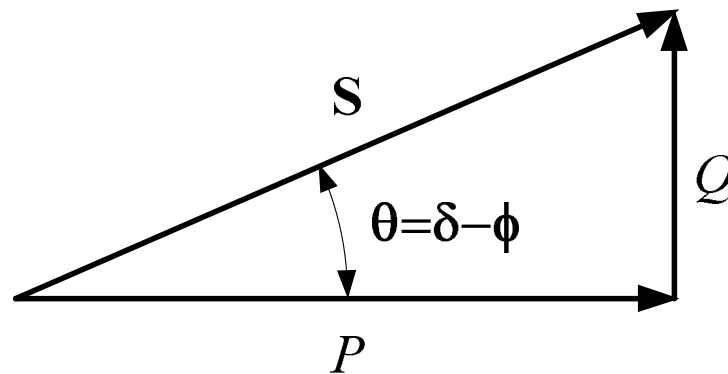

Single Phase Circuit

Review

General impedance load:

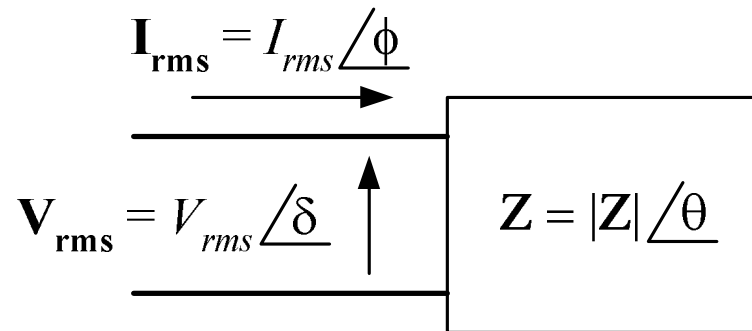

Power on a resistive load

$$P = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

Single Phase Circuit

Review

2.4 AC Circuit

Single Phase Circuit

Review

The circuit has voltage source and impedances

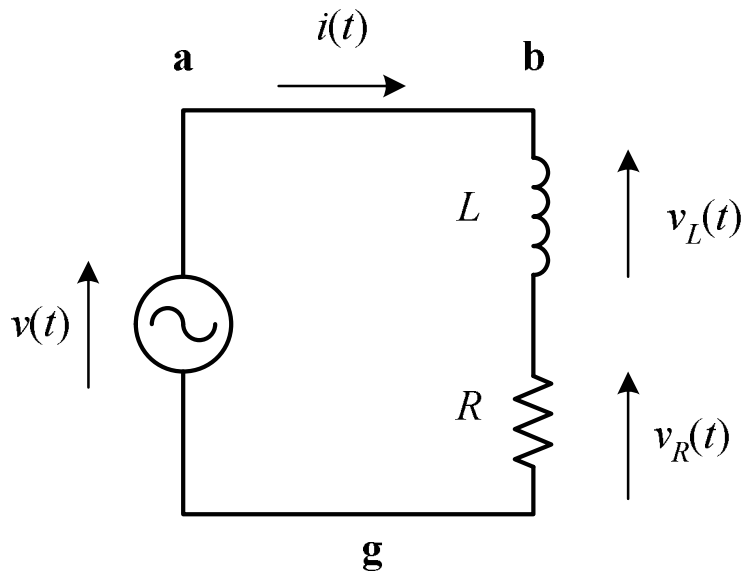


Fig. 2.13 Example single phase circuit


• **Generator current and voltage are in the same direction**

• **Load: current and voltage are in opposite direction**

Single Phase Circuit

Review

Lagging and leading current

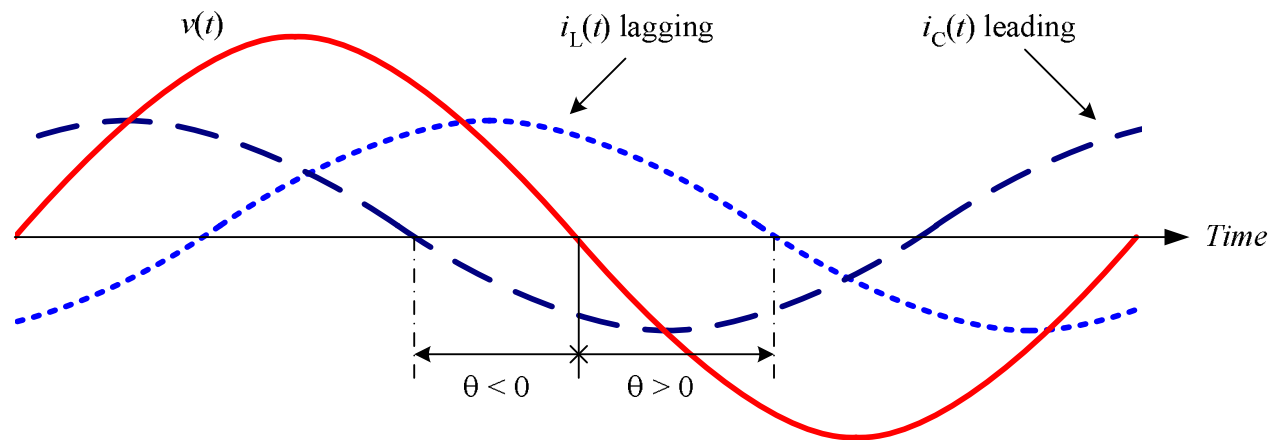

Single Phase Circuit

Review

- The current is calculated by the Ohm Law

$$\mathbf{I}_{\text{rms}} = \frac{\mathbf{V}_{\text{rms}}}{\mathbf{Z}}$$

$$|\mathbf{Z}| = \sqrt{R^2 + X_{ind}^2}$$

Single Phase Circuit

Transmission line supplies a load

- The load voltage must be +/- 5% of the generator voltage
- Voltage regulation is calculated
- The loss must be minimized
- The efficiency of transmission is calculated

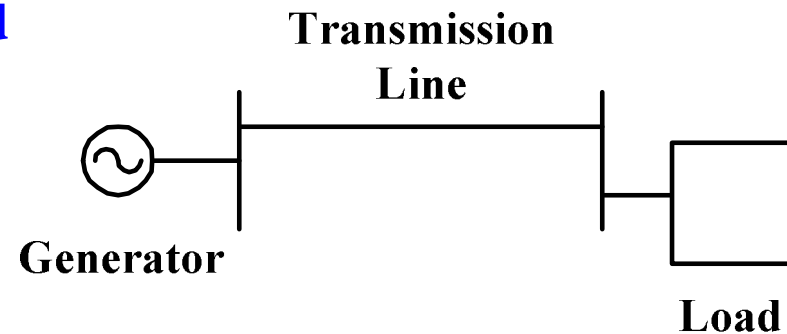


Fig 2.19 Load served by a line

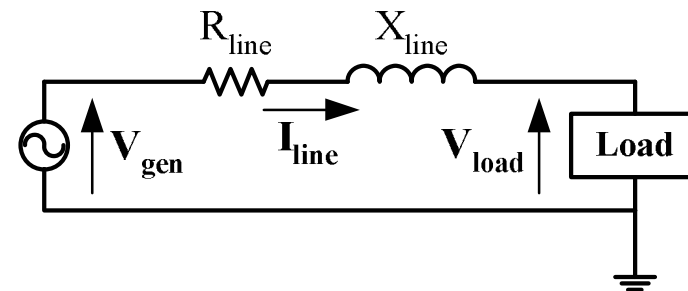


Fig 2.20 Equivalent circuit

Single Phase Circuit

Review

- The load current is:

$$I_{\text{load}} = \frac{V_{\text{load}}}{Z_{\text{load}}} = I_{\text{line}}$$

- The source voltage using loop equation is:

$$V_{\text{gen}} := V_{\text{load}} + I_{\text{line}}(R_{\text{line}} + j \cdot X_{\text{line}})$$

Single Phase Circuit

Voltage regulation

$$\text{Voltage Regulation} = \frac{|\mathbf{V}_{\text{no-load}}| - |\mathbf{V}_{\text{load}}|}{|\mathbf{V}_{\text{load}}|} \times 100\%$$

$$\text{Voltage Regulation} = \frac{|\mathbf{V}_{\text{gen}}| - |\mathbf{V}_{\text{load}}|}{|\mathbf{V}_{\text{load}}|} \times 100\%$$

Efficiency

$$\text{efficiency} = \frac{P_{\text{net}}}{P_{\text{gen}}} = \frac{P_{\text{gen}} - P_{\text{loss}}}{P_{\text{gen}}}$$