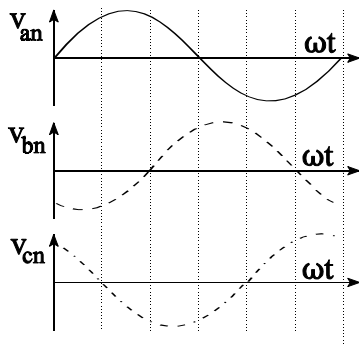


## A2: Three-phase Power Circuits

Wildi Text Chapter 8, All Sections, All Questions and Problems

Poly-phase power circuits are used for two main reasons; to make more efficient use of the conductors in a transmission line; and to enable the use of poly-phase rotating machines.



A three phase generator is a device that produces three ac voltages with the same frequency and rms value and whose relative phases are one third of an electrical cycle. These voltages may be written as:



$$v_{an} = \sqrt{2} V \sin \omega t \quad V$$

$$v_{bn} = \sqrt{2} V \sin \left( \omega t - \frac{2\pi}{3} \right) \quad V$$

$$v_{cn} = \sqrt{2} V \sin \left( \omega t + \frac{2\pi}{3} \right) \quad V$$

$$V_{an} \angle 0, V_{bn} \angle -120, V_{cn} \angle +120$$

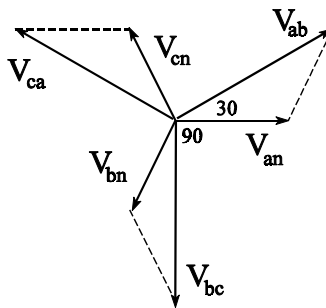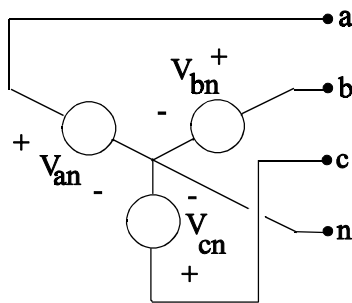There are three possible connections for three-phase devices: 4-wire **Y**, 3-wire **Y**, (3-wire) **Δ**.  
**4 Wire Wye Connection (Y)**



### Two sets of voltages LL, LN

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

In general - convert between LL & LN

$$V_{LL} = \sqrt{3} \angle 30 V_{LN}$$

If a "balanced" load is connected ( $Z_a = Z_b = Z_c = |Z| \angle \theta$ ) then the currents that flow are also balanced (i.e. symmetrical in magnitude and phase)

$$i_a = \sqrt{2} I \sin (\omega t - \theta) \quad A$$


$$i_b = \sqrt{2} I \sin \left( \omega t - \theta - \frac{2\pi}{3} \right) \quad A$$

$$i_c = \sqrt{2} I \sin \left( \omega t - \theta + \frac{2\pi}{3} \right) \quad A$$

$$\text{note that } i_n = i_a + i_b + i_c = 0 \quad A$$

If the load is not balanced, a neutral current will exist.


### 3 Wire Wye Connection (Y)

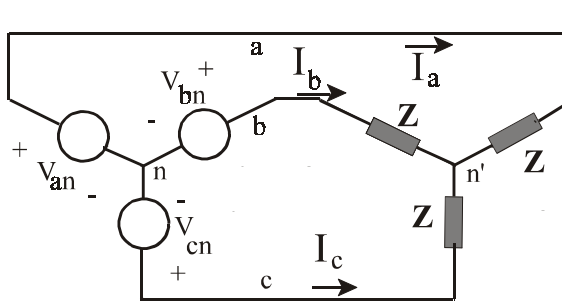

In a 3-wire Wye configuration the neutral wire is omitted. In this case - an unbalanced load will cause the load voltages to become unbalanced and  $v_{nn'} \neq 0$ . If however the load is balanced then  $v_{nn'} = 0$  and the presence of a neutral wire is immaterial. Note that  $i_a + i_b + i_c$  is constrained to be zero.
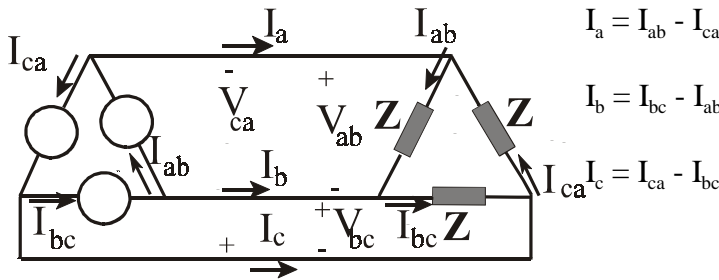
### Delta Connection ( $\Delta$ )

Two sets of currents: line, delta (L,  $\Delta$ )



$$I_a = I_{ab} - I_{ca}$$


$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

to convert between L &  $\Delta$

$$I_L = \sqrt{3} \angle -30^\circ I_\Delta$$
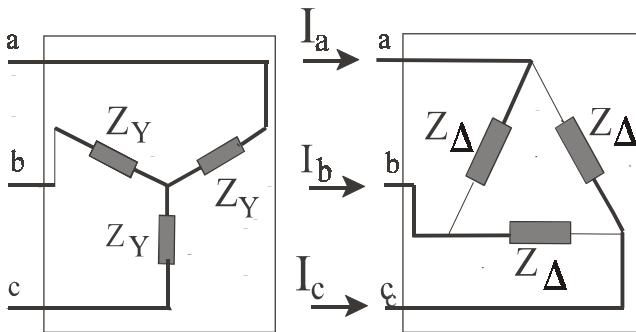
### Wye-Delta Transformations (Y to $\Delta$ and $\Delta$ to Y)



$$Z_\Delta = 3 Z_Y$$

$$Z_Y = \frac{1}{3} Z_\Delta$$

### Power Calculations

$$P = \sqrt{3} V_{LL} I_L \text{ PF (Y or } \Delta) = 3 V_{LN} I_L \text{ PF (Y)} = 3 V_{LL} I_\Delta \text{ PF } (\Delta), \text{ where PF} = \cos \theta$$

$$Q = \sqrt{3} V_{LL} I_L \sin \theta \text{ (Y or } \Delta) = 3 V_{LN} I_L \sin \theta \text{ (Y)} = 3 V_{LL} I_\Delta \sin \theta \text{ } (\Delta)$$

$$S = \sqrt{3} V_{LL} I_L \text{ (Y or } \Delta) = 3 V_{LN} I_L \text{ (Y)} = 3 V_{LL} I_\Delta \text{ } (\Delta)$$

To solve for current or voltage, use a Y-conn. per-phase circuit and  $V_{LN} = I_L \times Z_Y$