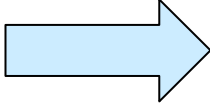


Complex amplitude technique


Step 1. Associate the actual voltage sources (or current sources) waveform with the complex amplitudes

Actual waveform		Complex amplitude
$v(t) = V_M \sin(\omega t)$	\implies	V_M
$i(t) = I_M \sin(\omega t)$	\implies	I_M
$v(t) = V_M \sin(\omega t + \phi)$	\implies	$V_M \angle \phi;$ (equivalent to the Euler's form $V_M e^{j\phi}$)
$i(t) = I_M \sin(\omega t + \phi)$	\implies	$I_M \angle \phi;$ (equivalent to the Euler's form $I_M e^{j\phi}$)

Complex amplitude technique

Step 1. Associate the actual voltage sources (or current sources) waveform with the complex amplitudes

Actual waveform

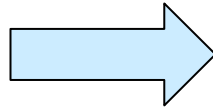

Complex amplitude

Examples

$$i(t) = 2.3 \times \sin(360 \cdot t) \text{ A} \quad \Rightarrow \quad \mathbf{2.3 \text{ A}}$$


$$v(t) = 6 \times \sin(5E7 \cdot t + 1.57) \text{ V} \quad \Rightarrow \quad \mathbf{6 \times e^{j1.57} \text{ V}}$$

or

$$\mathbf{6 \angle 1.57 \text{ V}}$$

Complex amplitude technique

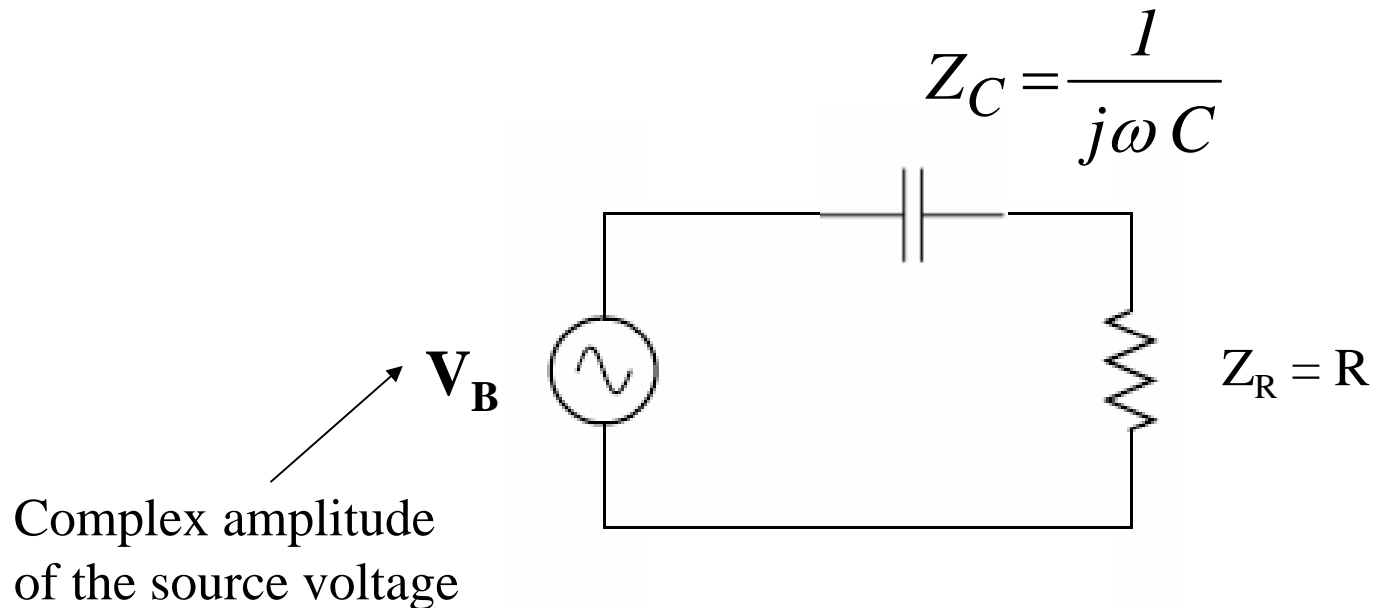
Step 2. Assign impedances (or admittances) to all the circuit components



Complex amplitude technique

Step 3. Find the complex current – complex voltage relations in the circuit using the “AC Ohm’s law”, KVL and KCL.

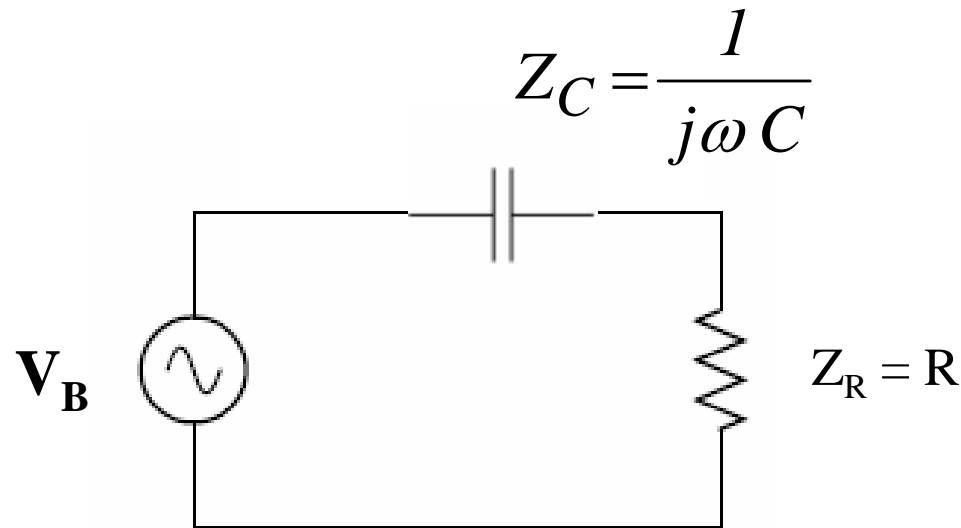Any method known for DC circuit analysis (series, parallel, mesh analysis, etc.) can be used.




In this series circuit, the complex current amplitude,
$$\mathbf{I}_M = \frac{\mathbf{V}_B}{Z_C + Z_R}$$

Complex amplitude technique

Step 4. Convert that found complex current and/or voltage amplitudes into the polar (Euler's) form
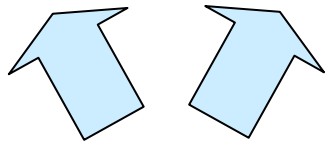
$$\mathbf{I}_M = I_{MR} + j I_{MIm} \quad \longrightarrow \quad I_M e^{j\varphi} = I_M \angle \varphi$$



Real and Imaginary components of the complex current (or voltage) amplitudes found in the step 3.

At this step, I_{MR} and I_{MIm} are the numbers.

Complex amplitude technique

Step 5. Convert the complex current and/or voltage amplitudes into the actual waveform

The found complex current amplitude has the form
(I_M and φ are real numbers):

$$I_M e^{j\varphi}$$

I_M is the modulus of the found complex amplitude;
 φ is the angle of the found complex amplitude


The actual current waveform has the same amplitude I_M and the same phase angle φ :

$$i(t) = I_M \sin(\omega t + \varphi)$$


The current amplitude = I_M

The current phase angle = φ .

Example 1: Series L-R circuit

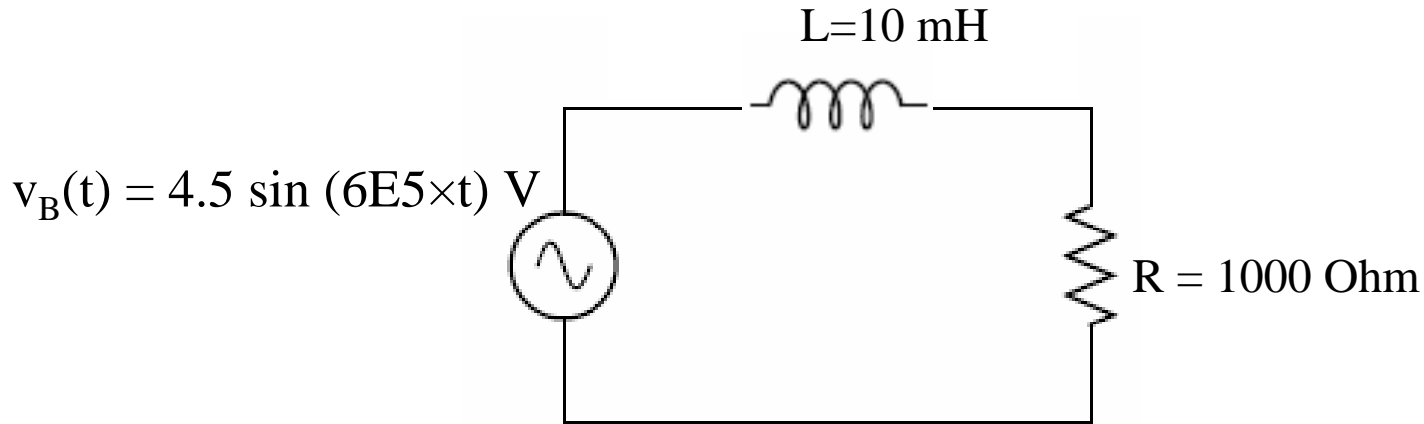

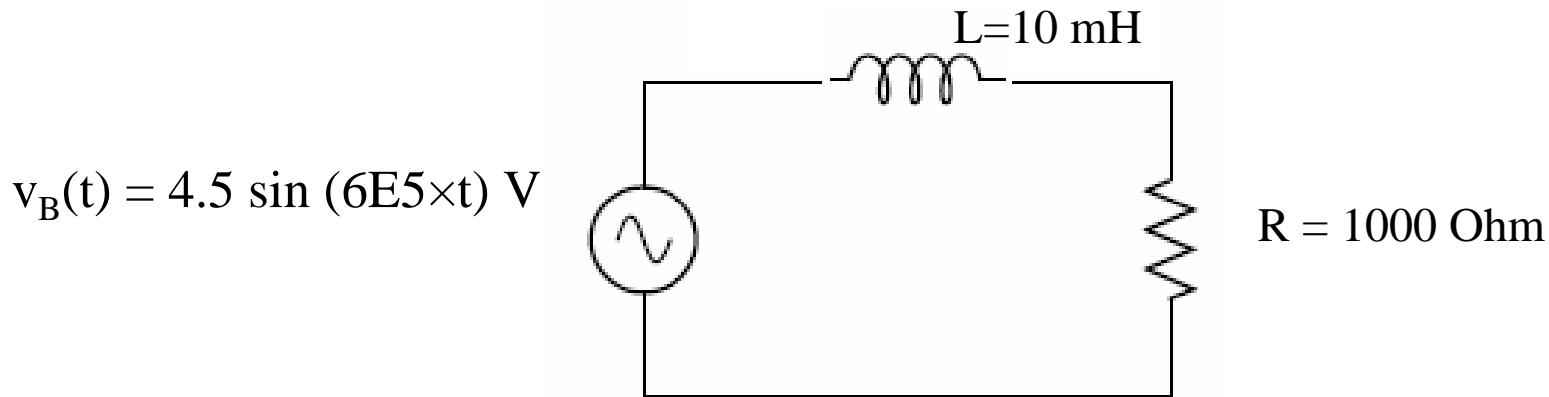1. Complex amplitude of the voltage source, $V_B = 4.5 \text{ V}$
2. Find the impedances. The angular frequency $\omega = 6E5 \text{ s}^{-1}$
 $Z_L = j\omega L = j * 6E5 * 10E-3 = j 6E3 \text{ Ohm};$
 $Z_R = R = 1E3 \text{ Ohm}$
3. This is a series circuit. Total impedance:
 $Z = Z_L + Z_R = 1E3 + j * 6E3 \text{ Ohm}$



4. Complex current amplitude using “the AC Ohm’s law”,

$$I = \mathbf{V}_B / Z = \mathbf{V}_B / (R + j\omega L)$$

$$I = 4.5 / (1E3 + j * 6E3) \text{ A} \quad \dots = 1.22E-4 - j7.3E-4$$

5. Convert complex current amplitude into a polar form


$$4.5 / (1E3 + j * 6E3) \Rightarrow \text{Polar}$$

The complex current amplitude: $\mathbf{I} = 7.4E-4 \angle -1.41 \text{ A}$;

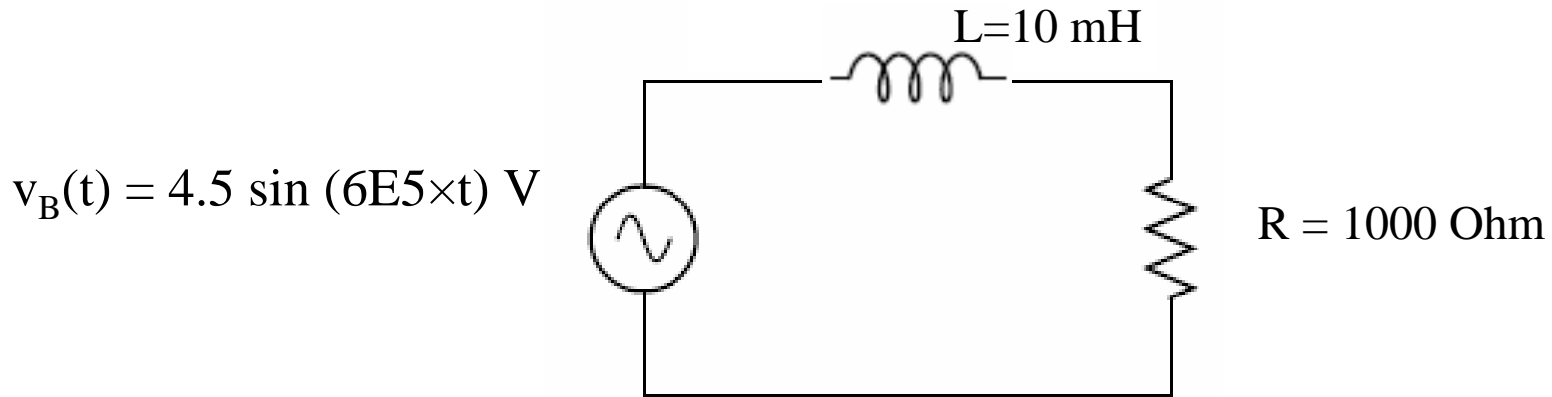6. Convert complex amplitude into the actual current waveform

$$i(t) = 7.4E-4 \sin(6E5 \times t - 1.41) \text{ A}$$

The current amplitude = $7.4E-4 \text{ A}$; the current phase angle = -1.41 rad



7. Find the voltage drop across the resistor R

The current, $i(t) = 7.4E-4 \sin(6E5 \times t - 1.41) \text{ A}$


The voltage across the resistor,

$$v_R(t) = R \times i(t) = 1000 \times 7.4E-4 \sin(6E5 \times t - 1.41) \text{ V} =$$

$$= 0.74 \sin(6E5 \times t - 1.41) \text{ V}$$

The resistor voltage amplitude = 0.74 V.

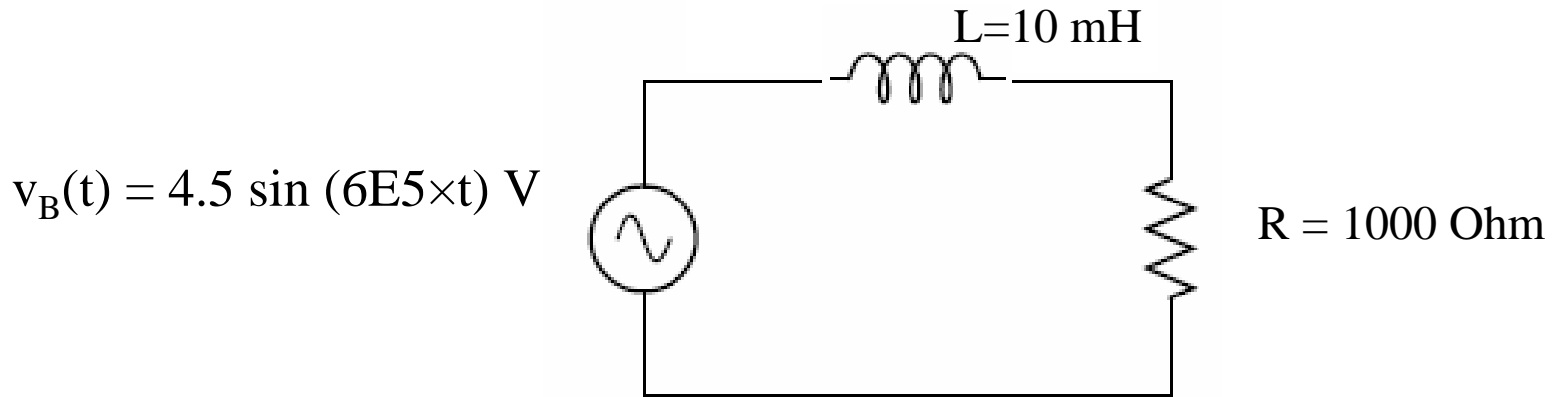The resistor voltage phase angle = -1.41 rad



8. Find the voltage drop across the inductor L

The complex current amplitude:

$$\mathbf{I} = 7.4E-4 \angle -1.41 \text{ A}$$

Complex impedance of the inductor:

$$\mathbf{Z}_L = j 6E3 \text{ Ohm}$$

Complex voltage across the inductor:


$$\mathbf{V}_L = \mathbf{Z}_L \times \mathbf{I} = j6E3 \times (7.4E-4 \angle -1.41) \Rightarrow \text{Polar} \Rightarrow 4.44 e^{j0.161} \text{ V} = 4.44 \angle 0.161 \text{ V}$$

$$\text{Actual voltage waveform: } v(t) = 4.44 \sin(6E5 \times t + 0.161) \text{ V}$$

The inductor voltage amplitude = 4.44 V.

The inductor voltage phase angle = 0.161 (*rad*)

Example 2: Parallel R-C circuit

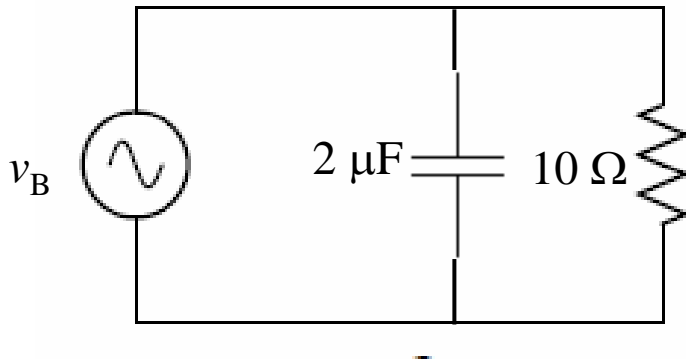


Given the AC voltage source with the amplitude $V_M = 9.3 \text{ V}$ and the frequency $f = 5 \text{ kHz}$,

find the total current in the circuit

1. $\omega = 2\pi f = 6.28 * 5\text{E}3 = 3.14\text{E}4 \text{ s}^{-1} = 3.14 \times 10^4 \text{ s}^{-1}$
2. Complex amplitude of the voltage source $V_M = 9.3 \text{ V}$;
3. Capacitor impedance: $Z_C = 1/(j\omega C) = -j15.9 \text{ Ohm}$.
Resistor impedance: $Z_R = R = 10 \text{ Ohm}$.
4. **This is a parallel circuit. Find total impedance:**
 - a) $1/Z = 1/Z_C + 1/Z_R = j0.063 + 0.1$.
 - b) $Z = 1/(j0.063 + 0.1) = 7.16 - j4.51$

Example 2: Parallel R-C circuit

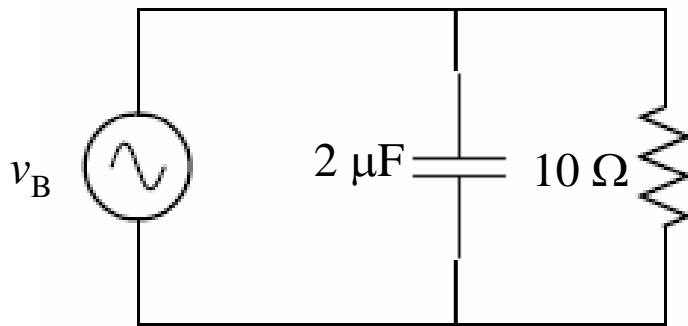

Given the AC voltage source with the amplitude $V_M = 9.3 \text{ V}$ and the frequency $f = 5 \text{ kHz}$,

find the total current in the circuit

4. The total impedance:

$$Z = 1/(j0.063 + 0.1) = 7.16 - j4.51$$

5. The total current complex amplitude:

$$I = V_M/Z = 9.3/(7.16 - j4.51) = 0.93 + j0.586 \text{ A}$$

6. Convert current complex amplitude into polar form:


$$0.93 + j0.586 \Rightarrow \text{Polar} \Rightarrow 1.1 e^{j0.562} = 1.1 \angle 0.562$$

7. Total current amplitude = 1.1 A.

The phase angle = 0.562 rad

The frequency = 5 kHz

Example 3: Series L-C-R circuit

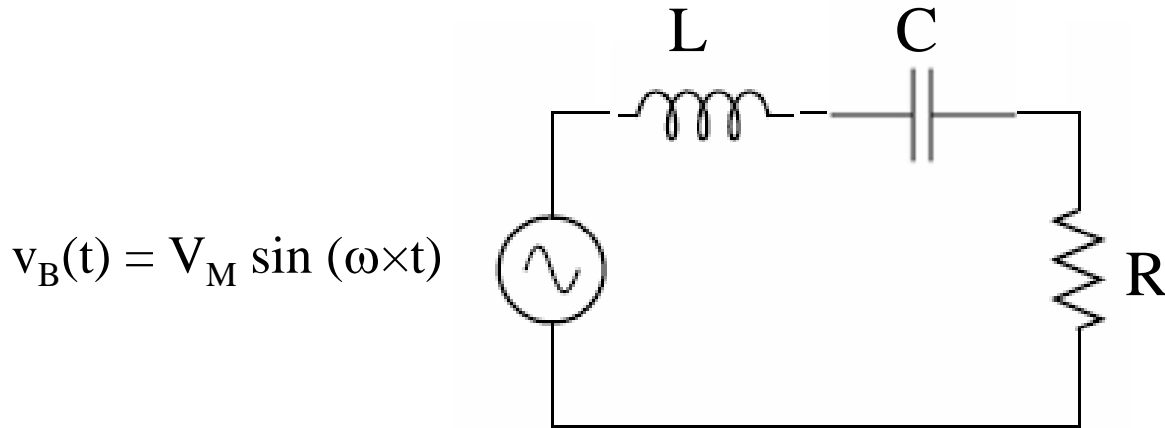

1. Find the impedances.

$$Z_L = j\omega L$$


$$Z_C = 1/j\omega C$$

$$Z_R = R$$

3. This is a series circuit. Total impedance:

$$Z = Z_L + Z_C + Z_R = j\omega L + 1/j\omega C + R$$

Resonance in series L-C-R circuit

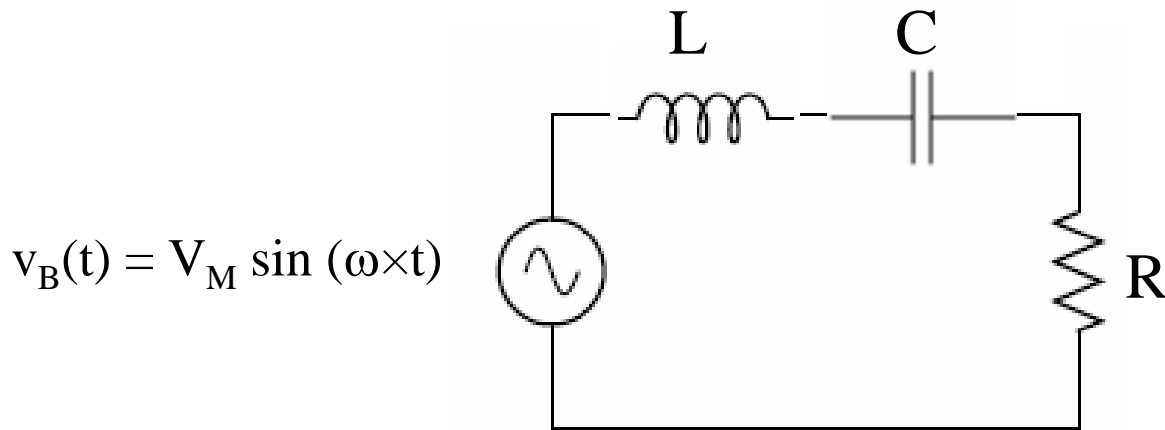

3. (cont) Total impedance:

$$Z = Z_L + Z_C + Z_R = j\omega L + 1/j\omega C + R$$

Note that


$$\frac{1}{j} = \frac{1}{j} \left(\frac{j}{j} \right) = \frac{j}{j^2} = -j$$

$$Z = R + j(\omega L - 1/\omega C)$$

Under certain conditions,

the imaginary part of this impedance = 0 (!)

Resonance in series L – C - R circuit

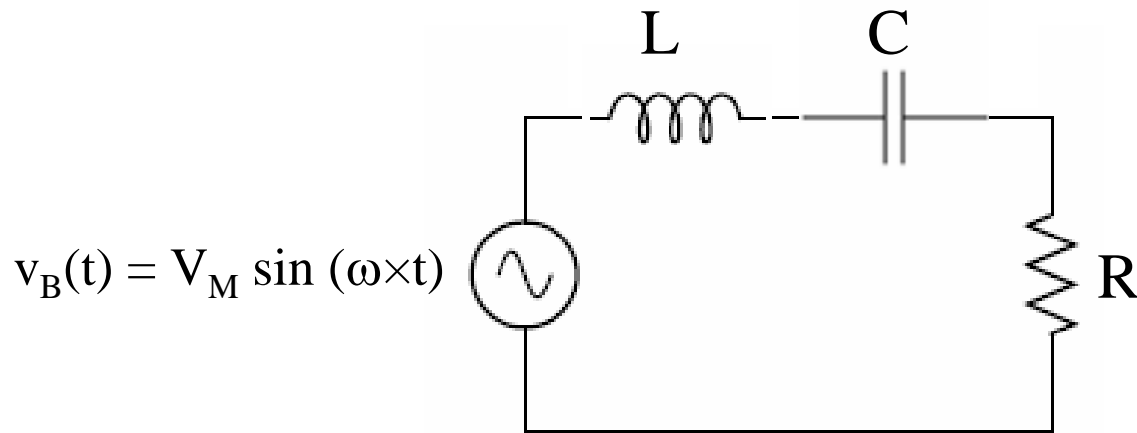

$$Z = R + j(\omega L - 1/\omega C)$$

Given L and C values, find the frequency f_0 at which

$$\text{Im}(Z) = (\omega_0 L - 1/\omega_0 C) = 0$$

$$\omega_0 L - \frac{1}{\omega_0 C} = \frac{\omega_0 \cdot L \cdot \omega_0 \cdot C - 1}{\omega_0 C} = \frac{\omega_0^2 \cdot L \cdot C - 1}{\omega_0 C} = 0$$

For $\text{Im}(Z) = 0$, $\omega_0^2 \cdot L \cdot C - 1 = 0$, or $\omega_0^2 \cdot L \cdot C = 1$,


$$\text{or } \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{and } f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Resonance in series L-C-R circuit

For any L-C circuit $\omega_0 = \frac{1}{\sqrt{LC}}$ and $f_0 = \frac{1}{2\pi\sqrt{LC}}$

are called the resonance angular frequency (ω_0) and the resonance frequency f_0 correspondingly.

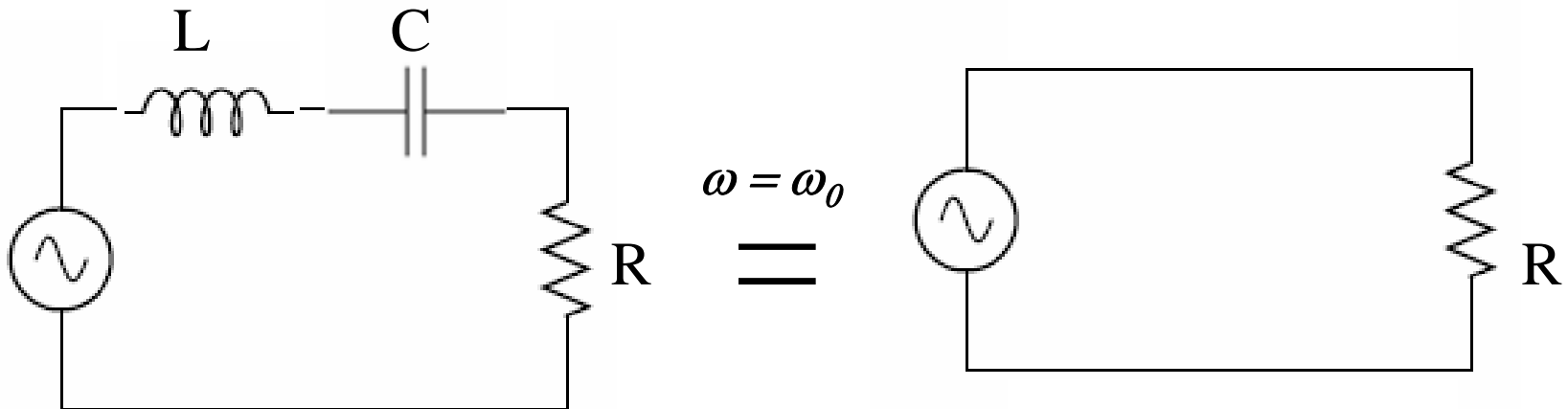
When the signal frequency f is chosen such that $f = f_0$,



because the total (equivalent) impedance of the series connection of L and C is zero: $Z_L + Z_C = 0$

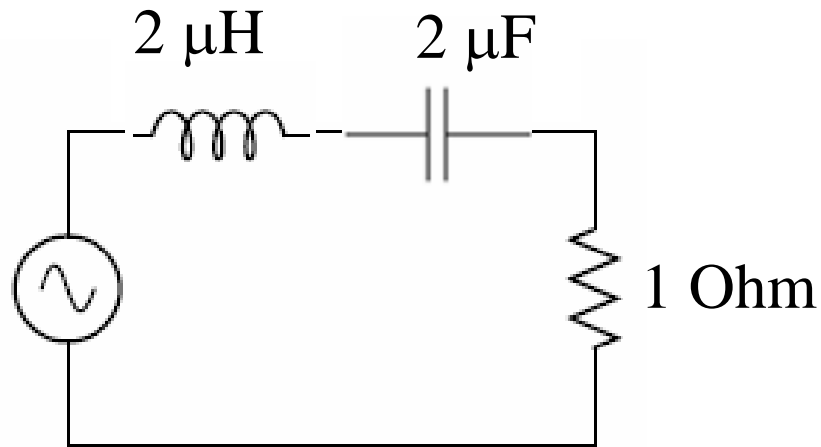Example 4: Resonance in series L-C-R circuit

Find the resonance frequency f_0 for the following circuit




$$\omega_0 = \frac{1}{\sqrt{LC}}; \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \cdot 3.14 \cdot \sqrt{2 \cdot 10^{-6} \cdot 2 \cdot 10^{-6}}} = 7.96 \cdot 10^4 \text{ Hz}$$

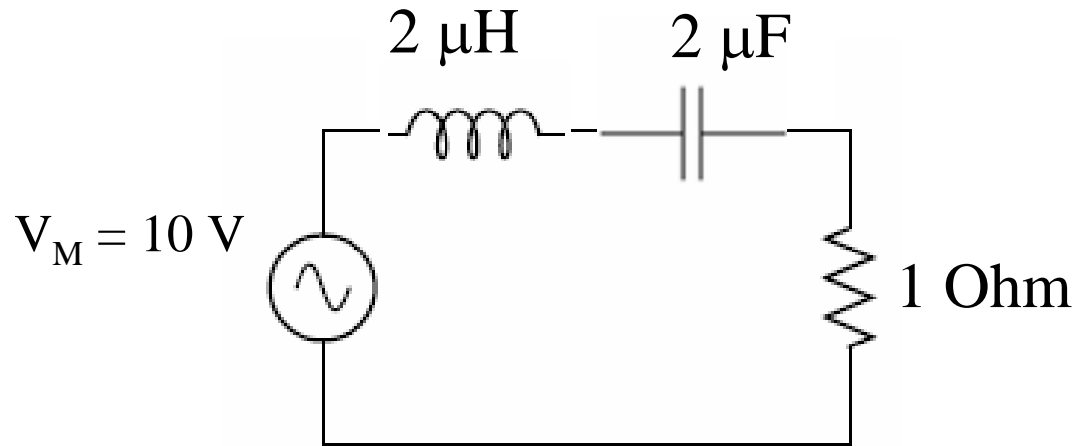Example 4: Resonance in series L-C-R circuit

For the following circuit, find the current amplitude dependence on the signal frequency f .



Total impedanc

$$Z = Z_L + Z_C + Z_R = j\omega L + 1/j\omega C + R = R + j^*(\omega L - 1/\omega C)$$

Complex amplitude of the current:

$$I = V_M / Z = V_M / [R + j^*(\omega L - 1/\omega C)]$$

here $\omega = 2\pi f$

Example 4: Resonance in series L-C-R circuit

MATLAB script to solve the problem

```
clear all
%circuit description
L=2e-6;
C=2e-6;
R=1;
VM=10;
% variable frequency
f=1e3:1e3:1e6;
%Circuit impedance
omega=2*pi*f;
Z=R+(omega*L-1./omega/C)*i;
I=VM./Z;
IM=abs(I);
figure(1)
plot(f,IM)
xlabel ('frequency, Hz')
ylabel ('Current amplitude, A')
```

Example 4: Resonance in series L-C-R circuit

MATLAB script explanation

```
clear all
```

```
%circuit description
```

```
L=2e-6;
```

```
C=2e-6;
```

```
R=1;
```

```
VM=10;
```

```
% variable frequency
```

```
f=1e3:1e3:1e6;
```

```
%Circuit impedance
```

```
omega=2*pi*f;
```

```
Z=R+(omega*L-1./omega/C)*i;
```

```
I=VM./Z;
```

```
IM=abs(I);
```

```
figure(1)
```

```
plot(f,IM)
```

```
xlabel ('frequency, Hz')
```

```
ylabel ('Current amplitude, A')
```

Definition of the
circuit components

Example 4: Resonance in series L-C-R circuit

MATLAB script explanation

```
clear all
%circuit description
L=2e-6;
C=2e-6;
R=1;
VM=10;
% variable frequency
f=1e3:1e3:1e6;
%Circuit impedance
omega=2*pi*f;
Z=R+(omega*L-1./omega/C)*i;
I=VM./Z;
IM=abs(I);
figure(1)
plot(f,IM)
xlabel ('frequency, Hz')
ylabel ('Current amplitude, A')
```

Definition of the
variable frequency

Example 4: Resonance in series L-C-R circuit

MATLAB script explanation

```
clear all
%circuit description
L=2e-6;
C=2e-6;
R=1;
VM=10;
% variable frequency
f=1e3:1e3:1e6;
%Circuit impedance
omega=2*pi*f;
Z=R+(omega*L-1./omega/C)*i;
I=VM./Z;
IM=abs(I);
figure(1)
plot(f,IM)
xlabel ('frequency, Hz')
ylabel ('Current amplitude, A')
```

Calculation of the complex current and current amplitude

Example 4: Resonance in series L-C-R circuit


MATLAB script explanation

```
clear all
%circuit description
L=2e-6;
C=2e-6;
R=1;
VM=10;
% variable frequency
f=1e3:1e3:1e6;
%Circuit impedance
omega=2*pi*f;
Z=R+(omega*L-1./omega/C)*i;
I=VM./Z;
IM=abs(I);
figure(1)
plot(f,IM)
xlabel ('frequency, Hz')
ylabel ('Current amplitude, A')
```


Plotting the results

Example 4: Resonance in series L-C-R circuit

MATLAB results

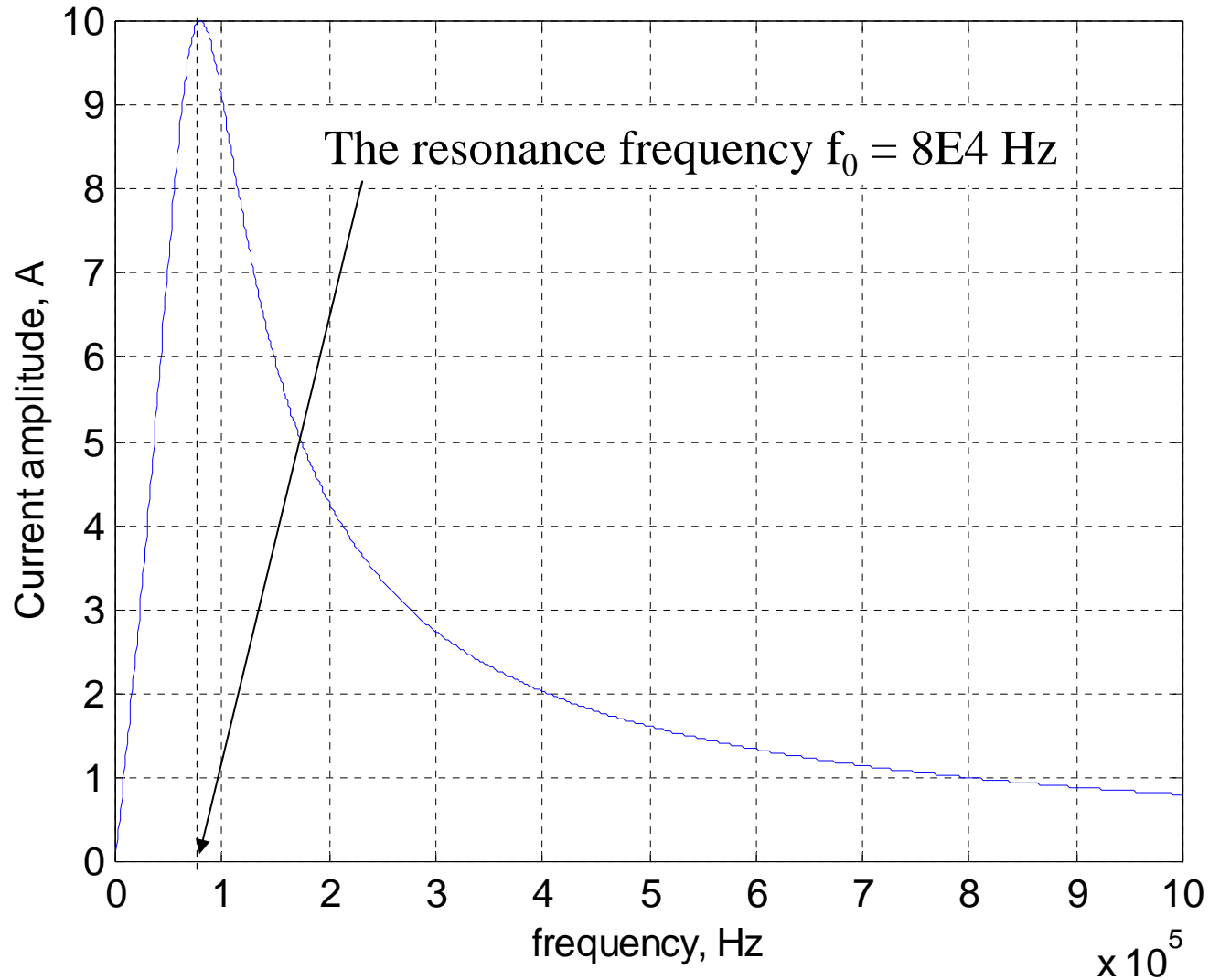

Resonance in parallel L – C circuit

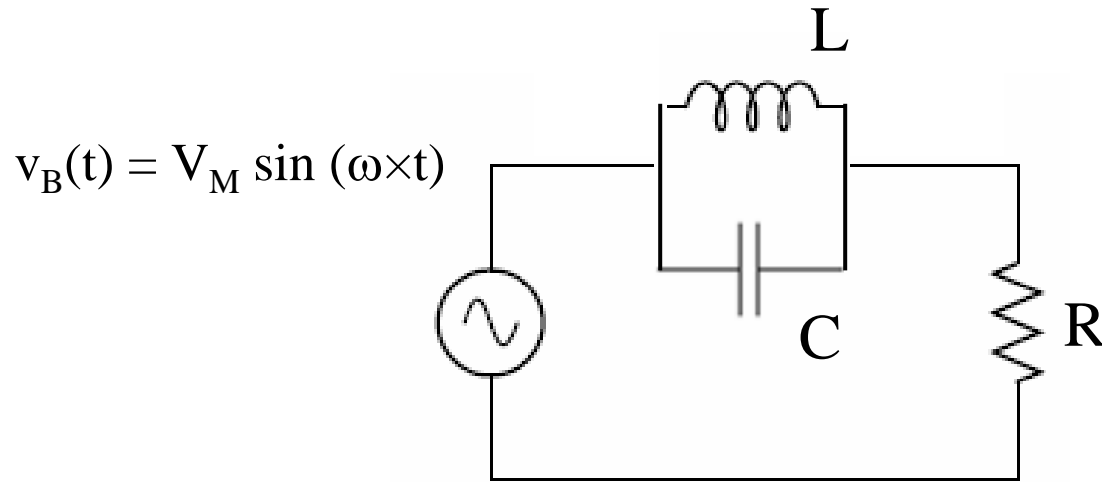

An impedance of parallel connection of L and C:


$$1/Z_L = j \left(\omega C - \frac{1}{\omega L} \right) = \frac{\omega^2 \cdot L \cdot C - 1}{\omega L}$$

$$Z_L = \frac{\omega L}{\omega^2 \cdot L \cdot C - 1}$$


When $\omega = \omega_0$, where $\omega_0 = \frac{1}{\sqrt{LC}}$, $\text{modulus}(Z_L) \Rightarrow \infty$

Resonance in parallel L – C circuit

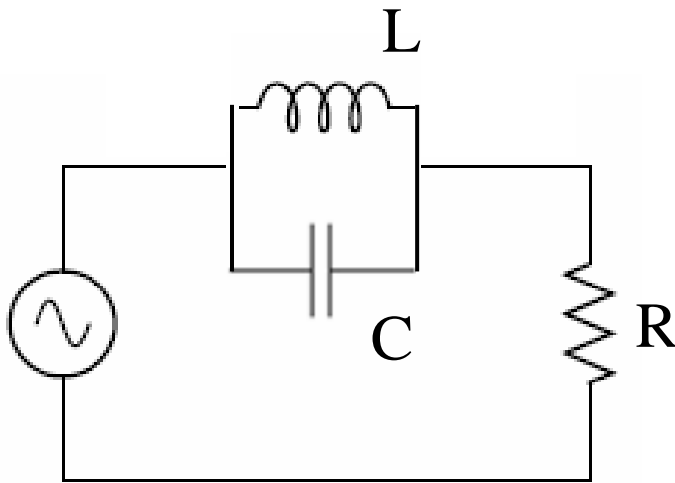
$$\text{At } \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$



$$\omega = \omega_0 \\ \equiv$$

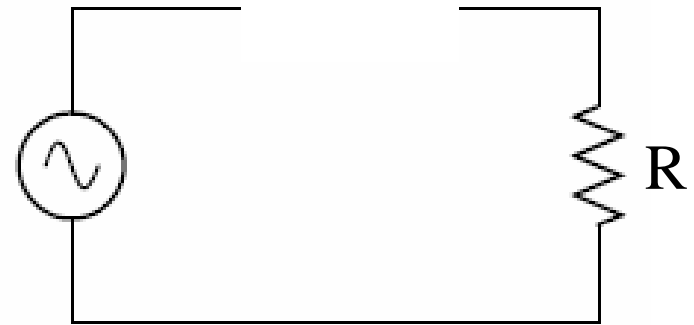

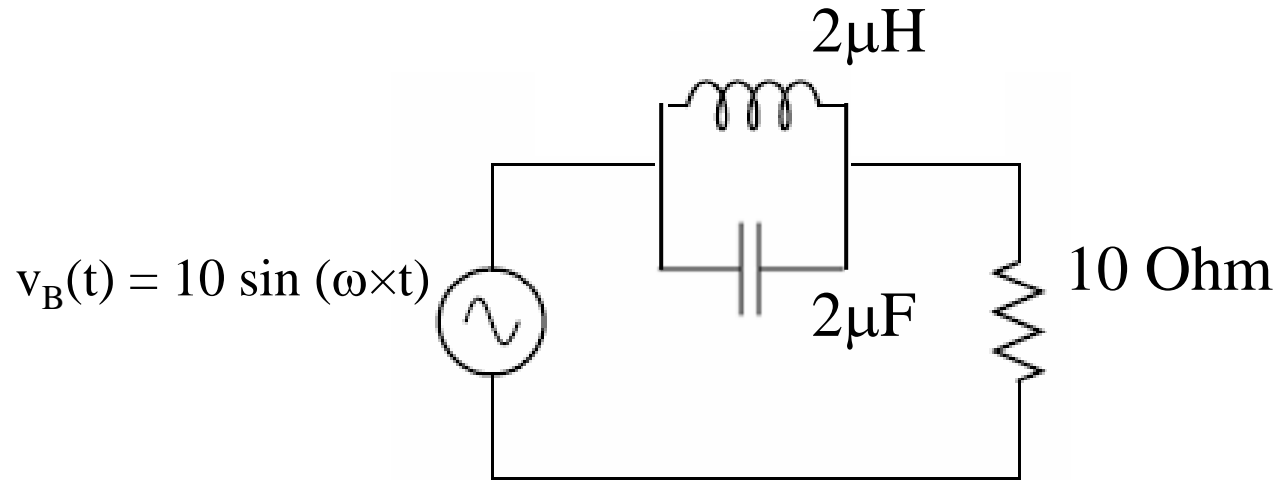Example 5: Find the resonance frequency and current – frequency dependence for the parallel L – C circuit




$$\omega_0 = \frac{1}{\sqrt{LC}}; \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \cdot 3.14 \cdot \sqrt{2 \cdot 10^{-6} \cdot 2 \cdot 10^{-6}}} = 7.96 \cdot 10^4 \text{ Hz}$$


MATLAB script

```
clear all
%circuit description
L=2e-6;
C=2e-6;
R=1;
VM=10;
% variable frequency
f=1e3:1e3:1e6;
%Circuit impedance
omega=2*pi*f;
YLC=i*(omega*C-1./omega/L);
ZLC=1./YLC;
Z=R+ZLC;
I=VM./Z;
IM=abs(I);
figure(1)
plot(f,IM)
xlabel('frequency, Hz')
ylabel('Current amplitude, A')
```


MATLAB results

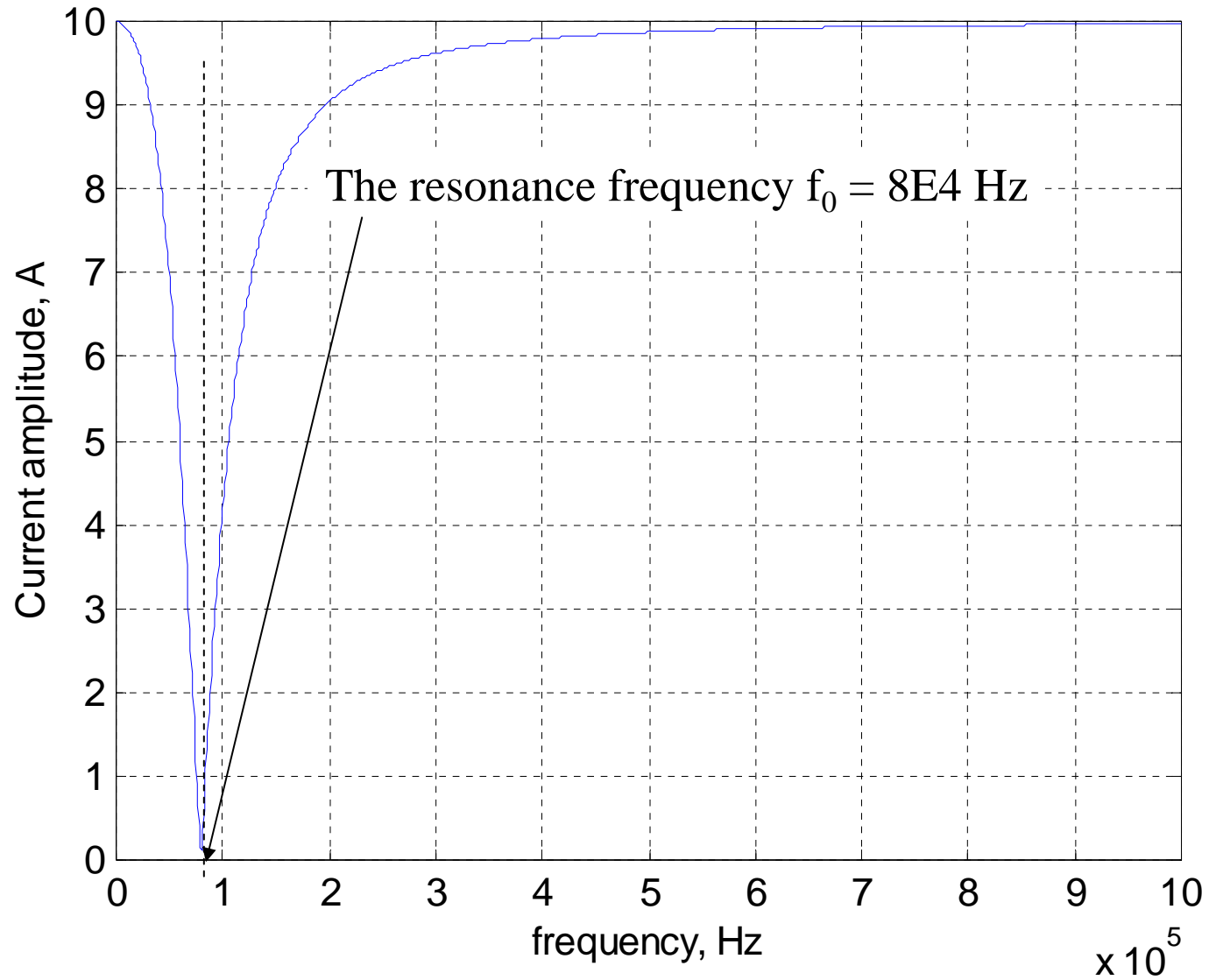


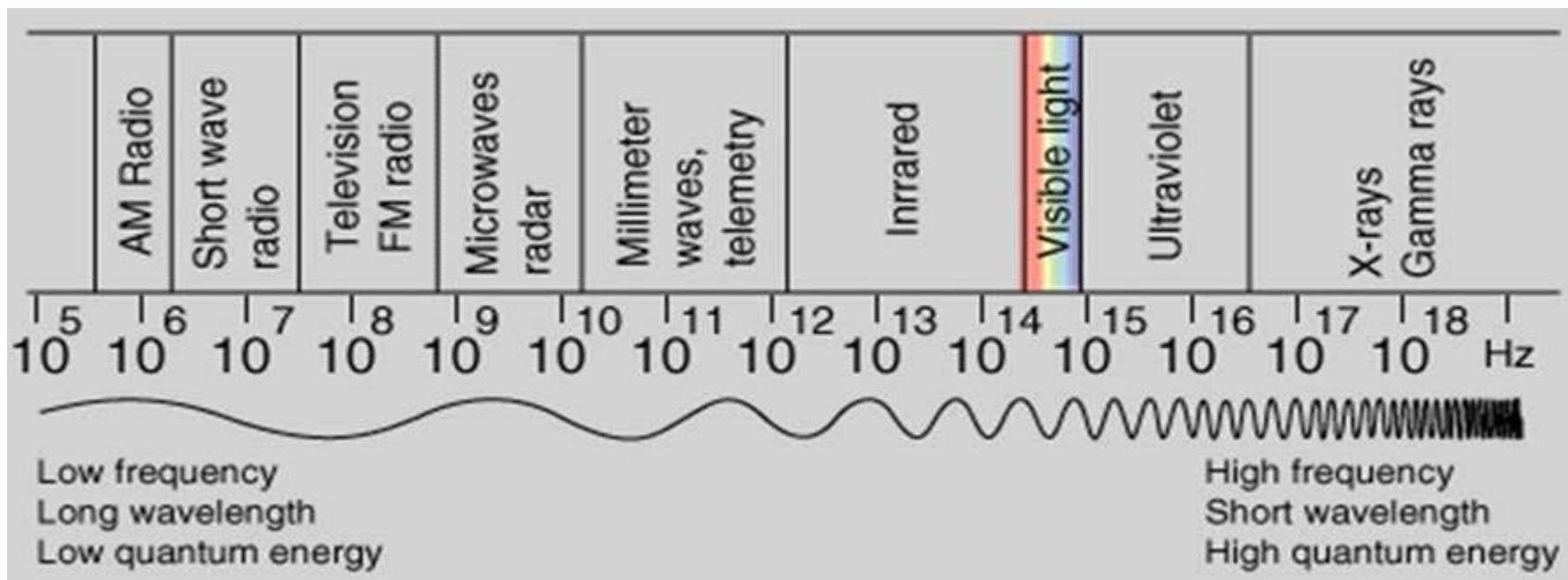
Frequency tuning in wireless communications




Transistor radio-receiver (1960)

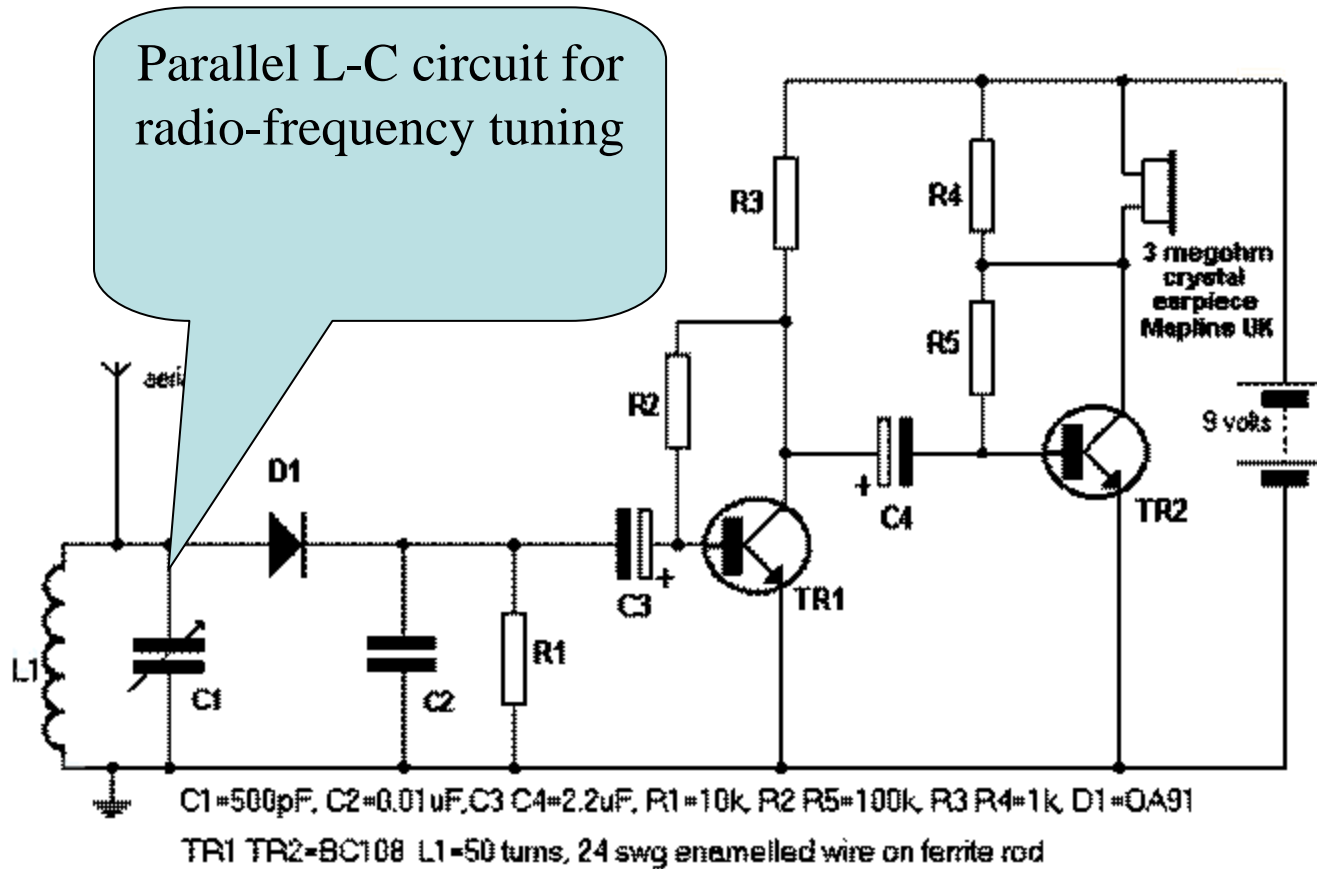

Mechanical variable capacitor

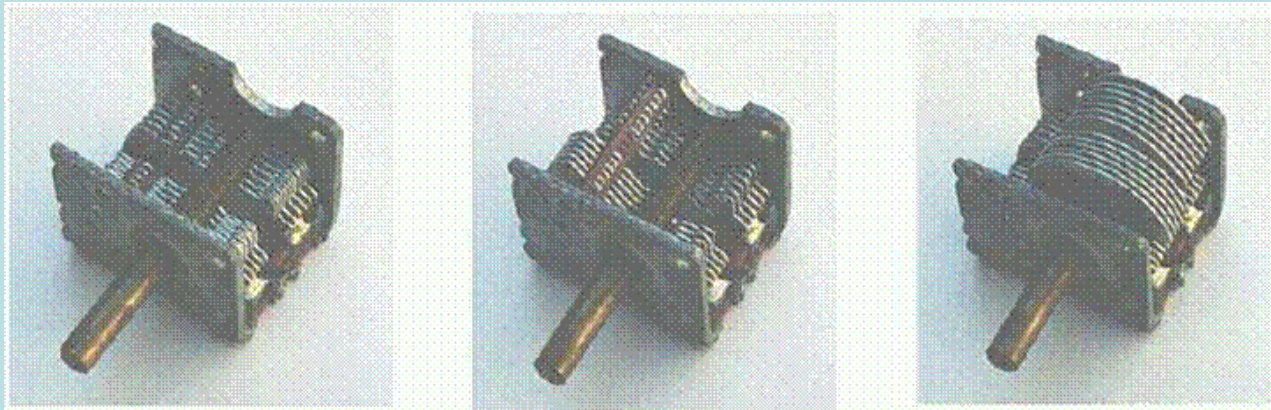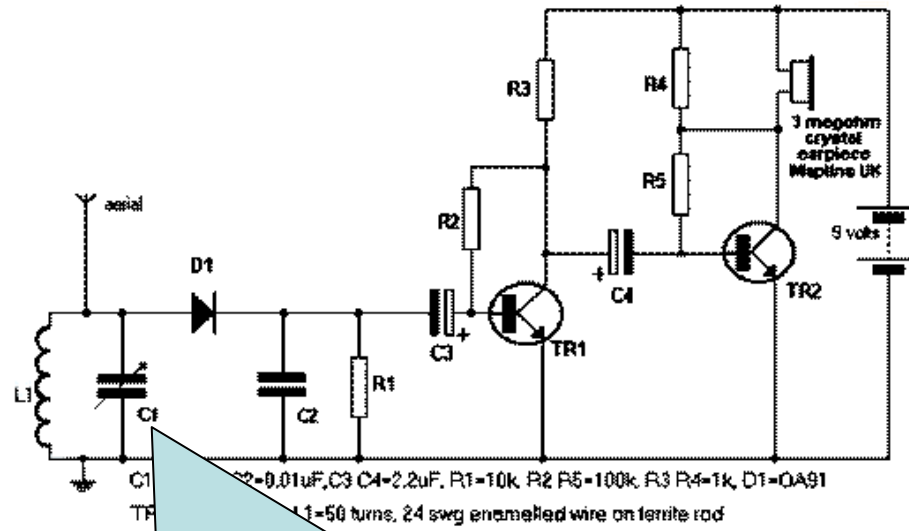

Vacuum-tube TV receiver (1932)

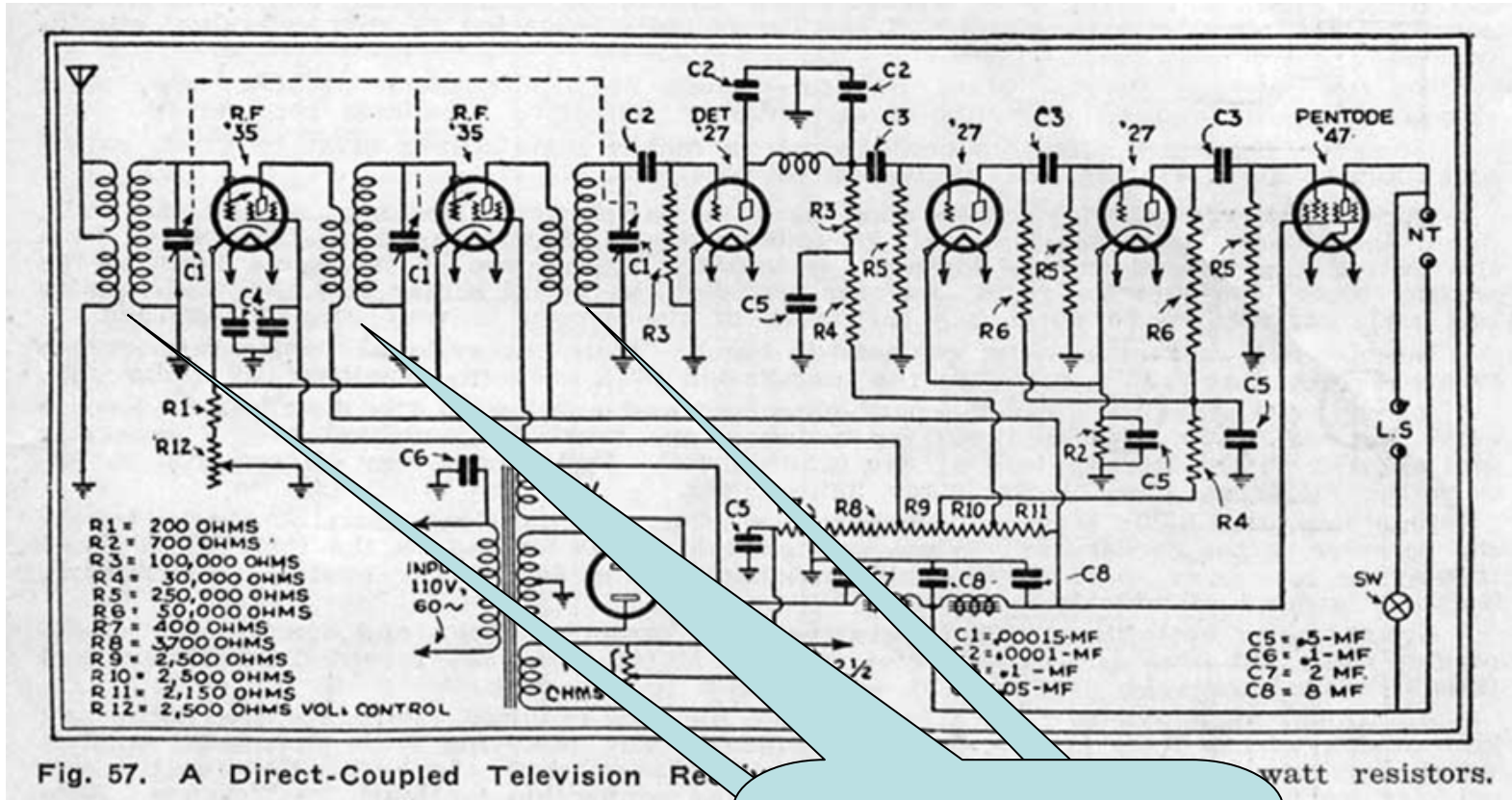

Parallel L-C circuits
for TV tuning

Integrated TV receiver (2000)

≈ 1" x 1" x 0.3"

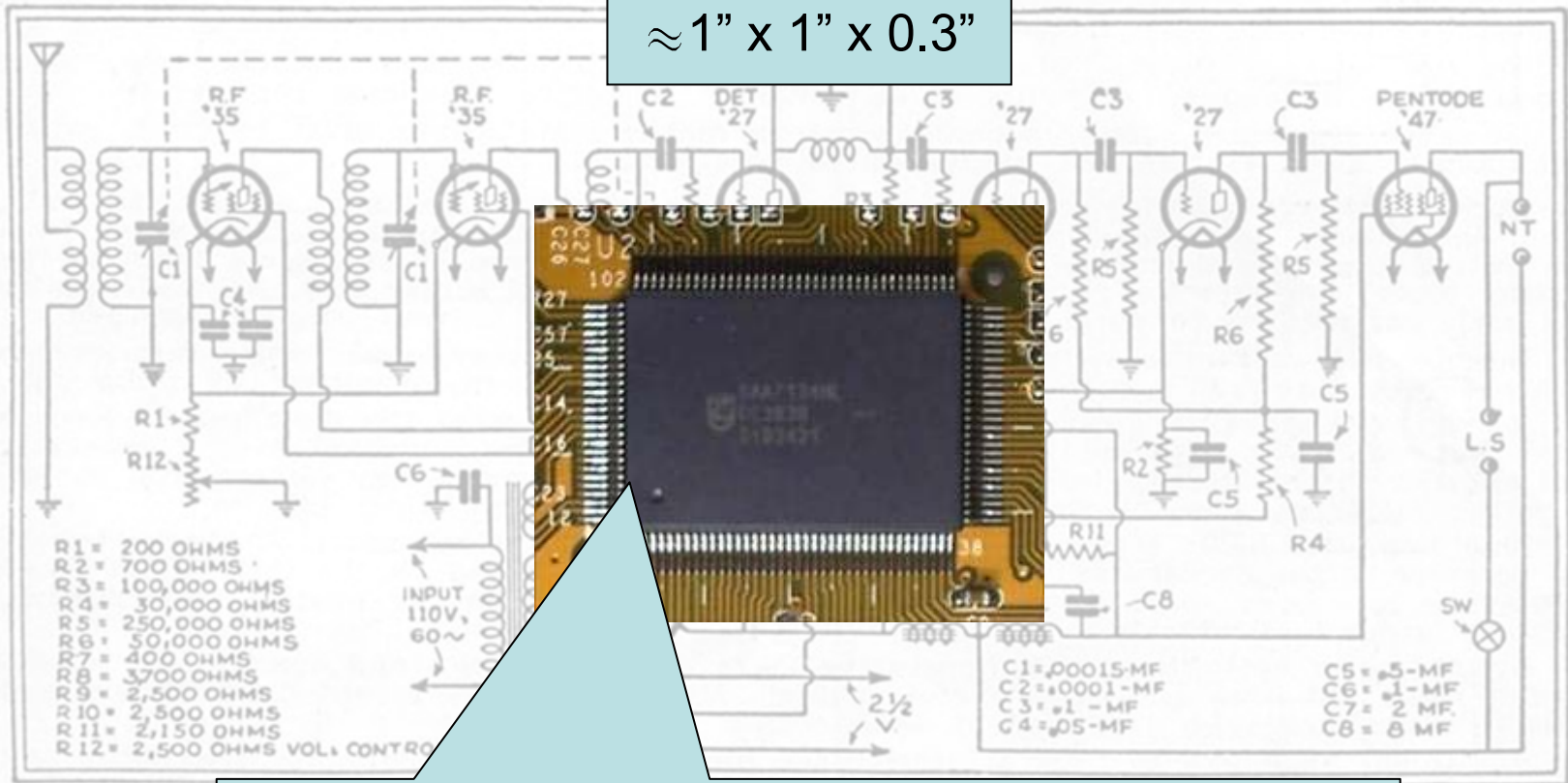


Fig. 57. A

t resistors.

All-channel TV tuning functions on-chip
Electronic tuning
100 smaller than discrete-component TV tuner