


# R-L and R-C Circuits

---

# R-L Circuit

---

Considering a R-L circuit:

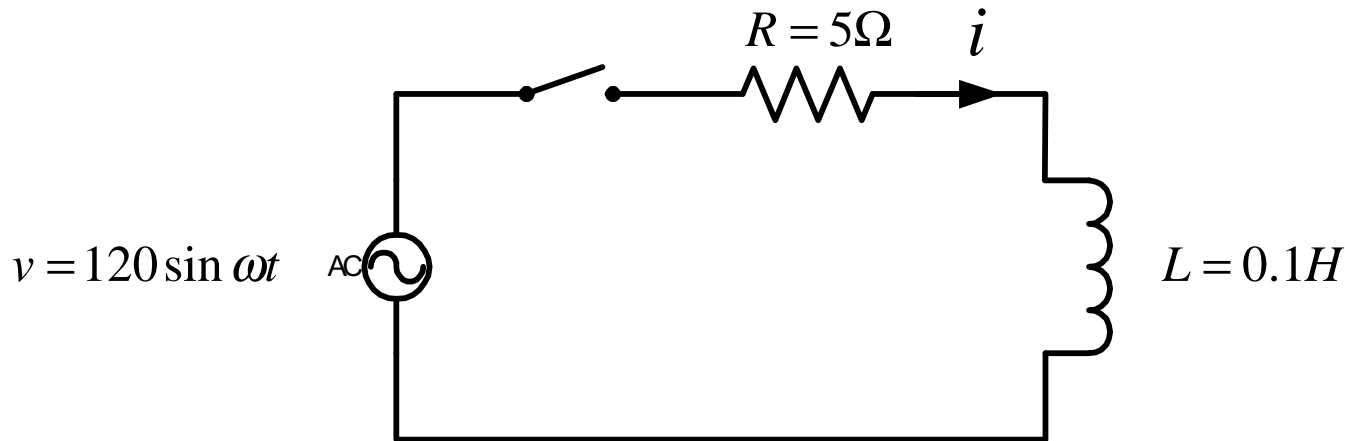


If at  $t=0$ , the switch is closed. What will be the response inductor current  $i$ ?

The system differential equation is:

$$v = Ri + L \frac{di}{dt}$$
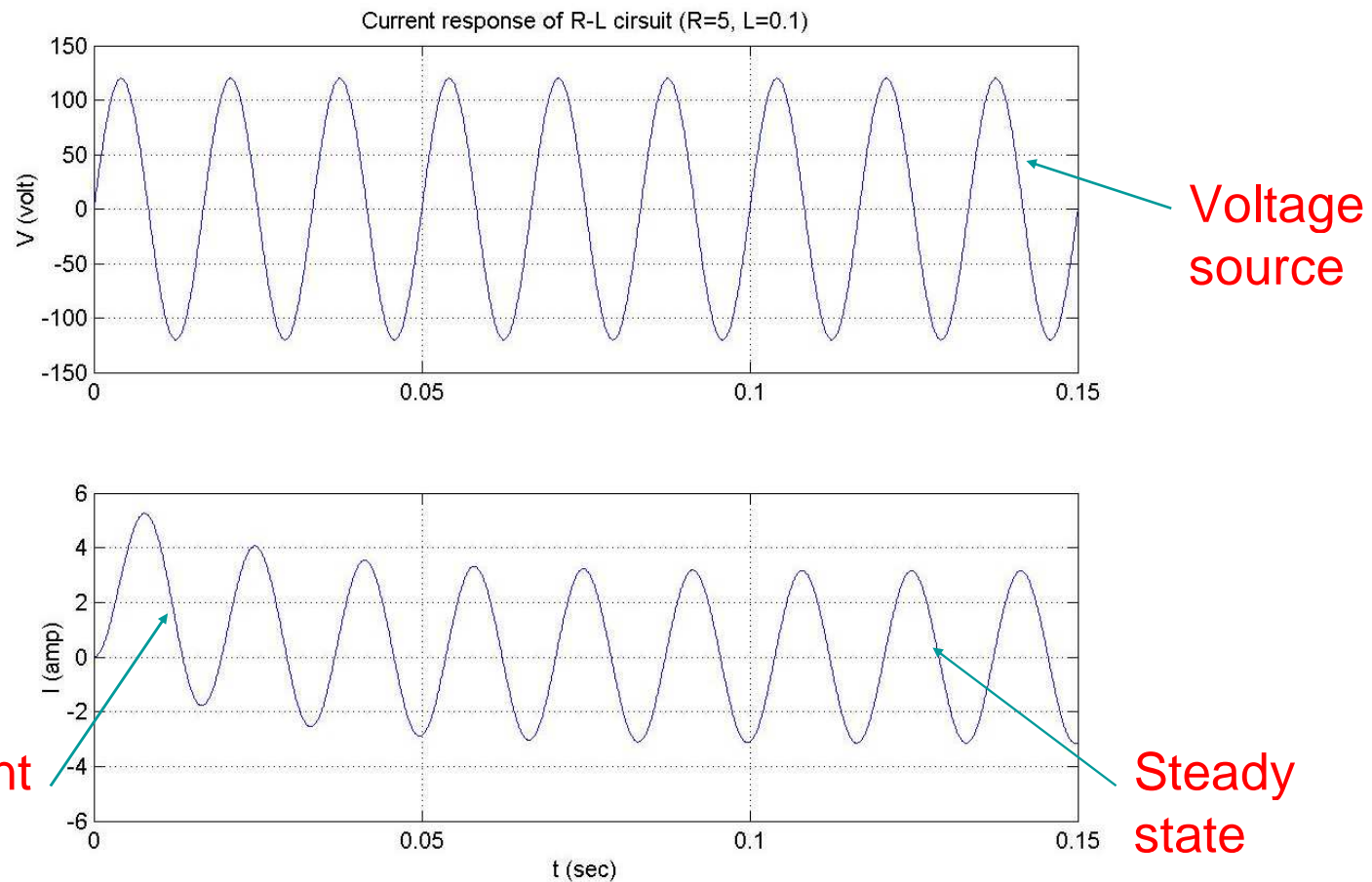
# R-L Circuit

After some time (transient state), the current reaches steady state as shown in the figure.



# R-L Circuit

---

At steady state,  $v$  and  $i$  can be represented by phasor  $V$  and  $I$ , where

$$V = V_{rms} \angle \theta_V \quad V_{rms} = \frac{120}{\sqrt{2}}$$

$$I = I_{rms} \angle \theta_I \quad \theta_I = \omega t + \theta_{I,0}$$

or

$$I = I_{rms} e^{j(\omega t + \theta_{I,0})} \Rightarrow \frac{dI}{dt} = j\omega I_{rms} e^{j(\omega t + \theta_{I,0})} = j\omega I$$

The differential equation becomes

$$V = (R + j\omega L)I$$

$\theta_V$  is the phase angle of  $V$ .

$\theta_I$  is the phase angle of  $I$ . It is determined by  $\theta_V$  and impedance angle  $\theta$  ( $\theta_I = \theta_V - \theta$ )

# R-L Circuit

---

Let  $X_L = \omega L$  Inductor Reactance

$$V = (R + jX_L)I$$

Let

$$Z = R + jX_L = |Z| \angle \theta \quad \theta = \tan^{-1}\left(\frac{X_L}{R}\right) > 0$$

We have  $\theta_V - \theta_I = \theta$

Generally we choose V as reference, then  $\theta_V = 0$

$$V = |V| \angle 0 \quad I = \frac{V}{Z} = |I| \angle -\theta \quad \text{I lags V}$$

# R-L Circuit

---

The power supplied by the power source is

$$S = VI^* = |V||I| \cos\theta + j|V||I| \sin\theta$$
$$= P + jQ$$

Lagging – positive  
reactive power


Or in other form,

$$S = VI^* = (R + jX_L)I \cdot I^*$$
$$= |I|^2 R + j|I|^2 X_L = P + jQ$$

# R-C Circuit

---

Considering a R-C circuit:

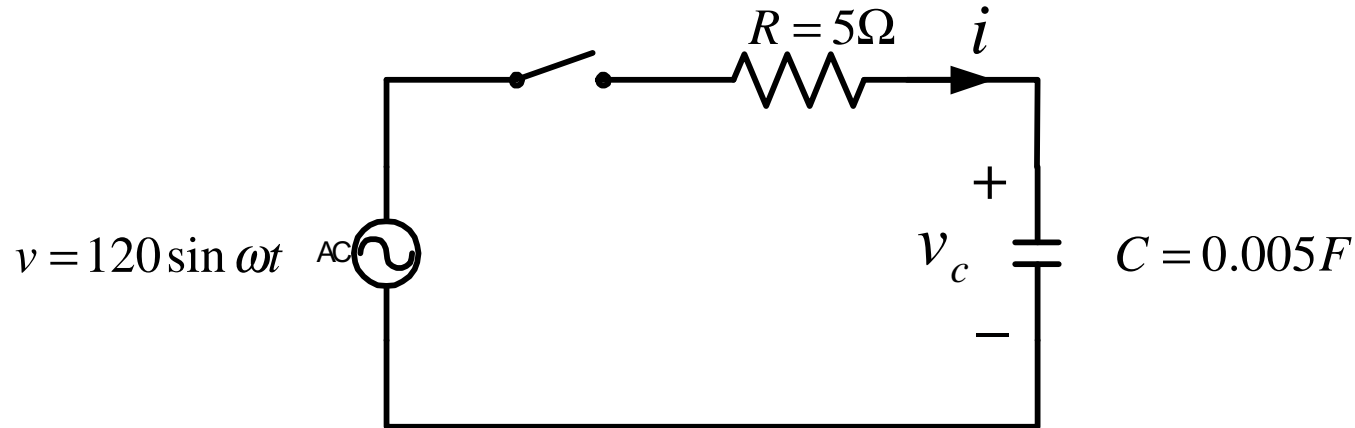


If at  $t=0$ , the switch is closed. What will be the response capacitor voltage  $v_c$ ?

The system differential equation is:

$$v = RC \frac{dv_c}{dt} + v_c$$
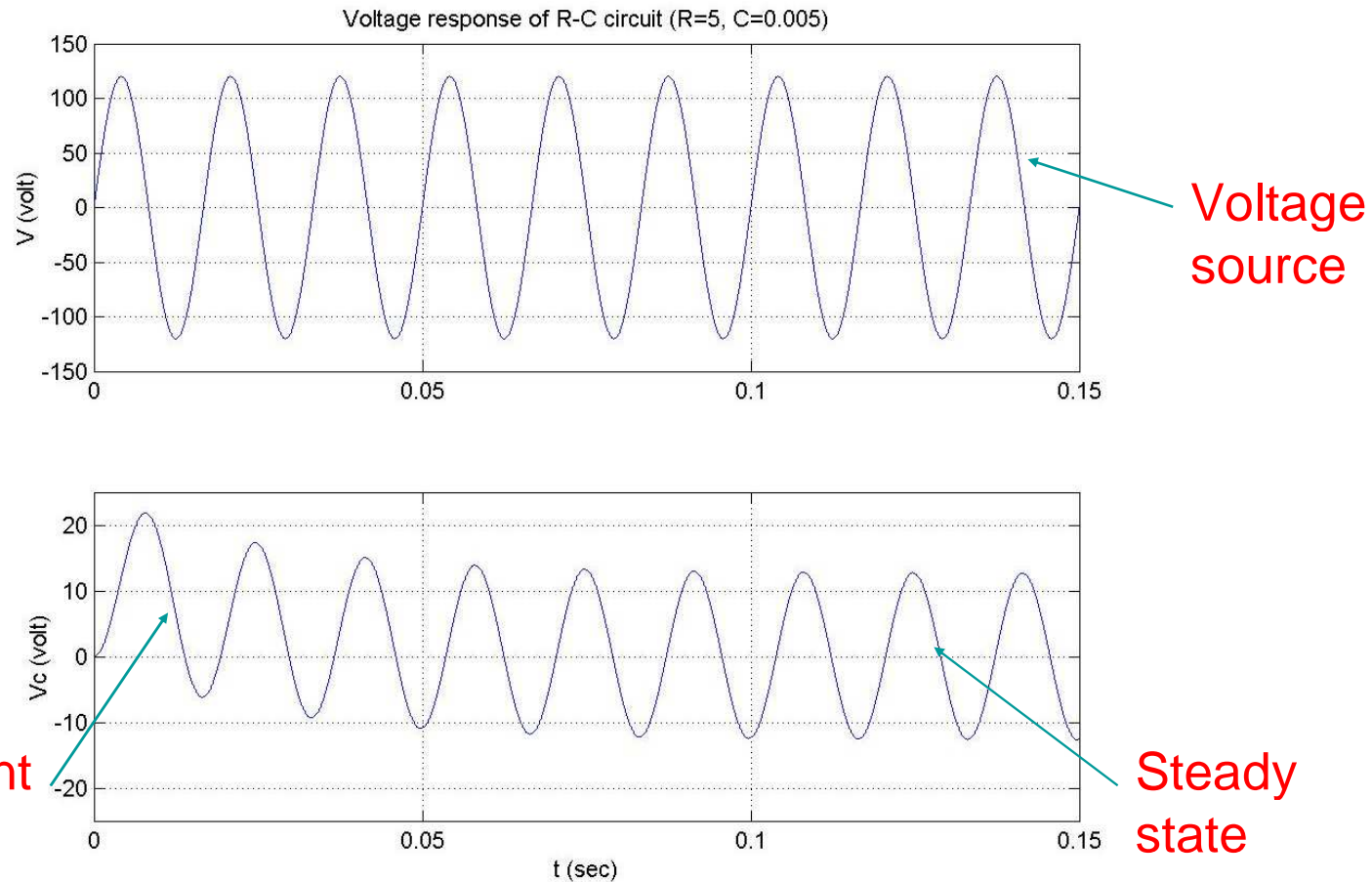
# R-C Circuit

After some time (transient state), the voltage reaches steady state as shown in the figure.



# R-C Circuit

---

At steady state,  $v$  and  $v_c$  can be represented by phasor  $V$  and  $V_C$ , where

$$V = V_{rms} \angle \theta_V \quad V_{rms} = \frac{120}{\sqrt{2}}$$

$$V_C = V_{C,rms} \angle \theta_{V_C}$$

$$\frac{dV_C}{dt} = j\omega V_C \quad I = C \frac{dV_C}{dt} = j\omega C V_C$$

or

$$V_C = I \left( \frac{1}{j\omega C} \right) = I \left( -j \frac{1}{\omega C} \right)$$

# R-C Circuit

---

so  $V = (R - j\frac{1}{\omega C})I$

Let  $X_C = \frac{1}{\omega C}$  Capacitor Reactance

$$V = (R - jX_C)I$$

Let  $Z = R - jX_C = |Z|\angle -\theta$      $\theta = \tan^{-1}\left(\frac{X_C}{R}\right)$

We have  $\theta_V - \theta_I = -\theta$

Generally we choose V as reference, then  $\theta_V = 0$

$$V = |V|\angle 0 \quad I = \frac{V}{Z} = |I|\angle \theta$$
 I leads V

# R-C Circuit

---

The power supplied by the power source is

$$S = VI^* = |V||I|\cos\theta - j|V||I|\sin\theta$$
$$= P - jQ$$

Leading – negative  
reactive power

Or in other form,

$$S = VI^* = (R - jX_C)I \cdot I^*$$
$$= |I|^2 R - j|I|^2 X_C = P - jQ$$